

BE(ECE) III - Semester Main Exam

Sub: Network Theory.

Question paper key - Set - 1.

- 1 a) Transmission parameters: ABCD parameters are also known as transmission parameters. Here voltage and current at port ① can be expressed in terms of voltage & current at port ②

$$V_1 = AV_2 - BI_2 \quad \text{--- (1)}$$

$$I_1 = CV_2 - DI_2 \quad \text{--- (2)}$$

When A, B, C & D are transmission parameters. If o/p port is open circuited, $I_2 = 0$. Then from eq (1) & (2) we get

$$A = \frac{V_1}{V_2} = \text{ratio of i/p voltage to o/p voltage when o/p port is open circuited.}$$

$$\text{Also } C = \frac{I_1}{V_2} = \text{ratio of i/p current to o/p voltage when o/p port is open circuited.}$$

If o/p port is short circuited, $V_2 = 0$, then from eq (1) & (2) we get

$$-B = \frac{V_1}{I_2} = \text{ratio of i/p voltage to o/p current}$$

$$\text{and } -D = \frac{I_1}{I_2} = \text{ratio of i/p current to o/p current}$$

- b) The condition for symmetry of a 2-port n/w in Z, Y, h & transmission parameters is given below.

$$Z_{11} = Z_{22}$$

$$Y_{11} = Y_{22}$$


$$\Delta h = 1$$

$$A = D$$


- c) Symmetrical n/w: If electrical characteristics of a n/w remains unchanged if its ports are interchanged, then the n/w is said to be symmetrical n/w.

Also, a symmetrical n/w has same impedance at both ports

Ex: i) a symmetrical T-n/w.

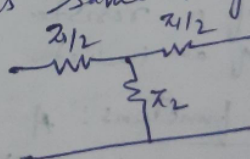

ii) a 1:1 transformer.

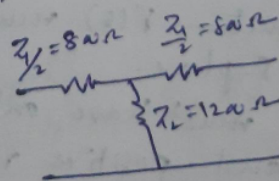

- d) Given $\frac{Z_1}{2} = 8\omega \Omega$ & $Z_2 = 12\omega \Omega$
 $\Rightarrow Z_1 = 16\omega \Omega$


Characteristic impedance

$$Z_{0T} = \sqrt{\frac{Z_1^2}{4} + Z_1 Z_2} = \sqrt{\frac{(16\omega)^2}{4} + 16\omega \times 12\omega} = 16\omega \Omega$$

- e) Constant K-filter: A constant K filter is a T or Π n/w in which the series and shunt impedances Z_1 and Z_2 are so designed that they have the relation $Z_1 Z_2 = R_K^2$ where R_K is a real constant, independent of frequency. It is termed as design impedance or nominal impedance of constant K-filter.

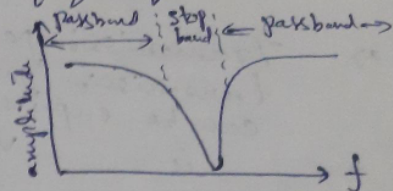f) Notch filter: Basically a notch filter is a band elimination filter with a narrow stop band. It passes all frequencies except those in a stop band centered on a center frequency.

The amplitude response of a notch filter is flat at all frequencies except for the stop band on either side of the center frequency.



9) Attenuation in decibel is

$$\alpha_{dB} = 20 \log_{10} \frac{V_i}{V_o} \quad \text{--- (1)}$$

Neper is defined as the natural logarithm of voltage at input port to voltage at output port.

$$\alpha_N = \log_e \frac{V_i}{V_o} \quad \text{--- (2)}$$

Consider

$$\alpha_{dB} = 20 \log_{10} \frac{V_i}{V_o}$$

using change of base theorem

$$\alpha_{dB} = 20 \frac{\log_e \frac{V_i}{V_o}}{\log_e 10} = 20 \frac{\alpha_N}{2.302}$$

$$\boxed{\alpha_{dB} = 8.686 \alpha_N}$$

$$\text{or } \alpha_N = 0.115 \alpha_{dB}$$

b) Two impedances Z_1 & Z_2 are said to be inverse when their geometric mean is a real number

$$\text{i.e. } Z_1 Z_2 = R^2 \quad \text{where } R \text{ is a resistance.}$$

Ex. Inverse of a resistor is another resistor.

Inverse of an inductor is capacitor & vice-versa.

c) positive real functions: A rational function $F(s)$ with real coefficients are said to be prf if it satisfies the following conditions.

i) n/w function $F(s)$ must have no poles in the right half of s -plane.

ii) $F(s)$ must have only simple poles on the $j\omega$ axis with real and positive residues.

d) Network analysis is a process through which we calculate various electrical parameters of a circuit elements connected in an electrical n/w.

Network synthesis is a design technique for linear electrical circuits. Synthesis starts from a prescribed impedance function of frequency and then determines the possible networks that will produce the required response.