

FACULTY OF ENGINEERING

B. E. (ECE)(AICTE) III – Semester (Main) Examination, December 2019

Subject: Electronic Devices

Time: 3 hours

Max. Marks: 70

Note: Answer all questions from Part-A. Answer any FIVE questions from Part-B.

PART – A (20 Marks)


1. What is the effect of temperature on reverse saturation current of diode? A silicon diode has a saturation current of 15nA at a temperature of 100⁰C. Calculate the reverse saturation current at 300⁰C. 2
2. Distinguish between Zener breakdown and avalanche breakdown. 2
3. Draw the circuit diagram of Half wave rectifier and draw input and output waveforms. 2
4. What is Bleeder resistance? Explain the need for bleeder resistor. 2
5. Define alpha, beta and gamma. Give the relation between them. 2
6. Sketch the input and output characteristics of BJT in common emitter configuration. 2
7. Compare CB, CE and CC in terms of Current gain, Voltage gain, input resistance, output resistance, application and phase shift. 2
8. Draw the h-parameter model of BJT in CB configuration. 2
9. Prove that the transconductance g_m of JFET is given by $g_m = \frac{2\sqrt{I_D I_{DSS}}}{V_p}$. 2
10. Define Pinch off Voltage. Sketch the depletion region before and after pinch off. 2

PART – B (50 Marks)

11. (a) Explain the formation and working of PN junction diode in forward and reverse bias with neat diagrams. Draw its V-I characteristics. 5
 (b) Derive the expression for transition capacitance. 5
12. (a) Derive the expression of ripple factor for Half wave rectifier with capacitor filter. 6
 (b) Design a Half wave rectifier with capacitor filter to provide dc output with 2% ripple for a 100 Ω load. 4
13. (a) Derive the stability factor of a Self bias circuit. 5
 (b) Explain how h-parameters are obtained graphically. 5
14. For the transistor amplifier shown in figure below, calculate A_I , A_V , R_I , R_O using exact and approximate analysis. Use $h_{fe}=50$, $h_{ie}=1.1k\Omega$, $h_{re}=250\mu$, $h_{oe}=25\mu A / V$. 10

.....2

-2-

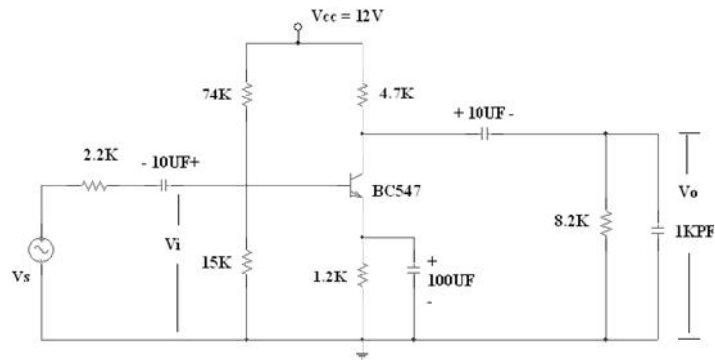

15. (a) Draw the structure of N-channel JFET. Explain the transfer and drain characteristics with neat diagrams. 7
- (b) A JFET has drain saturation current I_{DSS} of 12mA and I_D of 6mA with a pinch off voltage of -4Volts. Calculate V_{GS} and gm. 3
16. (a) Draw the circuit of CE amplifier using diode compensation for I_{co} . Describe how bias compensation is achieved. 5
- (b) What is Early Effect? What are its consequences? 5
17. Write short notes on:
- (a) Photo diode. 5
- (b) Fabrication Process. 5
