

# **Circuit, State Diagram, State Table**

Circuits with Flip-Flop = Sequential Circuit

Circuit = State Diagram = State Table


State Minimization

Sequential Circuit Design

Example: Sequence Detector

Example: Binary Counter


# Circuit, State Diagram, State Table

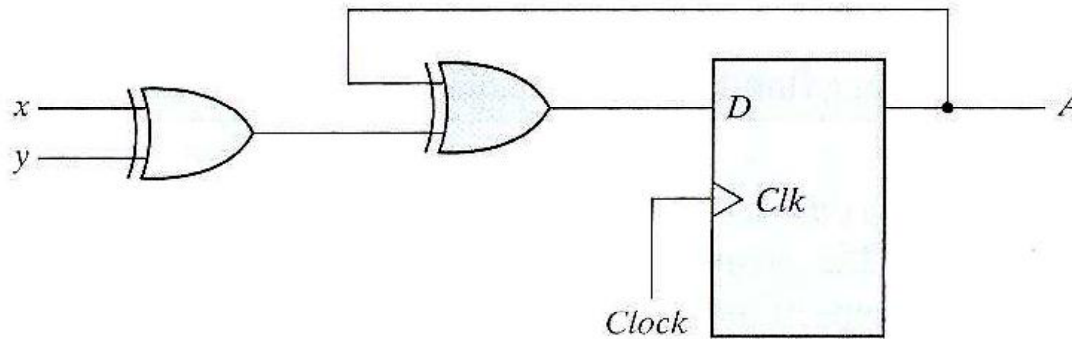

(a) Circuit diagram

Present state	Inputs		Next state
<i>A</i>	<i>x</i>	<i>y</i>	<i>A</i>
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1


(b) State table

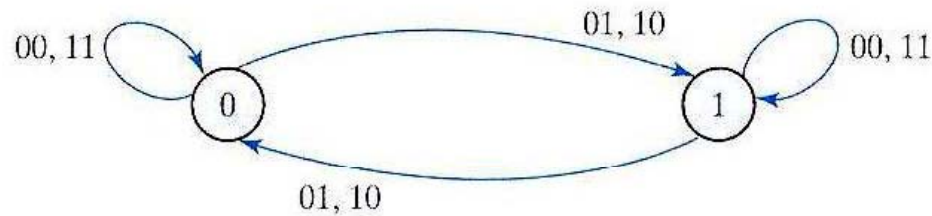

(c) State diagram

**FIGURE 5.17**  
Sequential circuit with *D* flip-flop

# Circuit, State Diagram, State Table

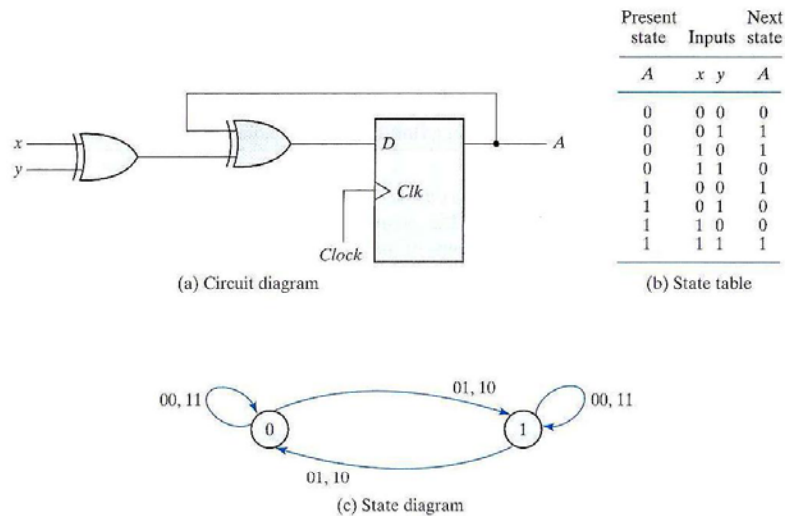

**FIGURE 5.17**  
Sequential circuit with D flip-flop

**Terms:**

**State:** flip-flop output combination

**Present state:** before clock

**Next state:** after clock

State transition  $\leq$  clock

1 flip-flop  $\Rightarrow$  2 states

2 flip-flops  $\Rightarrow$  4 states

3 flip-flops  $\Rightarrow$  8 states


4 flip-flops  $\Rightarrow$  16 states

...

N flip-flops  $\Rightarrow$   $2^N$  states

...

# Circuit, State Diagram, State Table

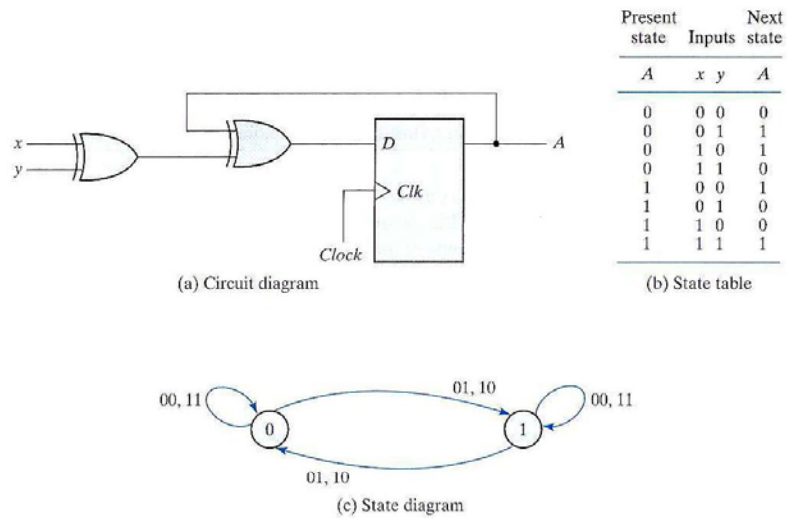


**FIGURE 5.17**  
Sequential circuit with *D* flip-flop

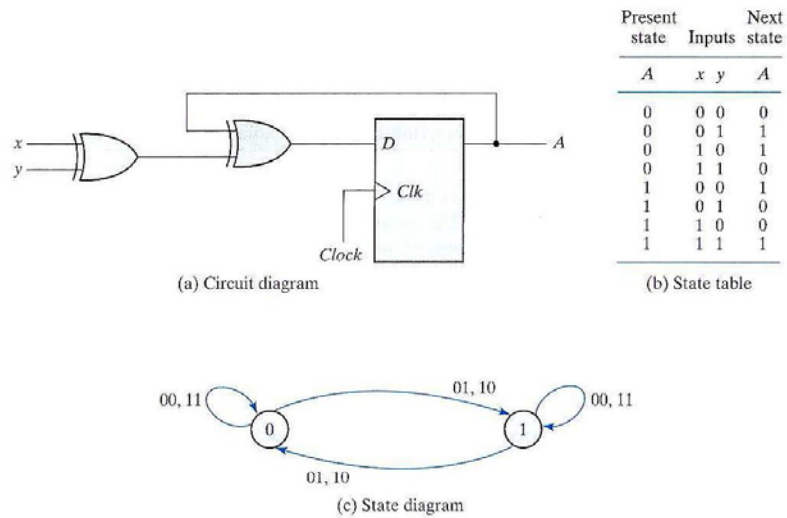Sequential circuit components:

- Flip-flop(s)
- Clock
- Logic gates
- Input
- Output

# Circuit, State Diagram, State Table




State diagram:

Circle => state

Arrow => transition  
input/output

**FIGURE 5.17**  
Sequential circuit with *D* flip-flop

# Circuit, State Diagram, State Table

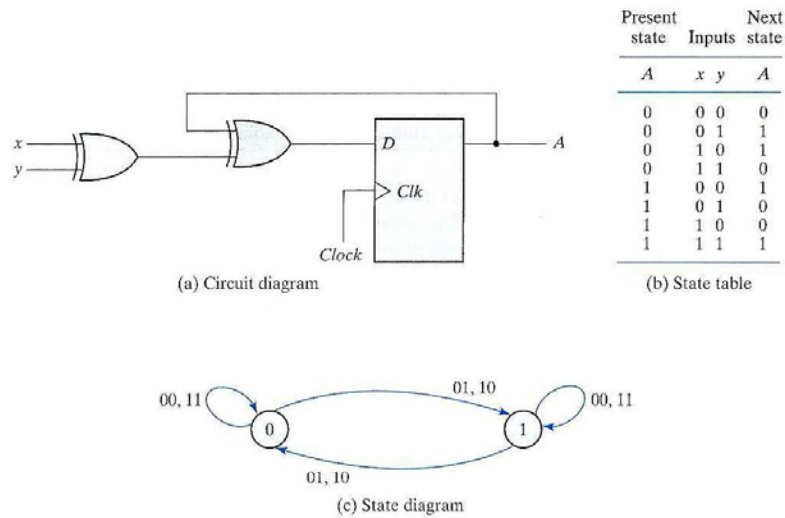

**FIGURE 5.17**  
Sequential circuit with *D* flip-flop


State table:

Left column => current state

Top row => input combination

Table entry => next state, output


# Example: Binary Counter

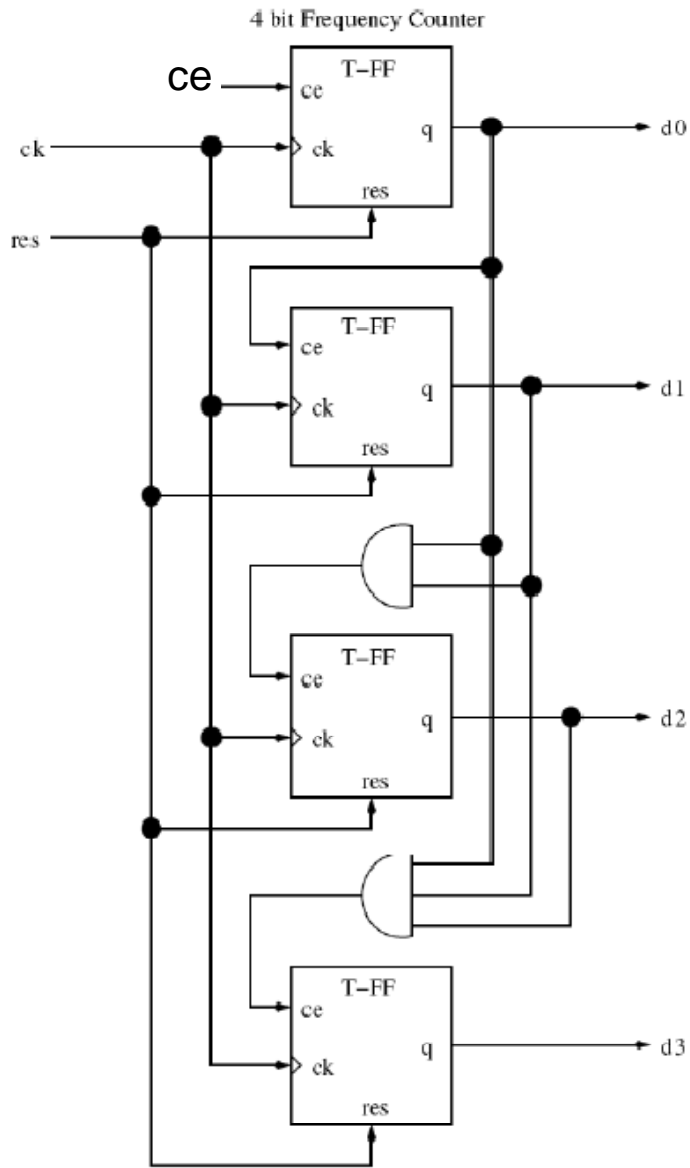

... → 1110 → 1111 → 0000 → 0001 →  
0010 → 0011 → 0100 → 0101 → ...


present state	next state	
	ce=0	ce=1
0000	0000	0001
0001	0001	0010
0010	0010	0011
...	...	...
1101	1101	1110
1110	1110	1111
1111	1111	0000

→ state table

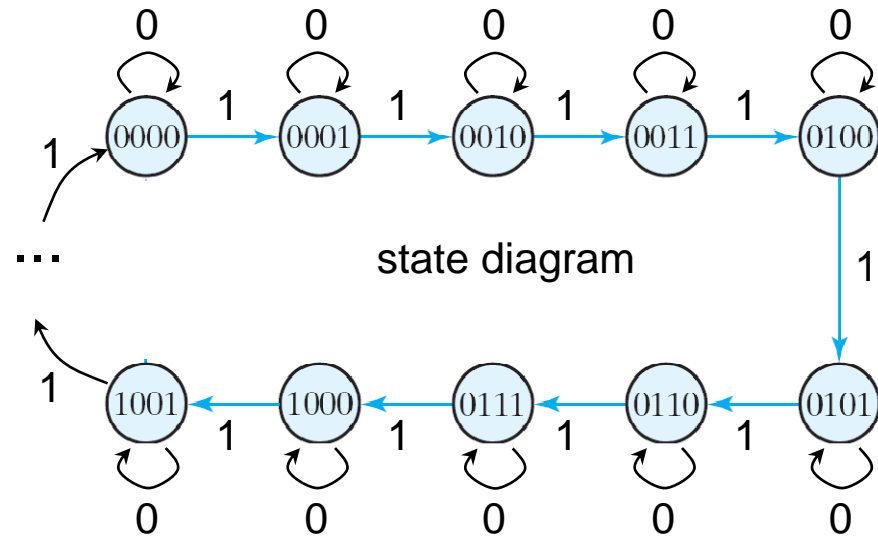

# Circuit, State Diagram, State Table

Example:

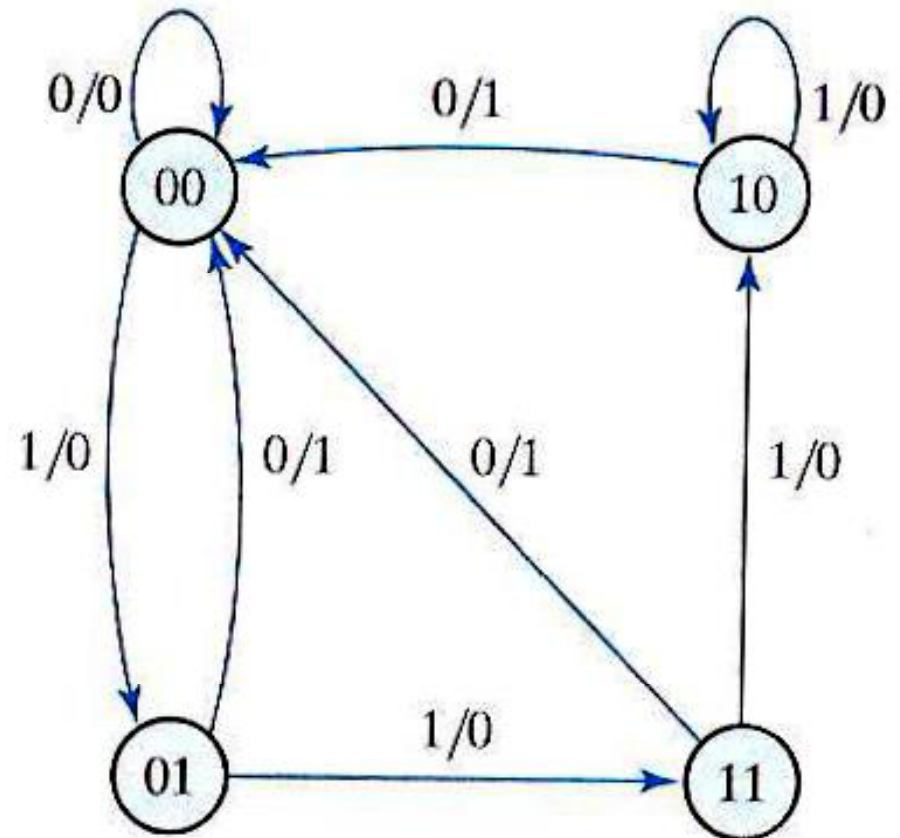


**FIGURE 5.16**

State diagram of the circuit of Fig. 5.15




# Circuit, State Diagram, State Table

Example:

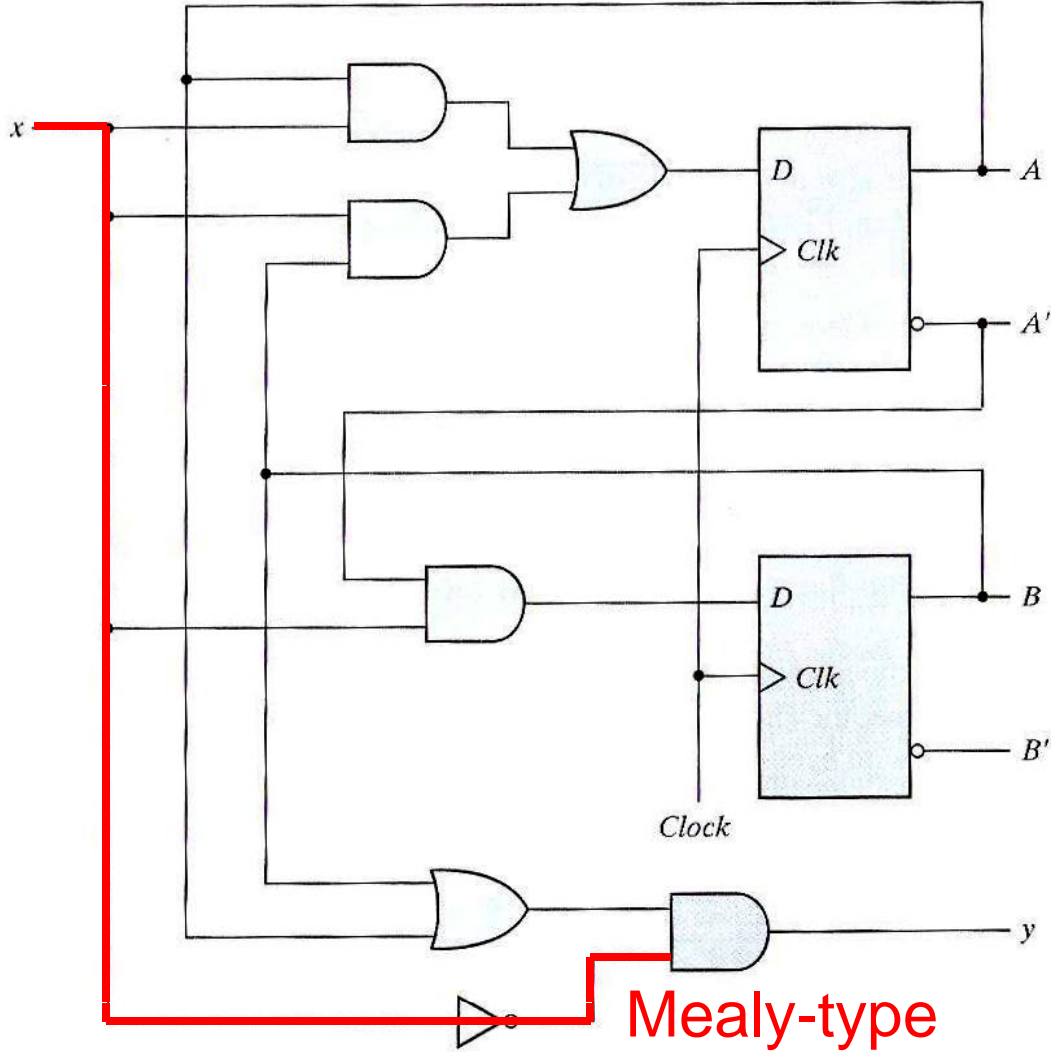

Mealy-type

Input and output values separated by dash along the directed lines

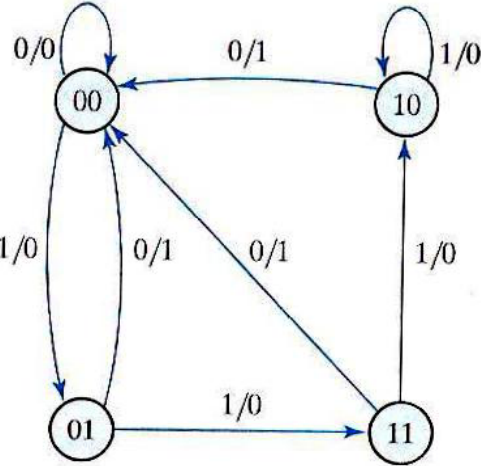

**FIGURE 5.15**  
Example of sequential circuit


of the circuit of Fig. 5.15

# Circuit, State Diagram, State Table


Example:

**Table 5.3**  
*Second Form of the State Table*

Present State		Next State				Output	
		$x = 0$		$x = 1$		$x = 0$	$x = 1$
<i>A</i>	<i>B</i>	<i>A</i>	<i>B</i>	<i>A</i>	<i>B</i>	<i>y</i>	<i>y</i>
0	0	0	0	0	1	0	0
0	1	0	0	1	1	1	0
1	0	0	0	1	0	1	0
1	1	0	0	1	0	1	0

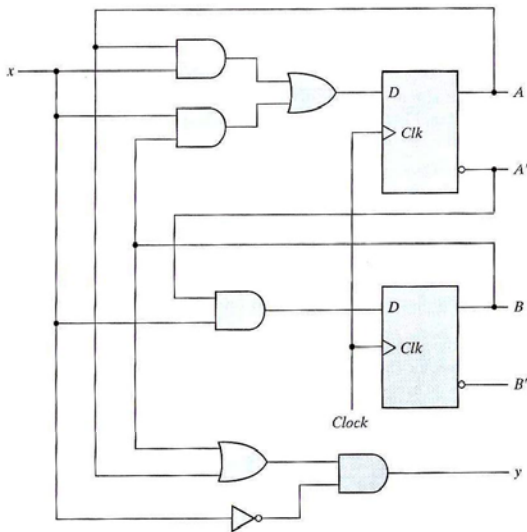

**FIGURE 5.15**  
Example of sequential circuit

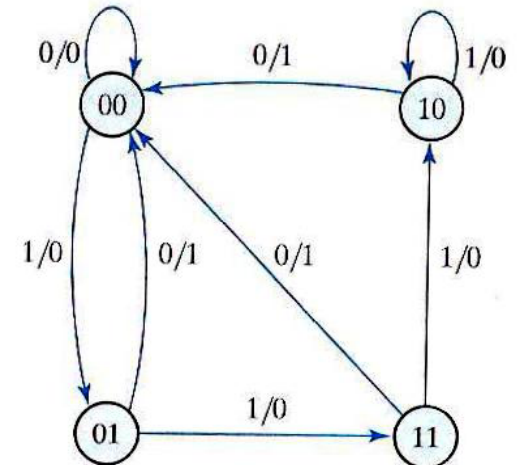

**FIGURE 5.16**  
State diagram of the circuit of Fig. 5.15


# Circuit, State Diagram, State Table

Example:


state diagram  
 → state table

**Table 5.3**  
*Second Form of the State Table*

Present State		Next State				Output	
		$x = 0$		$x = 1$		$x = 0$	$x = 1$
<i>A</i>	<i>B</i>	<i>A</i>	<i>B</i>	<i>A</i>	<i>B</i>	<i>y</i>	<i>y</i>

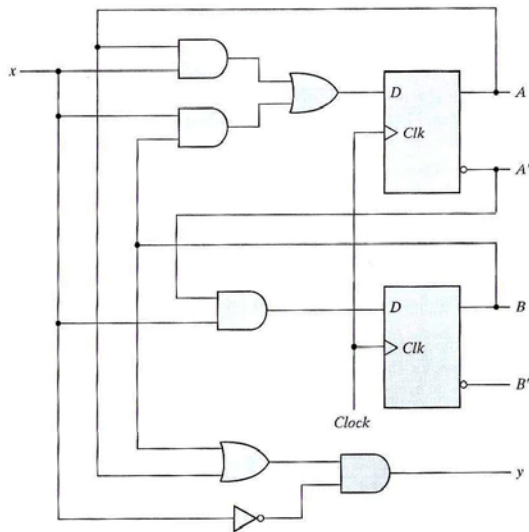


**FIGURE 5.15**  
 Example of sequential circuit

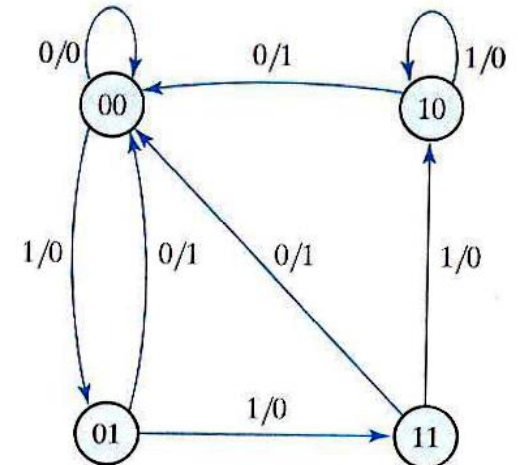

**FIGURE 5.16**  
 State diagram of the circuit of Fig. 5.15


# Circuit, State Diagram, State Table

Example:

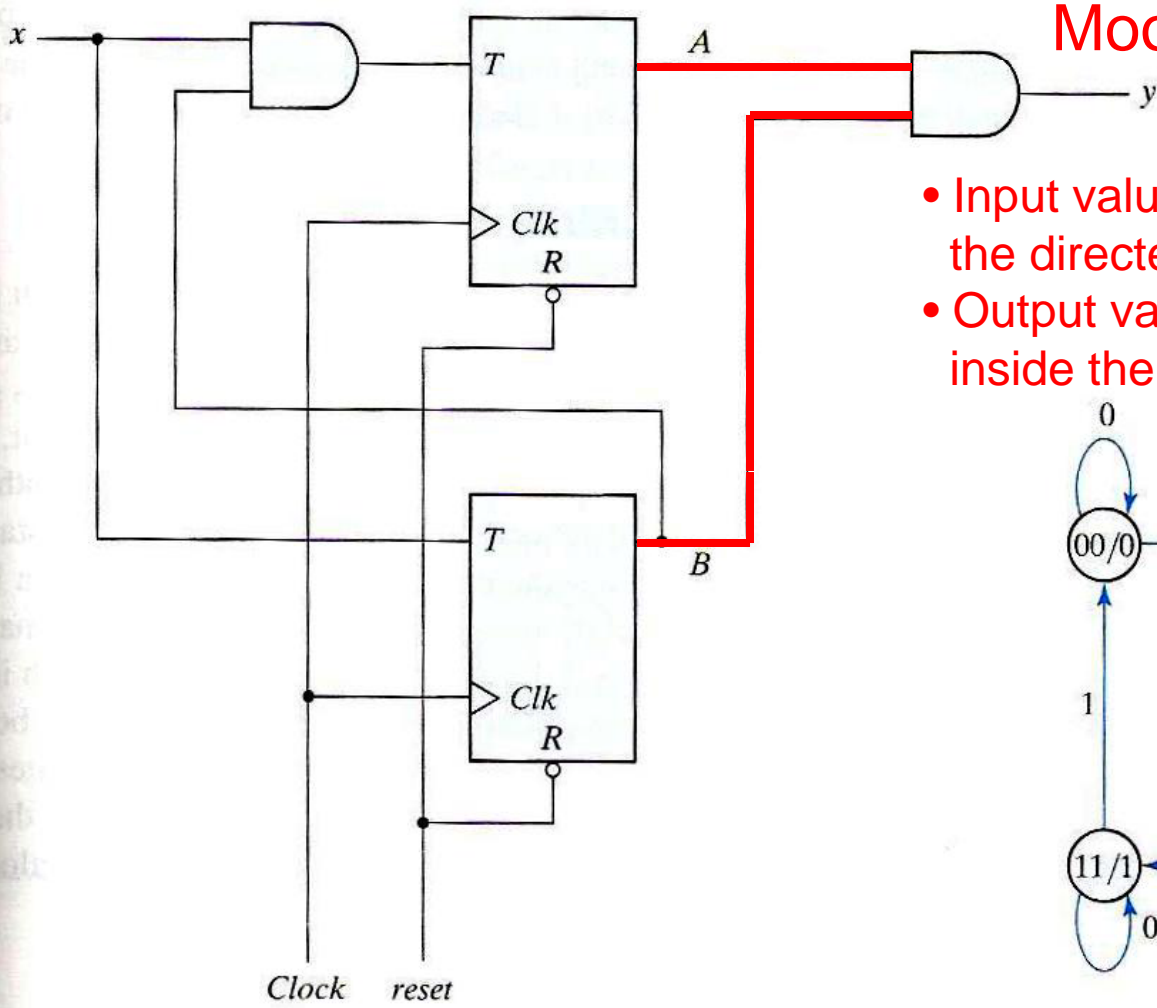

Moore-type

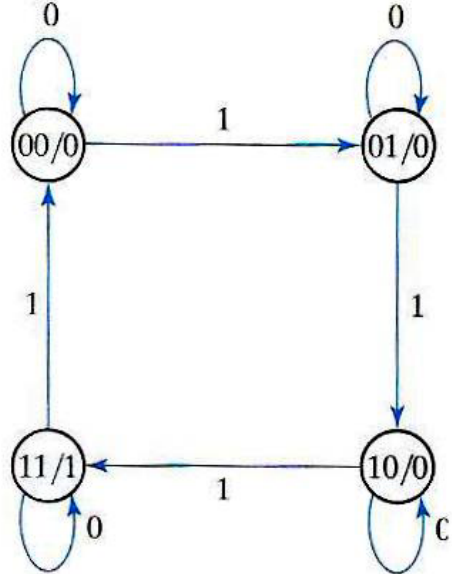- Input values labeled along the directed lines
- Output values indicated inside the circles




(a) Circuit diagram

(b) State diagram



**FIGURE 5.20**  
Sequential circuit with  $T$  flip-flops

# Circuit, State Diagram, State Table

**Example:** Show the second form truth table similar to Table 5.3

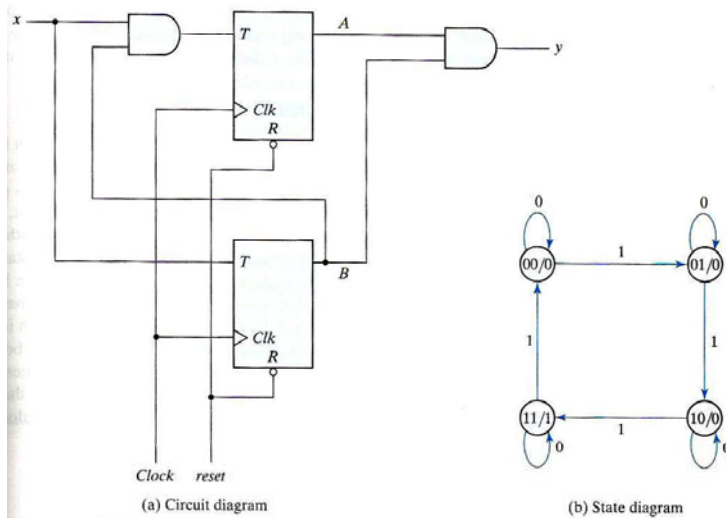

**FIGURE 5.20**  
Sequential circuit with T flip-flops

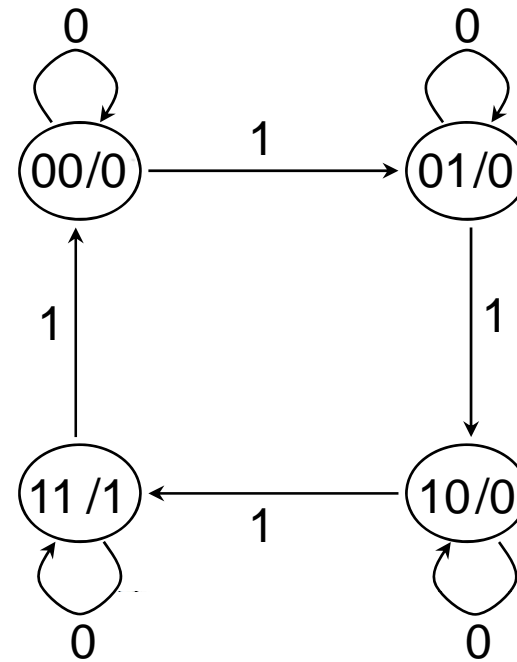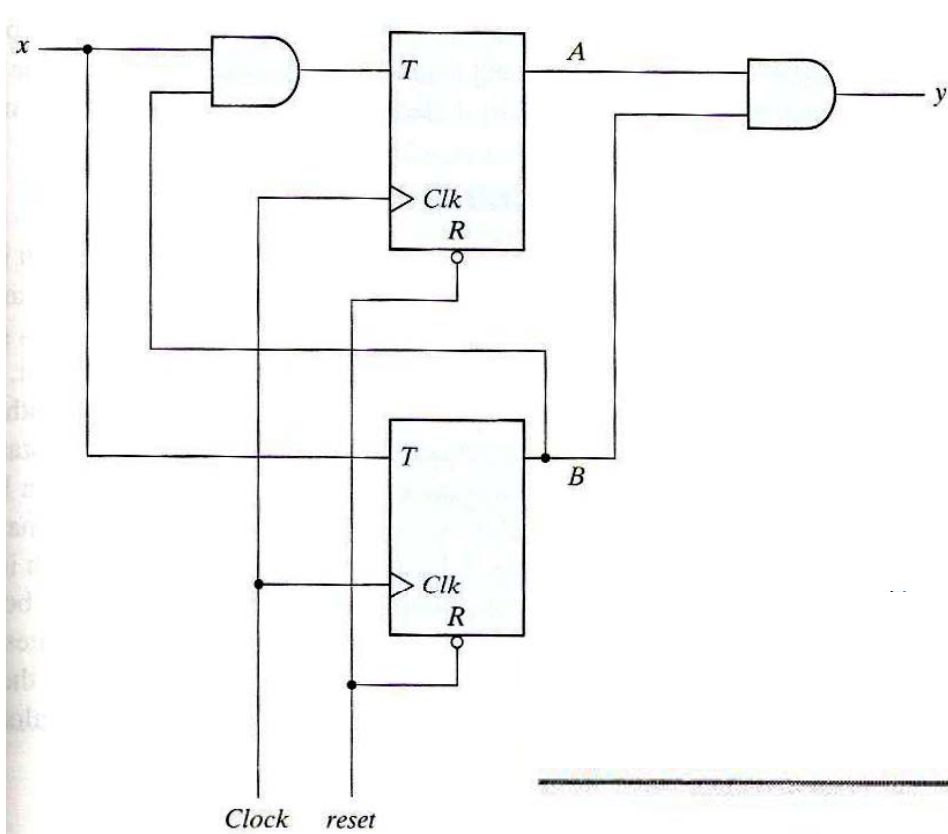

Present State	Next State		Output
	x = 0	x = 1	
A B	A B	A B	y
0 0	0 0	0 1	0
0 1	1 0	1 0	0
1 0	1 1	1 1	0
1 1	0 0	0 0	1

circuit


→ state table

→ state diagram

# Circuit, State Diagram, State Table

**Example:** state diagram = state table  
state table/state diagram

→ circuit

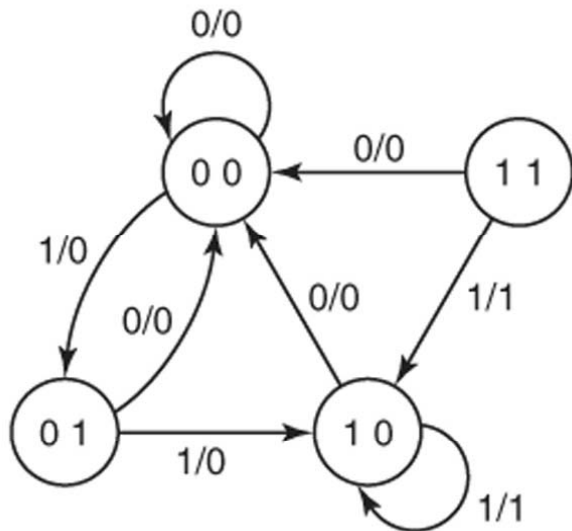

$q$	$q^*$		$z$	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
0 0	0 0	0 1	0	0
0 1	0 0	1 0	0	0
1 0	0 0	1 0	0	1
1 1	0 0	1 0	0	1

**D-FF characteristic eq:  $D = Q^*$**

		AB			
		00	01	11	10
$D_A$	$x$				
	0	0	0	0	0
1	0	1	1	1	


$$D_A = Ax + Bx$$

		AB			
		00	01	11	10
$D_B$	$x$				
	0	0	0	0	0
1	1	0	0	0	

$$D_B = A'B'x$$

		AB			
		00	01	11	10
$z$	$x$				
	0	0	0	0	0
1	0	0	1	1	


$$z = Ax$$

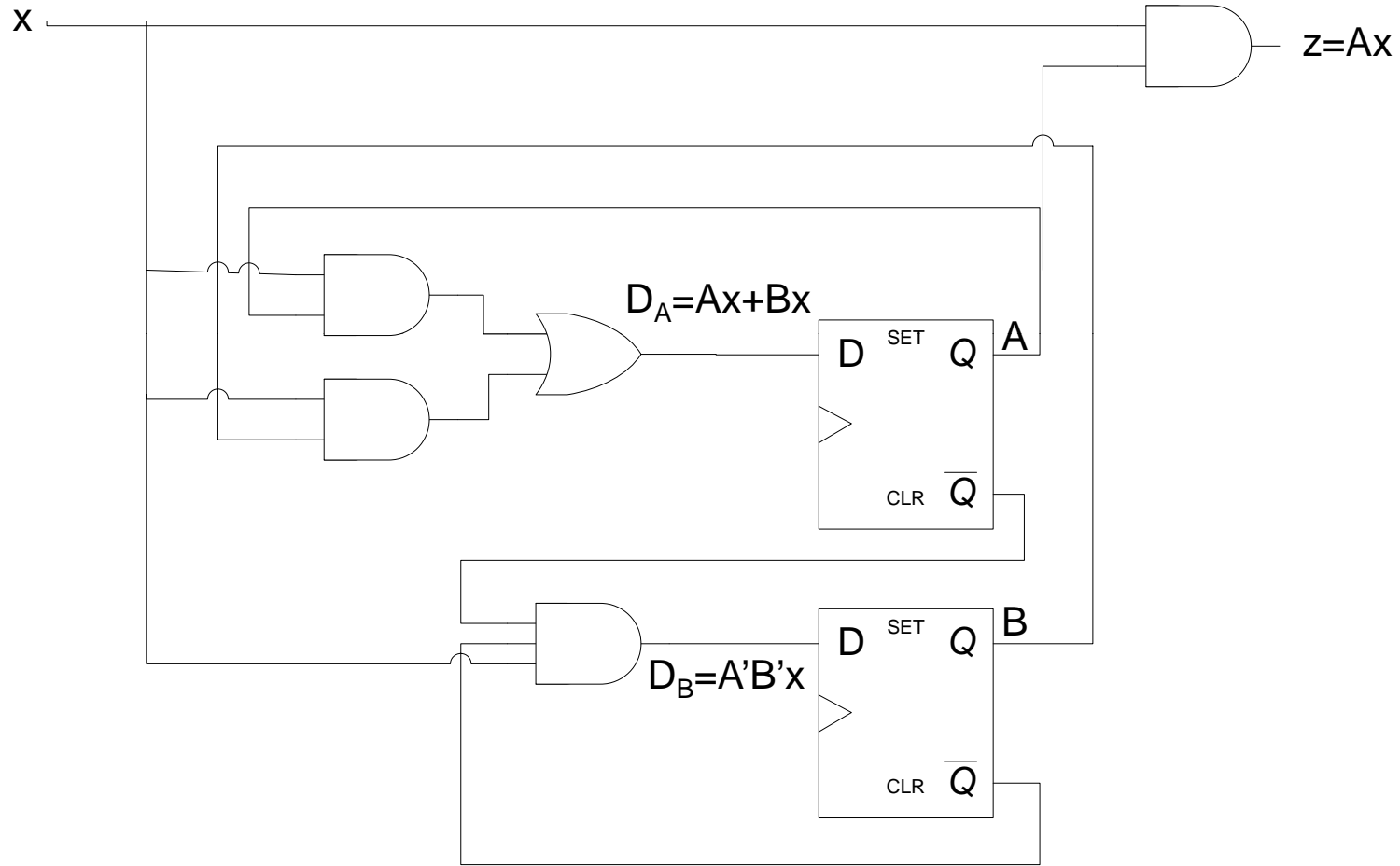



# Circuit, State Diagram, State Table


**Example:** Show the state diagram of following circuit

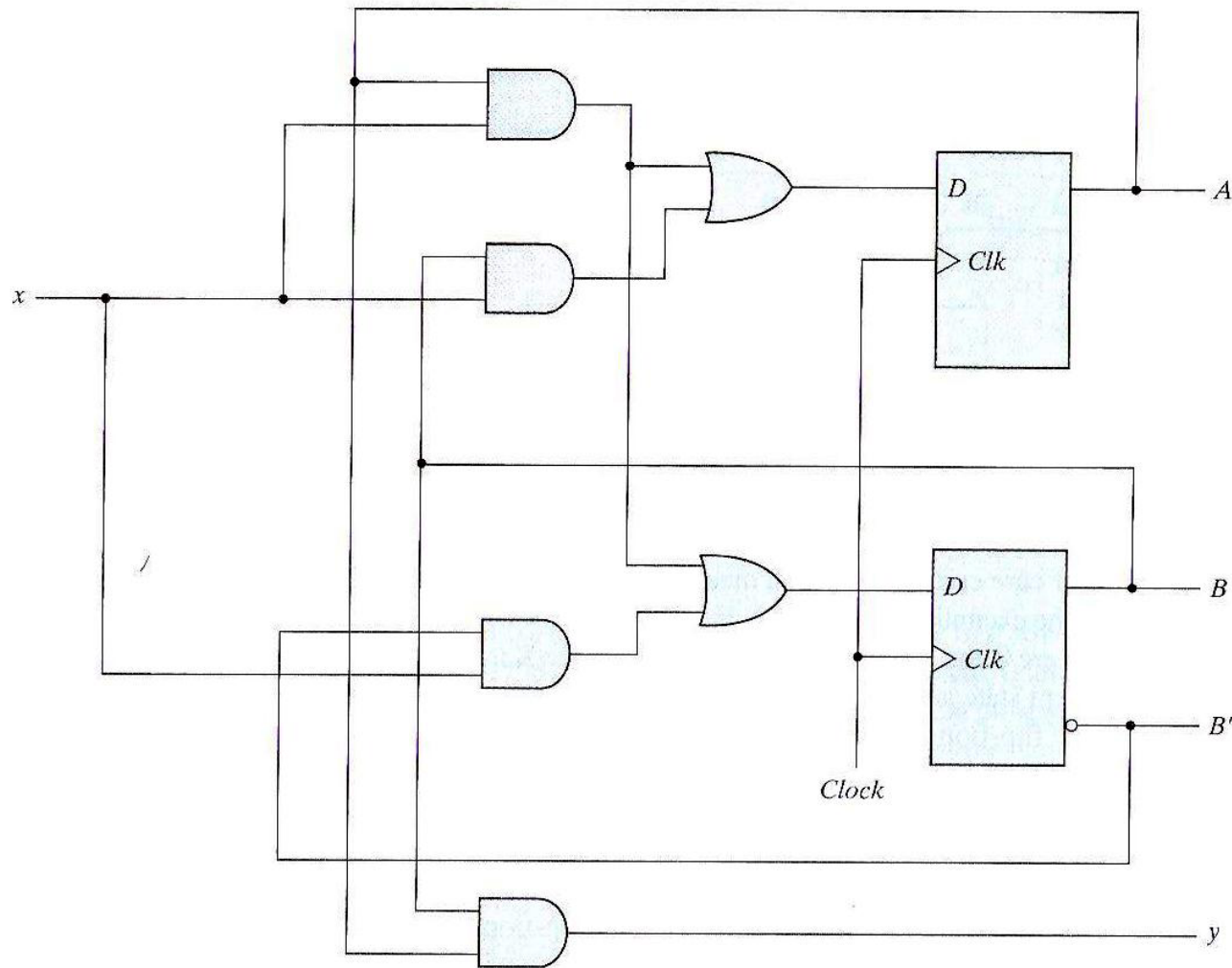


**FIGURE 5.29**  
Logic diagram of sequence detector

# Circuit, State Diagram, State Table

**Example:** Show the state diagram of following circuit

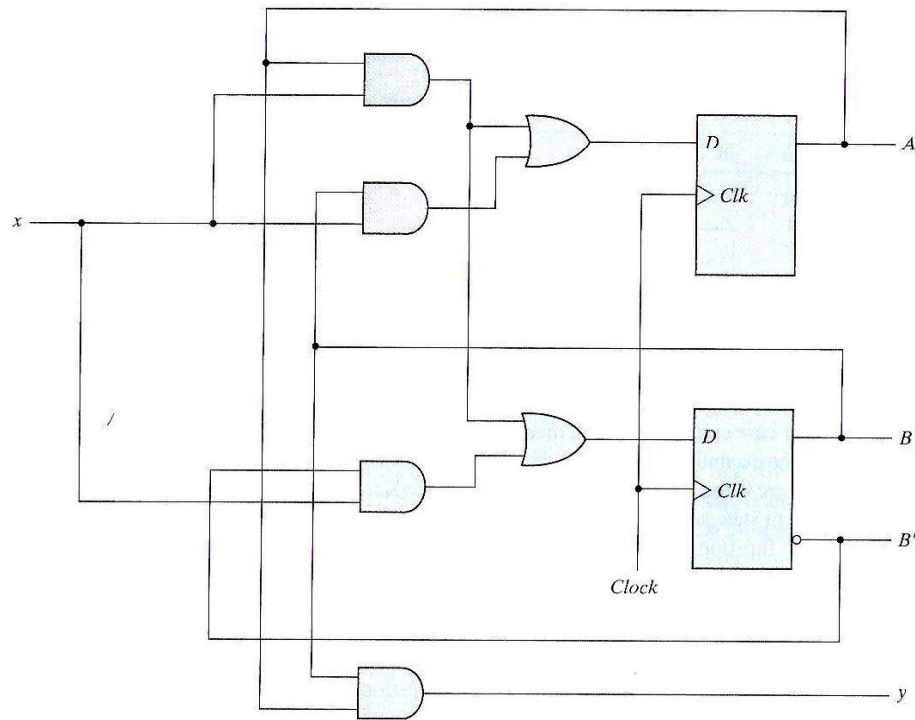

**FIGURE 5.29**  
Logic diagram of sequence detector

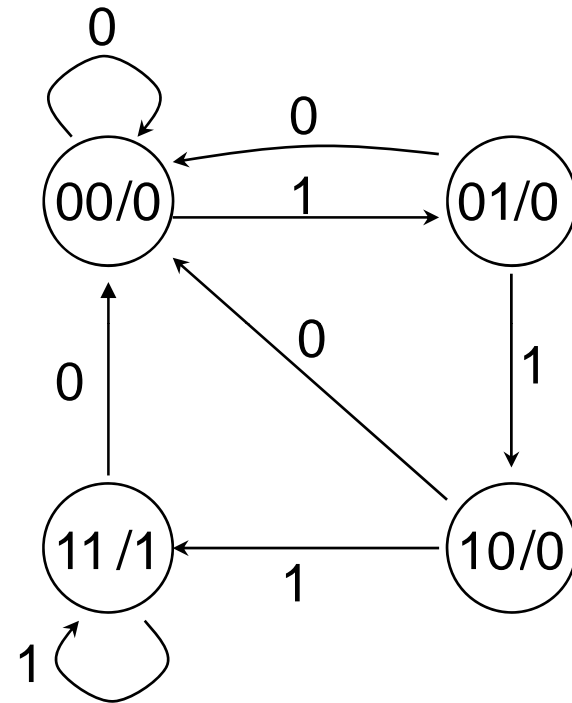


$$y = AB$$

$$D_A = Ax + Bx$$


$$D_B = Ax + B'x$$

# Circuit, State Diagram, State Table

**Example:** Show the second form truth table

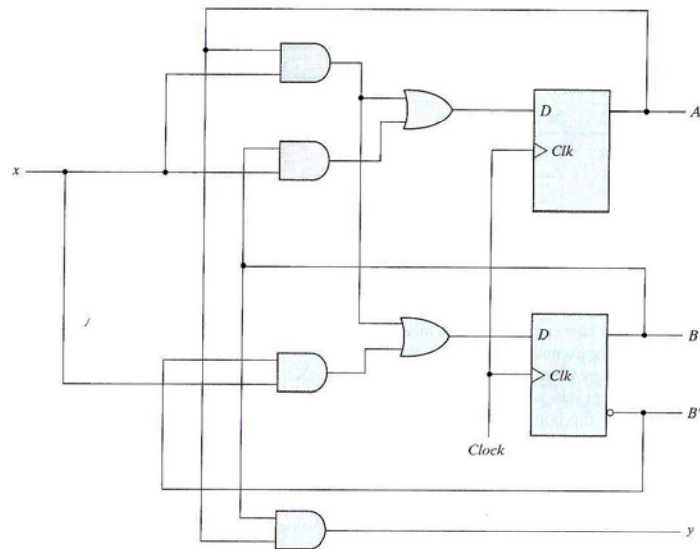

**FIGURE 5.29**  
Logic diagram of sequence detector

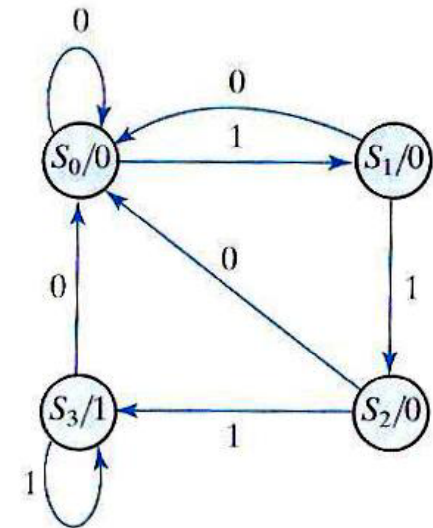

**FIGURE 5.27**  
State diagram for sequence detector

## From circuit (equations)

$$y = AB$$

$$D_A = Ax + Bx$$

$$D_B = Ax + B'x$$


x: input, y: output

A, B: present state

$D_A, D_B$ : next state (D-FF)

Present State		Next State				Output
		x = 0		x = 1		
A	B	A	B	A	B	y
		0	0	0	1	0
		0	0	1	0	0
		0	0	1	1	0
		0	0	1	1	1


From state diagram

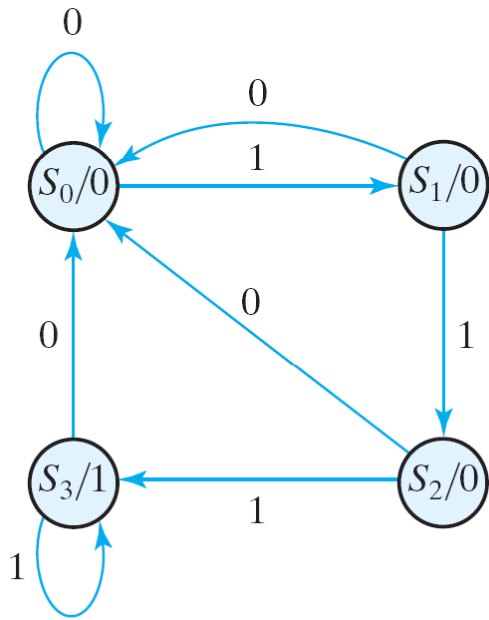

Present State		Next State				Output
		$x = 0$		$x = 1$		
<i>A</i>	<i>B</i>	<i>A</i>	<i>B</i>	<i>A</i>	<i>B</i>	<i>Y</i>
		0	0	0	1	0
		0	0	1	0	0
		0	0	1	1	0
		0	0	1	1	1

# Circuit, State Diagram, State Table

**More Example:** Binary Counter – show state diagram and table

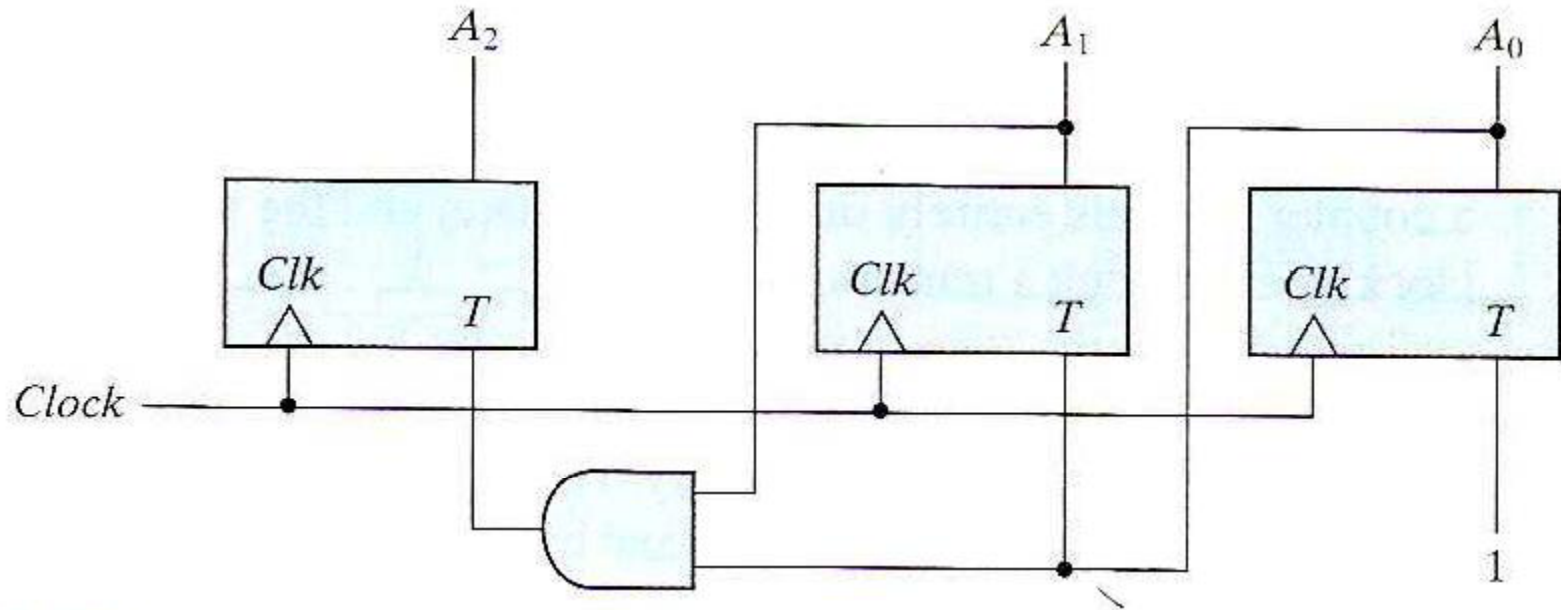


**FIGURE 5.34**

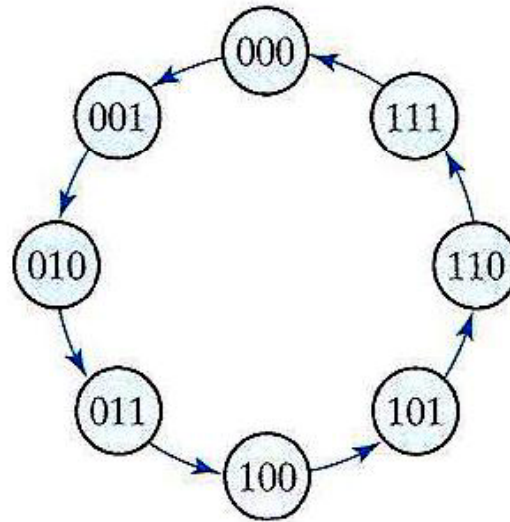Logic diagram of three-bit binary counter


# Circuit, State Diagram, State Table

**More Example:** Binary Counter – show state diagram and table



present state			next state		
$A_2$	$A_1$	$A_0$	$A_2$	$A_1$	$A_0$
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	0

**FIGURE 5.32**  
State diagram of three-bit binary counter

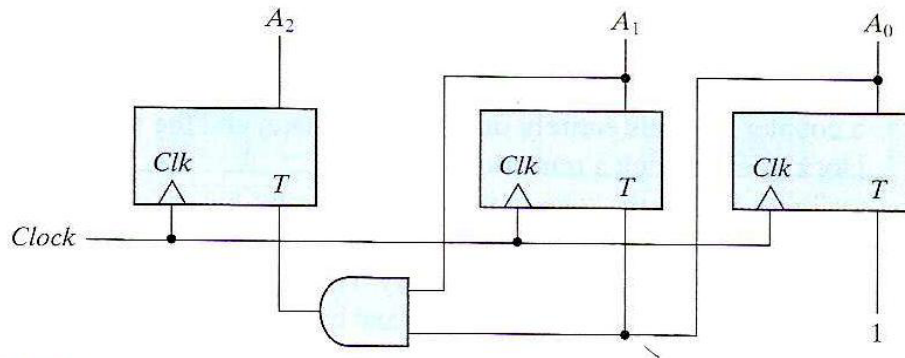


**FIGURE 5.34**  
Logic diagram of three-bit binary counter

# Circuit, State Diagram, State Table
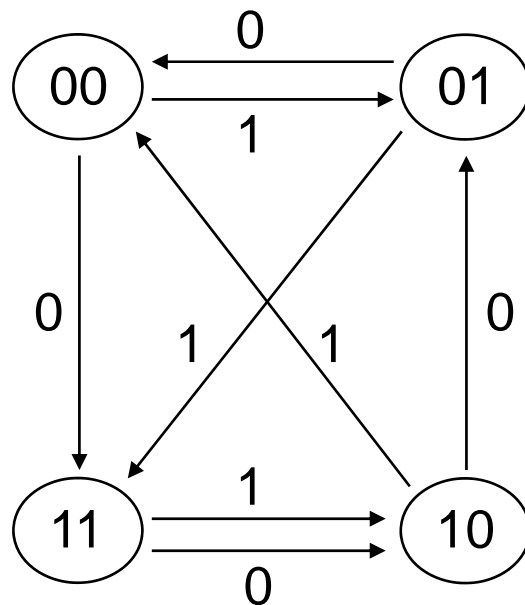
## More Example: Word Problem

Design a 2-bit complex counter with one input  $x$  that can be

- a down counter when  $x=0$  ( $\dots \rightarrow 11 \rightarrow 10 \rightarrow 01 \rightarrow 00 \rightarrow 11 \rightarrow \dots$ )
- a Johnson counter when  $x=1$  ( $\dots \rightarrow 00 \rightarrow 01 \rightarrow 11 \rightarrow 10 \rightarrow 00 \rightarrow \dots$ )



present state	next state	
	$x=0$	$x=1$
A B	A B	A B
0 0	1 1	0 1
0 1	0 0	1 1
1 0	0 1	0 0
1 1	1 0	1 0



present state	next state	
	x=0	x=1
A B	A B	A B
0 0	1 1	0 1
0 1	0 0	1 1
1 0	0 1	0 0
1 1	1 0	1 0

$D_A$


		AB			
		00	01	11	10
x	0	1	0	1	0
	1	0	1	1	0

$$D_A = AB + Bx + A'B'x'$$

$D_B$

		AB			
		00	01	11	10
x	0	1	0	0	1
	1	1	1	0	0

$$D_B = B'x' + A'x$$

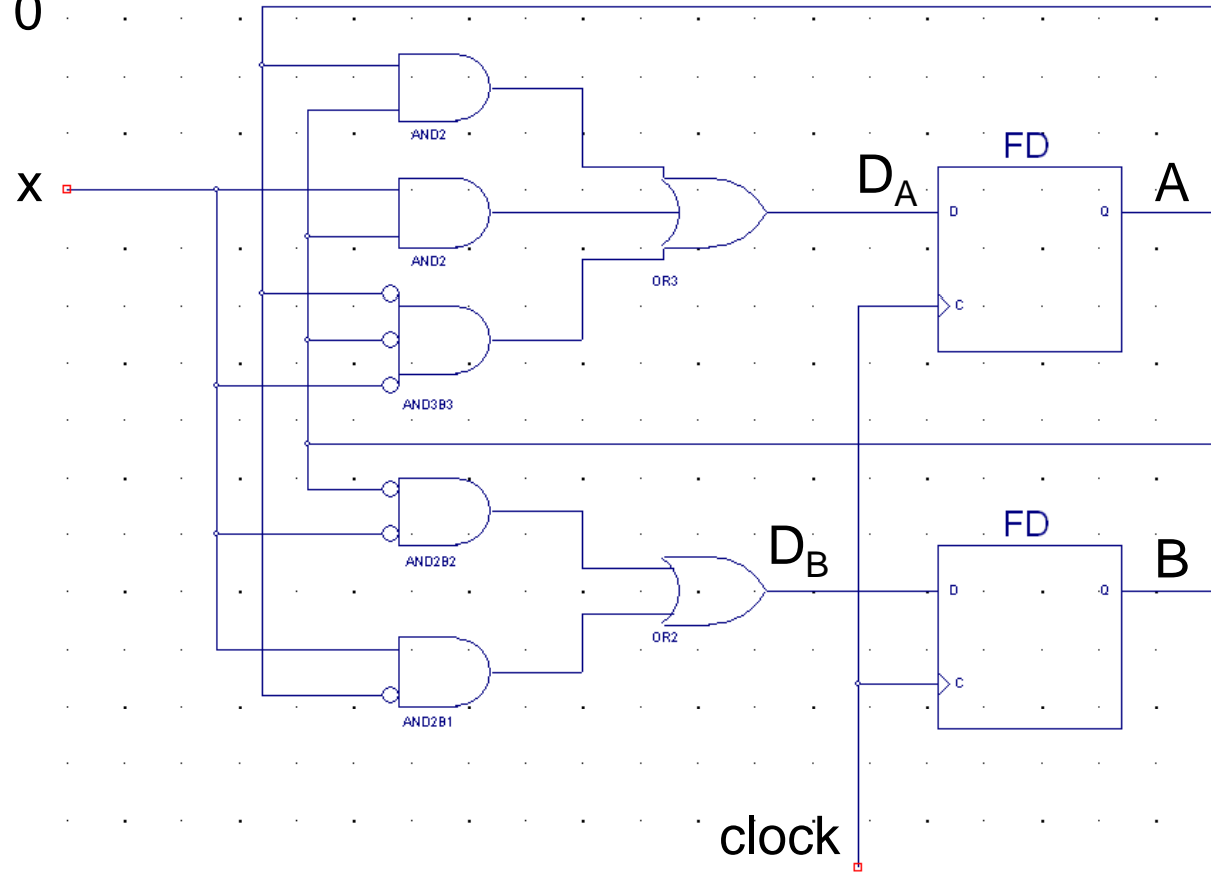

# Circuit, State Diagram, State Table

Quiz:

[http://www.eelab.usyd.edu.au/digital\\_tutorial/part3/t-diag.htm](http://www.eelab.usyd.edu.au/digital_tutorial/part3/t-diag.htm)

# Circuit, State Diagram, State Table

Quiz: solution

[http://www.eelab.usyd.edu.au/digital\\_tutorial/part3/t-diag.htm](http://www.eelab.usyd.edu.au/digital_tutorial/part3/t-diag.htm)

# Circuit, State Diagram, State Table

More Example:

[http://www.eelab.usyd.edu.au/digital\\_tutorial/part3/example1-1.htm](http://www.eelab.usyd.edu.au/digital_tutorial/part3/example1-1.htm)