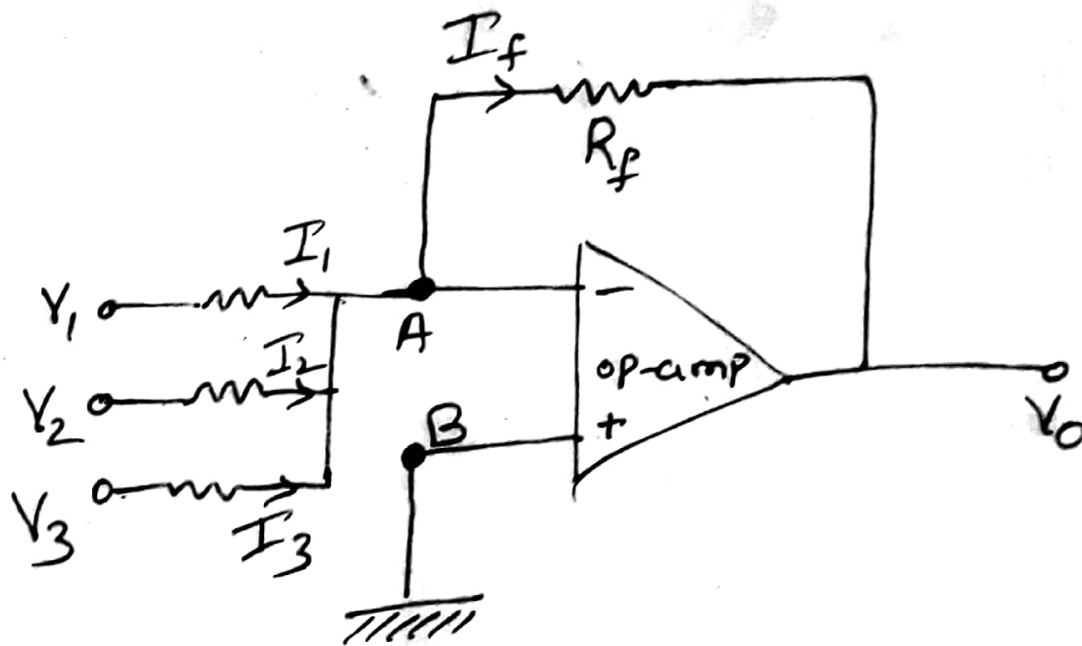


Inverting Summing Amplifier:-

→ In this ckt all the input voltage to be added are applied to the inverting terminal of the op-amp



As node B is grounded

Due to virtual ground concept, the node A is also at virtual ground potential

$$V_A = V_B = 0$$

→ Applying KCL at node A

$$I_1 + I_2 + I_3 = I_f$$

(2)

$$\frac{V_1 - V_A}{R_1} + \frac{V_2 - V_A}{R_2} + \frac{V_3 - V_A}{R_3} = \frac{V_A - V_0}{R_f}$$

Due to virtual ground concept

voltage at node "A" is zero potential

i.e. $V_A = 0$ substituting this in above equation

$$\frac{(V_1 - 0)}{R_1} + \frac{(V_2 - 0)}{R_2} + \frac{(V_3 - 0)}{R_3} = \frac{0 - V_0}{R_f}$$

$$V_0 = - \left[\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right]$$

if $R_f = R_1 = R_2 = R_3$


then o/p will be

$$V_0 = - [V_1 + V_2 + V_3]$$

∴ The o/p will be -ve of the sum of the i/p's. so it is called Inverting summer


Non-Inverting Summing Amplifier :- (3)

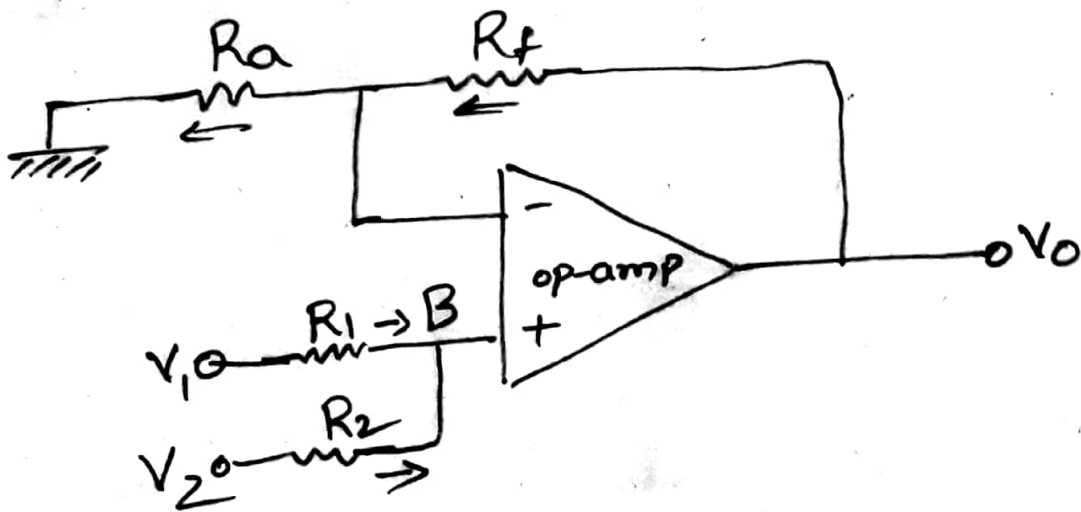In this ckt all the i/p voltage to be added are to be applied to the non-inverting amp of an op-amp.



To obtain an expression for o/p voltage make use of superposition theorem

① Consider V_1 only make $V_2 = 0$:-

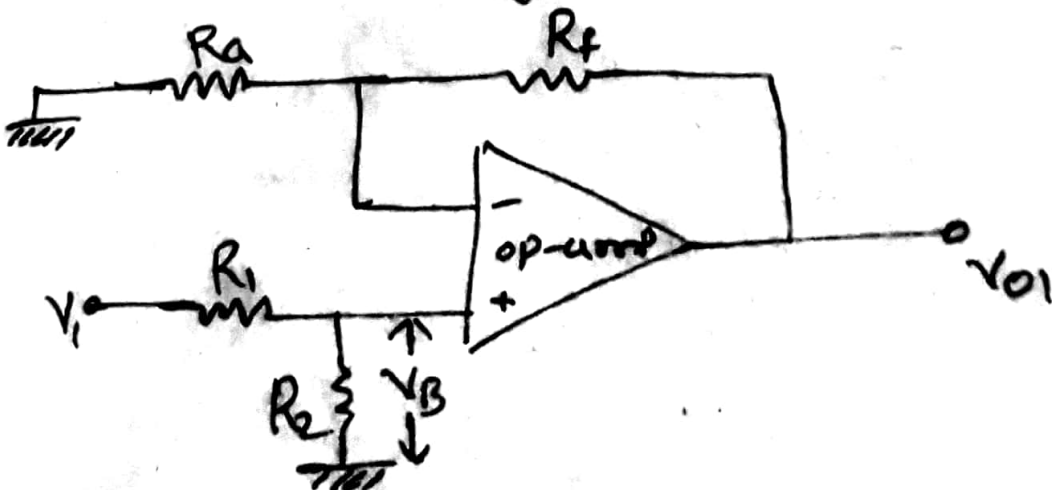

When $V_2 = 0$


$$V_B = \frac{R_2}{R_1 + R_2} V_1$$

O/P voltage for Non-inverting amp given by

$$V_{O1} = \left[1 + \frac{R_f}{R_a} \right] V_B$$

$$V_{O1} = \left[1 + \frac{R_f}{R_a} \right] \frac{R_2}{R_1 + R_2} V_1 \quad \text{--- (1)}$$

(2) If $V_1 = 0$

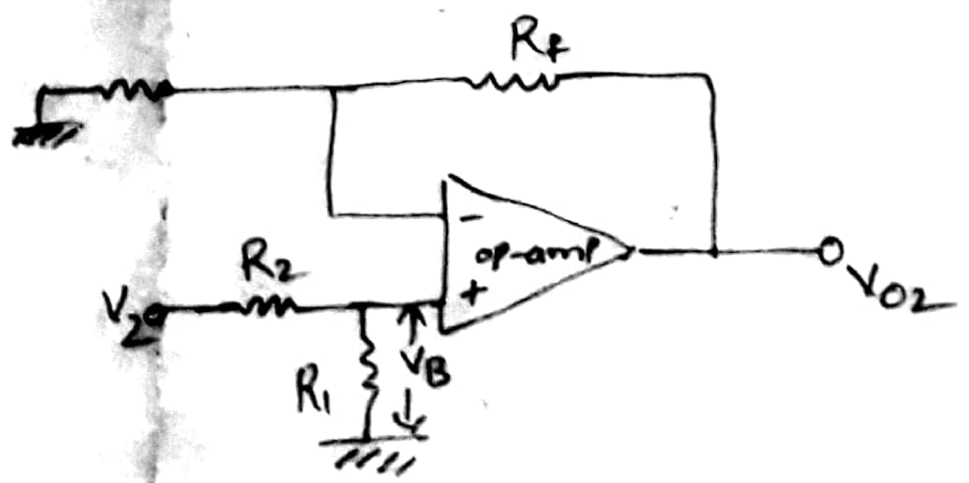

By using voltage division rule voltage at node 'B' is given by

$$V_B = \left[\frac{R_1}{R_1 + R_2} \right] V_2$$

O/P voltage for non-inverting amp)

$$V_{O2} = \left[1 + \frac{R_f}{R_a} \right] V_B$$

$$V_{O2} = \left[1 + \frac{R_f}{R_a} \right] \left[\frac{R_1}{R_1 + R_2} \right] V_2 \quad \text{--- (2)}$$

By superposition theorem
we have

$$V_o = V_{O1} + V_{O2} \quad \text{--- (3)}$$

sub eq (1) & (2) in (3) we get

$$V_o = \left[1 + \frac{R_f}{R_a} \right] \left[\frac{R_2}{R_1 + R_2} \right] V_1 + \left[\frac{R_1}{R_1 + R_2} \right] V_2$$

If we have $R = R_1 = R_2$ then

$$V_o = \left[1 + \frac{R_f}{R_a} \right] \left[\frac{V_1 + V_2}{2} \right]$$

This is required o/p of a Summing ⁽⁶⁾
amp for $R_f = 0$ & $R_1 = R_2 = R$ we have

$$V_o = \frac{V_1 + V_2}{2}$$

||

For four i/p summing ckt, the o/p
voltage given by

$$V_o = \frac{V_1 + V_2 + V_3 + V_4}{4}$$