

Unit - 3

①

1) What is attenuator? and what type elements are used in attenuator and why?

Ans → An attenuator is a two-port network and is used to reduce the signal level by a given amount. It is necessary to introduce a specified loss between source and a matched load without altering impedance relationship. In attenuators only resistances are used to reduce signal strength. Attenuation is always expressed in dB or Neper.

$$\text{Attenuation in dB} = 10 \log_{10} \left(\frac{P_1}{P_2} \right)$$


where P_1 is i/p power P_2 is o/p power

$$\text{or dB} = 20 \log \frac{V_1}{V_2}$$

$$\frac{V_1}{V_2} = \frac{I_1}{I_2} = N$$

$$\text{so } \Rightarrow N = \text{antilog}_{10} \left(\frac{\text{dB}}{20} \right)$$

2) Write different types of attenuators

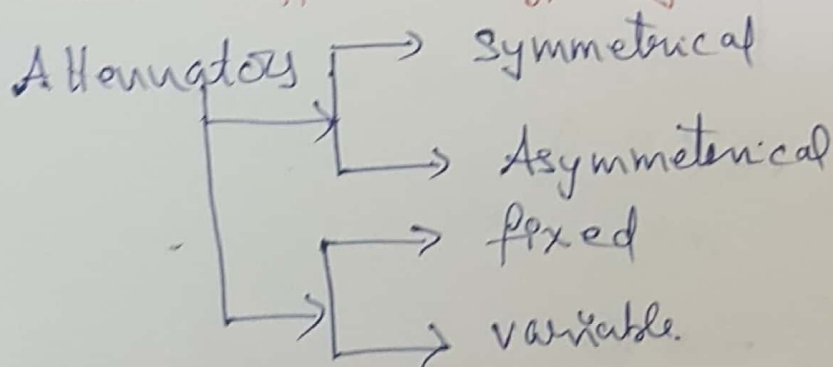

A fixed attenuator with constant attenuation is called 'pad'

Variable attenuators are used in volume control circuits

3) Write any four applications of attenuator. Write Network


Ans → ① Fixed attenuator are called pad. They are used to introduce fixed attenuation factor in the n/w. Generally to measuring high voltage or current we use attenuator at front end.

② Variable attenuator are used in volume control, ^{Automatic control.} gain circuits

③ In communication networks like radio broadcasting, telephone sections

④ In laboratory to obtain small value of voltage or current for testing circuits

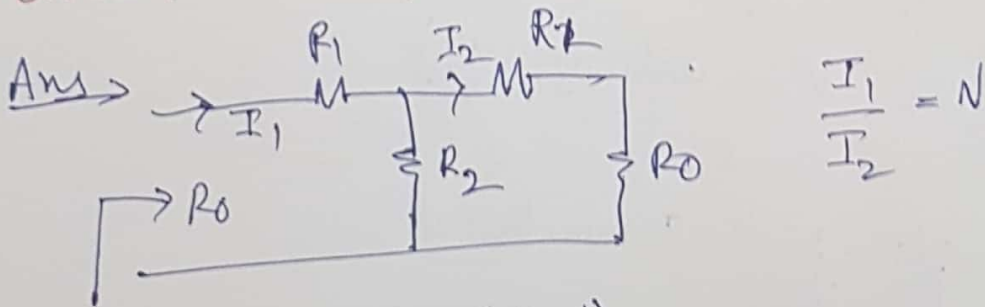4) Write the T-type symmetrical attenuator with circuit and formulae for R_1 & R_2 (design resistance)




$$\frac{I_1}{I_2} = N$$

$$R_1 = \frac{R_0 (N-1)}{N+1}$$

$$R_2 = \frac{2 N R_0}{N^2 - 1}$$

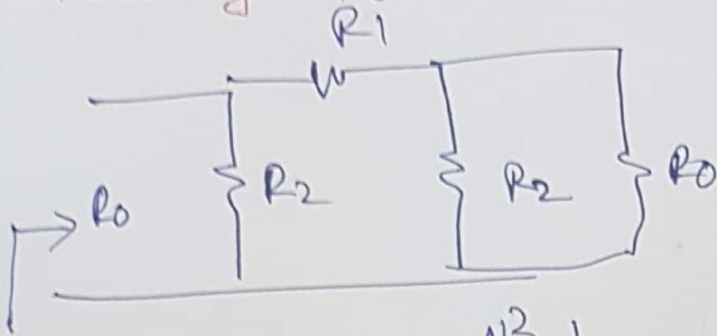Write π -type Symmetrical attenuator network with design resistance R_1 & R_2 values in terms of R_0 & N



$$R_1 = R_0 \frac{N^2 - 1}{2N}$$

$$R_2 = R_0 \frac{(N+1)}{(N-1)}$$

Wkt for π Sym N/w

$$R_1 = R_0 \sinh \alpha$$

$$R_2 = R_0 \coth \alpha/2$$

$$e^\alpha = \frac{I_1}{I_2} = N$$

(6) Design π -type attenuator to give 20 dB attenuation and to have the impedance R_0 of 100 Ω

Ans \rightarrow given $R_0 = 100 \Omega$

$$D \text{ Att dB} = 20 \text{ dB}$$

$$N = \text{Antilog} \frac{D}{20} = \text{Antilog} \frac{20}{20}$$


$$= 10$$

$$R_1 = R_0 (N^2 - 1) / 2N$$

$$= \frac{100 (100 - 1)}{20} = 99 \times 5 = 495 \Omega$$

$$R_2 = \frac{R_0 (N+1)}{N-1} = \frac{100 \times 11}{9} = 122.22 \Omega$$

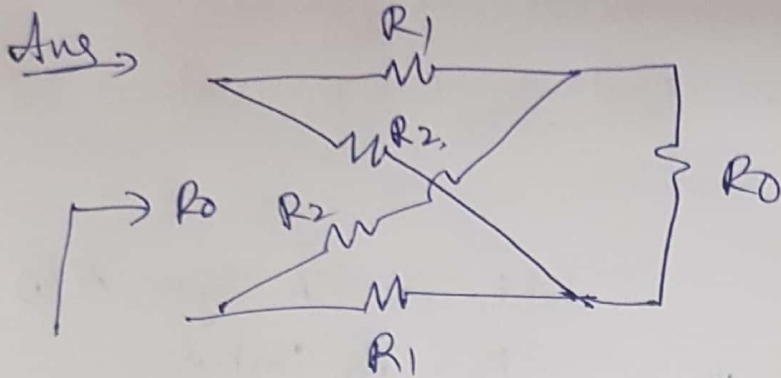(7) Write the Lattice (Symmetrical) attenuator N/w and formulae for series and shunt arm resistances.



Wkt $R_0 = \sqrt{R_1 R_2}$

$$R_1 = R_0 \left(\frac{N-1}{N+1} \right)$$

$$R_2 = R_0 \left(\frac{N+1}{N-1} \right)$$

(8) Design a symmetrical lattice attenuator to have Chg impedance of 800Ω and $D = 20\text{dB}$


Ans → $R_0 = 800\Omega$
 $D = 20\text{dB}$

So $N = \text{Antilog} \frac{20}{20} = 10$

$$R_1 = R_0 \left(\frac{N-1}{N+1} \right) = 800 \left(\frac{9}{11} \right) = 655\Omega$$

$$R_2 = R_0 \left(\frac{N+1}{N-1} \right) = 800 \left(\frac{11}{9} \right) = 978\Omega$$

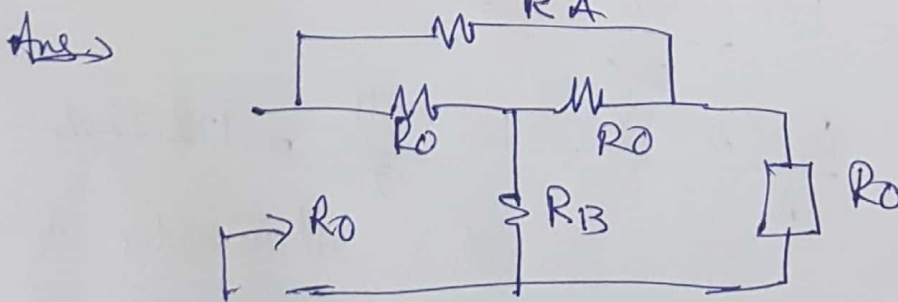(9) Write the Symmetric Bridge T attenuator with design formulae.



$$R_A = R_0 (N-1) \quad \& \quad R_B = \frac{R_0}{N-1}$$

Q) Design a symmetrical bridge T attenuator
 $D = 20$ & $R_0 = 500 \Omega$

Ans \rightarrow $N = \text{Anti log } \frac{D}{20}$
 $= \text{Anti log } \frac{20}{20}$
 $= 10$


$$R_A = R_0 (N-1) = 500 \Omega (10-1)$$

$$= 4500 \Omega$$

$$R_B = \frac{R_0}{N-1} = \frac{500}{(10-1)} = \frac{500}{9}$$

$$= 55.555 \Omega$$

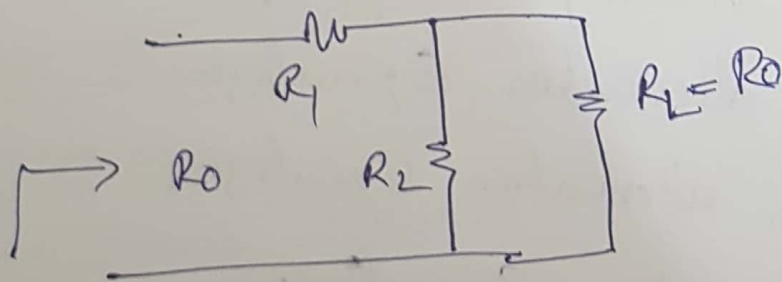11) Write L type (Asymmetrical) attenuator
 and its design formulae



$$R_2 = \frac{R_0}{N-1}$$

$$R_1 = R_0 \left(\frac{N-1}{N} \right)$$

12) Design L-type attenuator with load resistance
 of 600Ω with an attenuator of 20 dB

Ans →

$$\text{Given } R_L = R_0 = 600 \Omega \quad \times D = 20 \quad (6)$$

$$N = \text{Anti}(\log \left(\frac{D}{20} \right))$$

$$= 10$$

$$R_1 = R_0 \left(\frac{N-1}{N} \right) = 600 \left(\frac{10-1}{10} \right) = 60 \times 9 = 540 \Omega$$

$$R_2 = \frac{R_0}{N-1} = \frac{600}{9} = 66.66 \Omega$$

13) What is Equalizer? ^{write} Different type of Equalizers.

Ans → Equalizers are network designed to provide compensation against distortions that occur in a signal while passing through an electrical network. Different distortion occur are amplitude distortion, frequency distortion and phase (delay distortion). So there are mainly three types of Equalizers.

1) Amplitude attenuation Equalizer

2) Frequency attenuation Equalizer

3) Phase distortion Equalizer

14) Write any four applications of Equalizer Networks


Ans → ① medium and high freq carrier telephone

Systems ② Amplifiers, transmission lines

③ Speech reproduction Systems.

④ Phase distortion Equalizers are used in phase distortion network

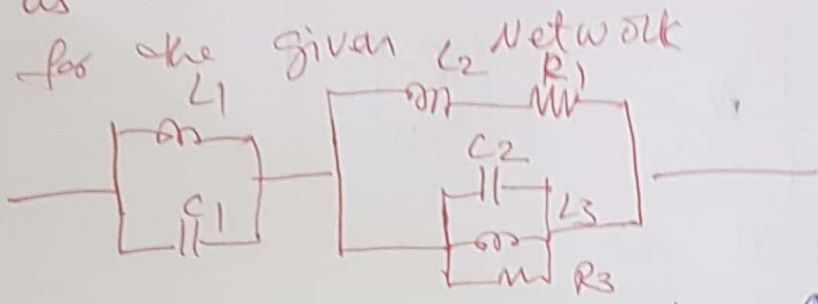What is inverse network, obtain the inverse network for the given network




Ans -> The geometrical mean of two impedances $Z_1 \times Z_2$ is a real number and they said to inverse if

$$Z_1 Z_2 = R_0^2$$

$$Z_1 Z_2 = \frac{j\omega L}{j\omega C} = \frac{L}{C}$$

For given n/w

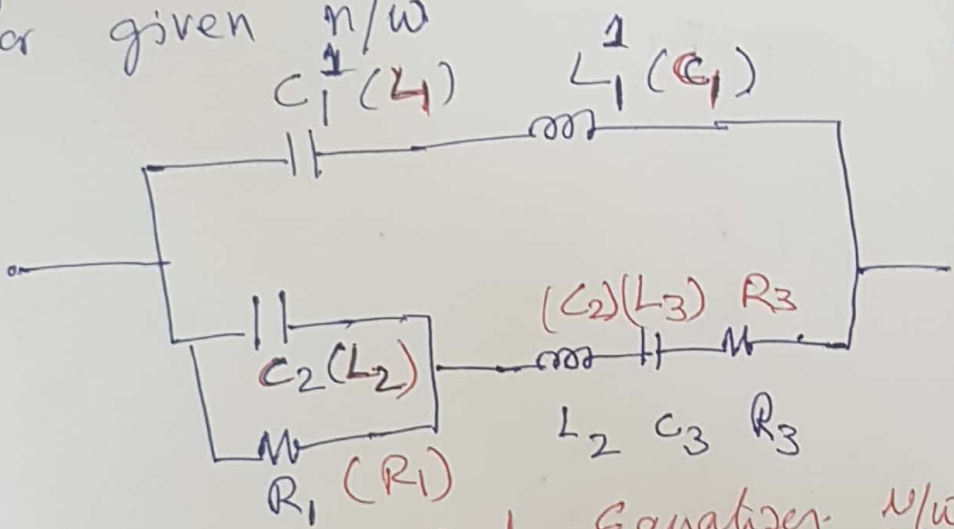


R - given
Y/P value

B - converted values

1) Write two terminal Equatizer. n/w along with design formulae


Series equalizer

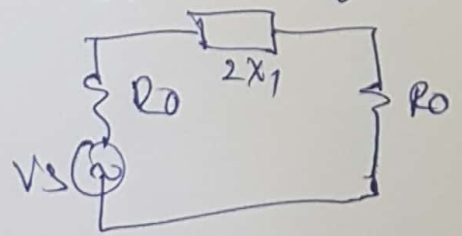

$$N = \frac{P_i}{P_o} = \frac{P_o}{P_L}$$

$$N = \text{Antilog } \frac{P}{20}$$

Shunt equalizer

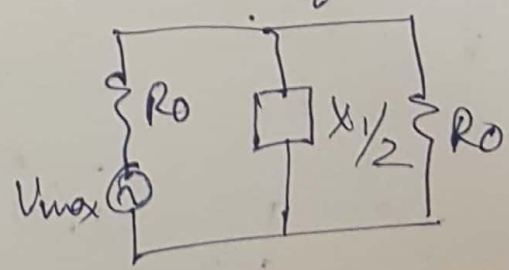

$$N = 1 + \frac{X^2}{R_0^2}$$


for series equalizer (two terminal)

Shunt (two terminal) Equalizer

(8)

$$N = 1 + \left(\frac{R_0}{X_1} \right)^2$$

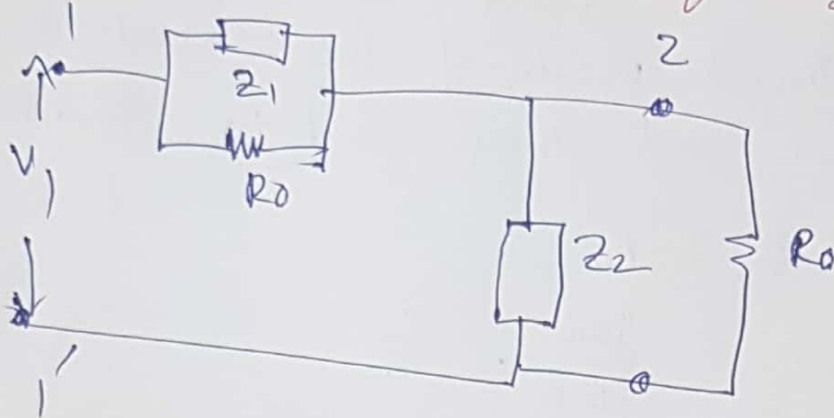17) Write Full Series Equalizer with formulae



$$N = 1 + \left(\frac{R_0}{X_2} \right)^2$$


$$Z_1 Z_2 = R_0^2$$

$$\frac{L}{C}$$

$$N = 1 + \frac{R_0^2}{\omega^2 Z_1^2}$$

if $Z_1 = \text{inductor}$
 $Z_2 = \text{capacitor}$

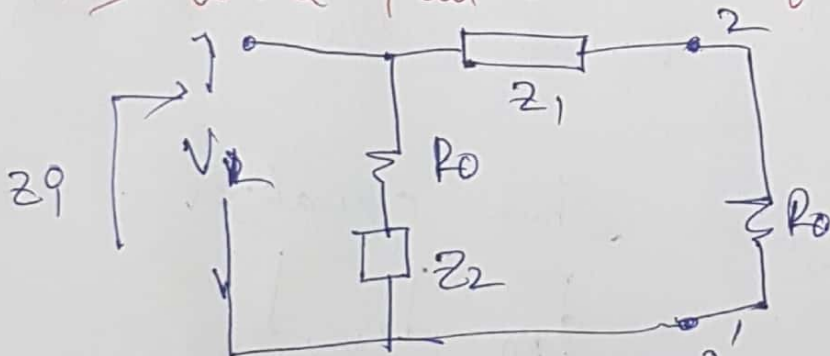18) Write full shunt equalizer with design formulae



$$N = 1 + \frac{R_0^2}{X_0^2}$$

