

UNIT - I

Network:- A N/w is interconnection of diff electrical components in any manner.

Classification of Networks:-

1. Active & passive N/w
2. Linear & Non-linear N/w
3. Unilateral & Bi-lateral N/w
4. Symmetrical & Asymmetrical N/w
5. Lumped & Distributed N/w
6. Recurrent & Non-recurrent N/w
7. Balanced & Unbalanced N/w.

1) Active N/w:- A N/w which consists sources of energy or A N/w which consists active elements like diodes & transistors etc.

passive N/w:- A N/w which consist only passive elements like R, L, C is called a passive N/w.

2) Linear & Non-linear N/w:-

- A N/w which consists only linear elements is called a linear N/w

ex: pure RLC N/w

["Elements which obey Ohm's law are called "Linear" elements"] (ex: RLC)

- A N/W which consists non-linear elements like diodes, transistors etc is called non-linear N/W.

3) Unilateral & Bi-lateral N/W:-

- If the magnitude of the current is same after changing the polarity of the battery then such elements are called "Bilateral elements". (ex: RLC)


- otherwise the elements are called "Unilateral elements". (ex: diode, transistors etc)

- The N/W which consists only bilateral elements is called "Bilateral N/W" & otherwise Unilateral N/W.


* 4) Symmetrical & Asymmetrical N/W:-

- A symmetrical N/W is a N/W in which the electrical properties doesn't change after interchanging its i/p & o/p terminals is "Symmetrical N/W" otherwise the N/W is "Asymmetrical N/W".

Examples of Symmetrical N/W:

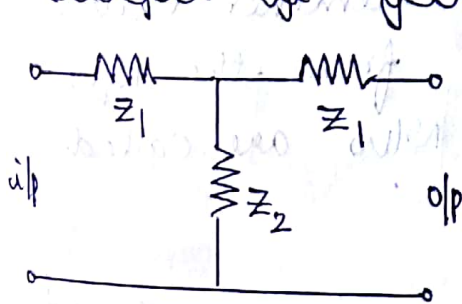


Symmetrical T-type

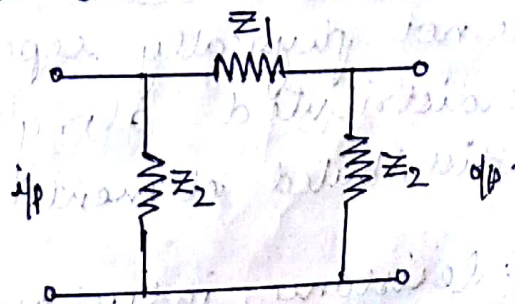


Symmetrical π -type



examples of asymmetrical N/w's :-

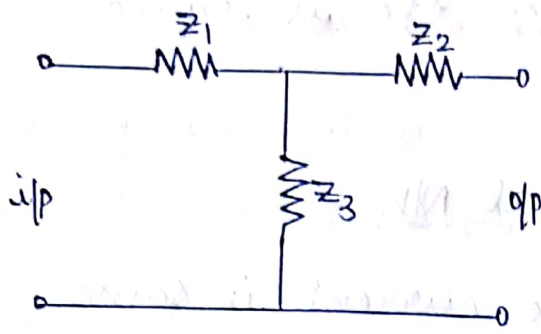

asymmetrical T-type

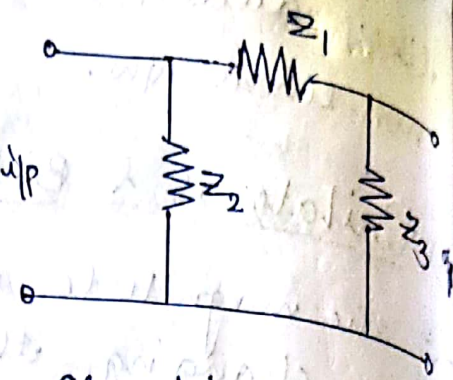

asymmetrical π -type

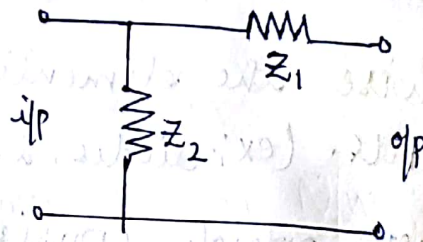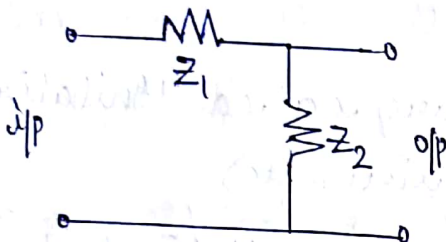

asymmetrical L-type.

5) Lumped & Distributed N/w's :-

- Lumped Elements:- An element which is physically separable from the N/w is called lumped element.

ex: discrete R, L, C components, diodes, transistors


- Distributed Elements:- The elements which are not physically separable from the N/w & distributed along the N/w are called distributed elements.

ex: Resistance, inductance & capacitance offered by a transmission line.

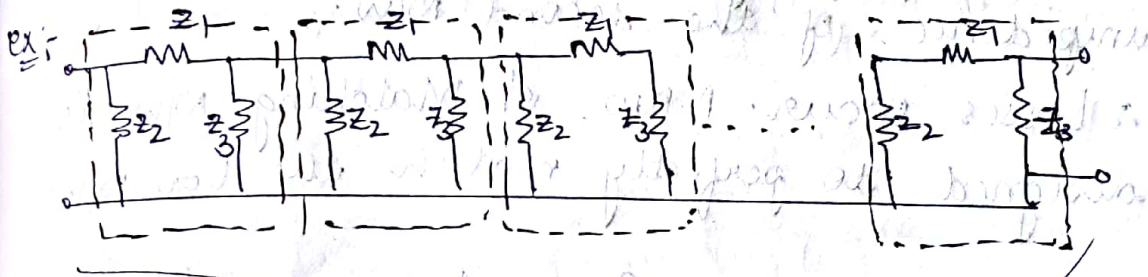
6) Recurrent & Non-Recurrent N/W:-

(cascaded) or (ladder)

- When a large ckt consists similar N/Ws connected in series one after the other, then the N/W is called recurrent N/W otherwise it is non-recurrent N/W.



Recurrent N/W.

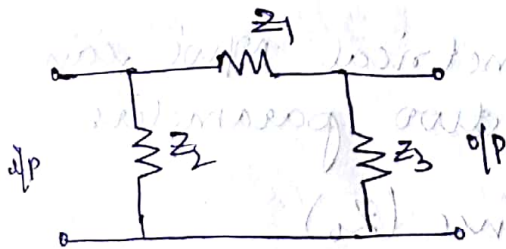

Non-recurrent N/W [only single N/W]

ex/for

Functional classification of N/W:-

Depending on the purpose for which a N/W is designed, N/Ws are classified into 4 types:-

1. Filters:- (unit-2): It is a N/W which allows a req'd (desired) frequencies & blocks the other frequencies.

2. Attenuators:- It is a N/W designed to reduce the i/p voltage by req'd amount (whatever may be the i/p frequency).

3) Equalizer:- It is a NW designed to counteract the (to regain the losses) attenuation & phase distortion occurred.

4) Matching NW:- At high frequencies reflection takes place if o/p impedance of the first NW is not perfectly matched with the i/p impedance of the second NW.


∴ Losses occur. Now, A Matching NW is designed to perfectly match the two NWs.

Properties of Symmetrical NWs:-

The properties of Symmetrical NWs can be described using two parameters

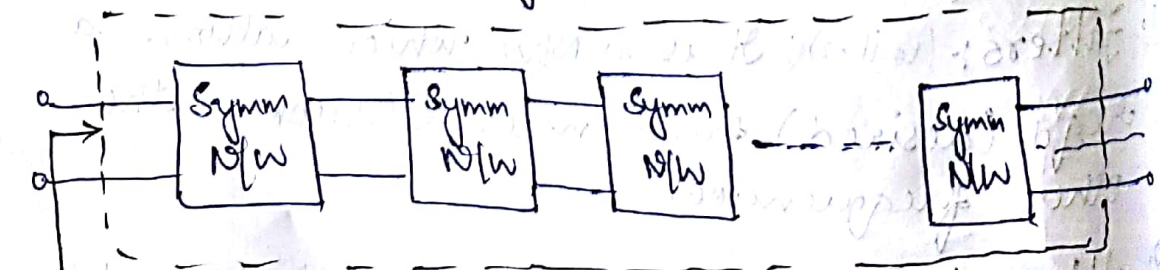- i) Characteristic Impedance (Z_0)
- ii) Propagation Constant (ρ or γ)

① Characteristic Impedance:- If infinite no. of symmetrical NWs cascaded, then the i/p impedance of first symmetrical NW is "characteristic Impedance".




$Z_{i/p} = Z_0$


Infinite Symm. Cascade NW

(or)

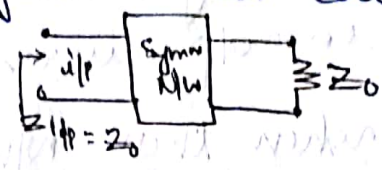→ The unique impedance of the Symm. N/W for which i/p impedance of the N/W becomes the load impedance is called "characteristic impedance Z_0 ".




properties of Z_0 :

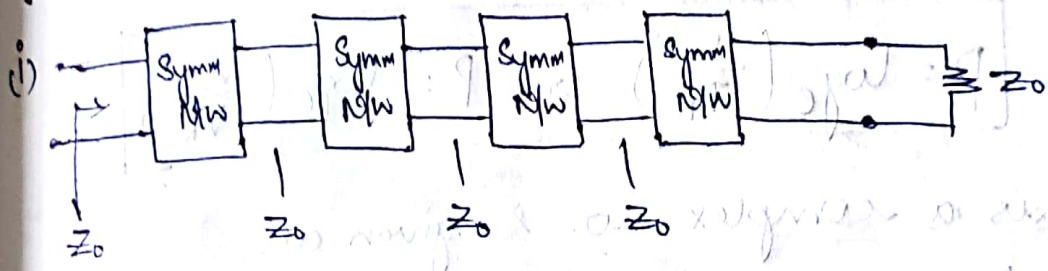

If finite no. of similar symmetrical N/W are cascaded & if last N/W terminated by Z_0 (characteristic impedance) then the impedance looking into any N/W is ' Z_0 '.

units:- ohms

② propagation constant (ρ or γ):

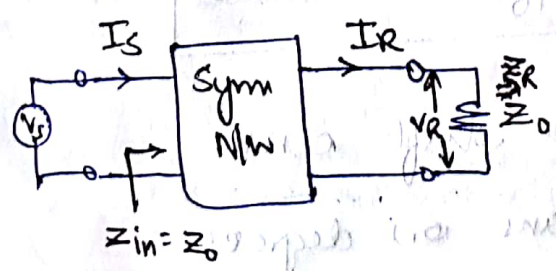

$$V_S = I_S Z_{in} \Rightarrow V_S = I_S Z_0$$

$$V_R = I_R Z_R \Rightarrow V_R = I_R Z_0$$

$$\frac{V_S}{V_R} = \frac{I_S}{I_R}$$

* propagation constant of a symm. NW is defined as the natural logarithm of ratio of input current to o/p current or i/p voltage to o/p voltage when then NW is terminated by 'Z₀'

$$P = \log_e \left(\frac{I_s}{I_R} \right) \text{ or } P = \log_e \left(\frac{V_s}{V_R} \right)$$

'P' is a complex no. & given as:

$$P = \alpha + j\beta$$

$$e^P = \frac{I_s}{I_R}$$


where (α) - attenuation const
units - Nepers or decibels

$$1 \text{ NP} = 20 \log_{10} e = 8.686 \text{ dB}$$

& (β) - phase shift const
units - radians or degrees

$$1 \text{ degree} = \frac{\pi}{180} \text{ rad}$$

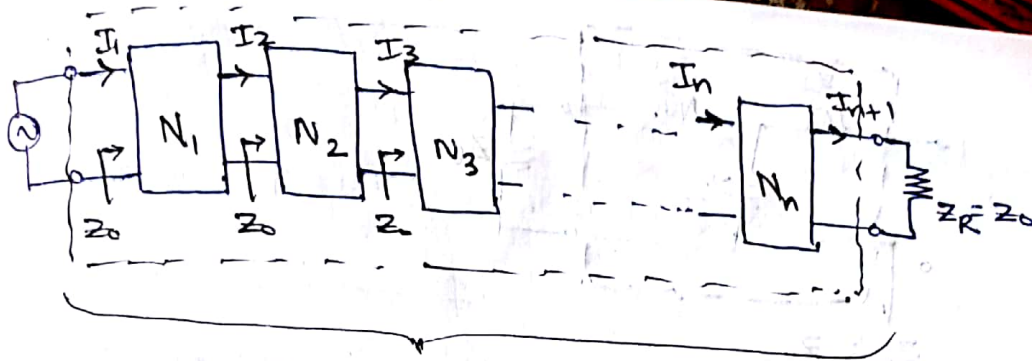→ If 'n' identical symm. NW's are cascaded & last NW is terminated by Z₀ then



n -identical symmetrical N/w's

$$1^{st} \text{ N/w } e^p = \frac{I_1}{I_2}$$

$$2^{nd} \text{ N/w } e^p = \frac{I_2}{I_3}$$

$$n^{th} \text{ N/w } e^p = \frac{I_n}{I_{n+1}}$$

then

$$\frac{I_1}{I_{n+1}} = \frac{I_1}{I_2} \times \frac{I_2}{I_3} \times \frac{I_3}{I_4} \dots \times \frac{I_n}{I_{n+1}}$$


$$= \underbrace{e^p \cdot e^p \cdot e^p \dots e^p}_{n\text{-times}}$$

$$\frac{I_1}{I_{n+1}} = e^{np}$$


$$\ln_e \left(\frac{I_1}{I_{n+1}} \right) = np \Rightarrow p = \frac{1}{n} \log_e \left(\frac{I_1}{I_{n+1}} \right)$$

Analysis of Symmetrical T-N/w :-

standard symmetrical T-N/w:

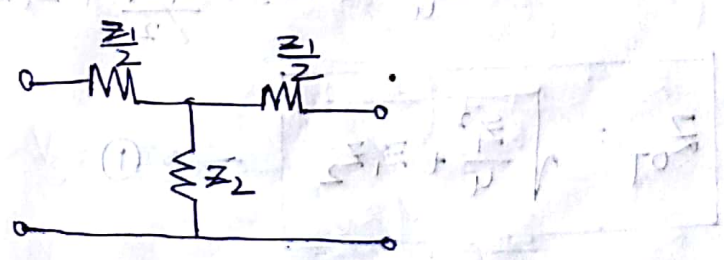

Characteristic Impedance (Z0) :-

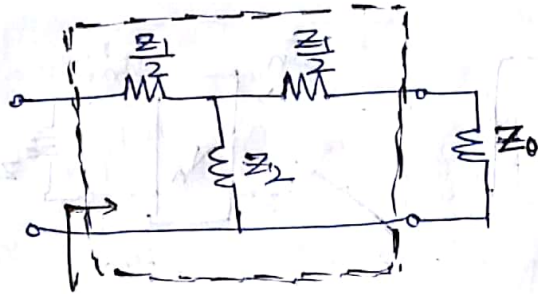

$$Z_{in} = Z_0$$

$$Z_{in} = \frac{Z_1}{2} + \left(\frac{Z_1}{2} + Z_0 \right) \parallel Z_2$$

$$\text{if } Z_R = Z_0 \Rightarrow Z_{in} = Z_0$$

$$Z_0 = \frac{Z_1}{2} + \frac{\left(\frac{Z_1}{2} + Z_0 \right) Z_2}{\frac{Z_1}{2} + Z_2 + Z_0}$$

$$Z_0 = \frac{\frac{Z_1}{2} \left(\frac{Z_1}{2} + Z_2 + Z_0 \right) + \left(\frac{Z_1}{2} + Z_0 \right) Z_2}{\left(\frac{Z_1}{2} + Z_2 + Z_0 \right)}$$


$$Z_0 \left(\frac{Z_1}{2} + Z_2 + Z_0 \right) = \frac{Z_1^2}{4} + \frac{Z_1 Z_2}{2} + \frac{Z_1 Z_0}{2} + \frac{Z_2 Z_0}{2} + Z_0 Z_2$$

$$\Rightarrow \frac{Z_0 Z_1}{2} + \frac{Z_0 Z_2}{2} + Z_0^2 = \frac{Z_1^2}{4} + Z_1 Z_2 + \frac{Z_1 Z_0}{2} + \frac{Z_0 Z_2}{2}$$

$$Z_{0T} = \sqrt{\frac{Z_1^2}{4} + Z_1 Z_2} \rightarrow \textcircled{1}$$

i) propagation Constant (p):-

W.K.T.
$$e^p = \frac{I_s}{I_R}$$

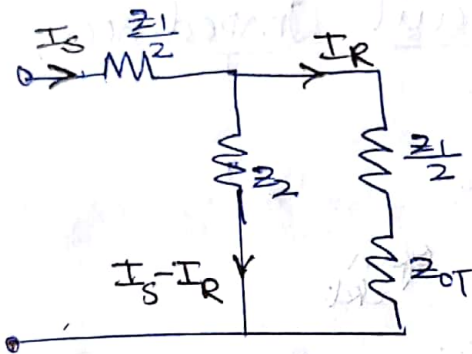

from the above fig

$$(I_s - I_R) Z_2 = \left(\frac{Z_1}{2} + Z_{OT} \right) I_R$$

$$I_s Z_2 = \left(\frac{Z_1}{2} + Z_{OT} + Z_2 \right) I_R$$

$$\frac{I_s}{I_R} = e^p = \frac{\frac{Z_1}{2} + Z_{OT} + Z_2}{Z_2}$$

$$\frac{I_s}{I_R} = e^p = \frac{Z_1}{2Z_2} + \frac{Z_{OT}}{Z_2} + 1$$

$$e^p = 1 + \frac{Z_1}{2Z_2} + \frac{Z_{OT}}{Z_2} \rightarrow (2a)$$

sub eq(1) in (2a)

$$e^p = 1 + \frac{Z_1}{2Z_2} + \frac{\sqrt{\frac{Z_1^2}{4} + Z_1 Z_2}}{Z_2}$$

$$e^p = 1 + \frac{Z_1}{2Z_2} + \frac{\sqrt{\frac{Z_1^2}{4Z_2^2} + \frac{Z_1 Z_2}{Z_2^2}}}{1}$$

$$e^p = 1 + \frac{z_1}{2z_2} + \sqrt{\frac{z_1}{z_2} \left[1 + \frac{z_1}{4z_2} \right]} \rightarrow (2b)$$

(iii) Open & Short Circuit Impedances;

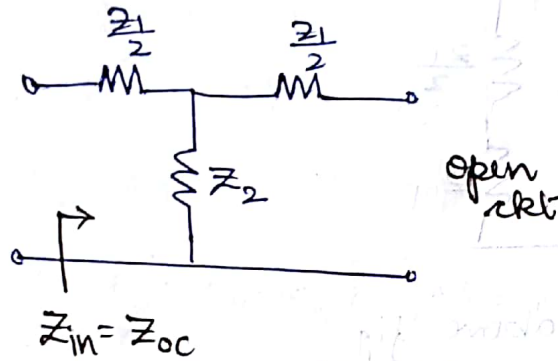


fig. (a)

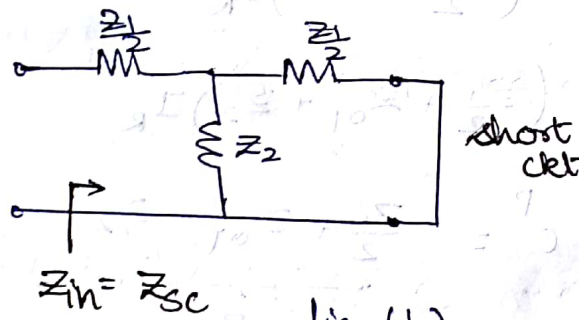


fig. (b)

from fig (a):

$$Z_{in} = Z_{oc} = \frac{z_1}{2} + z_2$$

from fig (b):

$$Z_{in} = Z_{sc} = \frac{z_1}{2} + \left(\frac{z_1}{2} \parallel z_2 \right)$$

$$Z_{sc} = \frac{z_1}{2} + \frac{\left(\frac{z_1 z_2}{2} \right)}{\frac{z_1}{2} + z_2}$$

$$Z_{sc} = \frac{\frac{z_1}{2} (z_2 + z_2) + \frac{z_1 z_2}{2}}{\left(\frac{z_1}{2} + z_2 \right)}$$


$$Z_{sc} \left(\frac{Z_1}{2} + Z_2 \right) = \frac{Z_1^2}{4} + Z_1 Z_2$$

$$Z_{sc} Z_{oc} = Z_{OT}^2$$


$$Z_{OT} = \sqrt{Z_{oc} Z_{sc}} \rightarrow \textcircled{3}$$

Analysis of Symmetrical π -NW:-

standard Symm. π -NW:

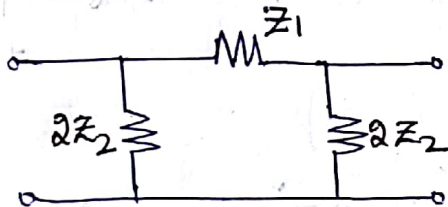

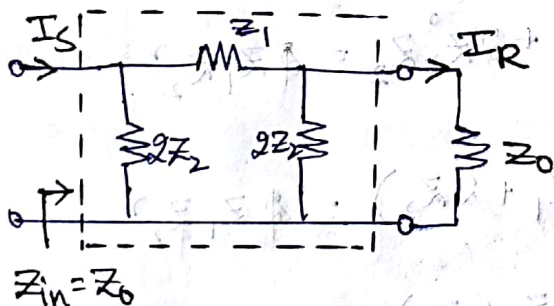(i) Characteristic Impedance: ($Z_{0\pi}$)



$$Z_{in} = \left[(2Z_2 \parallel Z_0) + Z_1 \right] \parallel (2Z_2)$$

if $Z_R = Z_0$ then $Z_{in} = Z_0$

$$Z_0 = \left[\left(\frac{2Z_2 Z_0}{Z_0 + 2Z_2} \right) + Z_1 \right] (2Z_2)$$

$$2Z_2 + Z_1 + \left(\frac{2Z_2 Z_0}{Z_0 + 2Z_2} \right)$$

$$z_0 = \frac{(2z_2 z_0 + z_1 z_0 + 2z_1 z_2)(2z_2)}{[(2z_2 + z_1)(z_0 + 2z_2) + 2z_2 z_0]}$$

$$z_0 [(2z_2 + z_1)(z_0 + 2z_2) + 2z_2 z_0] = [(2z_2 z_0 + z_1 z_0 + 2z_1 z_2)](2z_2)$$

$$z_0 [(2z_2 + z_1)(z_0 + 2z_2) + 2z_2 z_0] = 4z_2^2 z_0 + 2z_1 z_2 z_0 + 2z_1 z_2^2$$

$$z_0 [2z_0 z_2 + 4z_2^2 + z_0 z_1 + 2z_1 z_2 + 2z_2 z_0] = 4z_2^2 z_0 + 2z_1 z_2 z_0 + 2z_1 z_2^2$$

$$\Rightarrow 2z_0 z_2 + 4z_2^2 + z_0 z_1 + 2z_0 z_2 = 4z_2^2 z_0 + 2z_1 z_2 z_0 + 2z_1 z_2^2$$

$$2z_2 z_0 + z_0 z_1 + 2z_0 z_2 = 2z_1 z_2^2$$

$$z_0 (2z_2 + z_1 + 2z_2) = 2z_1 z_2^2$$

$$z_0 (4z_2 + z_1) = 2z_1 z_2^2$$

$$4z_0 z_2 + z_0 z_1 = 2z_1 z_2^2$$

$$z_0 = \frac{2z_1 z_2^2}{4z_2 + z_1}$$


$$z_0 = \frac{z_1 z_2^2}{2z_2 + z_1}$$

$$z_0 = \sqrt{\frac{4z_1 z_2^2}{z_1 + 4z_2}}$$

$$Z_0 = \sqrt{\frac{4Z_1 Z_2}{4Z_2 \left(1 + \frac{Z_1}{4Z_2}\right)}}$$


$$Z_{in} = \sqrt{\frac{Z_1 Z_2}{\left(1 + \frac{Z_1}{4Z_2}\right)}} \rightarrow \textcircled{4}$$

(ii) propagation constant:

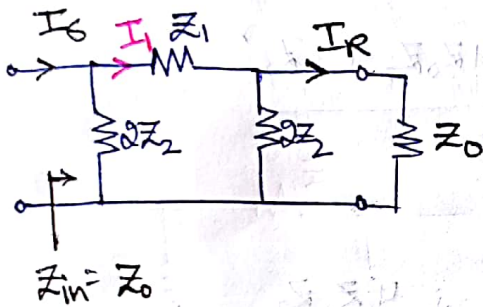

w.k.t $e^p = \frac{I_S}{I_R}$ or $p = \log_e \left(\frac{I_S}{I_R} \right)$

Redrawing the circuit

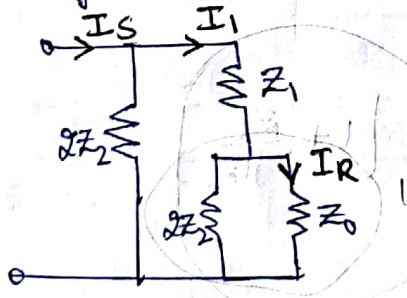

$$I_R = I_1 \left(\frac{2Z_2}{Z_0 + 2Z_2} \right)$$

Finding I_1 in terms of I_S

$$I_1 = \frac{(2Z_2)}{2Z_2 + Z_1 + \left(\frac{2Z_2 Z_0}{Z_0 + 2Z_2} \right)} \cdot I_S$$

$$I_1 = \frac{(2Z_2)(Z_0 + 2Z_2)}{(Z_1 + 2Z_2)(Z_0 + 2Z_2) + 2Z_0 Z_2} \cdot I_S$$

sub I_1 in I_R . we get

$$I_R = \left[\frac{(2z_2)(z_0 + 2z_2)}{(z_1 + 2z_2)(z_0 + 2z_2) + 2z_0z_2} \right] \cdot \left[\frac{(2z_2)}{(z_0 + 2z_2)} \right] I_S$$

$$I_R = \left[\frac{4z_2^2}{z_0z_1 + 2z_1z_2 + 2z_0z_2 + 4z_2^2 + 2z_0z_2} \right] \cdot I_S$$

$$\frac{I_S}{I_R} = \frac{z_0z_1 + 2z_1z_2 + 4z_0z_2 + 4z_2^2}{4z_2^2}$$

$$e^p = \frac{z_0z_1}{4z_2^2} + \frac{2z_1z_2}{4z_2^2} + \frac{4z_0z_2}{4z_2^2} + 1$$

$$e^p = 1 + \frac{z_1}{2z_2} + \frac{z_0}{z_2} + \frac{z_0z_1}{4z_2^2}$$

$$e^p = 1 + \frac{z_1}{2z_2} + \frac{z_0}{z_2} \left[1 + \frac{z_1}{4z_2} \right]$$

$$e^p = 1 + \frac{z_1}{2z_2} + z_0 \left[\frac{1}{z_2} + \frac{z_1}{4z_2^2} \right]$$

$$e^p = 1 + \frac{z_1}{2z_2} + z_0 \left[\frac{4z_2 + z_1}{4z_2^2} \right]$$

$$e^p = 1 + \frac{z_1}{2z_2} + \frac{z_0}{4z_2^2} (z_1 + 4z_2)$$

$$e^P = 1 + \frac{Z_1}{2Z_2} + \left(\sqrt{\frac{4Z_1Z_2^2}{Z_1 + 4Z_2}} \right) \left(\frac{Z_1 + 4Z_2}{4Z_2^2} \right) \quad [\because \text{From eqn (2)}]$$

$$e^P = 1 + \frac{Z_1}{2Z_2} + \sqrt{\frac{4Z_1Z_2^2 \cdot (Z_1 + 4Z_2)}{(Z_1 + 4Z_2) \cdot (4Z_2^2)}}$$

$$e^P = 1 + \frac{Z_1}{2Z_2} + \sqrt{\frac{Z_1(Z_1 + 4Z_2)}{4Z_2^2}}$$

$$e^P = 1 + \frac{Z_1}{2Z_2} + \sqrt{\frac{Z_1^2 + 4Z_1Z_2}{4Z_2^2}}$$


$$e^P = 1 + \frac{Z_1}{2Z_2} + \sqrt{\frac{Z_1^2}{4Z_2^2} + \frac{4Z_1Z_2}{4Z_2^2}}$$

$$e^P = 1 + \frac{Z_1}{2Z_2} + \sqrt{\frac{Z_1}{Z_2} \left[1 + \frac{Z_1}{4Z_2} \right]} \rightarrow \textcircled{5}$$

*NOTE:-

The above eqn (5) is similar to eqn (2b) i.e. propagation constant of symm. T & π networks are same but characteristic may change

(iii) Open & Short Circuit Impedence:-

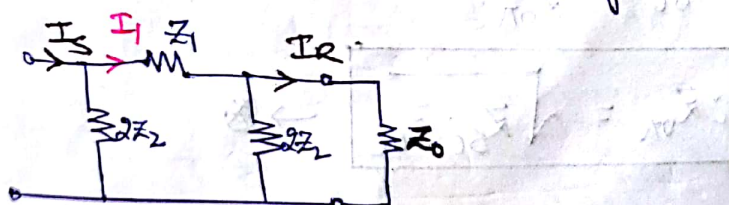

open ckt

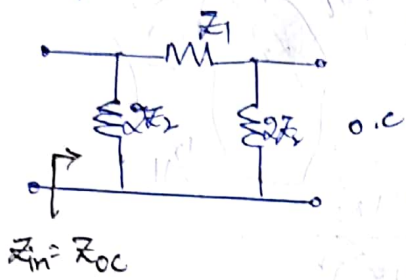


fig (a)

short ckt

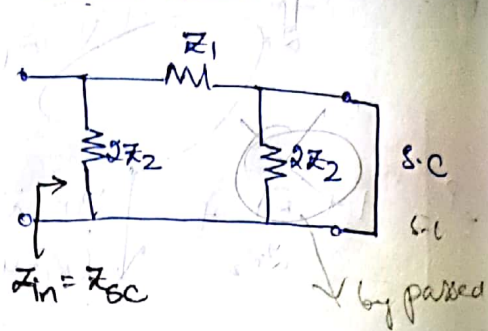


fig (b)

From fig (a):

$$Z_{in} = Z_{oc} = \frac{(2Z_2)(Z_1 + 2Z_2)}{Z_1 + 4Z_2}$$

From fig (b):

$$Z_{in} = Z_{sc} = \frac{(Z_1)(2Z_2)}{Z_1 + 2Z_2}$$

Now

$$Z_{oc} \cdot Z_{sc} = \left[\frac{(2Z_2)(Z_1 + 2Z_2)}{Z_1 + 4Z_2} \right] \cdot \left[\frac{(Z_1)(2Z_2)}{Z_1 + 2Z_2} \right]$$

$$Z_{sc} \cdot Z_{oc} = \frac{4Z_1 Z_2^2}{(Z_1 + 4Z_2)}$$



$$Z_{sc} \cdot Z_{oc} = Z_{0T}^2$$

$$\therefore Z_{0T} = \sqrt{Z_{sc} \cdot Z_{oc}} \rightarrow \otimes$$

*NOTE:-

→ For any Symm. N/w characteristic Impedance Z_0 is geometric mean of o.c & s.c impedances (i.e. Z_{oc} & Z_{sc})

Relation between Z_{OT} & Z_{ON}

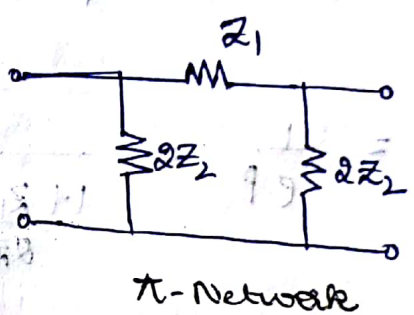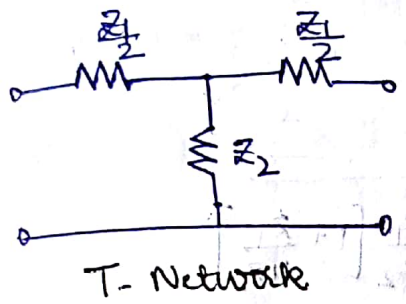

$$Z_{OT} = \sqrt{\frac{Z_1^2}{4} + Z_1 Z_2}$$

$$Z_{ON} = \sqrt{\frac{4Z_1 Z_2^2}{Z_1 + 4Z_2}}$$

Now, consider;

$$Z_{ON} = \frac{\sqrt{\frac{4Z_1 Z_2^2}{Z_1 + 4Z_2}} \times Z_1}{\sqrt{(Z_1 + 4Z_2) \cdot Z_1}}$$

$$= \sqrt{\frac{4Z_1^2 Z_2^2}{Z_1^2 + 4Z_1 Z_2}}$$

$$= \sqrt{\frac{Z_1^2 Z_2^2}{\frac{Z_1^2}{4} + Z_1 Z_2}}$$

$$= \frac{Z_1 Z_2}{\sqrt{\frac{Z_1^2}{4} + Z_1 Z_2}}$$

$$\sqrt{\frac{Z_1^2}{4} + Z_1 Z_2}$$

$$Z_{ON} \cdot Z_{OT} = Z_1 Z_2 \rightarrow \textcircled{6}$$

Design of symmetrical T-NW when Z_{OT}
& P are given:-

W.K.T

$$e^P = 1 + \frac{Z_1}{2Z_2} + \sqrt{\frac{Z_1}{Z_2} \left[1 + \frac{Z_1}{4Z_2} \right]}$$

$$e^{-P} = \frac{1}{e^P} \Rightarrow \frac{1}{1 + \frac{Z_1}{2Z_2} + \sqrt{\frac{Z_1}{Z_2} \left[1 + \frac{Z_1}{4Z_2} \right]}}$$

$$e^{-P} = \frac{1}{1 + \frac{Z_1}{2Z_2} + \sqrt{\frac{Z_1}{Z_2} \left[1 + \frac{Z_1}{4Z_2} \right]}} \times \frac{\left(1 + \frac{Z_1}{2Z_2} \right) - \sqrt{\frac{Z_1}{Z_2} \left[1 + \frac{Z_1}{4Z_2} \right]}}{\left(1 + \frac{Z_1}{2Z_2} \right) - \sqrt{\frac{Z_1}{Z_2} \left[1 + \frac{Z_1}{4Z_2} \right]}}$$

$$= \frac{\left(1 + \frac{Z_1}{2Z_2} \right) - \sqrt{\frac{Z_1}{Z_2} \left[1 + \frac{Z_1}{4Z_2} \right]}}{\left(1 + \frac{Z_1}{2Z_2} \right)^2 - \left(\sqrt{\frac{Z_1}{Z_2} \left[1 + \frac{Z_1}{4Z_2} \right]} \right)^2}$$

$$= \frac{\left(1 + \frac{Z_1}{2Z_2} \right) - \sqrt{\frac{Z_1}{Z_2} \left[1 + \frac{Z_1}{4Z_2} \right]}}{1 + \frac{Z_1^2}{4Z_2^2} + 2(1) \left[\frac{Z_1}{Z_2} \right] - \frac{Z_1}{Z_2} - \frac{Z_1}{4Z_2}}$$

$$e^{-P} = \left(1 + \frac{Z_1}{2Z_2} \right) - \sqrt{\frac{Z_1}{Z_2} \left[1 + \frac{Z_1}{4Z_2} \right]}$$

$$\textcircled{2} \rightarrow \frac{Z_1 Z_2}{Z_1 Z_2} = \frac{Z_1 Z_2}{Z_1 Z_2}$$

w.k.T

$$\cosh(p) = \frac{e^p + e^{-p}}{2}$$

$$\sinh(p) = \frac{e^p - e^{-p}}{2}$$

$$\Rightarrow \cosh(p) = \frac{2 \left(1 + \frac{z_1}{2z_2} \right)}{2}$$

$$\boxed{\cosh(p) = 1 + \frac{z_1}{2z_2}} \rightarrow \textcircled{7}$$

$$\Rightarrow \sinh(p) = \frac{2 \sqrt{\frac{z_1}{z_2} \left[1 + \frac{z_1}{4z_2} \right]}}{2}$$

$$\sinh(p) = \sqrt{\frac{z_1}{z_2} + \frac{z_1^2}{4z_2^2}}$$

$$\sinh(p) = \frac{\sqrt{z_1 z_2 + \frac{z_1^2}{4}}}{z_2}$$

$$\boxed{\sinh(p) = \frac{z_{0T}}{z_2}} \rightarrow \textcircled{8}$$

also w.k.T

$$\cosh(p) = \cosh^2(p/2) + \sinh^2(p/2)$$

$$\cosh(p) = 1 + 2 \sinh^2(p/2)$$

now, from eqn (7)

$$1 + \frac{z_1}{2z_2} = 1 + 2 \sinh^2(p/2)$$

$$\boxed{\sinh(p/2) = \sqrt{\frac{z_1}{4z_2}}} \rightarrow \textcircled{9a}$$

Now, consider

$$\sinh(p) = 2 \sinh(p/2) \cdot \cosh(p/2)$$

From eqn (8) & (9a)

$$\frac{Z_{OT}}{Z_2} = \sqrt{\frac{Z_1}{4Z_2}} \cdot \cosh(p/2)$$

$$\cosh(p/2) = \frac{Z_{OT}}{Z_2} \cdot \sqrt{\frac{Z_2}{Z_1}}$$

$$\cosh(p/2) = Z_{OT} \cdot \sqrt{\frac{Z_2}{4Z_1}}$$

$$\cosh(p/2) = \frac{Z_{OT}}{\sqrt{4Z_1 Z_2}} \rightarrow (9b)$$

$$\tanh(p/2) = \frac{\sinh(p/2)}{\cosh(p/2)}$$

$$= \frac{\sqrt{\frac{Z_1}{4Z_2}} \cdot \sqrt{4Z_1 Z_2}}{Z_{OT}}$$

$$= \frac{1}{Z_{OT}} \cdot \sqrt{\frac{Z_1^2 Z_2}{4Z_2}}$$

$$= \frac{Z_1}{2Z_{OT}}$$

$$\tanh(p/2) = \frac{Z_1}{2Z_{OT}} \rightarrow (9c)$$

∴ From eqn (8) & (9c)

$$Z_1 = 2Z_{OT} \cdot \tanh(P/2)$$

$$Z_2 = \frac{Z_{OT}}{\sinh(p)}$$

→ (10)

Design of Symmetrical π -NW when Z_{OT} & P are given:

W.K.T from eqn (6) & (10)

$$Z_{OT} Z_{OT} = Z_1 Z_2 \quad \text{--- (6)}$$

$$Z_{OT} = \frac{Z_1 Z_2}{Z_{OT}}$$

From (10) → $Z_1 = 2Z_{OT} \cdot \tanh(P/2)$

$$Z_1 = 2 \left[\frac{Z_1 Z_2}{Z_{OT}} \right] \cdot \tanh(P/2)$$

$$Z_2 = \frac{Z_{OT}}{2 \tanh(P/2)}$$

$$Z_2 = \frac{Z_1 Z_2}{(Z_{OT}) \sinh(p)}$$

$$Z_1 = Z_{OT} \sinh p$$

∴ For Symm. π -NW


$$* \quad Z_1 = Z_{OT} \sinh(p)$$

$$Z_a = \frac{Z_{OT}}{2 \tanh(p/2)}$$

→ (11)

Relation between p , Z_{sc} & Z_{oc}

consider T-NW

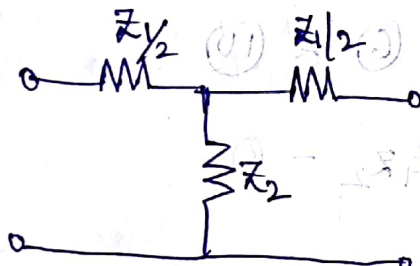

$$Z_{oc} = \frac{Z_1}{2} + Z_2 \Rightarrow Z_{oc} = \frac{Z_1 + 2Z_2}{2}$$

From eqn (4) & (8) we have

$$\cosh(p) = 1 + \frac{Z_1}{2Z_2}, \quad \sinh(p) = \frac{Z_{OT}}{Z_2}$$

$$\begin{aligned} \tanh(p) &= \frac{\sinh(p)}{\cosh(p)} = \frac{Z_{OT}}{Z_2} \left[\frac{2Z_2}{Z_1 + 2Z_2} \right] \\ &= Z_{OT} \left[\frac{1}{Z_{oc}} \right] \end{aligned}$$

w.k.T

$$Z_{OT} = \sqrt{Z_{oc} \cdot Z_{sc}}$$


$$\tanh(p) = \sqrt{Z_{oc} Z_{sc}} \left[\frac{1}{Z_{oc}} \right]$$

$$= \sqrt{\frac{Z_{oc} \cdot Z_{sc}}{Z_{oc}^2}}$$

$$\boxed{\tanh(p) = \sqrt{\frac{Z_{sc}}{Z_{oc}}}} \rightarrow (12)$$

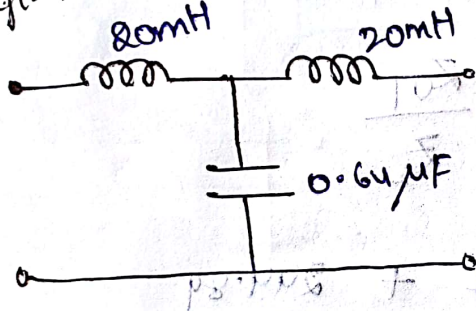problems:-

Ex-1:- Find the propagation const & characteristic impedance of symm. T-NW given at 400Hz given below:



Sol:

$$\frac{Z_1}{2} = j\omega L$$

$$Z_1 = 2j \times 2\pi \times 400 \times 20 \times 10^{-3}$$

$$\boxed{Z_1 = j 100.53 \Omega}$$

$$Z_2 = \frac{1}{j\omega C}$$

$$Z_2 = \frac{1}{j \times 2\pi \times 400 \times 0.64 \times 10^{-6}}$$

$$\boxed{Z_2 = -j 621.699 \Omega}$$

characteristic impedance u

$$Z_{OT} = \sqrt{\frac{Z_1^2}{4} + Z_1 Z_2}$$

$$= \sqrt{\frac{(j100.53)^2}{4} + (j100.53)(-j621.699)}$$

$$Z_{OT} = 244.89 \Omega$$

propagation const u

$$e^P = 1 + \frac{Z_1}{2Z_2} + \frac{Z_{OT}}{Z_2}$$

$$= 1 + \frac{j100.53}{2(-j621.69)} + \frac{244.89}{(-j621.69)}$$


$$e^P = 0.9192 + j0.3939$$

$$\ln[r \angle \theta] = \ln r + \left[\theta \times \frac{\pi}{180^\circ} + 2n\pi \right]$$

$$= \ln(1) + \left[(23.19) \times \frac{\pi}{180^\circ} + 2n\pi \right]$$

$$P = 0 + [0.404 + 2n\pi]$$

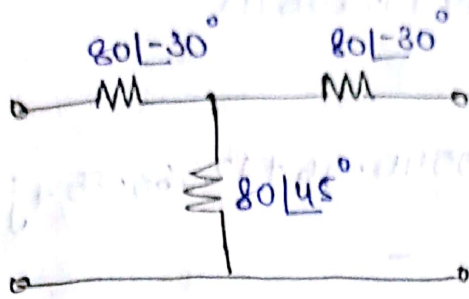Ex-2:- Calculate the characteristic impedance & propagation constant of the symmetrical T-network given below.



sol: $Z_L = 80\angle-30^\circ$

$$Z_1 = (2\angle 0^\circ) (80\angle-30^\circ)$$

$$Z_1 = 160\angle-30^\circ$$

$$Z_1 = 138.56 - j80$$

$$Z_2 = 80\angle 45^\circ$$

$$Z_2 = 56.56 + j56.56$$

Characteristic Imp:

$$Z_{0T} = \sqrt{\frac{Z_1^2}{4} + Z_1 Z_2}$$

$$Z_{0T} = \sqrt{\frac{(160\angle-30^\circ)^2}{4\angle 0^\circ} + (160\angle-30^\circ)(80\angle 45^\circ)}$$

$$Z_{0T} = \sqrt{\frac{160 \times 160 \angle -60^\circ}{4} + 12800\angle 15^\circ}$$

$$= \sqrt{160 \times 40 \angle -60^\circ + 12800 \angle 15^\circ}$$

$$= \sqrt{6400 \angle -60^\circ + 12800 \angle 15^\circ}$$

$$= \sqrt{3200 - j5540.56 + 12363.85 + j3812.82}$$

$$= \sqrt{15722.06 \angle -8.152^\circ}$$

$$\boxed{\sqrt{r \angle \theta} = \sqrt{r} \cdot \frac{\theta}{2}}$$

$$\boxed{Z_{TOT} = 125.39 \angle -4.076^\circ}$$

prop. const is

$$e^p = 1 + \frac{Z_1}{2Z_2} + \frac{Z_{TOT}}{Z_2}$$

$$= 1 + \frac{160 \angle -30^\circ}{160 \angle 45^\circ} + \frac{125.39 \angle -4.076^\circ}{80 \angle 45^\circ}$$

$$= 1 + 1 \angle -75^\circ + 1.56 \angle -49.076^\circ$$

$$= 1 + 0.258 - j0.965 + 1.026 - j1.184$$

$$e^p = 2.284 - j2.15$$

$$e^p = 3.138 \angle -43.25^\circ$$

$$p = \ln [3.138 \angle -43.25^\circ]$$

$$p = \ln(3.138) + j \left[-43.25 \times \frac{\pi}{180} + 2n\pi \right]$$

$$p = 1.14 + j [-0.7548 + 2n\pi]$$

$$\therefore p = \alpha + j\beta$$

$$p = 1.14 + j [-0.7548 + 2n\pi]$$

for $n=0$; $\beta = -0.7548$ Invalid

$$n=1; \beta = -0.7548 + 2\pi = 5.528$$

$$\therefore \boxed{\alpha = 1.14 \text{ Np}} \quad \& \quad \boxed{\beta = 5.528 \text{ rad}}$$

Ex-3; - A Symm. T. NW with unknown elements yields the following measurements

$$Z_{oc} = (50 + j0) \Omega; \quad Z_{sc} = (270 + j0) \Omega$$

Determine the characteristic imp, prop. const & also series & shunt arm impedances.

$$\text{eg: } Z_{OT} = \sqrt{Z_{sc} \cdot Z_{oc}}$$

$$= \sqrt{50 \cdot 270}$$

$$\boxed{Z_{OT} = 117 \Omega}$$

$$ii) \tanh(p) = \sqrt{\frac{Z_{oc}}{Z_{sc}}}$$

$$p = \tanh^{-1} \sqrt{\frac{450}{250}}$$

$$p = 0.693$$

$$\frac{e^p - e^{-p}}{e^p + e^{-p}} = \frac{0.6}{1}$$

componendo e dividendo

$$\frac{e^p - e^{-p}}{e^p + e^{-p}} = \frac{0.6 + 1}{0.6 - 1}$$

$$\frac{1 + e^{-2p}}{1 + e^{2p}} = \frac{1.6}{-0.4}$$

$$e^{2p} = 4$$

$$2p = \ln 4$$

$$p = \frac{\ln 4}{2}$$

$$p = 0.693$$

$$iii) Z_1 = 2 Z_{OT} \times \tanh(p/2)$$

$$Z_2 = \frac{Z_{OT}}{\sinh(p)}$$


$$\sinh(p)$$

$$Z_1 = 2 \times 450 \times \tanh\left(\frac{0.693}{2}\right)$$

$$Z_1 = 300 \Omega$$

$$Z_2 = \frac{Z_{OT}}{\sinh(p)} = \frac{450}{\sinh(0.693)}$$

$$Z_2 = 600.14 \Omega$$

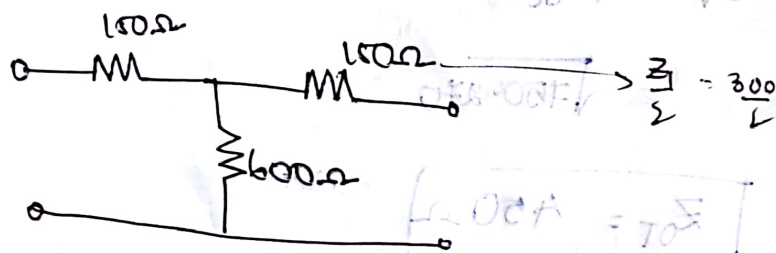

Ex-4: Design a symm. π -NW having
 o.c & s.c impedances as 375Ω , 240Ω
 respectively. Also find char. Imp & P.

(i) $Z_{oc} = 375\Omega$, $Z_{sc} = 240$

$$Z_{0\pi} = \sqrt{Z_{sc} Z_{oc}}$$

$$Z_{0\pi} = 300\Omega$$


(ii) $\tanh(p) = \sqrt{\frac{Z_{sc}}{Z_{oc}}}$

$$p = \tanh^{-1} \sqrt{\frac{240}{375}}$$

$$p = 1.098$$

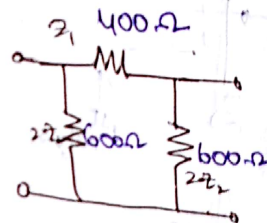(iii) ~~$Z_1 = 2Z_{0\pi} \times \tanh(p/2)$~~

~~$$= 2 \times 300 \times \tanh\left(\frac{1.098}{2}\right)$$~~



(iii) $Z_1 = Z_{oc} \sinh(p)$ & $Z_2 = \frac{Z_{oc}}{2 \tanh(p/2)}$


$$Z_1 = 300 \times \sinh(1.098)$$

$$Z_2 = \frac{300}{2 \tanh\left(\frac{1.098}{2}\right)}$$

$$Z_1 = 400\Omega$$

$$Z_2 = 300\Omega$$

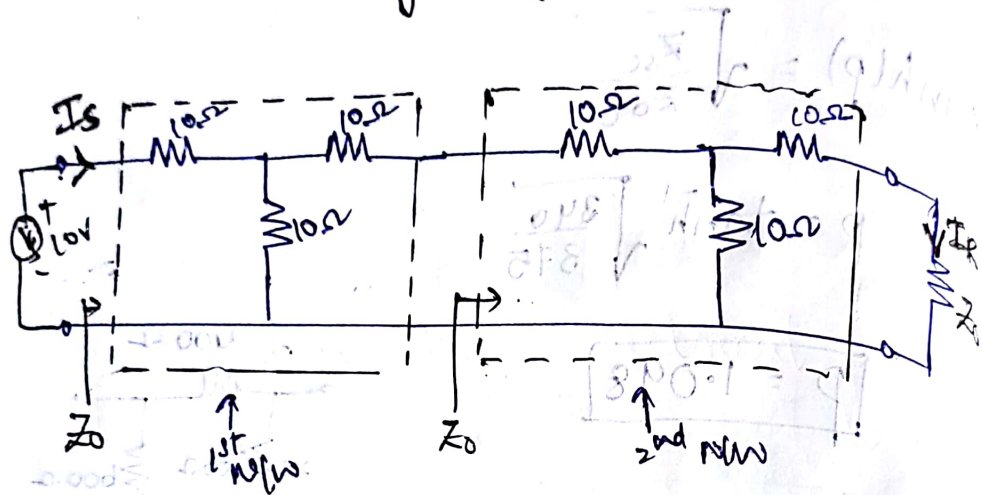Ex-5: 2 similar T-networks each consisting of a series arm impedance 20Ω & shunt arm impedance 10Ω respectively connected in series. The output of the series network is terminated by characteristic impedance Z_0 . & the input network is fed by 10V . Compute the current flowing through the terminating impedance Z_0 .



$$Z_0 = \sqrt{\frac{Z_1^2}{4} + Z_1 Z_2}$$

$$= \sqrt{\frac{20^2}{4} + (20)(10)}$$

$$Z_0 = 17.32\Omega$$

$$C_p = 1 + \frac{Z_1}{2Z_2} + \frac{Z_0}{Z_2}$$

$$= 1 + \frac{20}{20} + \frac{17.321}{10}$$

$$e^P = 3.7321$$

$$P = \ln(3.7321)$$

$$P = 1.316$$

w.k.T

$$\frac{I_S}{I_R} = \frac{I_S}{I_1} \times \frac{I_1}{I_R}$$

$$\frac{I_S}{I_R} = e^P \cdot e^P$$

$$\frac{I_S}{I_R} = (3.7321)^2$$


$$\frac{I_S}{I_R} = 13.928$$

$$I_S = \frac{V_S}{Z_0} = \frac{10}{17.321} = 0.577$$

$$I_R = \frac{I_S}{13.928} = \frac{0.577}{13.928} = 0.0414$$

$$\approx 41.4 \text{ mA}$$

using mesh Analysis

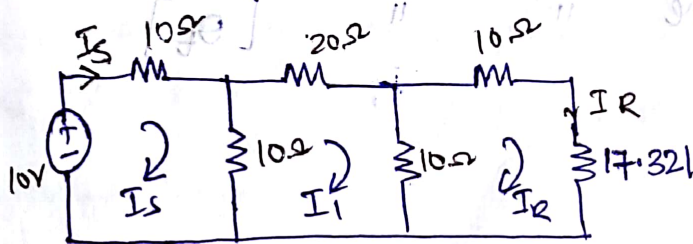

$$0 \text{ :- } -10 + 10I_S + 10(I_S - I_1) = 0$$

$$20I_S - 10I_1 + 0 \cdot I_R = 10 \quad \text{--- (1)}$$

$$\textcircled{2}: 10(I_1 - I_s) + 20I_1 + 10(I_1 - I_R) = 0$$

$$40I_1 - 10I_s - 10I_R = 0$$

$$\textcircled{3}: 10(I_R - I_1) + 10I_R + 17.32I_R = 0$$

$$0I_1 + 37.32I_R - 10I_1 = 0$$

$$I_s = 0.57 \text{ A}$$

$$I_1 = 0.154 \text{ A}$$

$$I_R = 0.0414 \text{ A}$$

$$I_R \approx 41.4 \text{ mA}$$

Asymmetrical N/w & electrical properties


Asymmetrical N/w can be described by four parameters

1) Image Impedances $[Z_{i1} \text{ \& } Z_{i2}]$

2) Iterative " $[Z_{t1} \text{ \& } Z_{t2}]$

3) Image Transfer Constant $[\theta_i]$



4) Iterative " $[\theta_t]$

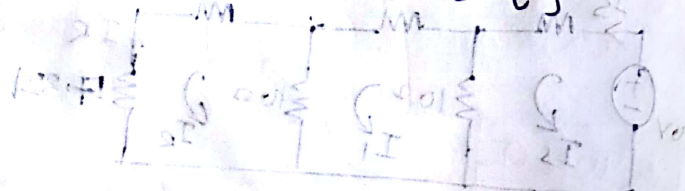

$$0 = (I_s - I_1)10 + I_120 + I_110 - I_210$$



$$0 = 20I_1 + I_110 - I_210$$

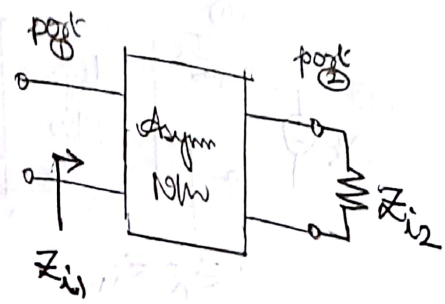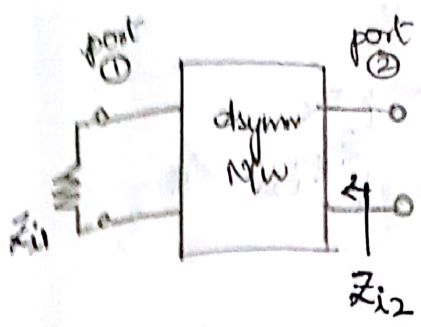1) Image Impedances: $[Z_{i1} \text{ \& } Z_{i2}]$




→ Two impedances Z_{i1} & Z_{i2} of an asymmetric NW are such that if port ② is terminated by Z_{i2} then impedance looking into port ① is Z_{i1} & if port ① is terminated by Z_{i1} then impedance looking into port ② is Z_{i2} then Z_{i1} & Z_{i2} are called "Image Impedances".

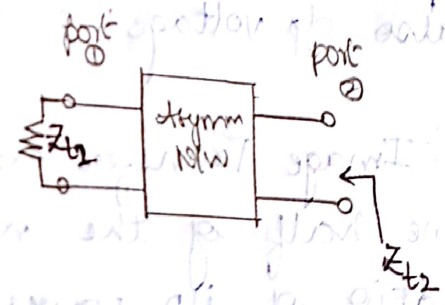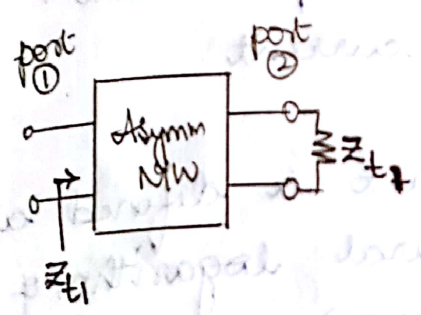2) Iterative Impedances: $[Z_{t1} \text{ \& } Z_{t2}]$



→ Two impedances Z_{t1} & Z_{t2} of an asymmetric NW are such that if port ② is terminated by Z_{t2} then impedance looking into port ① is Z_{t1} & if port ① is terminated by Z_{t1} then impedance looking into port ② is Z_{t2} then Z_{t1} & Z_{t2} are called "Iterative impedances".

3.) Image Transfer Constant (θ_i):

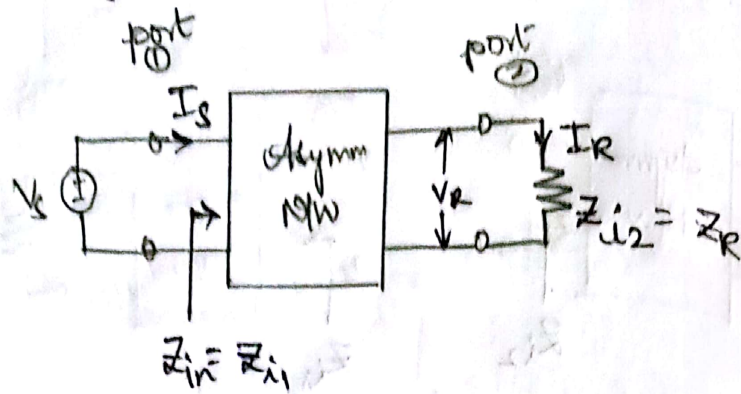

$$V_s = Z_{in} I_s \Rightarrow V_s = Z_{i1} I_s$$

$$V_R = I_R Z_R \Rightarrow V_R = I_R Z_{i2}$$

i.e. $\frac{V_s}{V_R} \neq \frac{I_s}{I_R}$

$$\theta_i = \frac{1}{2} \ln \left[\frac{V_s I_s}{V_R I_R} \right]$$

\therefore Image Transfer constant is defined in terms of both i/p voltage & i/p current & also o/p voltage & o/p current.

Def: Image Transfer constant is defined as "one half of the natural logarithm of ratio of i/p power ($V_s I_s$) to the o/p power ($V_R I_R$) of an asymmetrical N/w".

$$\Rightarrow \theta_i = \frac{1}{2} \ln \left[\frac{I_s^2 Z_{i1}}{I_R^2 Z_{i2}} \right]$$


$$\theta_i = \frac{1}{2} \ln \left[\frac{I_s^2 Z_{i1}}{I_R^2 Z_{i2}} \right]$$

$$\theta_i = \ln \left[\frac{I_s}{I_R} \sqrt{\frac{Z_{i1}}{Z_{i2}}} \right]$$

$$\theta_i = A_i + jB_i$$

A_i - Image Attenuation constant
 jB_i - Image phase shift const
 units :- Np or dB
 units: degree($^\circ$), radians

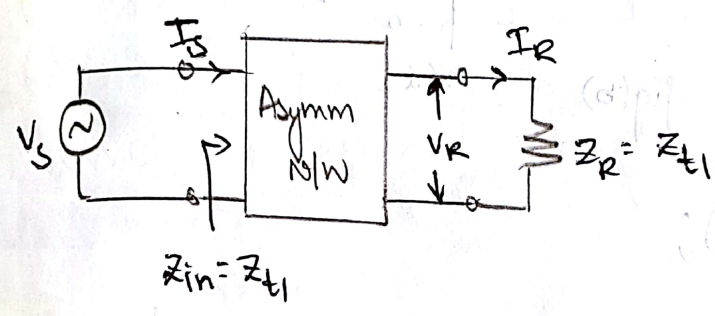4.) Iterative Transfer constant $[\theta_t]$:-



$$V_s = Z_{in} I_s = Z_{t1} I_s$$

$$V_R = Z_R I_R = Z_{t1} I_R$$



$$\frac{V_s}{V_R} = \frac{I_s}{I_R}$$

$$\theta_t = \ln \left[\frac{V_s}{V_R} \right] \text{ or } \ln \left[\frac{I_s}{I_R} \right]$$

$\theta_t = A_t + jB_t$
 \downarrow Iterative attenuation const
 \downarrow Iterative phase-shift const

Analysis of Asymmetrical T-N/W:-

Image Impedences:-

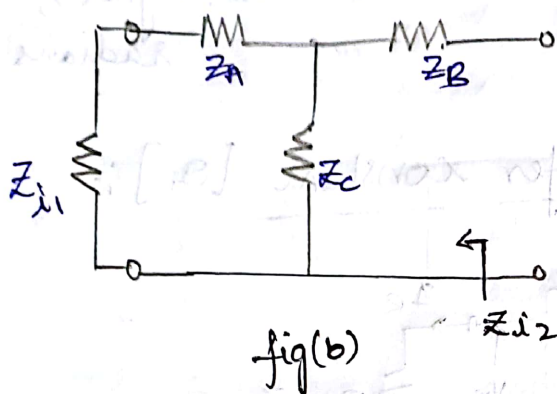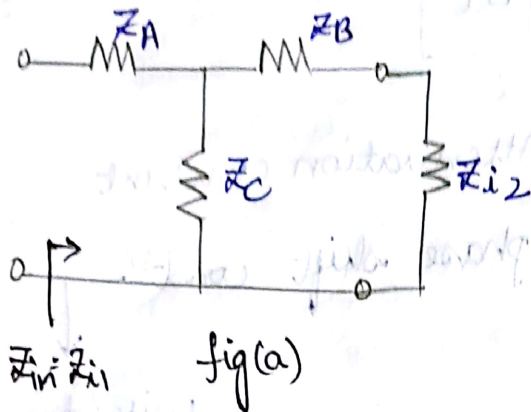

From fig(a);

$$Z_{in} = Z_{i1} = Z_A + Z_C \parallel (Z_B + Z_{i2})$$

$$Z_{i1} = Z_A + \frac{Z_C (Z_B + Z_{i2})}{Z_C + Z_B + Z_{i2}}$$

$$Z_{i1} (Z_C + Z_B + Z_{i2}) = Z_A (Z_C + Z_B + Z_{i2}) + Z_C (Z_B + Z_{i2})$$

$$Z_{i1} Z_{i2} + Z_{i1} (Z_C + Z_B) = Z_A Z_C + Z_A Z_B + Z_A Z_{i2}$$

$$+ Z_B Z_C + Z_C Z_{i2}$$

$$z_{i1} z_{i2} + z_{i1} (z_c + z_b) = (z_a z_b + z_b z_c + z_c z_a) + z_{i2} (z_a + z_c)$$

$$z_{i1} z_{i2} + z_{i1} (z_c + z_b) = z_a z_b + z_{i2} (z_a + z_c)$$

↳ (13a)

From fig (b);

$$z_{i1} = z_{i2} = z_b + z_c \parallel (z_a + z_{i1})$$

$$z_{i2} = z_b + z_c (z_a + z_{i1})$$

$$z_c + z_a + z_{i1}$$

$$z_{i2} (z_c + z_a + z_{i1}) = z_b (z_c + z_a + z_{i1}) + z_c (z_a + z_{i1})$$

$$z_{i1} z_{i2} + z_{i2} (z_a + z_c) = z_b z_c + z_a z_b + z_b z_{i1} + z_a z_c + z_c z_{i1}$$

$$z_{i1} z_{i2} + z_{i2} (z_a + z_c) = z_a z_b + z_{i1} (z_b + z_c)$$

↳ (13b)

$$(13a) - (13b)$$

$$z_{i1} (z_b + z_c) = z_{i2} (z_a + z_c)$$

$$\frac{z_{i1}}{z_{i2}} = \frac{(z_a + z_c)}{(z_b + z_c)} \rightarrow (13c)$$

$$(13a) + (13b)$$

$$\sqrt{z_1 z_2} = \sqrt{z_A z_B}$$

$$z_1 z_2 = z_A z_B \rightarrow (13d)$$

$$(13c) \times (13d)$$

$$\frac{z_{i1}}{z_{i2}} \times (z_{i1} z_{i2}) = \frac{z_A + z_C}{z_B + z_C} \times z_A z_B$$

$$z_{i1} = \sqrt{\frac{z_A + z_C}{z_B + z_C}} \times \sqrt{z_A z_B}$$

$$(13d) \div (13c)$$

$$\frac{z_{i1} z_{i2}}{z_{i1}} = \frac{z_A z_B}{z_A + z_C}$$

$$z_{i2} = \frac{z_A z_B}{z_A + z_C}$$

$$z_{i2} = \frac{z_A z_B \times (z_B + z_C)}{z_A + z_C}$$


$$z_{i2} = \sqrt{\frac{z_A z_B}{z_A + z_C}} \times \sqrt{\frac{z_B + z_C}{z_A + z_C}}$$

$$Z_{i1} = \sqrt{(Z_A Z_B) \left[\frac{Z_A + Z_B}{Z_B + Z_C} \right]}$$


$$Z_{i2} = \sqrt{(Z_A Z_B) \left[\frac{Z_B + Z_C}{Z_A + Z_C} \right]}$$

→ (4)

Iterative Impedances:-

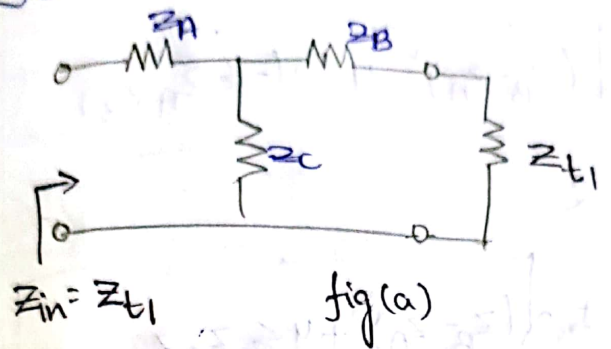

$Z_{in} = Z_{t1}$

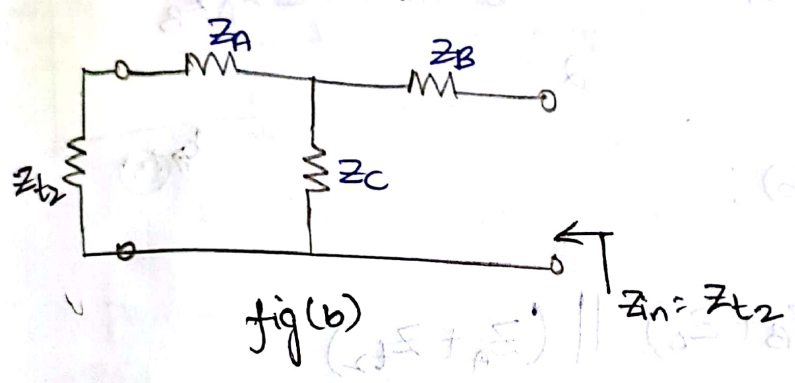

$Z_{in} = Z_{t2}$

From fig(a);

$$Z_{t1} = Z_A + Z_C \parallel (Z_B + Z_{t1})$$

$$Z_{t1} = Z_A + \frac{Z_C (Z_B + Z_{t1})}{Z_C + Z_B + Z_{t1}}$$

$$Z_{t1} (Z_C + Z_B + Z_{t1}) = Z_A (Z_C + Z_B + Z_{t1}) + Z_C (Z_B + Z_{t1})$$

$$Z_{t1}^2 + Z_{t1} (Z_C + Z_B) = Z_A Z_B + Z_{t1} (Z_A + Z_C)$$

$$z_{t1}^2 + z_{t1} (z_c + z_b - z_a - z_c) - \sum z_A z_B = 0$$

$$z_{t1}^2 + z_{t1} (z_b - z_a) - \sum z_A z_B = 0$$

$$an^2 + bn + c = 0$$

$$-b \pm \sqrt{b^2 - 4ac}$$

$$2a$$

$$z_{t1} \Rightarrow \frac{-(z_b - z_a) \pm \sqrt{(z_b - z_a)^2 - 4(1)(-\sum z_A z_B)}}{2}$$

$$z_{t1} \Rightarrow \frac{+(z_a - z_b) \pm \sqrt{(z_b - z_a)^2 + 4\sum z_A z_B}}{2}$$

From fig (b);

$$z_{t2} = (z_b + z_c) \parallel (z_a + z_{t2})$$

$$z_{t2} = \frac{z_b + z_c(z_a + z_{t2})}{z_c + z_a + z_{t2}}$$

$$z_{t2}(z_c + z_a + z_{t2}) = z_b(z_c + z_a + z_{t2}) + z_c(z_a + z_{t2})$$

$$z_{t2}^2 + z_{t2}(z_a + z_c) = \sum z_A z_B + z_{t2}(z_b + z_c)$$

$$z_{t2}^2 + z_{t2}(z_a + z_c - z_b - z_c) - \sum z_A z_B = 0$$



$$Z_{t2} + Z_{t2}(Z_A - Z_B) - \sum Z_A Z_B = 0$$

$$Z_{t2} = \frac{-(Z_A - Z_B) + \sqrt{(Z_A - Z_B)^2 + 4 \sum Z_A Z_B}}{2}$$

$$Z_{t2} = \frac{(Z_B - Z_A) + \sqrt{(Z_A - Z_B)^2 + 4 \sum Z_A Z_B}}{2} \quad (15)$$

Analysis of Asymmetrical T-N/W:

Image Impedances:-

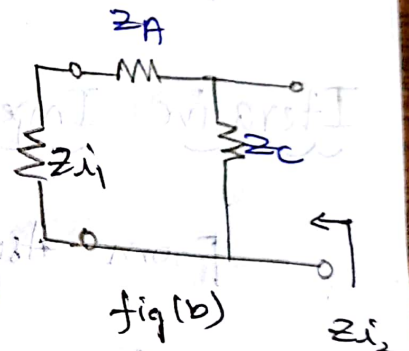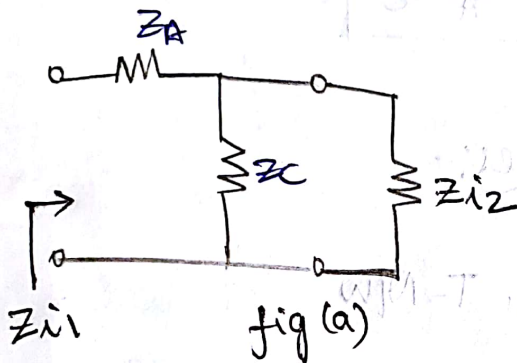

W.K.T for Asymm. T-N/W:

$$\sum Z_A Z_B = Z_A Z_B + Z_B Z_C + Z_C Z_A$$

$$\text{in } T\text{-N/W } \boxed{Z_B = 0}$$

$$\boxed{\sum Z_A Z_B = Z_A Z_C}$$

$$\therefore Z_{i1} = \sqrt{(\sum Z_A Z_B) \left[\frac{Z_A + Z_C}{Z_B + Z_C} \right]}$$

$$Z_{i1} = \sqrt{(Z_A Z_C) \left[\frac{Z_A + Z_C}{Z_C} \right]}$$

$$\boxed{Z_{i1} = \sqrt{Z_A^2 + Z_A Z_C}} \rightarrow (16)$$

11y

$$Z_{i2} = \sqrt{(\Sigma Z_A Z_B) \left[\frac{Z_B + Z_C}{Z_A + Z_C} \right]}$$

$$Z_{i2} = \sqrt{(Z_A Z_C) \left[\frac{Z_C}{Z_A + Z_C} \right]}$$

$$\boxed{Z_{i2} = Z_C \sqrt{\frac{Z_A}{Z_A + Z_C}}} \rightarrow (16)$$

Iterative Impedances:-

From Asymm. T-N/W

$$Z_{L1} = \frac{(Z_A - Z_B) + \sqrt{(Z_B - Z_A)^2 + 4 \Sigma Z_A Z_B}}{2}$$

$$\boxed{Z_B = 0}$$

$$\boxed{Z_{L1} = \frac{Z_A + \sqrt{Z_A^2 + 4 \Sigma Z_A Z_C}}{2}}$$

$$\cancel{Z_{L1} = \frac{Z_A (1 + \sqrt{1 + 4 \Sigma Z_A Z_C})}{2}}$$

$$Z_{t2} = \frac{(Z_B - Z_A) + \sqrt{(Z_A - Z_B)^2 + 4Z_A Z_B}}{2}$$

$Z_B = 0$

$$Z_{t2} = \frac{-Z_A + \sqrt{Z_A^2 + 4Z_A Z_C}}{2}$$


$$Z_{t2} = \frac{-Z_A + \sqrt{Z_A^2 + 4Z_A Z_C}}{2}$$

$$Z_{t1} = \frac{Z_A + \sqrt{Z_A^2 + 4Z_A Z_C}}{2}$$

→ (13)

problems:-

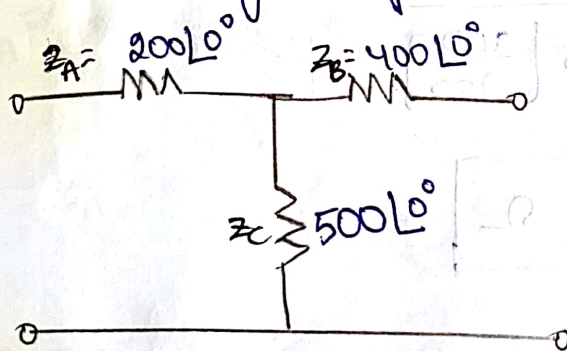Q1) calculate the image & iterative impedances of Asymm. T-N/W



Q2) For Asymm. T-N/W !

$$Z_{i1} = \sqrt{(Z_A Z_B)} \left[\frac{Z_A + Z_C}{Z_B + Z_C} \right]$$

$$Z_{i2} = \sqrt{(Z_A Z_B)} \left[\frac{Z_B + Z_C}{Z_A + Z_C} \right]$$

$$Z_{t1} = \frac{(Z_A - Z_B) + \sqrt{(Z_A - Z_B)^2 + 4 \sum Z_A Z_B}}{2}$$

$$Z_{t2} = \frac{(Z_B - Z_A) + \sqrt{(Z_A - Z_B)^2 + 4 \sum Z_A Z_B}}{2}$$

$$Z_A = 200 \angle 0^\circ = 200 \Omega$$

$$Z_B = 400 \angle 0^\circ = 400 \Omega$$

$$Z_C = 500 \angle 0^\circ = 500 \Omega$$

$$\sum Z_A Z_B = (200)(400) + (400)(500) + (500)(200)$$

$$\sum Z_A Z_B = 3,80,000$$

$$Z_{i1} = \sqrt{3,80,000 \left[\frac{700}{900} \right]}$$

$$Z_{i1} = 543.65 \Omega$$

$$Z_{i2} = \sqrt{3,80,000 \left[\frac{900}{700} \right]}$$

$$Z_{i2} = 698.97 \Omega$$


$$Z_{t1} = \frac{(200 - 400) + \sqrt{(200 - 400)^2 + 4(3,80,000)}}{2}$$

$$Z_{t1} = 524.49 \Omega$$

$$Z_{t2} = \frac{(400 - 200) + \sqrt{(200)^2 + 4(3,80,000)}}{2}$$

$$Z_{t2} = 724.49 \Omega$$

Q2) Calculate Image Impedances

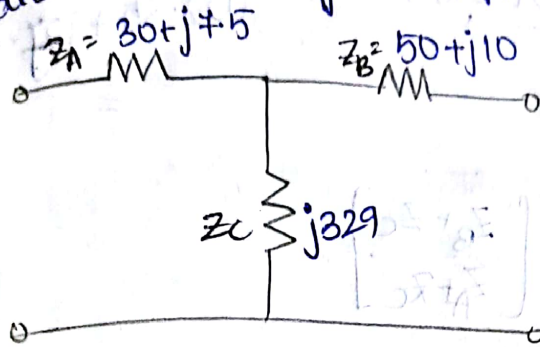

$$Z_{ii} = \sqrt{\sum Z_A Z_B \left[\frac{Z_A + Z_C}{Z_B + Z_C} \right]}$$

$$Z_A = 30 + j7.5$$

$$Z_B = 50 + j10$$

$$Z_C = j329$$

$$\sum Z_A Z_B = Z_A Z_B + Z_B Z_C + Z_C Z_A$$

$$= (30 + j7.5)(50 + j10) + (50 + j10)(j329) + (j329)(30 + j7.5)$$

$$\sum Z_A Z_B = -4332.5 + j26995$$

$$Z_{ii} = \sqrt{(-4332.5 + j26995) \left[\frac{30 + j7.5 + j329}{50 + j10 + j329} \right]}$$

$$Z_{i1} = \sqrt{-5794.31 + 26324.7j}$$

$$Z_{i1} = 26954.8 \angle 102.41$$

$$Z_{i1} = 164.1 \angle 51.205 \Rightarrow 102.85 + 127.9j$$


$$Z_{i2} = \sqrt{\left(\frac{Z_A Z_B}{Z_A + Z_B}\right) \left[\frac{Z_B + Z_C}{Z_A + Z_C}\right]}$$

$$= \sqrt{(-4332.5 + 26995j) \cdot [1.01 - 0.58j]}$$

$$= 166.853 \angle 48.123$$

$$Z_{i2} = 111.3 + 124.23j$$

Short circuit & Open Circuit Impedances
of Asymm. T-N/W:

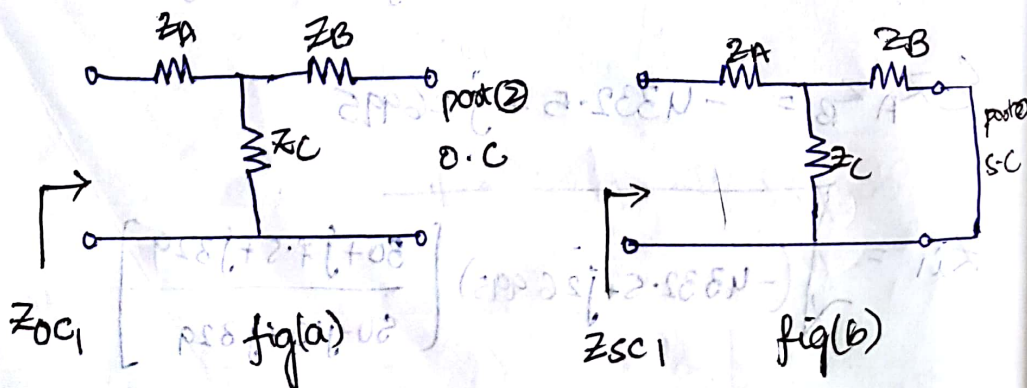

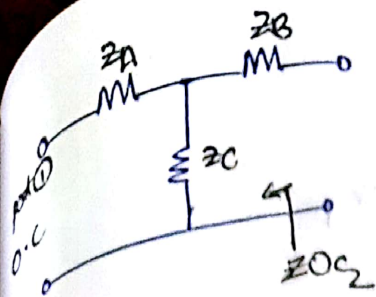


fig (c).

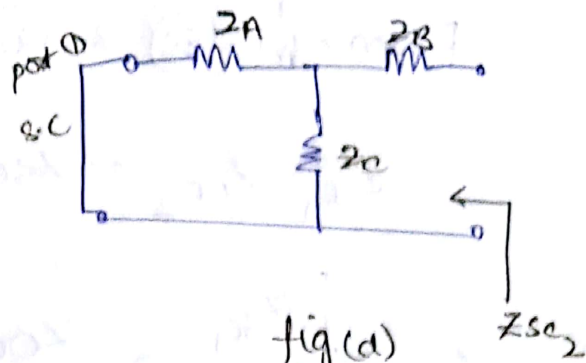


fig (d)

From fig (a); $Z_{OC1} = Z_A + Z_C \rightarrow (18a)$

" fig (c); $Z_{OC2} = Z_B + Z_C \rightarrow (18b)$

" fig (b); $Z_{SC1} = Z_A + \frac{Z_B Z_C}{Z_B + Z_C}$

$$Z_{SC1} = \frac{Z_A Z_B + Z_A Z_C + Z_B Z_C}{Z_B + Z_C} \quad \text{from (18b)}$$

$$Z_{SC1} = \frac{\sum Z_{AB}}{Z_{OC2}}$$

$$Z_{SC1} \cdot Z_{OC2} = \sum Z_A Z_B \rightarrow (18c)$$

From fig (d);

$$Z_{SC2} = Z_B + \frac{Z_A Z_C}{Z_A + Z_C}$$

$$Z_{SC2} = \frac{Z_A Z_B + Z_B Z_C + Z_A Z_C}{Z_A + Z_C}$$

$$Z_{SC2} \cdot Z_{OC1} = \sum Z_A Z_B \rightarrow (18d)$$

From eqn (18c) & (18d)

$$Z_{sc1} \cdot Z_{oc2} = Z_{sc2} \cdot Z_{oc1}$$

$$\frac{Z_{sc1}}{Z_{sc2}} = \frac{Z_{oc1}}{Z_{oc2}} \rightarrow (18e)$$

From (18d)

$$\frac{Z_{i1}}{Z_{i2}} = \frac{Z_A + Z_C}{Z_B + Z_C} = \frac{Z_{oc1}}{Z_{oc2}} \rightarrow (18f)$$

From (18e) & (18f)

$$\frac{Z_{sc1}}{Z_{sc2}} = \frac{Z_{oc1}}{Z_{oc2}} = \frac{Z_{i1}}{Z_{i2}} \rightarrow (19)$$

Now $Z_{oc1} \cdot Z_{sc1} = (Z_A + Z_C) \left[\frac{Z_A Z_B}{Z_B + Z_C} \right]$

$$Z_{i1}^2 = Z_{oc1} \cdot Z_{sc1}$$

$$Z_{i1} = \sqrt{Z_{oc1} \cdot Z_{sc1}} \rightarrow (20)$$


|| y

$$Z_{oc2} \cdot Z_{sc2} = (Z_B + Z_C) \left[\frac{Z_A Z_B}{Z_A + Z_C} \right]$$

$$Z_{i_2}^r = Z_{oc_2} Z_{sc_2}$$

$$Z_{i_2} = \sqrt{Z_{oc_2} Z_{sc_2}} \rightarrow (20)$$

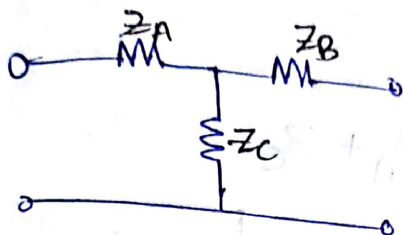Asymmetrical T-N/W Design in terms of
 Z_{sc_1} , Z_{oc_1} , Z_{oc_2} & Z_{sc_2} :-



$$Z_{oc_1} = Z_A + Z_C$$

$$Z_{oc_2} = Z_B + Z_C$$

$$Z_{oc_1} Z_{oc_2} = (Z_A + Z_C)(Z_B + Z_C)$$

$$= Z_A Z_B + Z_A Z_C + Z_B Z_C + Z_C^2$$

$$Z_{oc_1} Z_{oc_2} = \sum Z_A Z_B + Z_C^2 \rightarrow (21a)$$

w.k.T from eqn (13d)

$$Z_{i_1} Z_{i_2} = \sum Z_A Z_B$$

$$Z_{oc_1} Z_{oc_2} = Z_{i_1} Z_{i_2} + Z_C^2 \rightarrow (21b)$$

From eqn (18d)

$$Z_{sc_2} Z_{oc_1} = \left(\sum Z_A Z_B + Z_C^2 \right) - Z_C^2$$

From (21a)

$$Z_{sc2} \cdot Z_{oc1} = Z_{oc1} Z_{oc2} - Z_c^2$$

$$Z_c^2 = Z_{oc1} Z_{oc2} - Z_{oc1} Z_{sc2}$$

$$Z_c = \sqrt{Z_{oc1} [Z_{oc2} - Z_{sc2}]}$$

from

$$Z_{oc1} = Z_A + Z_c$$

$$Z_A = Z_{oc1} - \sqrt{Z_{oc1} [Z_{oc2} - Z_{sc2}]}$$


From $\rightarrow Z_{oc2} = Z_B + Z_c$

$$Z_B = Z_{oc2} - \sqrt{Z_{oc1} [Z_{oc2} - Z_{sc2}]}$$


$$\begin{aligned} \therefore Z_c &= \sqrt{Z_{oc1} [Z_{oc2} - Z_{sc2}]} \\ Z_B &= Z_{oc2} - \sqrt{Z_{oc1} [Z_{oc2} - Z_{sc2}]} \\ Z_A &= Z_{oc1} - \sqrt{Z_{oc1} [Z_{oc2} - Z_{sc2}]} \end{aligned}$$

(22)

Image Transfer Constant Intermis of Z_{oc1} , Z_{oc2} , Z_{sc1} & Z_{sc2} :-

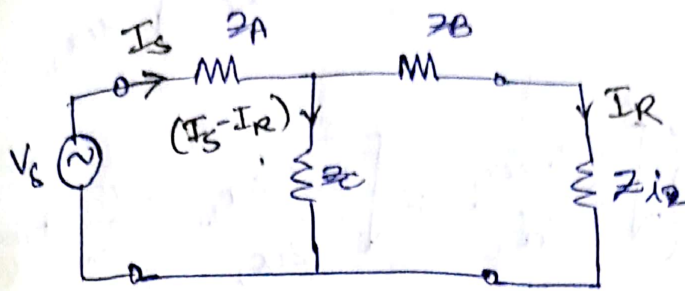

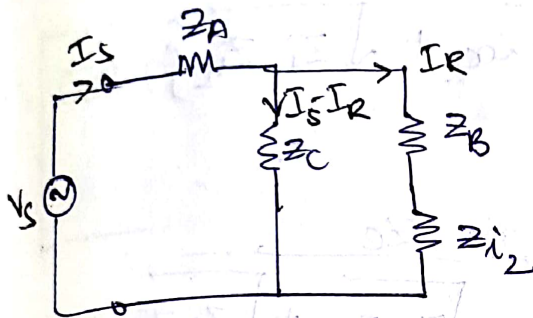w.r.t $e^{oi} = \frac{I_s}{I_R} \sqrt{\frac{Z_{i1}}{Z_{i2}}}$



$$Z_C (I_s - I_R) = (Z_B + Z_{i2}) I_R$$

$$Z_C I_s = (Z_B + Z_{i2} + Z_C) I_R$$

$$\frac{I_s}{I_R} = \frac{(Z_B + Z_C + Z_{i2})}{Z_C}$$

$$\boxed{\frac{I_s}{I_R} = \frac{Z_{oc2} + Z_{i2}}{Z_C}}$$

$$e^{oi} = \left[\frac{Z_{oc2} + Z_{i2}}{Z_C} \right] \sqrt{\frac{Z_{oc1}}{Z_{oc2}}}$$

∴ from eqn

(19)

$$e^{\theta_i} = \frac{Z_{oc2}}{Z_c} \sqrt{\frac{Z_{oc1}}{Z_{oc2}}} + \frac{Z_{i2}}{Z_c} \sqrt{\frac{Z_{oc1}}{Z_{oc2}}}$$

$$e^{\theta_i} = \frac{1}{Z_c} \left\{ \sqrt{\frac{Z_{oc1} Z_{oc2}}{Z_{oc2}}} + \sqrt{\frac{Z_{i2} Z_{oc1}}{Z_{oc2}}} \right\} \rightarrow \frac{Z_{i1}}{Z_{i2}} \text{ from (19)}$$

$$e^{\theta_i} = \frac{1}{Z_c} \left\{ \sqrt{Z_{oc1} Z_{oc2}} + \sqrt{\frac{Z_{i2} Z_{i1}}{Z_{i2}}} \right\}$$

$$e^{\theta_i} = \frac{1}{Z_c} \left\{ \sqrt{Z_{oc1} Z_{oc2}} + \sqrt{Z_{i1} Z_{i2}} \right\}$$

$$e^{-\theta_i} = \frac{1}{e^{\theta_i}} = \frac{Z_c}{\sqrt{Z_{oc1} Z_{oc2}} + \sqrt{Z_{i1} Z_{i2}}}$$

$$\cosh(\theta_i) = \frac{e^{\theta_i} + e^{-\theta_i}}{2}$$

$$\cosh \theta_i = \frac{1}{2} \left[\frac{\sqrt{Z_{oc1} Z_{oc2}} + \sqrt{Z_{i1} Z_{i2}}}{Z_c} + \frac{Z_c}{\sqrt{Z_{oc1} Z_{oc2}} + \sqrt{Z_{i1} Z_{i2}}} \right]$$

$$= \frac{1}{2} \left[\frac{Z_{oc1} Z_{oc2} + Z_{i1} Z_{i2} + 2 \sqrt{Z_{oc1} Z_{oc2}} \sqrt{Z_{i1} Z_{i2}}}{Z_c (\sqrt{Z_{oc1} Z_{oc2}} + \sqrt{Z_{i1} Z_{i2}})} \right]$$

from eqn (21b) $\cdot Z_{oc1} Z_{oc2} = Z_{i1} Z_{i2} + Z_c^2$

$$\cosh \theta_i = \frac{1}{2} \left[\frac{Z_{oc1} Z_{oc2} + Z_{oc1} Z_{oc2} + 2\sqrt{Z_{oc1} Z_{oc2} Z_{i1} Z_{i2}}}{Z_c (\sqrt{Z_{oc1} Z_{oc2}} + \sqrt{Z_{i1} Z_{i2}})} \right]$$

$$= \left[\frac{Z_{oc1} Z_{oc2} + \sqrt{Z_{oc1} Z_{oc2} Z_{i1} Z_{i2}}}{Z_c (\sqrt{Z_{oc1} Z_{oc2}} + \sqrt{Z_{i1} Z_{i2}})} \right]$$

$$= \frac{\sqrt{Z_{oc1} Z_{oc2}}}{Z_c} \left[\frac{\sqrt{Z_{oc1} Z_{oc2}} + \sqrt{Z_{i1} Z_{i2}}}{\sqrt{Z_{oc1} Z_{oc2}} + \sqrt{Z_{i1} Z_{i2}}} \right]$$

$$\boxed{\cosh \theta_i = \frac{\sqrt{Z_{oc1} Z_{oc2}}}{Z_c}}$$

w.k.T $\cosh^2 \theta_i - \sinh^2 \theta_i = 1$

$$\sinh^2 \theta_i = \cosh^2 \theta_i - 1$$

$$= \frac{Z_{oc1} Z_{oc2}}{Z_c^2} - 1$$

$$\sinh^2 \theta_i = \frac{Z_{oc1} Z_{oc2} - Z_c^2}{Z_c^2}$$

from eqn (21b), $\sinh^2 \theta_i = \frac{Z_{i1} Z_{i2}}{Z_c^2}$

$$\boxed{\sinh \theta_i = \frac{\sqrt{Z_{i1} Z_{i2}}}{Z_c}} \quad \Rightarrow \quad \text{(23a)}$$

$$\tanh \theta_i = \frac{\sinh \theta_i}{\cosh \theta_i} = \sqrt{\frac{Z_{i1} Z_{i2}}{Z_{oc1} Z_{oc2}}}$$

$$\tanh \theta_i = \sqrt{\frac{\sqrt{Z_{oc1} Z_{sc1} Z_{oc2} Z_{sc2}}}{Z_{oc1} Z_{oc2}}}$$

$$= \sqrt{\frac{\cancel{Z_{oc1}} \cancel{Z_{sc1}} \cancel{Z_{oc2}} \cancel{Z_{sc2}}}{Z_{oc1} Z_{oc2}}}$$

$$= \sqrt{\frac{Z_{sc1}}{Z_{oc1}} \cdot \frac{Z_{sc2}}{Z_{oc2}}} = \tanh \theta_i$$

from eqn (19)

$$\frac{Z_{sc1}}{Z_{oc1}} = \frac{Z_{oc1}}{Z_{sc1}}$$

$$\frac{Z_{sc2}}{Z_{oc2}} = \frac{Z_{oc2}}{Z_{sc2}}$$

$$\frac{Z_{sc1}}{Z_{oc1}} = \frac{Z_{sc2}}{Z_{oc2}}$$

$$\boxed{\tanh \theta_i = \sqrt{\frac{Z_{sc1}}{Z_{oc1}}} \quad \text{or} \quad \sqrt{\frac{Z_{sc2}}{Z_{oc2}}}}$$

Design of Asymmetrical T-Network when Z_{i1}, Z_{i2} & θ_i are given:-

$$\text{W.K.T } \sinh \theta_i = \frac{\sqrt{Z_{i1} Z_{i2}}}{Z_c}$$

$$\Rightarrow Z_c = \frac{\sqrt{Z_{i1} Z_{i2}}}{\sinh \theta_i}$$

consider;

$$\tanh \theta_i = \sqrt{\frac{Z_{i1} Z_{i2}}{Z_{oc1} Z_{oc2}}}$$

M & D by Z_{oc1}

$$\tanh \theta_i = \sqrt{\frac{Z_{i1} Z_{i2}}{Z_{oc1} Z_{oc2}} \times \frac{Z_{oc1}}{Z_{oc1}}}$$

$$\frac{Z_{oc1}}{Z_{oc2}} = \frac{Z_{i1}}{Z_{i2}}$$

$$= \sqrt{\frac{Z_{i1} Z_{i2}}{Z_{oc1}^2} \cdot \frac{Z_{i1}}{Z_{i2}}}$$

$$\tanh \theta_i = \frac{Z_{i1}}{Z_{oc1}}$$

$$\Rightarrow Z_{oc1} = \frac{Z_{i1}}{\tanh \theta_i}$$

$$Z_A = \frac{Z_i}{\tanh \theta_i} - Z_c$$

$$Z_A = \frac{Z_i}{\tanh \theta_i} - \frac{\sqrt{Z_{i1} Z_{i2}}}{\sinh \theta_i}$$

Now again;

$$\tanh \theta_i = \sqrt{\frac{Z_{i1} Z_{i2}}{Z_{OC1} Z_{OC2}} \times \frac{Z_{OC2}}{Z_{OC2}}}$$

$$\tanh \theta_i = \sqrt{\frac{Z_{i1} Z_{i2}}{Z_{i1}^2} \times \frac{Z_{i2}}{Z_{OC2}}}$$

$$\tanh \theta_i = \frac{Z_{i2}}{Z_{OC2}}$$

$$Z_{OC2} = \frac{Z_{i2}}{\tanh \theta_i}$$



$$Z_B = \frac{Z_{i2}}{\tanh \theta_i} - Z_C$$

$$Z_B = \frac{Z_{i2}}{\tanh \theta_i} - \frac{\sqrt{Z_{i1} Z_{i2}}}{\sinh \theta_i}$$

$$\boxed{\begin{aligned} Z_A &= \frac{Z_{i1}}{\tanh \theta_i} - \frac{\sqrt{Z_{i1} Z_{i2}}}{\sinh \theta_i} \\ Z_B &= \frac{Z_{i2}}{\tanh \theta_i} - \frac{\sqrt{Z_{i1} Z_{i2}}}{\sinh \theta_i} \\ Z_C &= \frac{\sqrt{Z_{i1} Z_{i2}}}{\sinh \theta_i} \end{aligned}}$$

→ (24)

Star-Delta Conversions:-

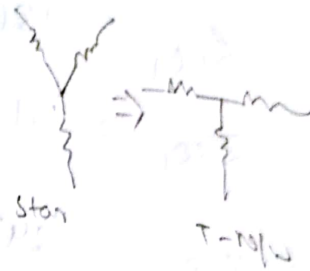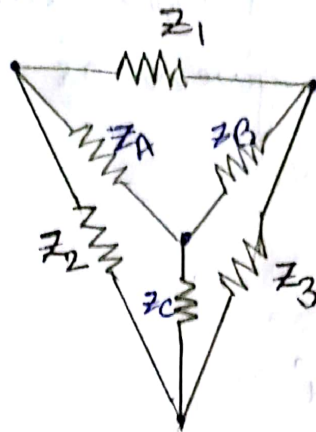

Star to Delta:-

$$Z_1 = \frac{Z_A Z_B + Z_B Z_C + Z_C Z_A}{Z_C} = \frac{\sum Z_A Z_B}{Z_C}$$

$$Z_2 = \frac{\sum Z_A Z_B}{Z_B}$$

$$Z_3 = \frac{\sum Z_A Z_B}{Z_A}$$

Delta to Star:-

$$Z_A = \frac{Z_1 Z_2}{Z_1 + Z_2 + Z_3} = \frac{Z_1 Z_2}{\sum Z_i}$$

$$Z_B = \frac{Z_1 Z_3}{\sum Z_i}$$

$$Z_C = \frac{Z_2 Z_3}{\sum Z_i}$$

problems:-

Q) For an Asymm. T-N/W O.C & S.C impedances are given as.

$$Z_{OC1} = 1260 \angle 30^\circ$$

$$Z_{SC1} = 318 \angle 72^\circ$$

$$Z_{OC2} = 2430 \angle -34^\circ$$

$$Z_{SC2} = 618 \angle 8^\circ$$

Then find;

- i, Image Impedances (Z_{i1}, Z_{i2})
- ii, Image Transfer Constant
- iii, Circuit elements (Z_A, Z_B, Z_C)

Sol:-

$$Z_{i1} = \sqrt{Z_{OC1} \cdot Z_{SC1}} ; Z_{i2} = \sqrt{Z_{OC2} \cdot Z_{SC2}}$$
$$Z_{i1} = \sqrt{1260 \angle 30^\circ \cdot 318 \angle 72^\circ} ; Z_{i2} = \sqrt{2430 \angle -34^\circ \cdot 618 \angle 8^\circ}$$

$$Z_{i1} = 632.99 \angle 51^\circ$$
$$= 1220.48 \angle -13^\circ$$

$$Z_{i2} = 1220.48 \angle -13^\circ$$

$$\tan \theta = \sqrt{\frac{Z_{SC1}}{Z_{OC1}}}$$
$$= \sqrt{\frac{318 \angle 72^\circ}{1260 \angle 30^\circ}} = 0.5 \angle 21^\circ$$

$$Z_A = Z_{OC1} - Z_C \rightarrow -427.94 + 218j$$

$$Z_B = Z_{OC2} - Z_C \rightarrow 435.62 - 1140.55j$$

$$Z_C = \sqrt{Z_{OC1} [Z_{OC2} - Z_{SC2}]}$$

$$\rightarrow \frac{e^{j\omega t} - e^{-j\omega t}}{e^{j\omega t} + e^{-j\omega t}} = \frac{0.46 + j0.17}{1}$$

Componendo & Dividendo

$$\frac{e^{j\omega t} - e^{-j\omega t} + e^{j\omega t} - e^{-j\omega t}}{e^{j\omega t} - e^{-j\omega t} - e^{j\omega t} - e^{-j\omega t}} = \frac{1.46 + j0.17}{-0.54 + j0.17}$$

$$\frac{2e^{j\omega t}}{-2e^{-j\omega t}} = \frac{1.46 \angle 6.64}{0.566 \angle 162.52^\circ}$$

2) For an asymmetrical T-N/W O.C & S.C impedances are given as

$$Z_{OC1} = 200 \angle 0^\circ \Omega$$

$$Z_{OC2} = 40 \angle 0^\circ \Omega$$

$$Z_{SC1} = 219 \angle 0^\circ \Omega$$

$$Z_{SC2} = 68 \angle 0^\circ \Omega$$

Calculate the image & Iterative impedances & image & iterative transfer constant.

Sol: Given:

$$Z_{OC1} = 200 \Omega$$

$$Z_{OC2} = 40 \Omega$$

$$Z_{SC1} = 219 \Omega$$

$$Z_{SC2} = 68 \Omega$$

$$Z_{i1} = \sqrt{Z_{OC1} \cdot Z_{SC1}}$$

$$Z_{i2} = \sqrt{Z_{OC2} \cdot Z_{SC2}}$$

$$Z_{i1} = \sqrt{200 \times 219} = 209.284 \Omega$$

$$Z_{i2} = \sqrt{40 \times 68} = \sqrt{2720} = 52.153 \Omega$$

Iterative Impedances

$$Z_{t1} = (Z_A - Z_B) + \sqrt{(Z_B \cdot Z_n)^2 + 4Z_A Z_B}$$

$$\begin{aligned} Z_A &= Z_{OC1} - \sqrt{Z_{OC1}(Z_{OC2} - Z_{SC2})} \\ &= 200 - \sqrt{200(40 - 60)} \end{aligned}$$

$$Z_A = 200 - j74.83$$

$$\begin{aligned} Z_B &= Z_{OC2} - \sqrt{Z_{OC1}(Z_{OC2} - Z_{SC2})} \\ &= 40 - \sqrt{200(40 - 60)} \end{aligned}$$

$$Z_B = 40 - j74.83$$

$$\begin{aligned} Z_C &= \sqrt{Z_{OC1}(Z_{OC2} - Z_{SC2})} \\ &= \sqrt{200(40 - 60)} \end{aligned}$$

$$Z_C = j74.83$$

$$Z_{t1} = (200 - j74.83) - (40 - j74.83) +$$

$$\sqrt{(40 - j74.83) - (200 - j74.83)} \cdot 4(13599.52)$$

2

$$Z_{t1} = 168.088 \Omega$$





$$Z_{t2} = -(Z_A - Z_B) + \sqrt{(Z_B - Z_A) + 4Z_A Z_B}$$

$$Z_{t3} = -168.688 \Omega$$

$$\therefore Z_{t4} = -Z_{t3}$$

==

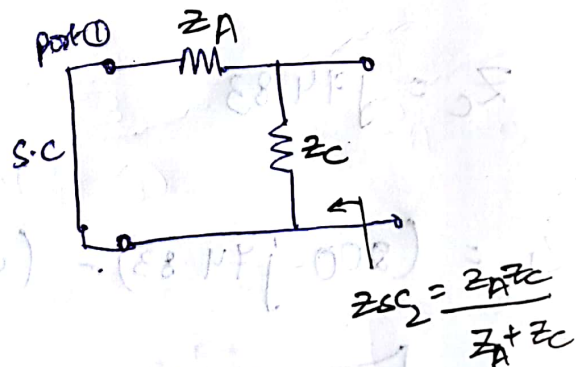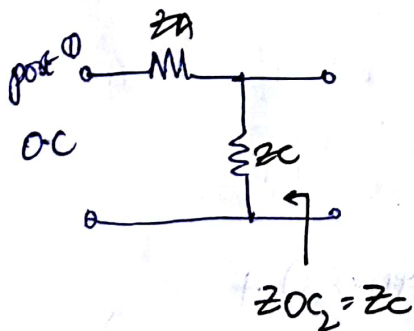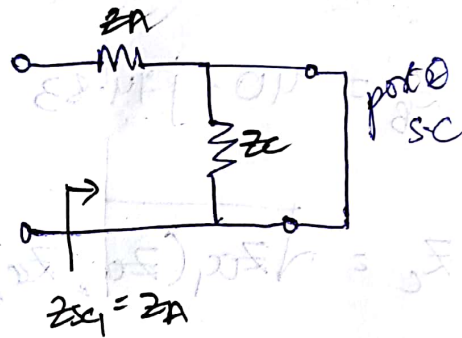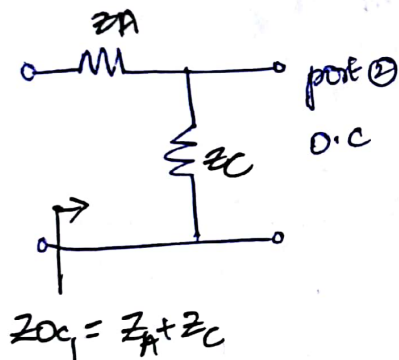Z_{i1} & Z_{i2} of L-N/W in terms of short & open circuit Impedances:-



$$Z_{sc1} Z_{oc2} = Z_A (Z_A + Z_C)$$

$$Z_{sc1} \cdot Z_{oc2} = Z_i^2$$

$$\therefore Z_{i1} = \sqrt{Z_A^2 + Z_A Z_C}$$

$$Z_{i1} = \sqrt{Z_{sc1} Z_{oc2}}$$

consider


$$Z_{SC2} Z_{OC2} = \frac{Z_A \cdot Z_C^2}{(Z_A + Z_C)}$$

$$= Z_{i2}^2$$



$$\therefore Z_{i2} = Z_C \sqrt{\frac{Z_A}{Z_A + Z_C}}$$

$$Z_{i2} = \sqrt{Z_{SC2} \cdot Z_{OC2}}$$


Half Sections:-

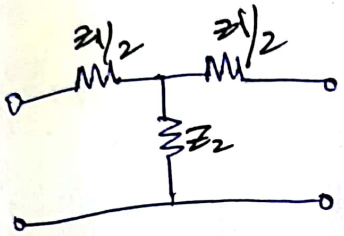

=

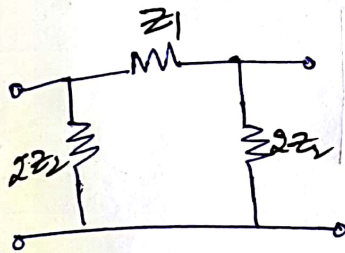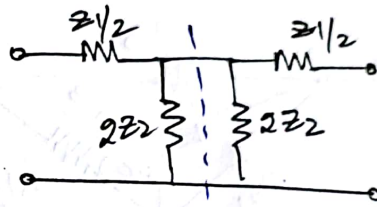


=

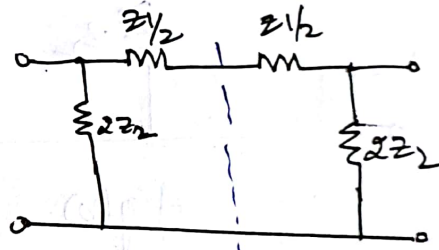

Half sections are the L-NW's extracted from either symmetrical π or T-NW, ^{when} equally divided

Bridged - T NW Analysis (Symmetrical):-

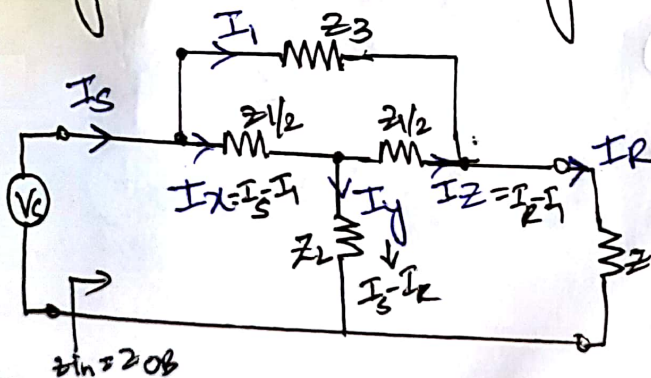

$Z_{OB} \rightarrow$ Characteristic impedance of Symmetrical Bridge T-NW

$$I_S = I_1 + I_x \Rightarrow I_x = I_S - I_1$$

$$I_R = I_1 + I_2 \Rightarrow I_2 = I_R - I_1$$

$$I_x = I_y + I_2$$

$$I_y = I_x - I_2$$

$$= I_S - I_1 - I_R + I_1$$

$$I_y = I_S - I_R$$

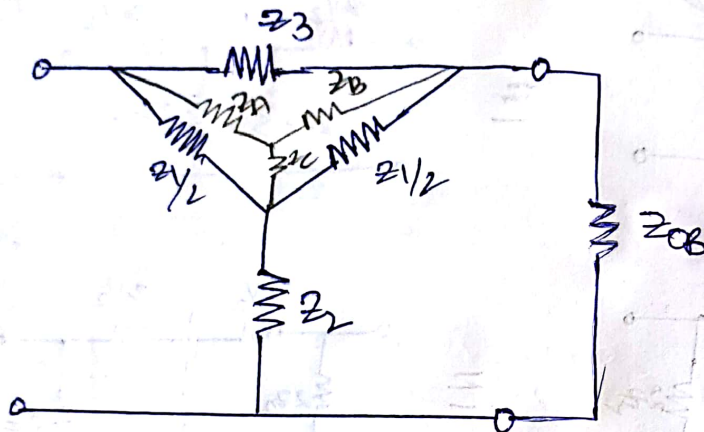



Fig (b).

$$Z_A = \frac{Z_1 \cdot Z_3}{Z_1 + Z_3} = \frac{Z_1 Z_3}{2(Z_1 + Z_3)}$$

i.e. $Z_A = Z_B$

$$Z_B = \frac{Z_1 Z_3}{2(Z_1 + Z_3)}$$
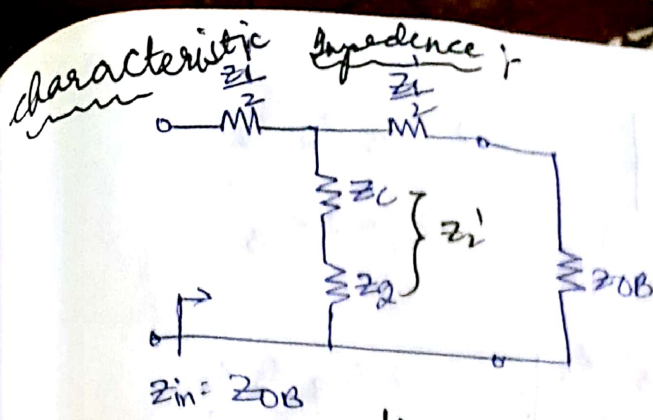
$$Z_C = \frac{\left(\frac{Z_1}{2}\right)^2}{Z_1 + Z_3}$$



$$\frac{Z_1'}{2} = \frac{Z_1 Z_3}{2(Z_1 + Z_3)} ; Z_2' = Z_2 + Z_c = Z_2 + \frac{Z_1'}{4(Z_1 + Z_3)}$$

$$Z_{OB} = \sqrt{\frac{Z_1'}{4} + Z_2' Z_2'}$$

$$= \sqrt{\frac{Z_1^2 Z_3^2}{4(Z_1 + Z_3)^2} + \frac{Z_1 Z_2 Z_3}{(Z_1 + Z_3)} + \frac{Z_1^3 Z_3}{4(Z_1 + Z_3)^2}}$$

$$= \sqrt{\frac{Z_1^2 Z_3 (Z_3 + Z_1)}{4(Z_1 + Z_3)^2} + \frac{Z_1 Z_2 Z_3}{(Z_1 + Z_3)}}$$

$$Z_{OB} = \sqrt{\frac{Z_1^2 Z_3}{4(Z_1 + Z_3)} + \frac{Z_1 Z_2 Z_3}{(Z_1 + Z_3)}}$$

But, in practical cases $\frac{Z_1}{2}$ is replaced by Z_{OB}

$\left[\frac{Z_1}{2} = Z_{OB} \right]$

$$Z_{OB}^2 = \frac{Z_{OB}^2 Z_3}{2Z_{OB} + Z_3} + \frac{2Z_{OB} Z_2 Z_3}{2Z_{OB} + Z_3}$$

$$Z_{OB} \left[1 - \frac{Z_3}{2Z_{OB} + Z_3} \right] = \frac{2Z_{OB} Z_2 Z_3}{Z_3 + 2Z_{OB}}$$

$$Z_{OB} = \left[\frac{Z_3 + 2Z_{OB} - Z_3}{Z_3 + 2Z_{OB}} \right] = \frac{2Z_{OB} Z_2 Z_3}{(Z_3 + 2Z_{OB})}$$

$$Z_{OB} = Z_2 Z_3$$

$$Z_{OB} = \sqrt{Z_2 * Z_3}$$

$$\text{for } \frac{Z_1}{2} = Z_{OB}$$

ii) propagation constant (p):-

$$V_S = Z_{in} I_S = Z_{OB} I_S ; \quad V_R = Z_R I_R = Z_{OB} I_R$$

Apply KVL to outer loop:-

$$V_S = Z_3 I_1 + V_R \rightarrow (25a)$$

$$\Rightarrow I_1 = \frac{V_S - V_R}{Z_3} = \frac{Z_{OB}}{Z_3} (I_S - I_R)$$

$$Z_3 I_1 = \frac{Z_1}{2} (I_S - I_1) + \frac{Z_1}{2} (I_R - I_1)$$

$$Z_3 I_1 = \frac{Z_1}{2} (I_S - 2I_1 + I_R) \rightarrow (25b)$$

Sub eqn (21b) in eqn (20a)

$$Z_{OB} I_S = \frac{Z_1}{2} (I_S - R I_1) + I_R + Z_{OB} I_R$$

$$Z_{OB} I_S = \frac{Z_1}{2} I_S - Z_1 I_1 + \left(\frac{Z_1}{2} + Z_{OB} \right) I_R$$

$$Z_{OB} I_S = \frac{Z_1}{2} I_S - \frac{Z_1 Z_{OB}}{Z_3} I_S + \frac{Z_1 Z_{OB}}{Z_3} I_R + \left(\frac{Z_1}{2} + Z_{OB} \right) I_R$$

$$I_S \left[Z_{OB} - \frac{Z_1}{2} + \frac{Z_1 Z_{OB}}{Z_3} \right] = \left[Z_{OB} + \frac{Z_1}{2} + \frac{Z_1 Z_{OB}}{Z_3} \right] I_R$$

$$\frac{I_S}{I_R} = e^P = \frac{\left[Z_{OB} + \frac{Z_1 Z_{OB}}{3} + \frac{Z_1}{2} \right]}{\left[Z_{OB} + \frac{Z_1 Z_{OB}}{3} - \frac{Z_1}{2} \right]}$$

But practically, we consider $\frac{Z_1}{2} = Z_{OB}$

$$e^P = \frac{\left[2Z_{OB} + \frac{2Z_{OB}^2}{Z_3} \right]}{2Z_{OB}}$$

$$e^P = \frac{2Z_{OB}}{\left(\frac{2Z_{OB}^2}{Z_3} \right)} + 1$$

$$e^P = 1 + \frac{Z_3}{Z_{OB}}$$

$$\text{W.T.T } Z_{OB} = \sqrt{Z_2 Z_3} \Rightarrow \frac{Z_{OB}^2}{Z_2} = Z_3$$

$$e^P = 1 + \frac{Z_{OB}^2}{Z_2 Z_{OB}}$$

$$e^P = 1 + \frac{Z_{OB}}{Z_2}$$


problem:-

Q1) Evaluate characteristic Impedence & propagation constant of a bridged T-network which consists of series arm resistance 1200Ω & shunt arm resistance 900Ω & bridged arm resistance 400Ω

Soln

$$Z_{OB} = \sqrt{\frac{Z_1^2 Z_3}{4(Z_1 + Z_3)} + \frac{Z_1 Z_2 Z_3}{(Z_1 + Z_3)}}$$
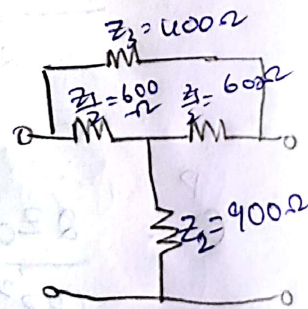
$$= \sqrt{\frac{Z_3}{(Z_1 + Z_3)} \left[\frac{Z_1^2}{4} + Z_1 Z_2 \right]}$$



$$\boxed{Z_{0B} = 600 \Omega}$$

propagation const :

$$e^P = 1 + \frac{Z_{0B}}{Z_2}$$

$$= 1 + \frac{600}{900}$$

$$e^P = 1.66 \text{ Np}$$

$$P = \ln(1.66)$$

$$\boxed{P = 0.506 \text{ Np}}$$