

UNIT - III

* ATTENUATORS & EQUALIZERS *

Attenuator:- It is a N/W which reduces the i/p signal strength by a given amount.

Attenuators are basically classified into 2 types;

1) Fixed Attenuators \rightarrow (PAD'S)

2) Variable Attenuators

\rightarrow In attenuators we only require attenuation i.e. 'no' phase shift is reqd.

\therefore Attenuators are designed by purely resistive elements.

\rightarrow w.k.T propagation const $P = \alpha + j\beta$


As we know attenuators doesn't consist any reactive elements (L & C) & hence

$$\boxed{\beta = 0} \Rightarrow \boxed{\therefore P = \alpha}$$

\rightarrow Attenuation is measured either in 'Neper' or decibels (dB)

$$\boxed{1 \text{ Neper} = 8.686 \text{ dB}}$$

* Consider an attenuator now shown below

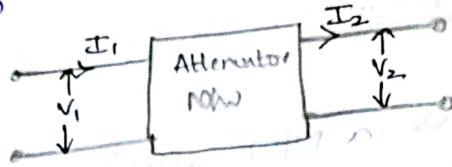

ip power $P_1 = V_1 I_1$

o/p power $P_2 = V_2 I_2$

Attenuation in decibels is

$$D = 10 \log_{10} \left(\frac{P_1}{P_2} \right) \rightarrow \textcircled{1}$$

let a parameter

$$N = \sqrt{\frac{P_1}{P_2}} \Rightarrow N^2 = \frac{P_1}{P_2}$$

$$D = 10 \log_{10} N^2$$

$$D = 20 \log_{10} N$$

(a)

$$N = 10^{D/20}$$

$$\rightarrow \textcircled{2}$$

→ Attenuators can be designed either in symm. (a) Asymm. form.

Symmetrica

- * → Symm.
- * → Symm.
- * → Symm.
- * → Symm.

Asymmetric

- * → asym
- * → asym
- * → asym


Symmetric

- Symm.
- * → Symm. T-pad **
 - * → Symm. π -pad **
 - * → Symm. Bridged T-pad
 - * → Symm. Lattice pad.

Asymmetrical Attenuators:

- * → asymm. T-pad **
- * → asymm. π -pad
- * → asymm. L-pad **

Symmetrical Attenuators:

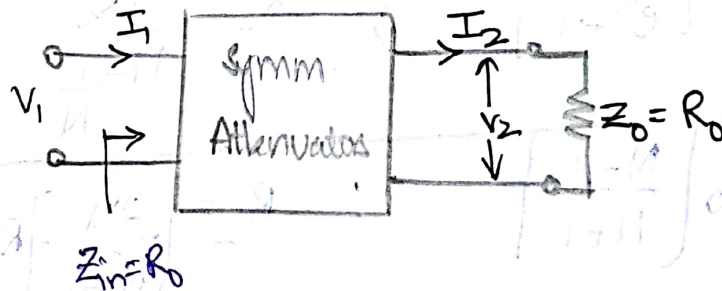

$P = \alpha$ (only Attenuation const)


$Z = R_0$ (only pure resistance)

$$\frac{P_1}{P_2} = \frac{V_1 I_1}{V_2 I_2} = \frac{I_1^2 R_0}{I_2^2 R_0}$$

$$\frac{P_1}{P_2} = \frac{I_1^2}{I_2^2} \quad \text{but } (N = \sqrt{\frac{P_1}{P_2}})$$

$$N = \sqrt{\frac{P_1}{P_2}} = \frac{I_1}{I_2} = e = 10^{D/20}$$

Symmetrical T-pad :-

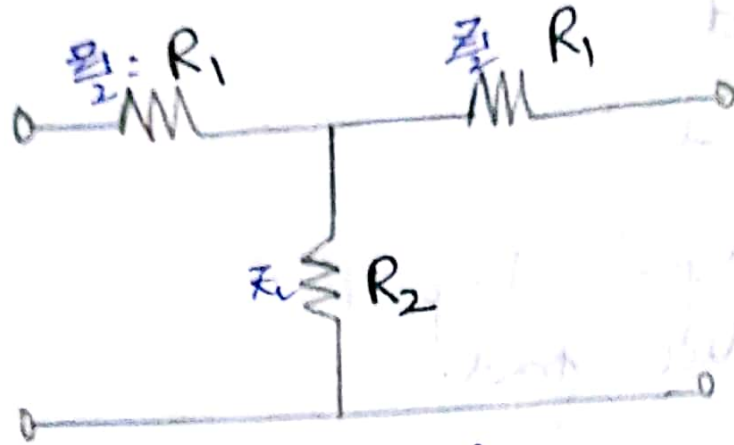

$$Z_{OT} = R_0$$

Symm. T-pad.

$$P = \alpha, \quad ; \quad Z_0 = R_0$$

$$R_1 = R_0 \tanh\left(\frac{\alpha}{2}\right) \quad ; \quad R_2 = \frac{R_0}{\sinh \alpha}$$

$$= R_0 \frac{e^{\frac{\alpha}{2}} - e^{-\frac{\alpha}{2}}}{e^{\frac{\alpha}{2}} + e^{-\frac{\alpha}{2}}} \quad ; \quad R_2 = \frac{2R_0}{e^{\alpha} - e^{-\alpha}}$$

\downarrow $\left(\frac{e^{\alpha}}{2}\right)$ common

$$= R_0 \left[\frac{e^{\alpha} - 1}{e^{\alpha} + 1} \right] \quad ; \quad R_2 = \frac{2R_0}{N - \frac{1}{N}}$$

$$\boxed{R_1 = R_0 \left[\frac{N-1}{N+1} \right] \quad ; \quad R_2 = \left[\frac{2N}{N^2-1} \right] R_0}$$

$$R_1 = R_0 \sinh \alpha$$

$$= R_0 \left[\frac{e^\alpha - e^{-\alpha}}{2} \right]$$

$$= \frac{R_0}{2} \left[N - \frac{1}{N} \right]$$

$$R_1 = R_0 \left[\frac{N^2 - 1}{2N} \right]$$

$$R_2 = \frac{R_0}{\tanh(\alpha/2)}$$

$$= R_0 \left[\frac{e^{\alpha/2} + e^{-\alpha/2}}{e^{\alpha/2} - e^{-\alpha/2}} \right]$$

$$= R_0 \left[\frac{e^\alpha + 1}{e^\alpha - 1} \right]$$

$$R_2 = R_0 \left[\frac{N+1}{N-1} \right]$$

problems:-

Q1) Design a T-pad Attenuator to give a attenuation of 20dB. calculate characteristic impedance is 600Ω

Sol) Given $R_0 = 600\Omega$

$$D = 20\text{dB}$$

For symm T-pad

$$N = 10^{D/20} = 10^{20/20} = 10$$

$$= 10 \quad \therefore N = 10$$

$$R_1 = R_0 \left[\frac{N-1}{N+1} \right]$$


$$= 600 \left[\frac{10-1}{10+1} \right]$$

$$R_1 = 490.9\Omega$$

$$R_2 = \left[\frac{2N}{N^2-1} \right]$$

$$R_2 = \left[\frac{2 \times 10}{10^2 - 1} \right]$$

$$R_2 = 121.21\Omega$$

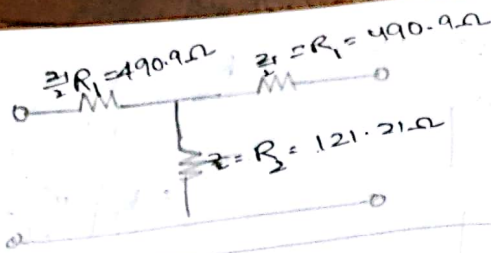

Q2) Design a π -type attenuator with 15dB attenuation to match impedance of $75 \angle 0^\circ \Omega$.

sol:- Given $D = 15 \text{ dB}$

& characteristic imp. $R_0 = 75 \angle 0^\circ = 75 \Omega$.


$$N = 10^{\frac{D}{20}} \Rightarrow 10^{\frac{15}{20}} \Rightarrow \boxed{N = 5.62}$$

$$R_1 = R_0 \left[\frac{N^2 - 1}{2N} \right] ; R_2 = R_0 \left[\frac{N + 1}{N - 1} \right]$$

$$= 75 \left[\frac{(5.62)^2 - 1}{2 \times 5.62} \right] ; = 75 \left[\frac{5.62 + 1}{5.62 - 1} \right]$$

$$\boxed{R_1 = 204.07 \Omega}$$
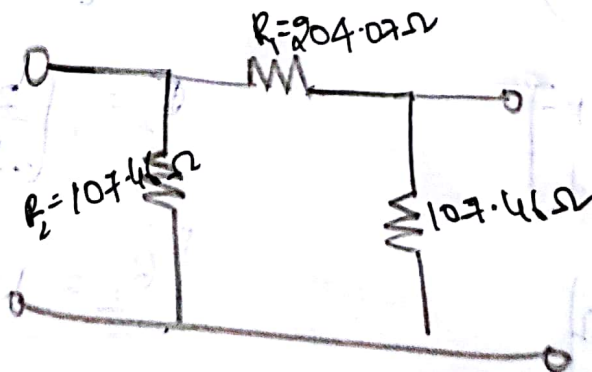
$$\therefore \boxed{R_2 = 107.46 \Omega}$$



Q3) Design symmetrical attenuation is 500Ω .

sol: T-pad:-

Given $\alpha = 2.0$
& $R_0 = 500$

$$N = e^\alpha = e^2$$

$$R_1 = R_0 \left[\frac{N - 1}{N + 1} \right]$$

$$= 500 \left[\frac{9.01 - 1}{9.01 + 1} \right]$$

$$\boxed{R_1 = 400 \Omega}$$

π -pad:-

$$R_1 = R_0 \left[\frac{N^2 - 1}{2N} \right]$$

$$= 500 \left[\frac{9.01 - 1}{2 \times 9.01} \right]$$

$$R_1 = 22 \dots$$

Q7 Design Symm Tl π -pad with attenuation 2.199 Np & design impedance is 500 Ω .

(a) T-pad:-

Given $\alpha = 2.199 N_p$
& $R_0 = 500 \Omega$


$$N = e^\alpha = e^{2.199} \Rightarrow \boxed{N = 9.01}$$

$$R_1 = R_0 \left[\frac{N-1}{N+1} \right] ; R_2 = \left[\frac{2N}{N^2-1} \right] R_0$$

$$= 500 \left[\frac{9.01-1}{9.01+1} \right] ; = \left[\frac{2 \times 9.01}{(9.01)^2 - 1} \right] \times 500$$

$$\boxed{R_1 = 400 \Omega}$$

$$\boxed{R_2 = 112.37 \Omega}$$

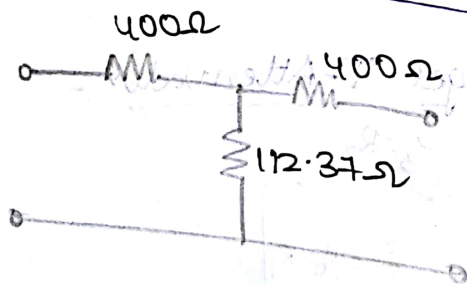

π -pad:-


$$R_1 = R_0 \left[\frac{N^2-1}{2N} \right] ; R_2 = R_0 \left[\frac{N+1}{N-1} \right]$$

$$= 500 \left[\frac{9.01^2-1}{2 \times 9.01} \right] = 500 \left[\frac{9.01+1}{9.01-1} \right]$$

$$R_1 = 2226.018$$

$$\boxed{R_2 = 624.76 \Omega}$$


$$\boxed{R_1 = 2.22 k\Omega}$$

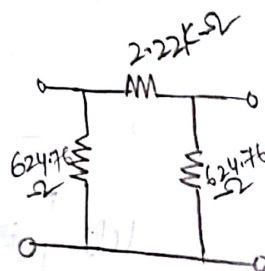

6/9/18

Symm. Bridged T-Attenuator:-

W.K.T Bridged T-N/W

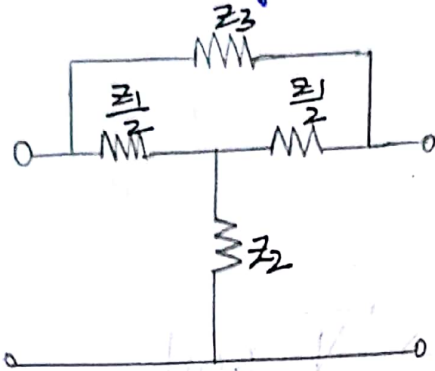


By considering $\frac{Z_1}{2} = Z_0$

then we get $Z_0 = \sqrt{Z_2 Z_3}$

$$e^p = 1 + \frac{Z_3}{Z_0} \quad \text{or} \quad e^p = 1 + \frac{Z_0}{Z_2}$$

Standard Bridged T-Attenuator:-

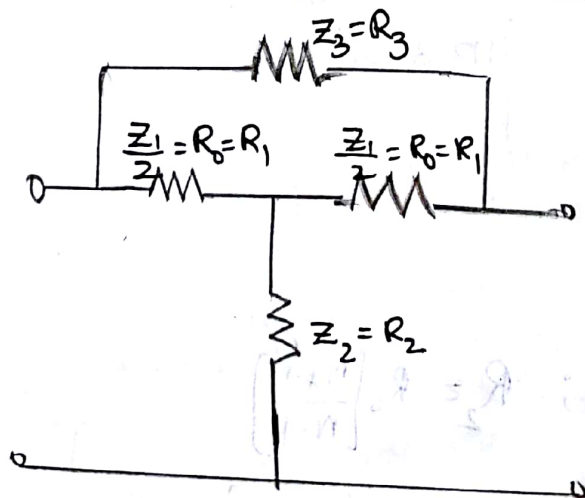

where
 $Z_0 = R_0$
 k
 $p = \alpha$

let $\frac{Z_1}{2} = R_0 = R_1$

$$\text{let } e^p = 1 + \frac{Z_3}{Z_0}$$

$$e^P = 1 + \frac{R_3}{R_0}$$

w.e.T for symm. N/w $e^\alpha = N = 10 \Rightarrow \frac{I_s}{I_R} \quad D/20$

$$\therefore N-1 = \frac{R_3}{R_0}$$

$$\boxed{R_3 = R_0(N-1)}$$

Also consider; $e^P = 1 + \frac{Z_0}{Z_2}$

$$e^\alpha = 1 + \frac{R_0}{R_2}$$

$$\frac{R_0}{R_2} = e^\alpha - 1$$

$$\frac{R_0}{R_2} = N - 1$$

$$\boxed{R_2 = \frac{R_0}{N-1}}$$


$$\therefore R_1 = R_0$$

$$R_2 = \frac{R_0}{(N-1)}$$

$$R_3 = R_0(N-1)$$

$$\boxed{N = e^\alpha = 10 \quad D/20 = \frac{I_s}{I_R}}$$

Symm. Lattice Network:-

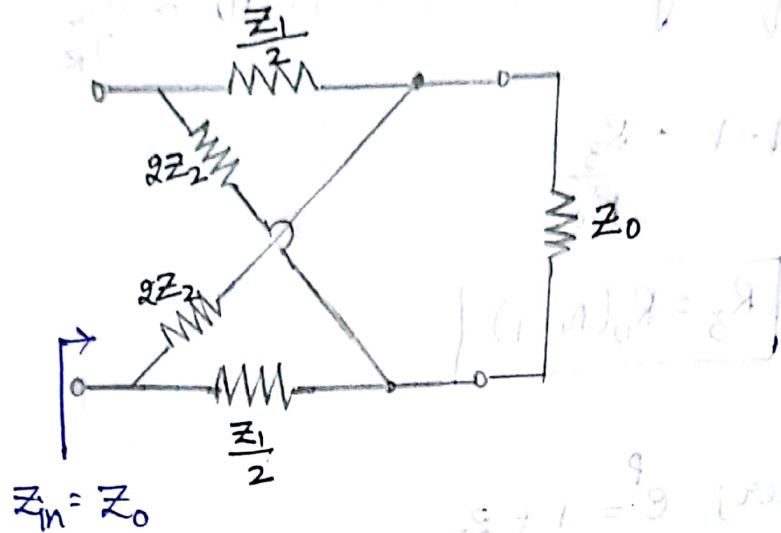


If P & Z_o are known

$$\frac{Z_1}{2} = Z_o \tanh\left(\frac{P}{2}\right)$$

$$2Z_2 = \frac{Z_o}{\tanh\left(\frac{P}{2}\right)}$$

Lattice Attenuator:-

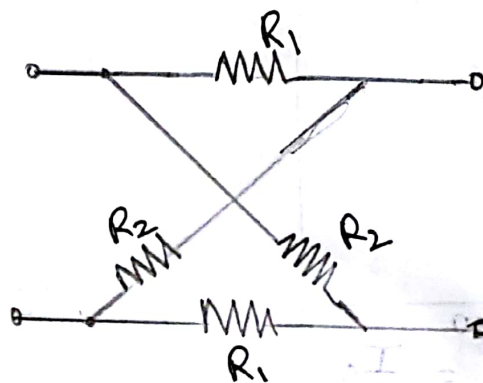Let $\frac{Z_1}{2} = R_1$
 $2Z_2 = R_2$ } → In lattice netw



$$Z_o = R_o \quad \& \quad P = \alpha$$

W.K.T for lattice N (w)

$$R_1 = Z_0 \tanh\left(\frac{P}{2}\right)$$

$$R_1 = R_0 \tanh\left(\frac{\alpha}{2}\right)$$

$$R_1 = R_0 \left[\frac{e^{\frac{\alpha}{2}} - e^{-\frac{\alpha}{2}}}{e^{\frac{\alpha}{2}} + e^{-\frac{\alpha}{2}}} \right]$$

$$= R_0 \frac{e^{-\frac{\alpha}{2}}}{e^{\frac{\alpha}{2}}} \left[\frac{e^{\alpha} - 1}{e^{\alpha} + 1} \right]$$

$$R_1 = R_0 \left[\frac{N-1}{N+1} \right]$$

$$2Z_0 = \frac{Z_0}{\tanh\left(\frac{P}{2}\right)}$$

$$R_2 = \frac{R_0}{\tanh\left(\frac{\alpha}{2}\right)}$$

$$R_2 = R_0 \left[\frac{e^{\frac{\alpha}{2}} + e^{-\frac{\alpha}{2}}}{e^{\frac{\alpha}{2}} - e^{-\frac{\alpha}{2}}} \right]$$

$$= R_0 \frac{e^{-\frac{\alpha}{2}}}{e^{\frac{\alpha}{2}}} \left[\frac{e^{\alpha} + 1}{e^{\alpha} - 1} \right]$$

$$R_2 = R_0 \left[\frac{N+1}{N-1} \right]$$

09/18

Problem:

Q1) Design a following
 with 40dBⁿ Symm. Bridged T- attenuator
 600Ωⁿ attenuation & design impedance

i) Bridged-T

ii) lattice Attenuator.

Sol: $R_0 = 600\Omega$

$D = 40\text{dB}$

$N = 10^{\frac{D}{20}} \Rightarrow 10^{\frac{40}{20}} = 100$


$\therefore N = 100$

i. Bridged T-Attenuator :-

$$R_1 = R_0 = 600 \Omega$$

$$R_2 = \frac{R_0}{N-1} = \frac{600}{100-1} = 6.06 \Omega$$
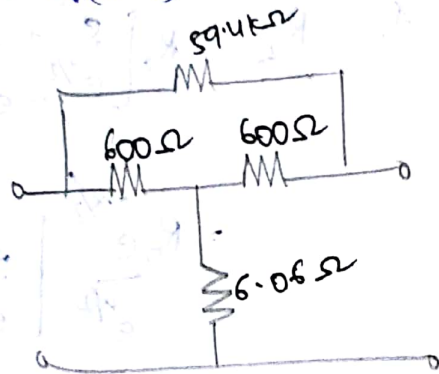
$$R_3 = R_0(N-1) = 59.4 \text{ K}\Omega$$



ii. Lattice Attenuator :-

$$R_1 = R_0 \left[\frac{N-1}{N+1} \right]$$


$$R_2 = R_0 \left[\frac{N+1}{N-1} \right]$$

$$= 600 \left[\frac{100-1}{10+1} \right]$$

$$= 600 \left[\frac{100+1}{100-1} \right]$$

$$R_1 = 588.11 \Omega$$

$$R_2 = 612.12 \Omega$$

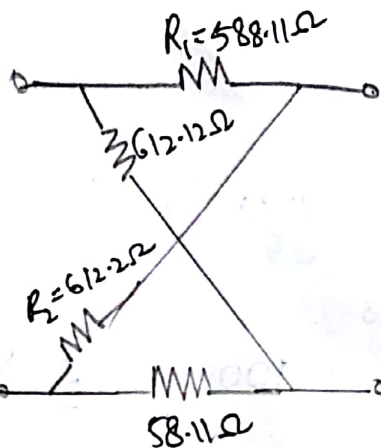

Design 'balanced' symm. T-Attenuator
 design imp. 500Ω & 20dB attenuation

$R_0 = 500\Omega$
 $D = 20dB$

$N = 10^{D/20} = 10^{20/20} = 10$

Symm. T-Attenuator :-

$$R_1 = R_0 \left[\frac{N-1}{N+1} \right]$$


$$R_2 = \left[\frac{2N}{N^2-1} \right] R_0$$

$$= 500 \left[\frac{10-1}{10+1} \right]$$


$$= \left[\frac{2 \cdot 10}{10^2-1} \right] \times 500$$

$R_1 = 409.09\Omega$

$R_2 = 101.01\Omega$

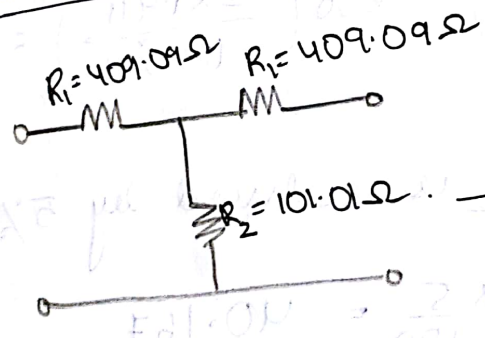

Unbalanced symm. T-pad

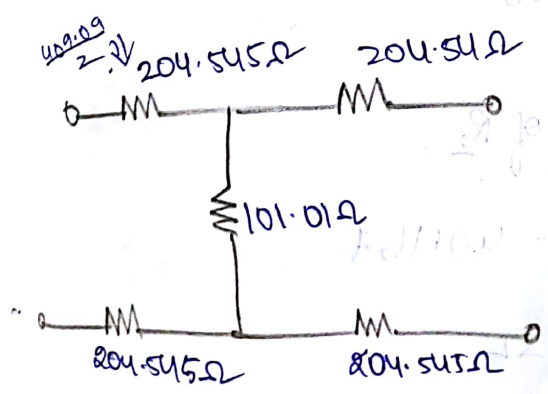

Balanced symm. T-pad.

Q3. Design a symm. T-pad to operate b/w 600Ω resistances & to provide an attenuation of 6dB. What would be the error in the attenuation when shunt arm resistor is reduced by 5%.

sol: $R_0 = 600 \Omega$

let $D_1 = 6 \text{ dB}$

$$N = 10^{\frac{D/20}{10}} \Rightarrow 10^{\frac{6/20}{10}} = 1.995$$

$$R_1 = R_0 \left(\frac{N-1}{N+1} \right) = 600 \left(\frac{1.995-1}{1.995+1} \right) = 199.33 \Omega$$

$$R_2 = R_0 \left(\frac{2N}{N^2-1} \right) = 600 \left(\frac{2 \times 1.995}{(1.995)^2-1} \right) = 803.34 \Omega$$

Given that R_2 is reduced by 5%.

$$803.34 \times \frac{5}{100} = 40.167$$

$$R_2' \Rightarrow R_2 - 5\% \text{ of } R_2$$

$$= 803.34 - 40.167$$

$$R_2' = 763.17 \Omega$$

$$R_2' = R_0 \left[\frac{2N'}{N'^2-1} \right] \Rightarrow 600 \left[\frac{2N'}{N'^2-1} \right]$$

symm. T-pad to
 Ω resistances &
 attenuation of 6dB.
 error in the
 shunt arm resistor
 %.

$$163.17 = 600 \left[\frac{2N'}{N'^2 - 1} \right]$$

$$\frac{163.17}{600} \cdot (N'^2 - 1) = 2N'$$

$$\Rightarrow 1.27N'^2 - 2N' - 1.27 = 0$$

$$N' = 2.06 \text{ or } -0.48 \times$$

$$\boxed{N' = 2.06}$$

$$N' = 10^{\frac{D_2}{20}}$$

$$2.06 = 10^{\frac{D_2}{20}}$$

$$D_2 = 20 \log N'$$

$$D_2 = 20 \log(2.06)$$

$$\boxed{D_2 = 6.27 \text{ dB}}$$

$$\text{Error} = D_2 - D_1$$


$$= 6.27 - 6$$

$$\boxed{\text{Error} = 0.27 \text{ dB}}$$

\therefore Error detected 24%

Asymmetrical Attenuators:-

For unequal Impedences:-

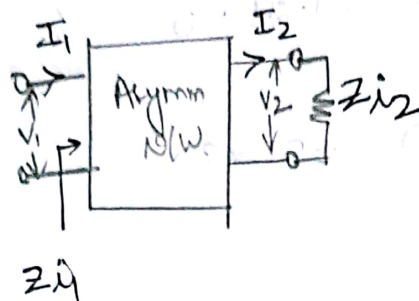

w.k.T

$$N = \sqrt{\frac{P_1}{P_2}} = \sqrt{\frac{V_1 I_1}{V_2 I_2}} = \sqrt{\frac{I_1^2 Z_{i1}}{I_2^2 Z_{i2}}} = \frac{I_1}{I_2} \sqrt{\frac{Z_{i1}}{Z_{i2}}}$$

$$e^{j\theta_i} = e^{j\theta_i}$$


Since Attenuators are pure, resistive


$$\theta_i = A_i \quad \& \quad \theta_t = A_t$$

$$Z_{i1} = R_{i1} \quad \& \quad Z_{i2} = R_{i2}$$

$$N = \sqrt{\frac{P_1}{P_2}} = \frac{I_1}{I_2} \sqrt{\frac{R_{i1}}{R_{i2}}} = e^{A_i} = 10$$

For Equal Impedences:-

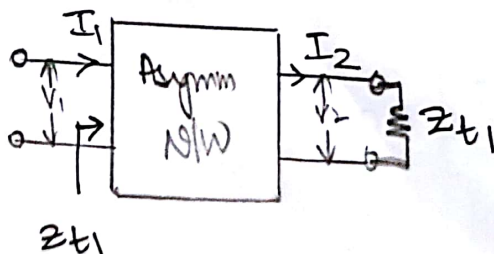

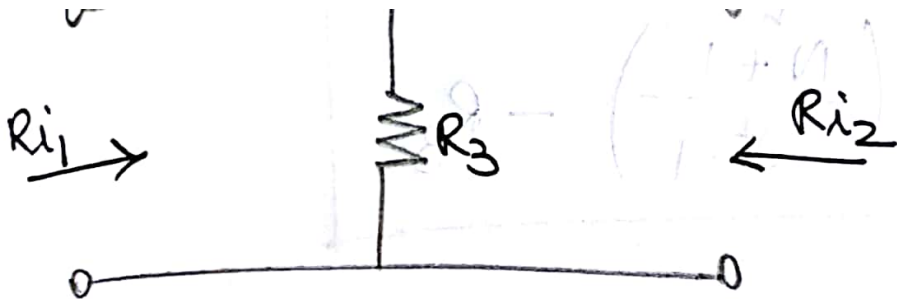

let $Z_A = R_1$

$Z_B = R_2$

$Z_C = R_3$

since attenuation is a resistive θ

$\theta_i = A_i$, $Z_{i1} = R_{i1}$ & $Z_{i2} = R_{i2}$

$$R_3 = \frac{\sqrt{R_{i1} R_{i2}}}{\sinh A_i} = \frac{\sqrt{R_{i1} R_{i2}}}{\frac{e^{A_i} - e^{-A_i}}{2}}$$

$$R_3 = \frac{2\sqrt{R_{i1} R_{i2}}}{e^{-Ai} \left[(e^{Ai})^2 - 1 \right]}$$

$$e^{-Ai} \left[(e^{Ai})^2 - 1 \right]$$

$$R_3 = \frac{2N}{N^2 - 1} \sqrt{R_{i1} R_{i2}}$$

Now;

$$R_1 = \frac{R_{i1}}{\tanh(Ai)} - R_3$$


$$= \frac{R_{i1} (e^{Ai} + e^{-Ai})}{e^{Ai} - e^{-Ai}} - R_3$$

$$R_1 = R_{i1} \left(\frac{N^2 + 1}{N^2 - 1} \right) - R_3$$

$$R_2 = \frac{R_{i2}}{\tanh Ai} - R_3$$

$$R_2 = R_{i2} \left(\frac{N^2 + 1}{N^2 - 1} \right) - R_3$$

Asymmetrical π - Attenuator :-

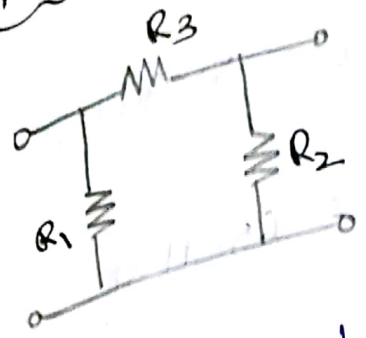

$$\frac{1}{R_{i1}} = G_{i1} \quad ; \quad \frac{1}{R_{i2}} = G_{i2}$$

$$O_i = A_i$$

From formula paper

$$G_3 = \frac{\sqrt{G_{i1} G_{i2}}}{\sinh A_i} = \frac{2N}{N^2 - 1} \sqrt{G_{i1} G_{i2}}$$

$$G_{i1} = \frac{G_{i1}}{\tanh A_i} - G_3 \Rightarrow G_{i1} \left(\frac{N+1}{N^2-1} \right) - G_3$$

$$G_{i2} = \frac{G_{i2}}{\tanh A_i} - G_3 \Rightarrow G_{i2} \left(\frac{N+1}{N^2-1} \right) - G_3$$

Problems :-

Q1) Design asymmetrical T-Attenuators of T-type & π -type to provide an attenuation of 40dB & to work b/w a source of 70Ω & a load of 600Ω .

Given: $R_{i1} = 70\Omega$, $R_{i2} = 600\Omega$


$$D = 40\text{dB} \Rightarrow N = 10^{D/20} \quad \boxed{N = 100}$$

i) Asymmetrical T-pad:-

$$R_3 = \left(\frac{2N}{N^2-1} \right) \sqrt{R_{i1} R_{i2}} \Rightarrow 4.1 \Omega$$

$$R_2 = R_{i1} \left(\frac{N+1}{N^2-1} \right) - R_3 \Rightarrow 65.91 \Omega$$
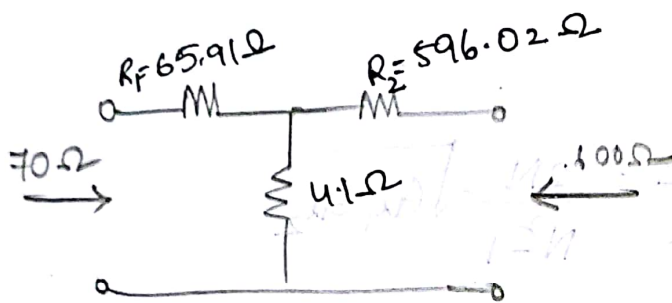
$$R_1 = R_{i2} \left(\frac{N+1}{N^2-1} \right) - R_3 \Rightarrow 596.02 \Omega$$



ii) Asymmetrical π-pad:-

$$G_{i1} = \frac{1}{R_{i1}} = 0.014 \text{ S}$$

$$G_{i2} = \frac{1}{R_{i2}} = 1.6 \times 10^{-3} \text{ S}$$


$$G_3 = \frac{2 \times 100}{100^2 - 1} \cdot \sqrt{0.014 \times 1.6 \times 10^{-3}}$$

$$G_3 = 94.6 \times 10^{-6} \Rightarrow \boxed{R_3 = 10.57 \text{ k}\Omega}$$


$$G_1 = 0.014 \left(\frac{100+1}{100^2-1} \right) - 94.6 \times 10^{-6}$$

$$G_1 = 13.908 \times 10^{-3} \text{ S} \Rightarrow \boxed{R_1 = 71.9 \Omega}$$
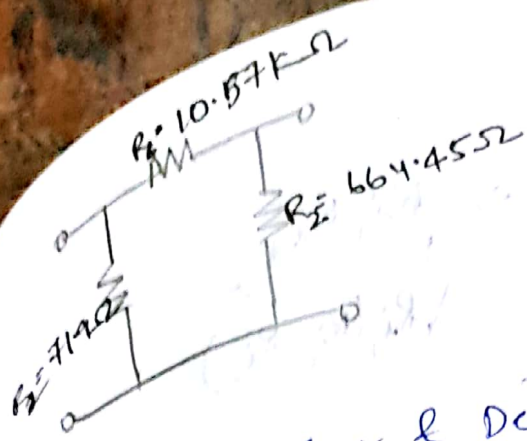
$$G_2 = 1.505 \times 10^{-3} \text{ S} \Rightarrow \boxed{R_2 = 664.45 \Omega}$$



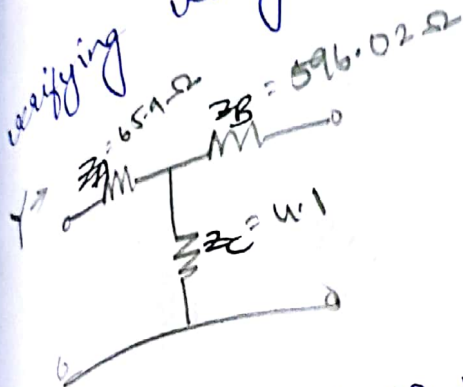Verifying using Star & Delta connections.



$$Z_3 = \frac{65.9 \times 596.02 + 596.02 \times 4.1 + 4.1 \times 65.9}{4.1}$$

$$Z_3 = 10.24 \times 10^3 \text{ approx near value}$$

Asymmetrical

L-Attenuator :-


I] Minimum Attenuation L-Attenuator
for "Unequal Impedances" :-

$$R_{i1} = \sqrt{R_1(R_1 + R_3)}$$

$$R_{i1}^2 = R_1^2 + R_1 R_3$$

$$R_{i1}^2 = R_1^2 + R_{i1} R_{i2}$$

$$R_1 = \sqrt{R_{i1}(R_{i1} - R_{i2})}$$

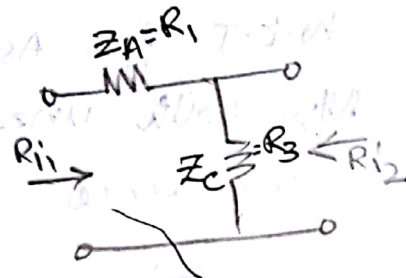

$$(\therefore R_1 R_3 = R_{i1} R_{i2})$$

W.K.T

$$R_3 = \frac{R_{i1} R_{i2}}{R_1} \Rightarrow \frac{R_{i1} R_{i2}}{\sqrt{R_{i1}(R_{i1} - R_{i2})}}$$

$$R_3 = \sqrt{\frac{R_{i1} R_{i2}^2}{R_{i1}(R_{i1} - R_{i2})}}$$

$$R_3 = \sqrt{\frac{R_{i1} R_{i2}^2}{R_{i1} - R_{i2}}}$$

$$R_1 = \sqrt{R_{i1}(R_{i1} - R_{i2})}$$


$$R_3 = \sqrt{\frac{R_{i1} R_{i2}^2}{R_{i1} - R_{i2}}}$$

→ minimum Attenuation
L-attenuator

II.] L-Attenuator with required attenuation for unequal Impedences:-

W.K.T for Asymmetrical N/W with unequal impedance
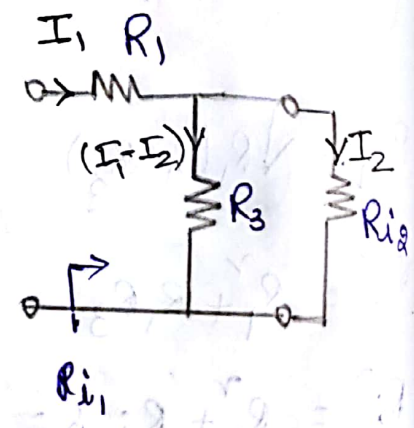
$$N = e^{\alpha l} = \frac{I_1}{I_2} \sqrt{\frac{Z_{i1}}{Z_{i2}}}$$



$$N = e^{a_i} = \frac{I_1}{I_2} \sqrt{\frac{R_{i1}}{R_{i2}}} = 10 \text{ dB}$$

from fig:

$$(I_1 - I_2) R_3 = R_{i2} I_2$$

$$I_1 = I_2 \frac{(R_{i2} + R_3)}{R_3}$$

$$\frac{I_1}{I_2} = \frac{R_{i2} + R_3}{R_3}$$

$$\frac{I_1}{I_2} \sqrt{\frac{R_{i1}}{R_{i2}}} = \sqrt{\frac{R_{i1}}{R_{i2}}} \left[\frac{R_{i2} + R_3}{R_3} \right]$$

wrong

$$\text{let } \sqrt{\frac{R_{i1}}{R_{i2}}} = K$$

$$N = K \left(\frac{R_{i2} + R_3}{R_3} \right)$$

$$\frac{N}{K} - R_{i2} = R_3$$

$$\frac{I_1}{I_2} \sqrt{\frac{R_{i1}}{R_{i2}}} = \left[1 + \frac{R_{i2}}{R_3} \right] \sqrt{\frac{R_{i1}}{R_{i2}}}$$

$$\text{let } K = \sqrt{\frac{R_{i1}}{R_{i2}}}$$

$$N = \left(1 + \frac{R_{i2}}{R_3} \right) K$$

$$\frac{N}{K} - 1 = \frac{R_{i2}}{R_3}$$

$$R_{i2} = \frac{(N - K) R_3}{K}$$

$$R_3 = \frac{K R_{i2}}{N - K}$$

Also w.e.T: $Z_A Z_C = Z_{i1} Z_{i2}$

$$R_1 R_3 = R_{i1} R_{i2}$$

$$R_1 = \frac{R_{i1} R_{i2}}{R_3}$$

$$R_1 = \frac{(N - K) R_{i1} R_{i2}}{(N - K) \frac{R_{i2}}{K}}$$

$$R_1 = \frac{R_{i1} (N - K)}{K}$$



For an Attenuation

$$N = 10^{D/20} = e^{Ai}$$

$$K = \sqrt{\frac{R_{i1}}{R_{i2}}}$$

$$R_1 = \left[\frac{K R_{i1} R_{i2}}{N - R_{i2} K} \right]$$

$$R_3 = \frac{N}{K} - R_{i2}$$

$$R_1 = \frac{R_{i1} (N - K)}{K}$$


$$R_3 = \frac{K R_{i2}}{(N - K)}$$

III.] L-Attenuator for equal impedances:-

for Asymm. N/w
with equal impedance

$$N = e^{At} = \frac{I_1}{I_2} = 10^{D/20}$$

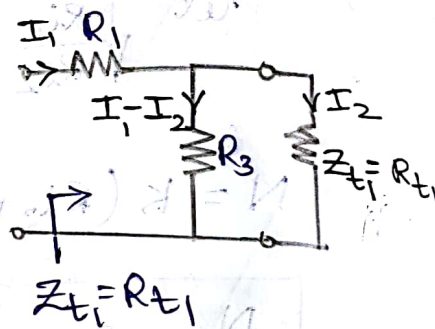for attenuator $\theta_t = A_t$, $Z_{t1} = R_{t1}$



$$(I_1 - I_2) R_3 = R_{t1} I_2$$

$$R_3 I_1 = I_2 (R_{t1} + R_3)$$

$$\frac{I_1}{I_2} = N = \frac{R_{t1} + R_3}{R_3}$$

$$N = 1 + \frac{R_{t1}}{R_3} \Rightarrow \frac{R_{t1}}{R_3} = N - 1$$

$$R_3 = \frac{R_{t1}}{N-1}$$

W.E.T

$$Z_{t1} = \frac{Z_A + \sqrt{Z_A^2 + 4Z_A Z_C}}{2}$$

$$R_{t1} = \frac{R_1 + \sqrt{R_1^2 + 4R_1 R_3}}{2}$$

$$R_{t1} - \frac{R_1}{2} = \frac{\sqrt{R_1^2 + 4R_1 R_3}}{2}$$

$$\left(R_{t1} - \frac{R_1}{2}\right)^2 = \frac{1}{4} (R_1^2 + 4R_1 R_3)$$

$$R_{t1}^2 + \frac{R_1^2}{4} - 2R_{t1} \left(\frac{R_1}{2}\right) = \frac{R_1^2}{4} + R_1 R_3$$

$$R_{t1}^2 - R_1 R_{t1} - R_1 R_3 = 0$$

$$R_{t1}^2 = R_1 (R_{t1} + R_3)$$

$$R_1 = \frac{R_{t1}^2}{R_{t1} + R_3}$$

$$R_1 = \frac{R_{t1}^2}{R_{t1} + R_{t1}} \cdot (N-1)$$

$$R_1 = \frac{R_{t1}^2 (N-1)}{R_{t1} (N-1+1)}$$


$$R_1 = \frac{R_{t1} (N-1)}{N}$$

In general, for equal impedance $R_{t1} = R_0$

$$R_1 = \frac{R_0 (N-1)}{N}$$

$$R_3 = \frac{R_0}{(N-1)}$$

Summary of L-Attenuator:-

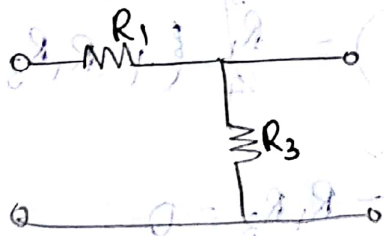

I.] For unequal impedances " R_{i1} & R_{i2} " :-

(A) Minimum loss L-attenuator :-

$$R_1 = \sqrt{R_{i1} (R_{i1} - R_{i2})}$$

$$R_3 = \sqrt{\frac{R_{i1} R_{i2}^2}{R_{i1} - R_{i2}}}$$

$$K = \sqrt{\frac{R_{i1}}{R_{i2}}}$$

where

with some attenuation $N = 10^{1.2}$

$$R_1 = \frac{R_{i1}}{k} (N - k) \quad R_3 = \frac{R_{i2} k}{(N - k)}$$

For Equal Impedences:-

$$R_1 = \frac{R_0(N-1)}{N}, \quad R_3 = \frac{R_0}{N-1}$$

problems:-


Design a minimum loss L-Attenuator to match a source of 150Ω & a load of 75Ω .

Sol: $R_{i1} = 150 \Omega, R_{i2} = 75 \Omega$

$$R_1 = \sqrt{R_{i1}(R_{i1} - R_{i2})} \quad ; \quad R_3 = \sqrt{\frac{R_{i1} R_{i2}^2}{(R_{i1} - R_{i2})}}$$

$$= \sqrt{150(150 - 75)} \quad = \sqrt{\frac{150 \cdot 75^2}{(150 - 75)}}$$
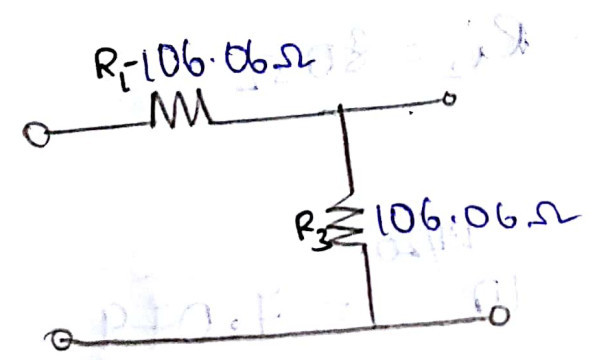
$$R_1 = 106.06 \Omega \quad R_3 = 106.06 \Omega$$



R_{i2} :-

$$k = \sqrt{\frac{R_{i1}}{R_{i2}}}$$

where

Q2. Design a minimum loss L-Attenuator to match impedances $100\ \Omega$ of source resistance $75\ \Omega$ of load resistance with 10dB .

Sol: $R_{i1} = 100\ \Omega$, $R_{i2} = 75\ \Omega$


$$R_1 = \sqrt{R_{i1}(R_{i1} - R_{i2})} \quad N = 10^{10/20} \Rightarrow$$

$$= \sqrt{100(100 - 75)}$$

$$R_2 = \sqrt{\frac{R_{i1} R_{i2}^2}{(R_{i1} - R_{i2})}}$$

$$R_1 = 50\ \Omega$$
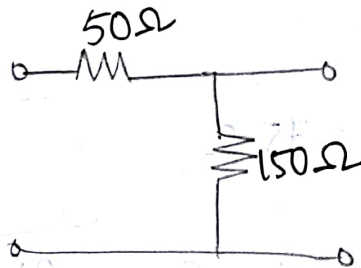
$$= \sqrt{\frac{100 \times 75^2}{25}} = 150\ \Omega$$



Q3. Design an L-attenuator to operate b/w two impedances $120\ \Omega$ & $80\ \Omega$ & to provide 17dB attenuation.

Sol: $R_{i1} = 120\ \Omega$, $R_{i2} = 80\ \Omega$

$$D = 17\text{dB}$$

$$N = 10^{D/20} \Rightarrow 10^{17/20} = 7.079$$

$$R_1 = \frac{R_{i1}(N - K)}{K}$$

$$R_2 = \frac{R_{i2} K}{(N - K)}$$


$$K = \sqrt{\frac{R_{i1}}{R_{i2}}} = \sqrt{\frac{120\Omega}{8\Omega}} = 1.224$$

$$R_1 = \frac{R_i(N-K)}{K} = \frac{120(7.079 - 1.224)}{1.224}$$

$$R_3 = \frac{R_{i2}K}{(N-K)} = \frac{80 \times 1.224}{(7.079 - 1.224)}$$

$$R_1 = 574.01 \Omega$$

$$R_3 = 16.74 \Omega$$

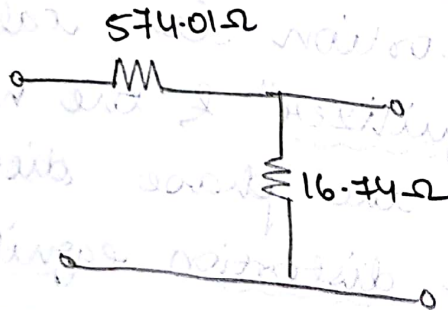

Q4) Design L-attenuator to provide 40dB attenuation & to operate w/ a design impedance of 500Ω.

$$R_1 = R_0 = 500 \Omega$$

$$D = 40 \text{ dB}$$


$$N = 10^{\frac{40}{20}} = 100$$

w.k.t (equal impedance)

$$R_1 = \frac{R_0(N-1)}{N} \Rightarrow \frac{500(100-1)}{100} \quad ; \quad R_3 = \frac{R_0}{N-1} \Rightarrow \frac{500}{99}$$

$$R_1 = 495 \Omega$$

$$R_3 = 5.05 \Omega$$

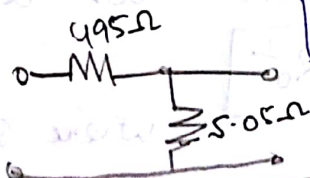

EQUILIZERS :-

An equalizer is a network, which is designed to counteract (regain) the attenuation & phase distortions occurred when a signal is passed through a network.

The network that counteract the attenuation distortion is called an "Attenuation Equalizer". & the network that counteract the phase distortion is called "phase distortion equalizer".

→ Based on "Counteraction":

- 1) Attenuation Equalizer
- 2) phase Equalizer

→ Based on "Terminals":

- 1) Two terminal equalizer
- 2) Four terminal equalizer / constant resistance equalizer

INVERSE IMPEDENCE :-

Two impedances Z_1 & Z_2 are said to be inverse impedances "if their geometric mean is a constant".


$$Z_1 Z_2 = R_0^2$$

where R_0 - design impedance

Case - (i):

If Z_1 is a resistance i.e. $Z_1 = R_1$ &
 then $Z_2 = \frac{R_0^2}{Z_1}$ i.e. $Z_2 = R_2 = \frac{R_0^2}{R_1}$

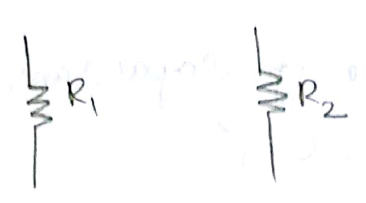
∴ Inverse impedance of a resistor is another resistor



Case - (ii):


If Z_1 is an inductance i.e. $Z_1 = j\omega L$
 then $Z_2 = \frac{R_0^2}{j\omega L}$ & $Z_2 = \frac{1}{j\omega(\frac{L}{R_0^2})}$

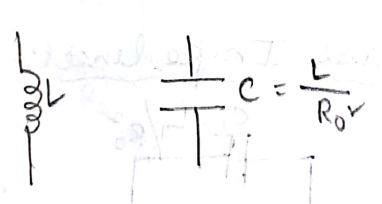∴ Inverse impedance of inductor is a capacitor whose capacitance value is $C = \frac{L}{R_0^2}$



Case - (iii): If Z_1 is a capacitance i.e. $Z_1 = \frac{1}{j\omega C}$
 then $Z_2 = \frac{R_0^2}{\frac{1}{j\omega C}} = j\omega(CR_0^2)$

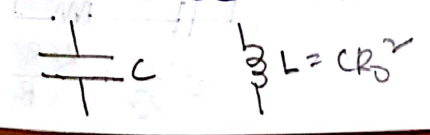∴ Inverse impedance of capacitor is an inductor whose value $L = CR_0^2$



Summary of Inverse Impedance

→ Inverse impedance of Resistor is another resistor whose value is $Z_2 = R_2 = \frac{R_0^2}{R_1}$

→ Inverse impedance of inductance is Capacitor whose value $C = \frac{L}{R_0^2}$



→ Inverse impedance of capacitance is inductor whose value $L = C R_0^2$

→ Inverse of a series connection is a parallel connection & vice-versa.

NOTE:

The inverse N/W of a complex (Giant) N/W is obtained by splitting the complex N/W into small units, then find the inverse of each small N/W & we build up total network.

Examples of Inverse Impedances:-

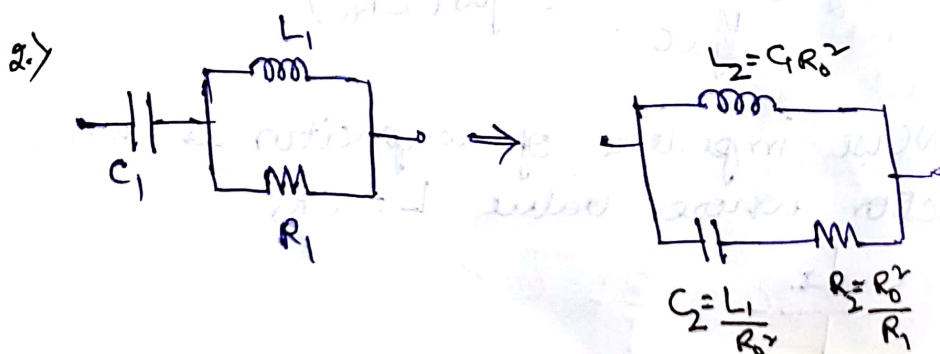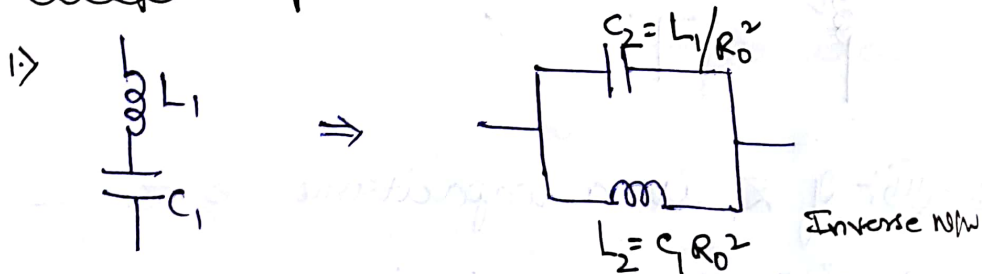

Impedance

Inductor is another

$$Z_2 = R_2 = \frac{R_0^2}{R_1}$$

Inductance in Capacitor


Capacitance in inductor

Connection is vice-versa.



Complex (Giant) N/W
the complex
then find the
& we build

Impedance:-


Inverse N/W

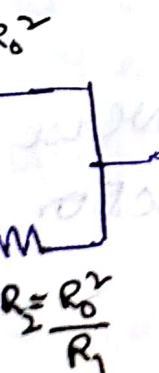

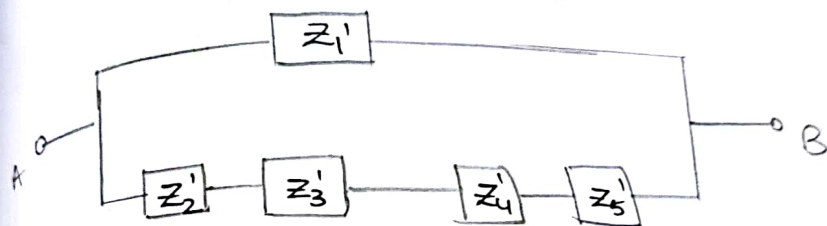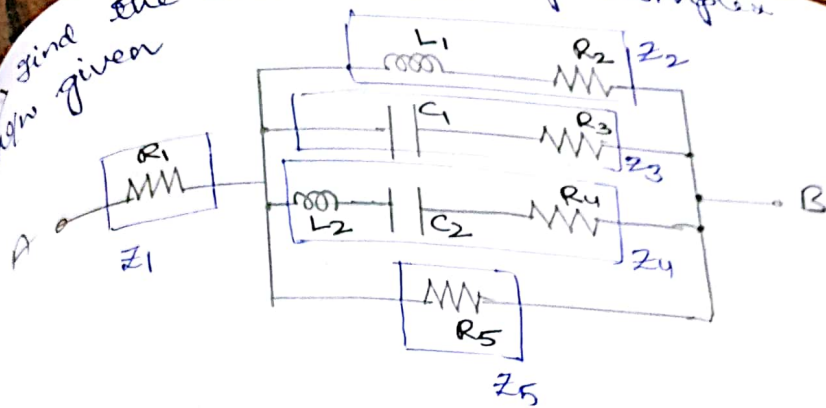Find the inverse N/W of complex N/W given



$$R_1' = Z_1' = \frac{R_0^2}{R_1}$$

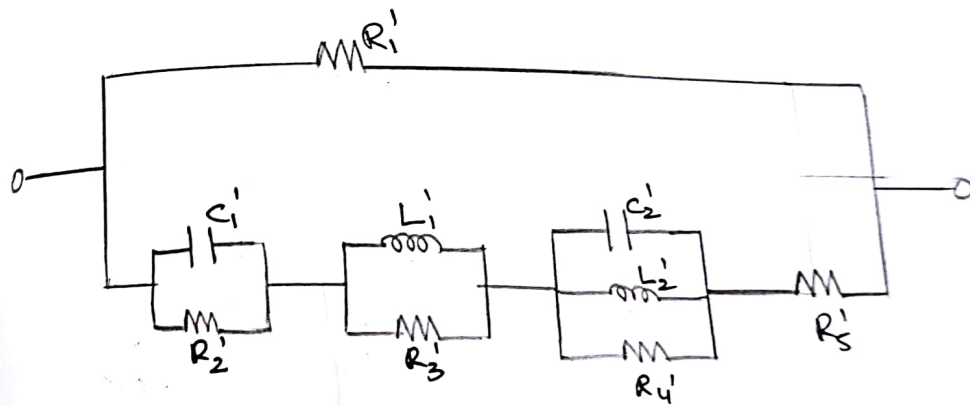

$$R_1' = \frac{R_0^2}{R_1}$$

$$C_1' = \frac{L_1}{R_0^2} \quad ; \quad L_1' = C_1 R_0^2$$

$$C_2' = \frac{L_2}{R_0^2} \quad ; \quad L_2' = C_2 R_0^2$$

$$R_2' = \frac{R_0^2}{R_2}$$

$$R_3' = \frac{R_0^2}{R_3}$$



$$R_4' = \frac{R_0^2}{R_4}, \quad R_5' = \frac{R_0^2}{R_5}$$

As name suggests two terminal equalizer consists only two terminals & it is connected either in series or in shunt to the transmission network.

There are two types of 2-terminal equalizer

1. Series equalizer

2. Shunt Equalizer

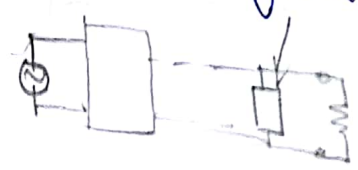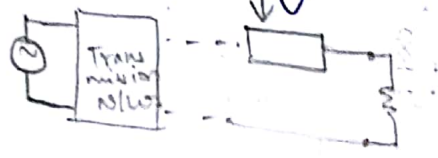


Series equalizer:-

Standard two terminal series equalizer is shown in fig. where X_1 is a reactance.

$$N = \sqrt{\frac{P_1}{P_2}}$$


P_1 - power i/p without equalizer

P_2 - power o/p with equalizer.

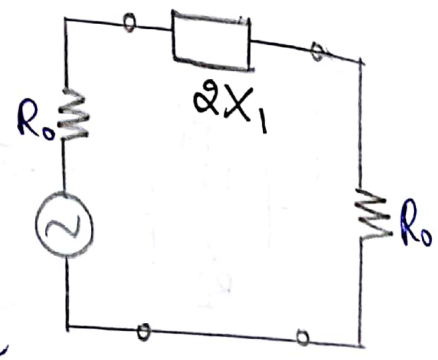


To calculate input power "without" equalizer: consider fig. shown

$$|I_{in}| = \frac{V_{in}}{2R_0}$$

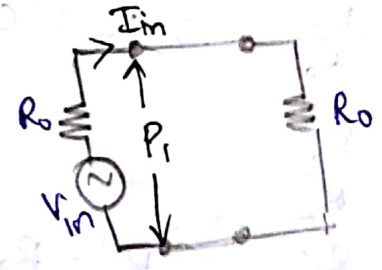


Equalizers:-

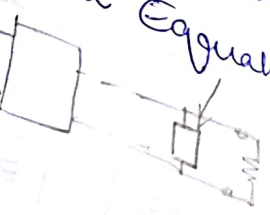two terminal
only two terminal
in series on
transmission network
2-terminal equalizer
hunt Equalizer



series equalizer
is a

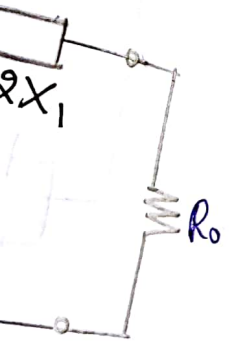

out

Ro

Sri Sai

$$P_1 = |V_{in}| |I_{in}| = |I_{in}|^2 R_0$$


$$P_1 = \left(\frac{V_{in}^2}{4R_0^2} \right) R_0 \rightarrow \text{input power without equalizer}$$

To calculate output power 'with' equalizer
consider the fig. shown

$$I_{out} = \frac{V_{in}}{2R_0 + j2X_1}$$

$$|I_{out}| = \left| \frac{V_{in}}{2R_0 + j2X_1} \right|$$

$$|I_{out}| = \frac{V_{in}}{\sqrt{4R_0^2 + 4X_1^2}}$$

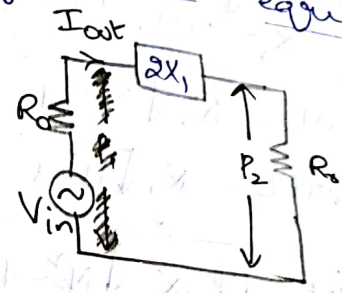

$$P_2 = |I_{out}|^2 \cdot R_0$$

$$P_2 = \frac{V_{in}^2 \cdot R_0}{4(R_0^2 + X_1^2)}$$

Now; $N^2 = \frac{P_1}{P_2}$

$$= \left(\frac{V_{in}^2}{4R_0^2} \right) R_0 \cdot \frac{4 \cdot (R_0^2 + X_1^2)}{V_{in}^2 R_0}$$

$$N^2 = 1 + \frac{X_1^2}{R_0^2}$$

$$X_1 = R_0 \sqrt{N^2 - 1}$$

$$X_1 = R_0 \sqrt{N^2 - 1}$$

→ 'X₁' may be an inductor or a capacitor
→ If X₁ = ωL (inductor), then:

$$\omega L = R_0 \sqrt{N^2 - 1}$$

$$2\pi f L = R_0 \sqrt{N^2 - 1}$$

i.e. $f \propto \sqrt{N^2 - 1}$

∴ If increased attenuation is req'd with increase of frequency then X₁ must be an inductor whose value

$$L = \frac{R_0 \sqrt{N^2 - 1}}{2\pi f}$$

→ If X₁ = $\frac{1}{\omega C}$ (capacitor), then:

$$\omega C = \frac{1}{R_0 \sqrt{N^2 - 1}}$$

$$2\pi f C = \frac{1}{R_0 \sqrt{N^2 - 1}}$$


i.e. $f \propto \frac{1}{\sqrt{N^2 - 1}}$

∴ If decreased attenuation is required

When increase of frequency then X_1
 we a capacitor whose value is

$$C = \frac{1}{R_0 2\pi f N^2 - 1}$$

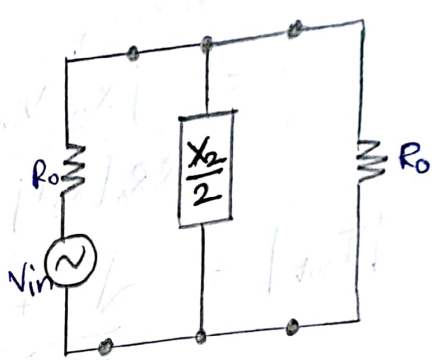Shunt Equalizer :-
 consider stand. shunt
 equalizer as shown
 in fig. where X_2 is
 reactance.




Input power without Equalizer (P_1):-

$$I_{in} = \frac{V_{in}}{2R_0}$$

$$P_1 = |I_{in}|^2 R_0$$


$$P_1 = \left| \frac{V_{in}}{2R_0} \right|^2 R_0$$

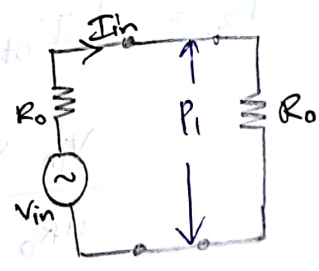

Input power with equalizer (P_2):-

$$I_1 = \frac{V_{in}}{R_0 + jR_0 \frac{X_2}{2}}$$
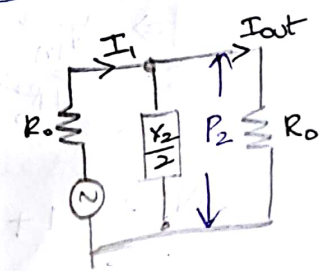
$$I_1 = \frac{V_{in}}{R_0 + j \frac{X_2}{2}}$$



$$I_1 = \frac{V_{in} (2R_0 + jX_2)}{R_0 (2R_0 + jX_2) + jX_2 R_0}$$

Now,

$$I_{out} = \frac{(j \frac{x_2}{2})}{R_0 + j \frac{x_2}{2}} \cdot \pm_1$$

$$= \frac{j x_2}{(2R_0 + j x_2)} \times \frac{V_{in} (2R_0 + j x_2)}{[2R_0^2 + j 2x_2 R_0]}$$

$$= \frac{j x_2 V_{in}}{2R_0 [R_0 + j x_2]}$$

$$|I_{out}| = \frac{\sqrt{0^2 + (x_2 V_{in})^2}}{2R_0 \sqrt{R_0^2 + x_2^2}}$$

$$P_2 = |I_{out}|^2 \cdot R_0$$

$$= \frac{V_{in}^2 x_2^2 \cdot R_0}{4R_0^2 (R_0^2 + x_2^2)}$$

$$\text{Now } N^2 = \frac{P_1}{P_2}$$

$$\Rightarrow \frac{V_{in}^2}{4R_0^2} \cdot R_0 \times \frac{4R_0^2 (R_0^2 + x_2^2)}{V_{in}^2 x_2^2 R_0}$$

$$N^2 \Rightarrow 1 + \frac{R_0^2}{x_2^2}$$

$$\frac{R_0^2}{x_2^2} = N^2 - 1$$

$$\therefore x_2 = \frac{R_0}{\sqrt{N^2 - 1}}$$

X_2 may be an inductor or capacitor

$X_2 = \omega L$ (inductor), then:

$$\omega L = \frac{R_0}{\sqrt{N^2 - 1}}$$

$$f \propto \frac{R_0}{\sqrt{N^2 - 1}}$$

Decreased attenuation is obtained with increase of frequency then,

X_2 must be an inductor whose value

$$L = \frac{R_0}{2\pi f \sqrt{N^2 - 1}}$$

$X_2 = \frac{1}{\omega C}$ (capacitor), then:

$$\frac{1}{\omega C} = \frac{R_0}{\sqrt{N^2 - 1}}$$

$$f \propto \sqrt{N^2 - 1}$$

\therefore if increased attenuation is req'd with increase of frequency then

X_2 must be a capacitor. whose value

$$C = \frac{\sqrt{N^2 - 1}}{2\pi f R_0}$$

Problem:

Q1) Design a series equalizer with increased attenuation with increase of frequency & to provide 10dB attenuation at 100 kHz. & $R_0 = 600\Omega$

Sol: $X_1 = R_0 \sqrt{N^2 - 1}$

$$N = 10^{10/20} \Rightarrow 10^{1/2} \Rightarrow \sqrt{10}$$

$$X_1 = 600 \sqrt{(\sqrt{10})^2 - 1}$$

$$\boxed{X_1 = 1800}$$


$\therefore X_1$ is an inductor.

$$X_1 = \omega L$$

$$L = \frac{X_1}{\omega}$$

$$= \frac{1800}{2\pi \times 100\text{kHz}}$$

$$\boxed{L = 2.86\text{mH}}$$

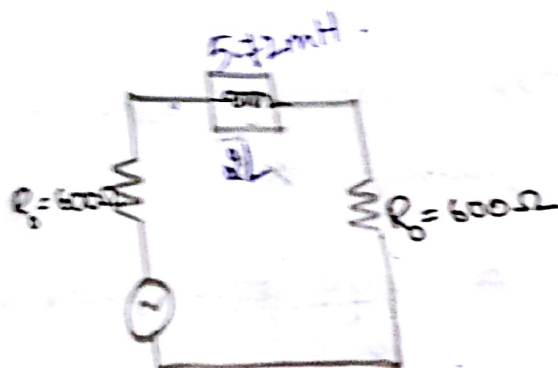

equalizer with
with increase
provide 10dB
of $R_0 = 600\Omega$

Design a shunt equalizer to provide
attenuation at 100kHz frequency.
 $R_0 = 600\Omega$

$N = 10 \Rightarrow 10^{10/20} \Rightarrow \sqrt{10}$
 $R_0 = 600\Omega$

Increased attenuation with increase of
frequency $\therefore X_2 \rightarrow$ capacitor

$$C = \frac{\sqrt{N^2 - 1}}{2\pi f \cdot R_0} \Rightarrow \frac{\sqrt{(\sqrt{10})^2 - 1}}{2\pi \times 100 \times 10^3 \times 600}$$



$C = 7.95nF \Rightarrow 2C = 15.9nF$

Decreased attenuation with increase of
frequency $\therefore X_2 \rightarrow$ Inductor

$$L = \frac{R_0}{2\pi f \sqrt{N^2 - 1}}$$

$L = \frac{600}{2\pi \times 100 \times 10^3 \times \sqrt{(\sqrt{10})^2 - 1}} \Rightarrow 0.318mH$

$\frac{L}{2} = 0.159mH$

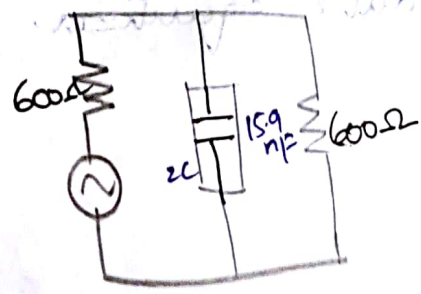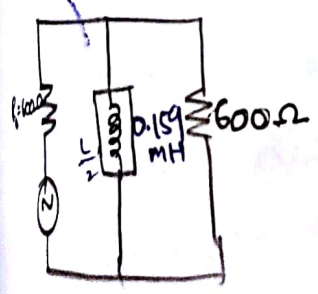

Drawbacks of Two-terminal equalizer:-

→ The impedance of two-terminal equalizers changes ~~to~~ w.r.t frequency i.e. not maintaining a constant impedance in the circuit. Due to this impedance mismatch occurs so that maximum is not transferred from source to load.


FOUR-terminal Equalizers:-

Four-terminal equalizers provide constant impedance irrespective of frequency. Hence, they are also called "constant-resistance Equalizers".

Types of 4-terminal equalizers;

- 1) Full-series equalizer
- 2) Full-shunt equalizer
- 3) Bridged-T equalizer
- 4) Lattice equalizer.

Series Equalizer:-

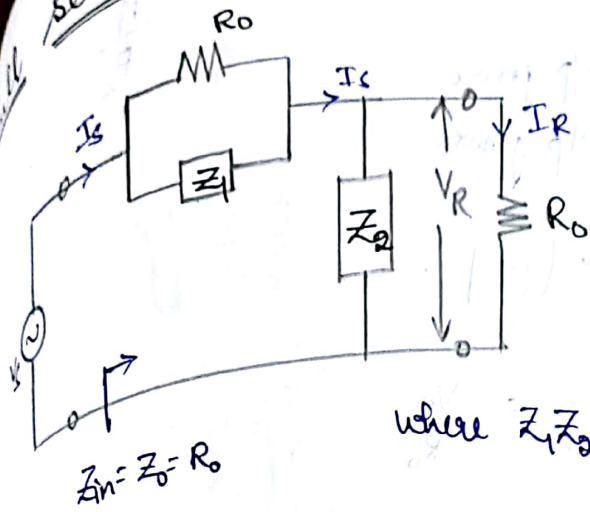

where $Z_1 Z_2 = R_0^2$ (Inverse Impedance)

$$Z_{in} = \frac{R_0 Z_2}{R_0 + Z_2} + \frac{R_0 Z_1}{R_0 + Z_1}$$

$$= \frac{R_0 Z_2 (R_0 + Z_1) + R_0 Z_1 (R_0 + Z_2)}{(R_0 + Z_2)(R_0 + Z_1)}$$

$$= \frac{R_0 [R_0 Z_2 + Z_1 Z_2 + Z_1 R_0 + Z_1 Z_2]}{R_0^2 + R_0 Z_2 + R_0 Z_1 + Z_1 Z_2}$$

$$= \frac{R_0 [R_0 (Z_1 + Z_2) + 2 Z_1 Z_2]}{[R_0 (Z_1 + Z_2) + 2 Z_1 Z_2]}$$

$$Z_{in} = R_0$$

ie Insertion of full series equalizer does not disturb the impedance of circuit

Now, w.k.T $N = \sqrt{\frac{P_1}{P_2}} \Rightarrow N^2 = \frac{P_1}{P_2}$

where $P_1 \rightarrow$ i/p power
 $P_2 \rightarrow$ o/p power

Input power [P_1]:-

$$I_s = \frac{V_s}{Z_{in}} = \frac{V_s}{R_0}$$

$$|I_s| = \frac{V_s}{R_0}$$

$$P_1 = |I_s|^2 \cdot R_0 \Rightarrow \left(\frac{V_s}{R_0}\right)^2 \cdot R_0$$

Output power [P_2]:-

$$I_R = \left(\frac{Z_2}{R_0 + Z_2}\right) I_s$$

$$|I_R| = \left|\frac{Z_2}{R_0 + Z_2} I_s\right|$$

$$P_2 = |I_R|^2 \cdot R_0$$

$$P_2 = \left|\frac{Z_2 I_s}{R_0 + Z_2}\right|^2 \cdot R_0$$

Now w.k.T $N^2 = \frac{P_1}{P_2}$

$$N^2 = \frac{|I_s|^2 R_0}{\left| \frac{Z_2 I_s}{Z_2 + R_0} \right|^2 R_0}$$

$$N^2 = \left\{ \left| \frac{I_s (Z_2 + R_0)}{Z_2} \right|^2 \right\}$$

$$N^2 = \left\{ \left| \frac{Z_2 + R_0}{Z_2} \right|^2 \right\} \quad \text{or} \quad N^2 = \left\{ \left| \frac{R_0 + Z_1}{R_0} \right|^2 \right\} \rightarrow \text{①}$$

where Z_1 & Z_2 are considered as Reactances

Case 1: If $Z_1 = j\omega L_1$ (inductor)

wkt $Z_1 Z_2 = R_0^2$

$$Z_2 = \frac{R_0^2}{j\omega L_1} \Rightarrow \frac{1}{j\omega C_2}$$

$$C_2 = \frac{L_1}{R_0^2}$$

from eqn ①

$$N^2 = \left\{ \left| \frac{R_0 + j\omega L_1}{R_0 + 0} \right|^2 \right\}$$

$$N^2 = \left\{ \frac{\sqrt{R_0^2 + \omega^2 L_1^2}}{\sqrt{R_0^2 + 0}} \right\}$$

$$N^2 = \frac{R_0^r + \omega^2 L_1^2}{R_0^r}$$

$$N^2 = 1 + \frac{\omega^2 L_1^2}{R_0^r}$$

$$N^2 - 1 = \frac{\omega^2 L_1^2}{R_0^r} \Rightarrow X_1$$

$$X_1^2 = R_0^r (N^2 - 1)$$


$$X_1 = R_0 \sqrt{N^2 - 1} \rightarrow X_1 \propto \sqrt{N^2 - 1}$$

$$L_1 = \frac{R_0 \sqrt{N^2 - 1}}{\omega}$$

$$\Rightarrow C_2 = \frac{L_1}{R_0} = \frac{R_0 \sqrt{N^2 - 1}}{R_0^2 \omega}$$

$$C_2 = \frac{\sqrt{N^2 - 1}}{R_0 \omega}$$

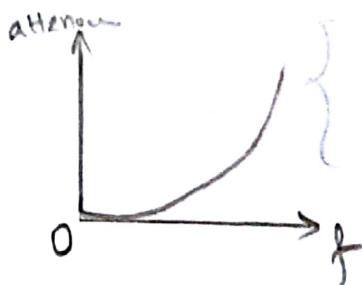→ Increased attenuation is req'd with increase of frequency then:
 $Z_1 \rightarrow$ inductor & $Z_2 \rightarrow$ capacitor.



$$L_1 = \frac{R_0 \sqrt{N^2 - 1}}{\omega}$$

$$C_2 = \frac{\sqrt{N^2 - 1}}{R_0 \omega}$$

if $Z_1 = \frac{1}{j\omega C}$ (capacitor)

$Z_1 Z_2 = R_0^2 \Rightarrow Z_2 = j\omega (C_1 R_0^2)$

$\therefore L_2 = C_1 R_0^2$

from eqn ①

$N^2 = \left| \frac{R_0 + \frac{1}{j\omega C_1}}{R_0} \right|^2$

$N^2 = \left| \frac{1 + j\omega R_0 C_1}{1 + j\omega R_0 C_1} \right|^2$

$N^2 = \frac{\sqrt{1 + \omega^2 R_0^2 C_1^2}}{\sqrt{1 + \omega^2 R_0^2 C_1^2}}$

$N^2 = \frac{1 + \omega^2 R_0^2 C_1^2}{\omega^2 R_0^2 C_1^2}$

$N^2 = 1 + \frac{1}{\omega^2 R_0^2 C_1^2}$

$C_1^2 = \frac{1}{\omega^2 R_0^2 (N^2 - 1)}$

$C_1 = \frac{1}{R_0 \omega \sqrt{N^2 - 1}}$

$\rightarrow X_1 \propto$

$L_2 = C_1 R_0^2 \Rightarrow L_2 = \frac{R_0}{\omega \sqrt{N^2 - 1}}$

$\rightarrow X_1 \propto \sqrt{N^2 - 1}$

read with capacitor.

$L_1 = \frac{R_0 \sqrt{N^2 - 1}}{\omega}$
 $C_2 = \frac{\sqrt{N^2 - 1}}{R_0 \omega}$

Decreased attenuation is reqd with increase of frequency then

$Z_1 \rightarrow$ capacitor & $Z_2 \rightarrow$ inductor.

$$C_1 = \frac{1}{\omega R_0 \sqrt{N^2 - 1}}$$

$$L_2 = \frac{R_0}{\omega \sqrt{N^2 - 1}}$$

problems:-

Q1) Design a full series equalizer to provide 15dB attenuation at 20kHz & with a design impedance 600Ω. Assume Increased attenuation with increase of frequency.

Sol: $N = 10 \Rightarrow 10^{15/20} \Rightarrow 5.623$

$f = 20\text{kHz}$

$R_0 = 600\Omega$

$\therefore Z_1 \rightarrow$ inductor & $Z_2 \rightarrow$ capacitor.

$$L_1 = \frac{R_0 \sqrt{N^2 - 1}}{2\pi f}$$


$$= \frac{600 \sqrt{(5.623)^2 - 1}}{2\pi \times 20\text{kHz}}$$

$$L = 26.41\text{mH}$$

$$C_2 = \frac{\sqrt{N^2 - 1}}{R_0 \cdot 2\pi f}$$

$$= \frac{\sqrt{(5.623)^2 - 1}}{2\pi \times 20\text{kHz} \times 600}$$

$$C_2 = 73.38\text{nF}$$

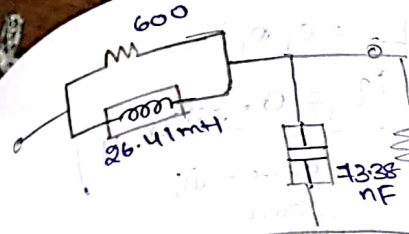

Design Full series equalizer
impedance 500Ω
attenuation of 20dB

Sol: $N = 10 \Rightarrow 10^{20/20}$
 $f = 12\text{kHz}$
 $R_0 = 500\Omega$

Increased attenuation
 $\therefore Z_1 \rightarrow$ inductor &

$$L_1 = \frac{R_0 \sqrt{N^2 - 1}}{2\pi f}$$


$$L_1 = \frac{500 \sqrt{(10)^2 - 1}}{2 \times \pi \times 12\text{kHz}}$$

$$L_1 = 117.72\text{mH}$$

Decreased attenuation
 $Z_1 \rightarrow$ capacitor

$$C_1 = \frac{1}{2\pi f R_0 \sqrt{N^2 - 1}}$$

is req'd with
then
inductor.

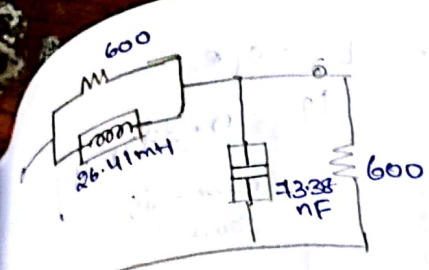

Design Full series equalizer with design impedance 500Ω & to provide a attenuation of 25dB at 12kHz.

$$N = 10 \Rightarrow 10^{25/20} \Rightarrow 17.78$$

$$f = 12 \text{ kHz}$$

$$R_0 = 500 \Omega$$

→ Increased attenuation with increase of frequency
∴ $Z_1 \rightarrow$ inductor & $Z_2 \rightarrow$ capacitor

$$L_1 = \frac{R_0 \sqrt{N^2 - 1}}{2\pi f}$$

$$C_2 = \frac{\sqrt{N^2 - 1}}{2\pi f \cdot R_0}$$

$$L_1 = \frac{500 \sqrt{(17.78)^2 - 1}}{2 \times \pi \times 12 \text{ kHz}}$$

$$= \frac{\sqrt{(17.78)^2 - 1}}{2\pi \times 12 \text{ kHz} \times 500}$$

$$L_1 = 117.72 \text{ mH}$$

$$C_2 = 470.88 \text{ nF}$$

→ Decreased attenuation with increase of frequency
 $Z_1 \rightarrow$ capacitor & $Z_2 \rightarrow$ inductor

$$C_1 = \frac{1}{2\pi f R_0 \sqrt{N^2 - 1}}$$

$$L_2 = \frac{R_0}{2\pi f \sqrt{N^2 - 1}}$$


$$38 \text{ nF}$$

$$C_1 = 1.49 \mu\text{F}$$


$$L_2 = C_1 R_0^2$$

$$L_2 = 0.373 \text{ mH}$$


Case - i;

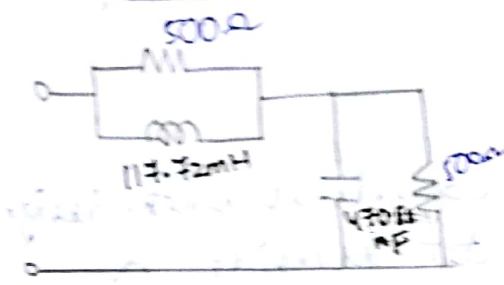

Case - ii;

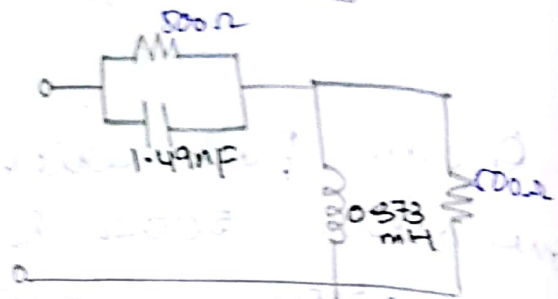

Full - Shunt Equalizer

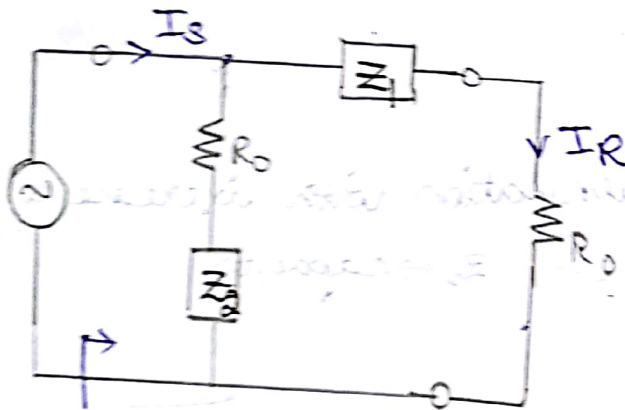

$$Z_{in} = (Z_1 + R_0) \parallel (Z_2 + R_0)$$

$$= \frac{(Z_1 + R_0)(Z_2 + R_0)}{Z_1 + Z_2 + 2R_0}$$

$$Z_1 + Z_2 + 2R_0$$

$$\Rightarrow \frac{Z_1 Z_2 + Z_1 R_0 + Z_2 R_0 + R_0^2}{Z_1 + Z_2 + 2R_0}$$

$$Z_1 + Z_2 + 2R_0$$

$$\frac{R_0 + R_0(z_1 + z_2) + R_0^2}{2R_0 + z_1 + z_2}$$

$$\frac{2R_0^2 + R_0(z_1 + z_2)}{2R_0 + z_1 + z_2}$$

$$\frac{R_0(2R_0 + z_1 + z_2)}{2R_0 + z_1 + z_2}$$

$$Z_{in} = R_0$$

w.k.T $N^2 = \frac{P_1}{P_2}$

Input power $[P_1]$:-

$$I_s = \frac{V_s}{Z_{in}} = \frac{V_s}{R_0}$$

$$|I_s| = \frac{V_s}{R_0}$$

$$P_1 = |I_s|^2 \cdot R_0$$

Output power $[P_2]$:-

$$I_r = \left(\frac{R_0 + z_2}{(R_0 + z_2) + z_1 + R_0} \right) \cdot I_s$$

$$|I_r| = \left| \frac{R_0 + z_2}{(R_0 + z_2) + (z_1 + R_0)} \cdot I_s \right|$$

$$|I_R| = \left| \frac{R_0 + Z_2}{2R_0 + Z_1 + Z_2} \cdot I_s \right|$$

$$P_2 = |I_R|^2 \cdot R_0$$

$$P_2 = \left| \frac{R_0 + Z_2}{2R_0 + Z_1 + Z_2} \cdot I_s \right|^2 \cdot R_0$$

Now ; $N^2 = \frac{P_1}{P_2}$

$$N^2 = \frac{|I_s|^2 R_0}{\left| \frac{(R_0 + Z_2) I_s}{2R_0 + Z_1 + Z_2} \right|^2 \cdot R_0}$$

$$N^2 = \left[\frac{2R_0 + Z_1 + Z_2}{R_0 + Z_2} \right]^2 \cdot \frac{R_0}{R_0} = \left[\frac{2R_0 + Z_1 + Z_2}{R_0 + Z_2} \right]^2$$

& $Z_1 Z_2 = R_0^2 \Rightarrow Z_2 = \frac{R_0^2}{Z_1}$

$$N^2 = \left[\frac{2R_0 + Z_1 + \frac{R_0^2}{Z_1}}{R_0 + \frac{R_0^2}{Z_1}} \right]^2 = 1$$

$$N^2 = \left[\frac{2R_0 Z_1 + Z_1^2 + R_0^2}{R_0 Z_1 + R_0^2} \right]^2 = 1$$

where $Z_1 = j\omega L_1$

$$C_2 = \frac{L_1}{R_0^2}$$

$$\Rightarrow Z_2 = \frac{R_0^2}{Z_1} = \frac{R_0^2}{j\omega L_1}$$

$$= \frac{1}{j\omega \left(\frac{L_1}{R_0^2}\right)}$$

$$\approx \frac{1}{j\omega C_2}$$

$$N^2 = \left\{ \frac{2R_0(j\omega L_1) + R_0^2 + (j\omega L_1)^2}{R_0(j\omega L_1) + R_0^2} \right\}^2$$

$$D^2 = \left\{ \frac{(R_0^2 - \omega^2 L_1^2) + j(2\omega L_1 R_0)}{R_0^2 + j\omega R_0 L_1} \right\}^2$$

$$= \frac{(R_0^2 - \omega^2 L_1^2)^2 + (2\omega L_1 R_0)^2}{R_0^4 + (R_0 \omega L_1)^2}$$

$$= \frac{(R_0^2)^2 + (\omega^2 L_1^2)^2 - 2R_0^2 \omega^2 L_1^2 + 4R_0^2 \omega^2 L_1^2}{R_0^4 + R_0^2 \omega^2 L_1^2}$$

$$= \frac{(R_0^2)^2 + (\omega^2 L_1^2)^2 + 2R_0^2 \omega^2 L_1^2}{R_0^4 + R_0^2 \omega^2 L_1^2}$$

$$= \frac{[(R_0^2)^2 + R_0^2 \omega^2 L_1^2] + \omega^2 L_1^2 [R_0^2 + \omega^2 L_1^2]}{(R_0^2)^2 + R_0^2 \omega^2 L_1^2}$$

$$= \frac{(R_0^2)^2 + R_0^2 \omega^2 L_1^2}{(R_0^2)^2 + R_0^2 \omega^2 L_1^2} + \frac{\omega^2 L_1^2 [R_0^2 + \omega^2 L_1^2]}{R_0^2 (R_0^2 + \omega^2 L_1^2)}$$

$$N^2 = 1 + \frac{\omega^2 L_1^2}{R_0^2}$$

$$(N^2 - 1) R_0^2 = \omega^2 L_1^2$$

$$\rightarrow \omega = \frac{R_0 \sqrt{N^2 - 1}}{L_1}$$

$$f \propto \sqrt{N^2 - 1}$$

$$L_1 = \frac{R_0 \sqrt{N^2 - 1}}{\omega}$$

$$\text{Now } C_2 = \frac{L_1}{R_0^2} = \frac{R_0 \sqrt{N^2 - 1}}{R_0^2 \omega} = \frac{\sqrt{N^2 - 1}}{R_0 \omega}$$

$$\therefore \boxed{L_1 = \frac{R_0 \sqrt{N^2 - 1}}{\omega} \quad ; \quad C_2 = \frac{\sqrt{N^2 - 1}}{R_0 \omega}}$$

From above eqn's it is evident that $f \propto \sqrt{N^2 - 1}$, i.e. increased attenuation is required with increase of frequency, then $\therefore Z_1$ must be an Inductor.

Case-2 if $Z_1 = \frac{1}{j\omega C_1} \Rightarrow Z_2 = \frac{R_0^2}{Z_1} = \frac{R_0^2}{\frac{1}{j\omega C_1}}$

$$\therefore \boxed{L_2 = C_1 R_0^2}$$

$$Z_2 = j\omega(C_1 R_0^2) \approx j\omega L_2$$

$$\text{Now } N^2 = \frac{2R_0 \left(\frac{1}{j\omega C_1}\right) + R_0^2 + \left(\frac{1}{j\omega C_1}\right)^2}{\frac{R_0}{j\omega C_1} + R_0^2}$$

$$N^2 = \left\{ \frac{[(j\omega C_1) 2R_0 + R_0^2 (j\omega C_1)^2 + 1] / (j\omega C_1)^2}{(R_0 + R_0^2 j\omega C_1) / j\omega C_1} \right\}^2$$

$$\omega = \frac{R_0 \sqrt{N^2 - 1}}{4}$$

$$f \propto \sqrt{N^2 - 1}$$

$$\frac{\sqrt{N^2 - 1}}{R_0 \omega}$$

$$\frac{\sqrt{N^2 - 1}}{R_0 \omega}$$

that $f \propto \sqrt{N^2 - 1}$
 required with
 Z_1' must be

$$\frac{R_0}{Z_1} = \frac{R_0}{\frac{1}{j\omega C_1}}$$

$$j\omega(C_1 R_0) \approx j\omega L_2$$

$$\left| \frac{1}{j\omega C_1} \right|^2$$

$$\left| \frac{R_0(j\omega C_1) + 1 - \tilde{\omega} C_1 R_0}{R_0 j\omega C_1 - R_0 \tilde{\omega} C_1} \right|^2$$

$$N^2 = \frac{(1 - \tilde{\omega} C_1 R_0)^2 + (2R_0 \omega C_1)^2}{(R_0 \omega C_1)^2 + (R_0 \tilde{\omega} C_1)^2}$$

$$N^2 = \frac{1 + (\tilde{\omega} C_1 R_0)^2 - 2\tilde{\omega} C_1 R_0 + 4R_0^2 \omega^2 C_1^2}{(R_0 \omega C_1)^2 + (R_0 \tilde{\omega} C_1)^2}$$

$$N^2 = \frac{1 + (\tilde{\omega} C_1 R_0)^2 + 2R_0^2 \omega^2 C_1^2}{R_0^2 \omega^2 C_1^2 + (R_0 \tilde{\omega} C_1)^2}$$

$$= \frac{1 + R_0^2 \omega^2 C_1^2 + R_0^2 \tilde{\omega}^2 C_1^2 + (\tilde{\omega} C_1 R_0)^2}{R_0^2 \omega^2 C_1^2 + (R_0 \tilde{\omega} C_1)^2}$$

$$= \frac{1 + \cancel{R_0^2 \omega^2 C_1^2}}{R_0^2 \omega^2 C_1^2 (1 + \cancel{R_0^2 \omega^2 C_1^2})} + \frac{R_0^2 \tilde{\omega}^2 C_1^2 + (\tilde{\omega} C_1 R_0)^2}{R_0^2 \tilde{\omega}^2 C_1^2 + (R_0 \tilde{\omega} C_1)^2}$$

$$N^2 = \frac{1}{R_0^2 \omega^2 C_1^2} + 1$$

$$N^2 - 1 = \frac{1}{R_0^2 \omega^2 C_1^2}$$

$$R_0^2 \omega^2 C_1^2 = \frac{1}{N^2 - 1}$$

$$\therefore f \propto \frac{1}{\sqrt{N^2 - 1}}$$

$$\therefore C = \frac{1}{R_0 \omega \sqrt{N^2 - 1}}$$

$$L_2 = C_1 R_0^2 = \frac{R_0}{\omega \sqrt{N^2 - 1}}$$


From the above eq's it is evident that

$$f \propto \frac{1}{\sqrt{N^2 - 1}}$$

\therefore If decreased attenuation is required with increase of frequency then Z_1' must be a "capacitor".

Alternative Method:-

Lattice Attenuator Equalizer:-

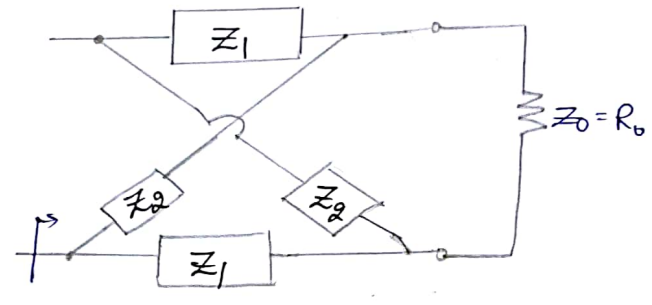

$Z_{in} = Z_0 = R_0$

w.k.t $Z_1 Z_2 = R_0^2$
(inverse impedance)

$Z_1 = R_1 + jX_1$

Design Equations:-

case-i, :- if $X_1 = \omega L_1$

$$N^2 = \frac{A^2 + f^2}{B^2 + f^2}$$

where $A = \frac{R_0 + R_1}{2\pi L_1}$ & $B = \frac{R_0 - R_1}{2\pi L_1}$

case-ii, :- if $X_1 = \frac{1}{\omega C_1}$

$$N^2 = \frac{P f^2 + 1}{Q f^2 + 1}$$

where $P = (R_0 + R_1)$
 $Q = (R_0 - R_1)$

Note: if attenuation of a load is calculated, then can calculate

Design a lattice 17dB attenuator & $R_0 = 600\Omega$.

Given:

17db a
3db a

w.k.t [case-i]:

$$N^2 = \frac{A^2 + f^2}{B^2 + f^2}$$

where $A = \frac{R_0 + R_1}{2\pi L_1}$

At $f = 50$

so $N =$

where

$$P = (R_0 + R_1) 2\pi C_1$$

$$Q = (R_0 - R_1) 2\pi C_1$$

If attenuation at two frequencies are known then A, B & P, Q values are calculated. From these constants we can calculate Z_1 & Z_2 .

Design a lattice attenuation equalizer with 17dB attenuation at 50Hz & 3dB at 2kHz
 $R_0 = 600 \Omega$.

Given:

17dB at 50Hz
 3dB at 2kHz

Let (case-i):

$$N^2 = \frac{A + f^2}{B + f^2}$$

$$Z_1 = R_1 + jX_1$$

where $A = \frac{R_0 + R_1}{2\pi L_1}$, $B = \frac{R_0 - R_1}{2\pi L_1}$

At $f = 50\text{Hz}$; $D = 17\text{dB}$

$$\Rightarrow N = 10^{0.17/20} \Rightarrow 10^{17/200} = 7.079$$

$$\rightarrow \text{At } f = 2 \text{ kHz}, D = 3 \text{ dB}$$

$$N = 10^{\frac{D}{20}} \rightarrow 10^{\frac{3}{20}} = 1.4125$$

$$\text{Now sub}^n \text{ in } N^r = \frac{A^r + f^r}{B^r + f^r}$$

$$(4.079)^r = \frac{A^r + 50^r}{B^r + 50^r}$$

$$(50 \cdot 11)(B^r + 50^r) = A^r + 50^r$$

$$50 \cdot 11 B^r + 122775 = A^r + 50^r$$

$$A^r - 50 \cdot 11 B^r = 122775 \rightarrow \textcircled{1}$$

$$\rightarrow \text{At } f = 2 \text{ kHz}, D = 3 \text{ dB}$$

$$N^r = \frac{A^r + f^r}{B^r + f^r}$$

$$(1.4125)^r = \frac{A^r + (2 \times 10^3)^r}{B^r + (2 \times 10^3)^r}$$

$$(1.993)(B^r + (2 \times 10^3)^r) = A^r + (2 \times 10^3)^r$$

$$B^r(1.993) + 3986000 = A^r + (2 \times 10^3)^r$$

$$A^r - B^r(1.993) = 3972000 \rightarrow \textcircled{2}$$

on solving $\textcircled{1}$ & $\textcircled{2}$

$$A^r = 4131434.408 \quad ; \quad B^r = 79997.194$$

$$A = 2032.59$$

$$B = 282.84$$

$$A = \frac{R_0 + R_1}{2\pi L_1}$$

$$B = \frac{R_0 - R_1}{2\pi L_1}$$

$$2032.59 = \frac{R_0 + R_1}{2\pi L_1}$$

$$282.84 = \frac{R_0 - R_1}{2\pi L_1}$$

$$R_0 + R_1 = (2032.59)2\pi L_1 \quad ; \quad \rightarrow \textcircled{3}$$

$$R_0 - R_1 = (282.84)2\pi L_1 \quad ; \quad \rightarrow \textcircled{4}$$

Solving $\textcircled{3}$ & $\textcircled{4}$

$$\begin{aligned} R_0 + R_1 &= (2032.59)2\pi L_1 \\ R_0 - R_1 &= (282.84)2\pi L_1 \\ \hline 2R_0 &= 2\pi L_1 [2032.59 + 282.84] \end{aligned}$$

$$\frac{600}{\pi(2032.59 + 282.84)} = L_1$$

$$L_1 = 82.48 \text{ mH}$$

$$C_2 = \frac{L_1}{R_0} = \frac{82.48 \text{ mH}}{(600)^2} \Rightarrow C_2 = 229.12 \text{ nF}$$

In order to get 'R₁'?

subⁿ L₁ in eqn $\textcircled{3}$ i.e

$$R_1 = (2032.59)2\pi L_1 - R_0$$

$$R_1 = 453.86 \Omega$$

W.K.T $R_1 R_2 = R_0^2$

$$R_2 = \frac{R_0^2}{R_1}$$

$$R_2 = \frac{600^2}{453.36}$$

$$R_2 = 794.07 \Omega$$