

# CHAPTER 9: ASYNCHRONOUS SEQUENTIAL CIRCUITS



# Chapter Objectives

2

- Sequential circuits that *are not synchronized by a clock* – Asynchronous circuits
- *Analysis* of Asynchronous circuits
- *Synthesis* of Asynchronous circuits
- *Hazards* that cause incorrect behavior of a circuit


# Asynchronous sequential circuits

3

- Synchronous sequential circuits
  - ▣ state variables : F/Fs
  - ▣ controlled by a clock
  - ▣ operate in *pulse mode*
  
- Asynchronous sequential circuits
  - ▣ do not operate in *pulse mode*
  - ▣ do not use F/Fs to represent state variables
  - ▣ Changes in state are dependent on whether *each of inputs* to the circuit has the logic level 0 or 1 at any given time
  
- To achieve reliable operation (focus on the simplest case)
  - ▣ the inputs to the circuit must *change one at a time*
  - ▣ there must be *sufficient time between the changes* in input signals to allow the circuit to reach a stable state
  
- ▣ A circuit that adheres to these constraints is said to operate *in the fundamental mode*

# Asynchronous behavior

4

 

two NOR gate delay

(a) Circuit with modeled gate delay

$$Y = \overline{\overline{(y + S)} + R}$$

Present state <i>y</i>	Next state			
	<i>SR</i> = 00	01	10	11
<i>y</i>	<i>Y</i>	<i>Y</i>	<i>Y</i>	<i>Y</i>
0	0	0	1	0
1	1	0	1	0

stable state


(b) State-assigned table

# FSM model for the SR latch

5

Present state	Next state				Output Q
	$SR = 00$	01	10	11	
A	(A)	(A)	B	(A)	0
B	(B)	A	(B)	A	1

(a) State table

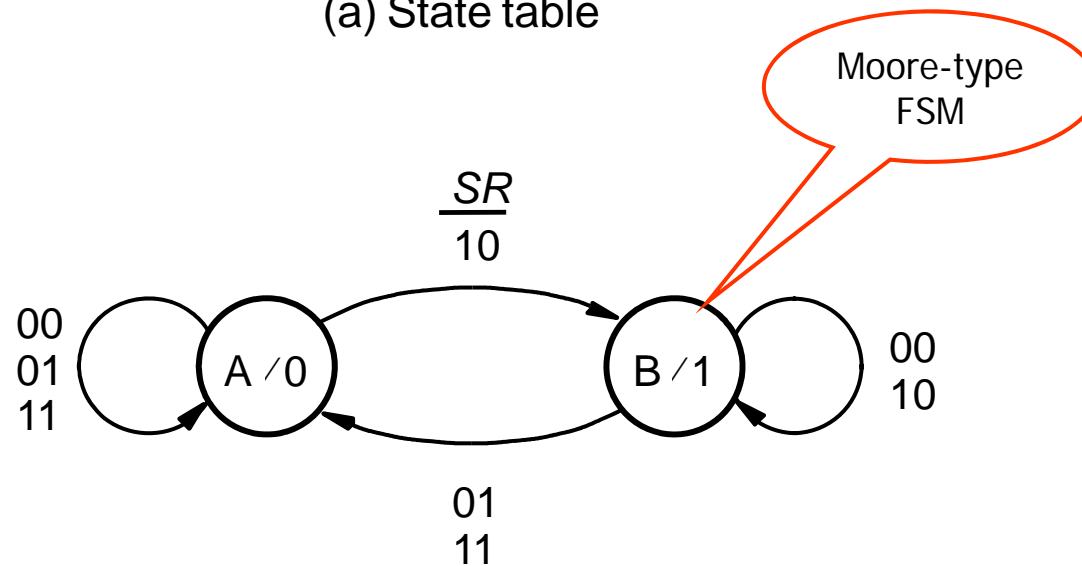

(b) State diagram

# Synthesis of an asynchronous circuit

6


Present state	Nextstate				Output Q
	SR = 00	01	10	11	
A	(A)	(A)	B	(A)	0
B	(B)	A	(B)	A	1

(a) State table

Present state	Nextstate			
	SR = 00	01	10	11
y	Y	Y	Y	Y
0	(0)	(0)	1	(0)
1	(1)	0	(1)	0

 (b) State-assigned table

$$\begin{aligned}
 Y &= \overline{\overline{R}} \bullet (S + y) \\
 &= \overline{\overline{R}} \bullet (S + y) \\
 &= \overline{(\overline{R} + (S + y))} \\
 &= (R + (S + y)) \\
 z &= y
 \end{aligned}$$




# Mealy representation of the SR latch

7

Present state	Next state				Output, Q			
	SR = 00	01	10	11	00	01	10	11
A	(A)	(A)	B	(A)	0	0	—	0
B	(B)	A	(B)	A	1	—	1	—

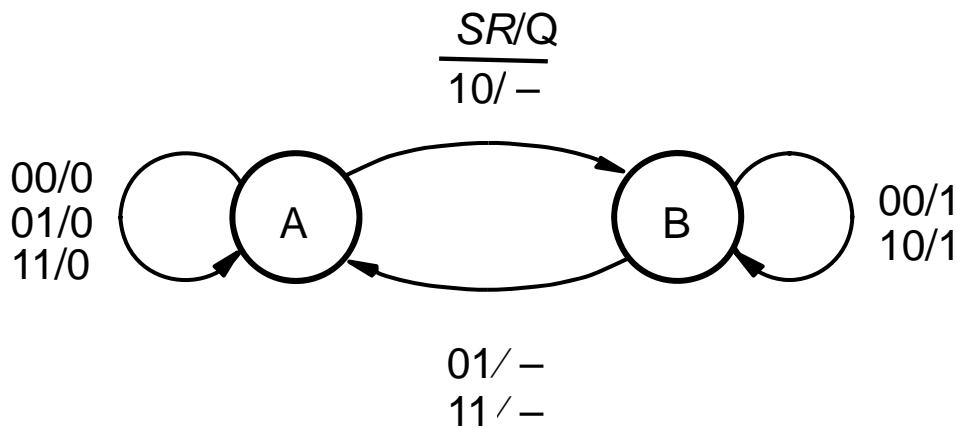(a) State table

there is little to be gained in trying to make output Q go to 1 a little sooner



(b) State diagram

$$\begin{aligned}
 Y &= \overline{R} \bullet (S + y) \\
 &= \overline{\overline{R} \bullet (S + y)} \\
 &= \overline{(\overline{R} + (S + y))} \\
 &= (R + (S + y)) \\
 Q &= y
 \end{aligned}$$

# Terminology

8


- Asynchronous circuits
  - ▣ state table → flow table
  - ▣ state-assigned table → transition table or  
excitation table
  
- We will use the term *flow table and excitation table*



# Analysis of Asynchronous Circuits

# Analysis of Asynchronous circuits

10

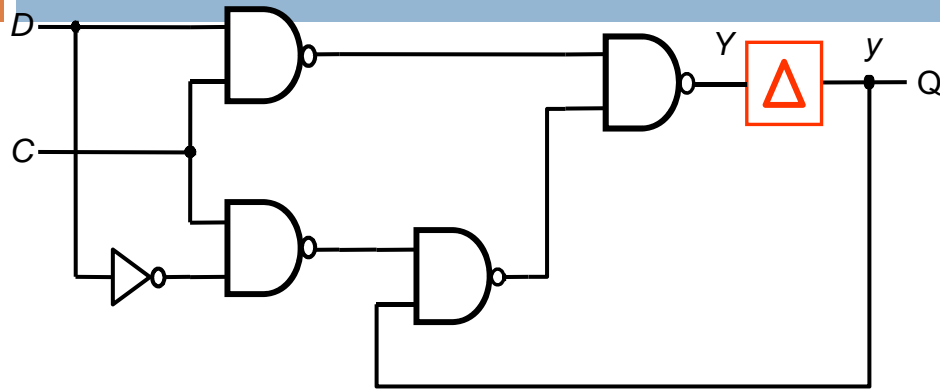

(a) gated D latch

$$\begin{aligned}
 Y &= \overline{(\overline{C \cdot D}) \cdot ((\overline{C \cdot D}) \cdot y)} \\
 &= \overline{(\overline{C \cdot D})} + \overline{((\overline{C \cdot D}) \cdot y)} \\
 &= CD + ((\overline{C} + D) \cdot y) \\
 &= CD + \overline{C}y + Dy \\
 &= CD + \overline{C}y
 \end{aligned}$$


redundant term to solve a hazard

Present state	Next state				Q
	CD = 00	01	10	11	
y	Y	Y	Y	Y	
0	0	0	0	1	0
1	1	1	0	1	1

(b) Excitation table

Present state	Next state				Q
	CD = 00	01	10	11	
A	A	A	A	B	0
B	B	B	A	B	1


(c) Flow table

 

(d) State diagram

# Analysis of the circuit in example 9.3

11

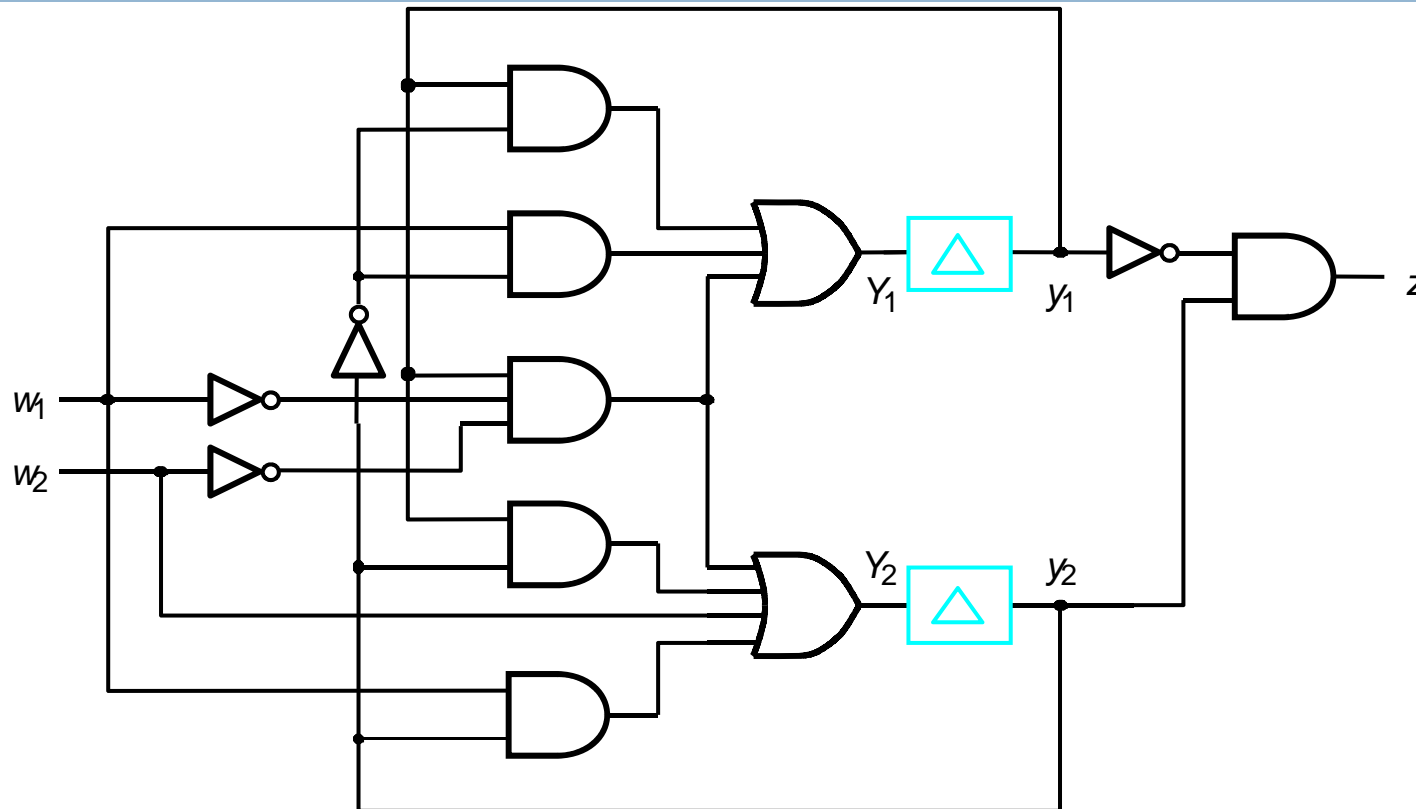

$$Y_1 = y_1 \bar{y}_2 + w_1 \bar{y}_2 + \bar{w}_1 \bar{w}_2 y_1$$
$$Y_2 = y_1 y_2 + w_1 y_2 + w_2 + \bar{w}_1 \bar{w}_2 y_1$$
$$z = \bar{y}_1 y_2$$

# Excitation and flow tables for the circuit in example 9.3

12

Present state $y_2 y_1$	Nextstate				Output $z$
	$w_2 w_1 =$				
	00	01	10	11	
	$Y_2 Y_1$	$Y_2 Y_1$	$Y_2 Y_1$	$Y_2 Y_1$	
00	00	01	10	11	0
01	11	01	11	11	0
10	00	10	10	10	1
11	11	10	10	10	0

(a) Excitation table

Present state	Nextstate				Output $z$	
	$w_2 w_1 =$	00	01	10		11
A		A	B	C	D	0
B		D	B	D	D	0
C		A	C	C	C	1
D		D	C	C	C	0

(b) Flow table


# Modified flow table for Example 9.3.

13

Present state	Nextstate				Output Z
	$w_2 w_1 =$ 00	01	10	11	
A	(A)	B	C	-	0
B	D	(B)	-	D	0
C	A	(C)	(C)	(C)	1
D	(D)	C	C	C	0

# State table for Example 9.3

14

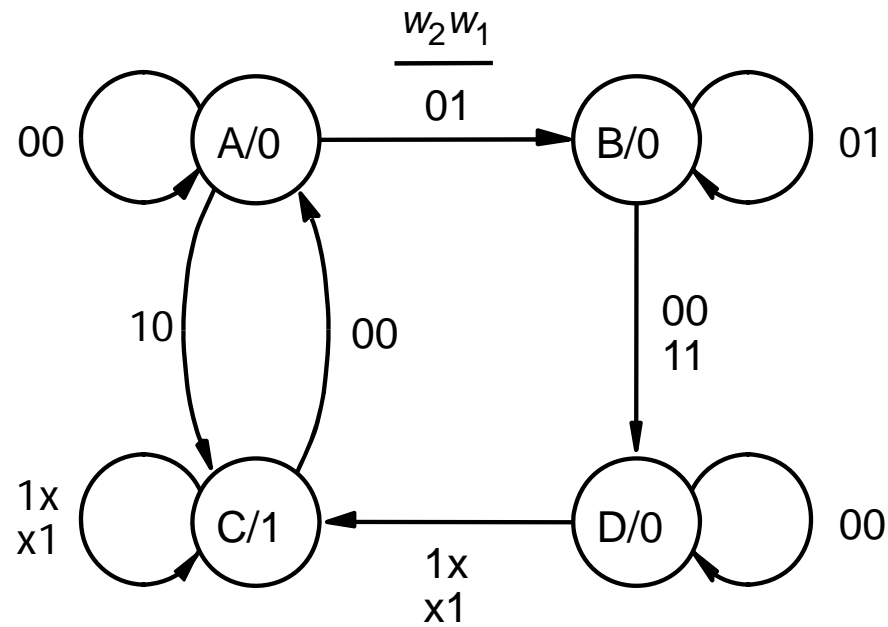

# Flow table for a simple vending machine

15

Present state	Nextstate				Output $Z$	
	$w_2 w_1 =$	00	01	10		11
A		(A)	B	C	-	0
B		D	(B)	-	-	0
C		A	(C)	(C)	-	1
D		(D)	C	C	-	0

$w_2 \equiv$  dime     $w_1 \equiv$  nickel

# Steps in the Analysis Process

16

- Each feedback path **is cut**
  - ▣ A delay element is inserted at the point where the cut is made
  - ▣ A cut can be made anywhere in a particular loop formed by feedback connection, as long as there is only one cut per (state variable) loop
- **Next-state and output expressions** are derived from the circuit
- **The excitation table** is derived
- **A flow table** is obtained
- A corresponding **state diagram** is derived from the flow table if desired



# Synthesis of Asynchronous Circuits

# Synthesis of Asynchronous Circuits

18


- the same basic steps used to synthesize the synchronous circuits
  - ▣ Devise *a state diagram* for an FSM
  - ▣ Derive *the flow table* and reduce the number of states if possible
  - ▣ Perform the state assignment and derive *the excitation table*
  - ▣ Obtain *the next-state and output* expressions
  - ▣ Construct a circuit that implements these expressions

# Example: serial parity generator

19

 
## Serial parity generator

- input  $w$  : pulses are applied to  $w$
- output  $z$
- $z=1$  if the number of previously applied pulses is odd



# Parity-generating asynchronous FSM

20

 

(a) State diagram

Present State	Nextstate		Output $z$
	$w = 0$	$w = 1$	
A	Ⓐ	B	0
B	C	Ⓑ	1
C	Ⓒ	D	1
D	A	Ⓓ	0

(b) Flow table

# State assignment

21

Present state $y_2y_1$	Next state		Output $z$
	$w = 0$	$w = 1$	
	$Y_2Y_1$		
00	00	01	0
01	10	01	1
10	10	11	1
11	00	11	0

(a) Poor state assignment

Present state $y_2y_1$	Next state		Output $z$
	$w = 0$	$w = 1$	
	$Y_2Y_1$		
00	00	01	0
01	11	01	1
11	11	10	1
10	00	10	0

(b) Good state assignment

- State assignment (a) has a major flaw
  - state D = 11 :  $w=0 \rightarrow$  state A
  - $y_2y_1=11 \rightarrow y_2y_1=00$
  - the values of the next-state variables determined by the networks of logic gates with varying delays
    - suppose  $y_1$  changes first
      - $y_2y_1=10 \rightarrow$  state C(10)
      - state C is stable when  $w=0$
    - suppose  $y_2$  changes first
      - $y_2y_1=01 \rightarrow$  state B (01)
      - try to change to  $y_2y_1=10$  when  $w=0$
      - if  $y_1$  changes first,  $y_2y_1=00$

■ *race condition occurs*


# Circuit that implements the FSM

22


$$Y_1 = w\bar{y}_2 + \bar{w}y_1 + y_1\bar{y}_2$$

$$Y_2 = wy_2 + \bar{w}y_1 + y_1y_2$$

$$z = y_1$$

 

Synchronous solution

 

Asynchronous solution

# Circuit that implements a parity-generating asynchronous FSM

23

- The asynchronous implementation is *more complex* than the synchronous one?
- It's a negative-edge-triggered master/slave F/F
  - ▣ With the complement of its output connected to its D input


# Master-slave D F/F(example 9.2)

- Analyze synchronous circuit as if it were an asynchronous circuit.
  - ▣ Actually all circuits are asynchronous

$Y = CD + \bar{C}y + Dy$   
in the previous example  
of gated D - Latch

$$Y_m = CD + \bar{C}y_m + Dy_m$$

$$Y_s = \bar{C}y_m + Cy_s + y_my_s$$

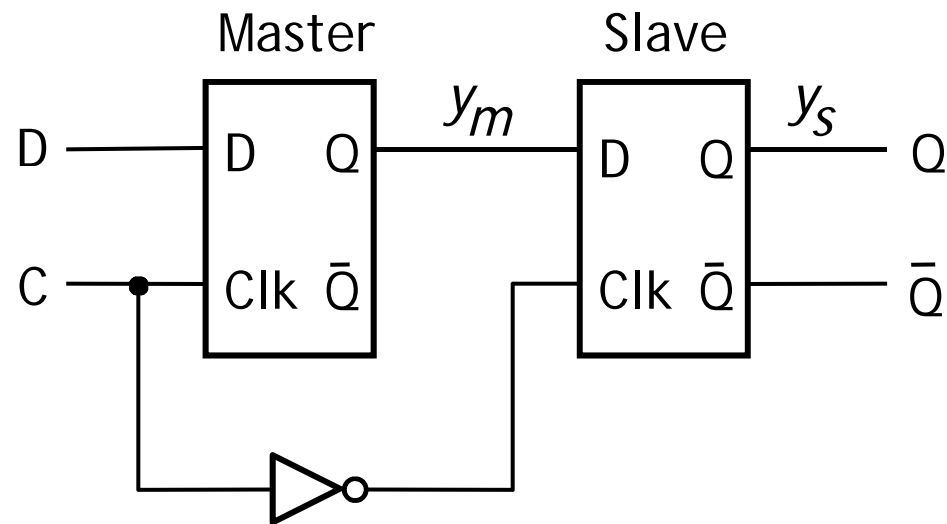

Circuit for the master-slave D flip-flop.



# Excitation table for example 9.2

25

Present state $y_m y_s$	Next state				Output Q	
	$CD =$	00	01	10		11
	$Y_m Y_s$					
00		00	00	00	10	0
01		00	00	01	11	1
10		11	11	00	10	0
11		11	11	01	11	1

(a) Excitation table

# Flow tables for Example 9.2


Present state	Next state				Output Q
	<i>CD</i> = 00	01	10	11	
S1	(S1)	(S1)	(S1)	S3	0
S2	S1	S1	(S2)	S4	1
S3	S4	S4	S1	(S3)	0
S4	(S4)	(S4)	S2	(S4)	1

(b) Flow table

Present state	Next state				Output Q
	<i>CD</i> = 00	01	10	11	
S1	(S1)	(S1)	(S1)	S3	0
S2	S1	-	(S2)	S4	1
S3	-	S4	S1	(S3)	0
S4	(S4)	(S4)	S2	(S4)	1

(c) Flow Table with unspecified entries
 
# State diagram for the master-slave D Flip/Flop



# Parity generating FSM and Master-slave D F/F

28

$$Y_1 = w\bar{y}_2 + \bar{w}y_1 + y_1\bar{y}_2$$

$$Y_2 = wy_2 + \bar{w}y_1 + y_1y_2$$

$$z = y_1$$

$Y = CD + \bar{C}y + Dy$   
in the previous example  
of gated D-Latch


$$Y_m = CD + \bar{C}y_m + Dy_m$$

$$Y_s = \bar{C}y_m + Cy_s + y_my_s$$

$$y_1 = y_m, y_2 = y_s$$

$$w = C, \bar{y}_2 = D,$$

$$z = y_1 = y_m$$

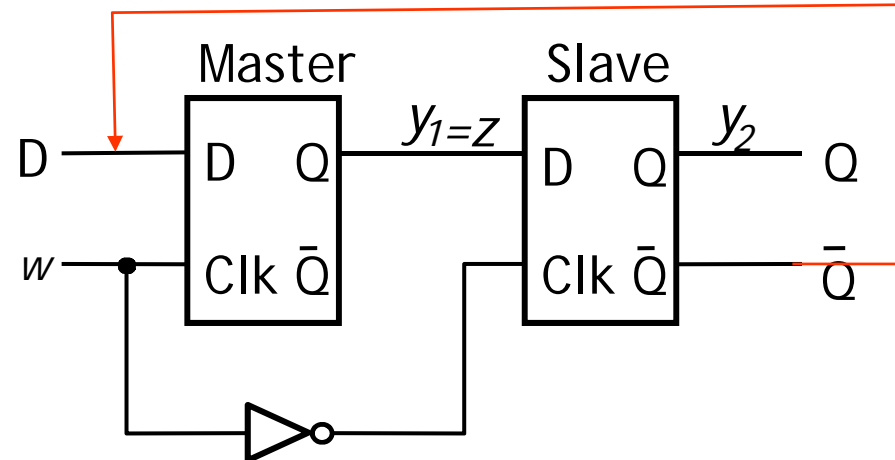

# Hazard and Glitches

# Hazards and glitches

30

- In asynchronous circuits
  - ▣ undesirable glitches on signals should not occur
  - ▣ hazards
    - the glitches cause by the structure of a given circuit and propagation delays in the circuit
  - ▣ two types of hazards
    - static
      - the signal undergoes a momentary change in its required value
    - dynamic
      - when a signal is supposed to change from 1 to 0 or from 0 to 1
      - a change involves a short oscillation before the signal settles into its new level

# Definition of hazards

31



(a) Static hazard



(b) Dynamic hazard

# Hazards and glitches


32

- Usual solutions
  - ▣ wait until signals are stable by using a clock
    - preferable
    - easiest to design when there is a clock
    - synchronous circuits
  - ▣ design hazard-free circuits
    - sometimes necessary
    - asynchronous design




# Static hazards

33

 


(a) Circuit with a hazard

 

(b) Karnaugh map

$$f = x_1x_2 + \bar{x}_1x_3$$

$$f = x_1x_2 + \bar{x}_1x_3 + x_2x_3$$

 

(c) Hazard-free circuit


hazard-free if more than one bit of inputs change simultaneously ?

# Two-level implementation of master-slave D flip-flop

34

Present state $y_m y_s$	Next state				Output Q
	$CD =$				
	00	01	10	11	
	$Y_m Y_s$				
00	00	00	00	10	0
01	00	00	01	11	1
10	11	11	00	10	0
11	11	11	01	11	1

(a) Excitation table

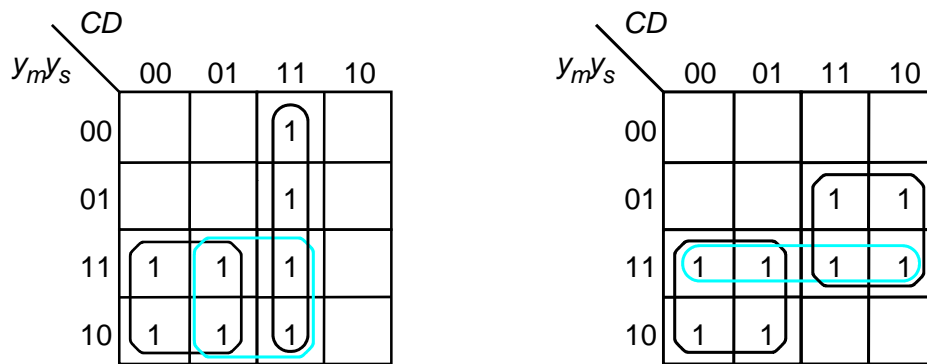


(b) Karnaugh maps for  $Y_m$  and  $Y_s$  in Figure 9.6a

$$Y_m = CD + \bar{C}y_m + Dy_m$$


$$Y_s = \bar{C}y_m + Cy_s + y_m y_s$$

# Two-level implementation of master-slave D flip-flop (2)

35

 

(a) Minimum-cost circuit

 


(c) Hazard-free circuit

$$Y_m = CD + \bar{C}y_m + Dy_m$$

$$Y_s = \bar{C}y_m + Cy_s + y_my_s$$

# Static hazard in a POS circuit (0-hazard)


36

 

(a) Circuit with a hazard

	$x_1 x_2$			
	00	01	11	10
$x_3$	0	0	0	1
	1	1	1	1

(b) Karnaugh map


 


(c) Hazard-free circuit
  
# dynamic hazards

37

- there exist multiple paths for a given signal change to propagate along
- neither easy to detect nor easy to deal with
- using two-level hazard-free circuits





CLOCK  
SYNCHRONIZATION  
(CHAPTER 10.3)
  
# Clock skew


39

- the clock signal arrives at different times at different F/Fs
  - ▣ with or without clock enable circuits
  - ▣ wires whose lengths vary appreciably



# An H-tree clock distribution network

40

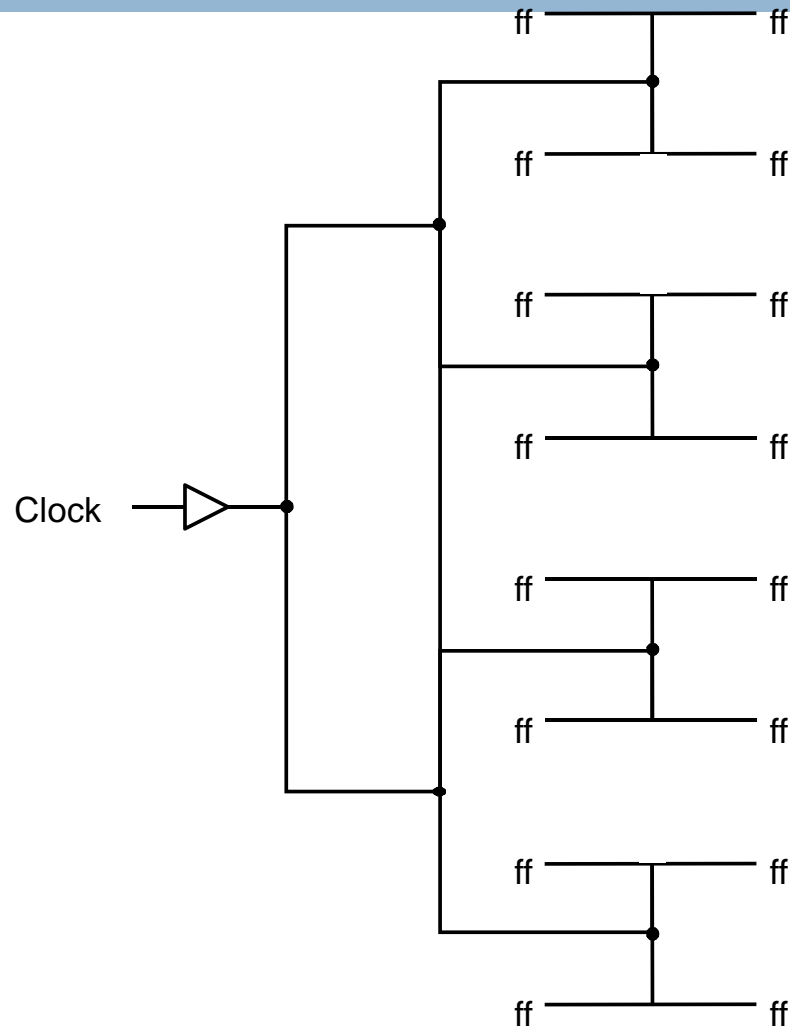



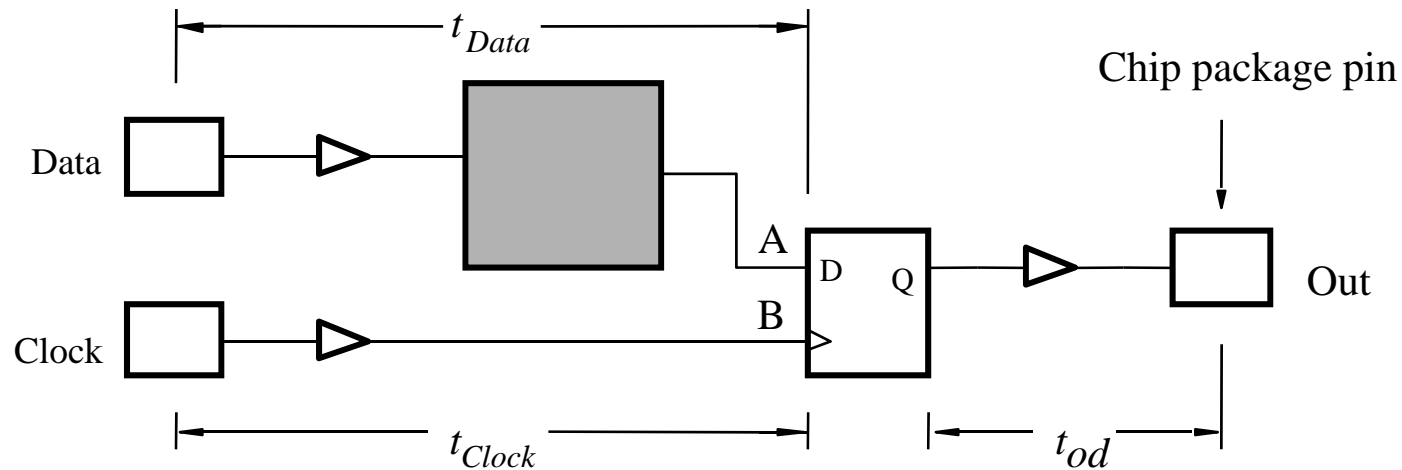
# F/F timing parameters

41

- setup time  $t_{su}$
- hold time  $t_h$
- register delay or propagation delay  $t_{rd}$
- output delay time  $t_{od}$ 
  - ▣ required for the change in Q to propagate to an output pin on the chip




A flip-flop in an integrated circuit
 
# F/F timing parameters, cont'd

42

- $t_{co}$  delay : active clock edge  $\rightarrow$  output change at an output pin
  - $t_{Clock} + t_{rd} + t_{od}$
  - Example
    - $t_{Clock} = 1.5ns, t_{rd} = 1ns, t_{od} = 2ns \rightarrow t_{co} = 4.5 ns$
- F/F timing in a chip
  - $t_{Clock} = 1.5 ns, t_{Data} = 4.5 ns, t_{su} = 3 ns$



# Metastability and Asynchronous Inputs

43

## ***Asynchronous Inputs Are Dangerous!***

**Since they take effect immediately, glitches can be disastrous**


**Synchronous inputs are greatly preferred!**

**But sometimes, asynchronous inputs cannot be avoided  
e.g., reset signal, memory wait signal**

# Metastability and Asynchronous Inputs

44

## Handling Asynchronous Inputs

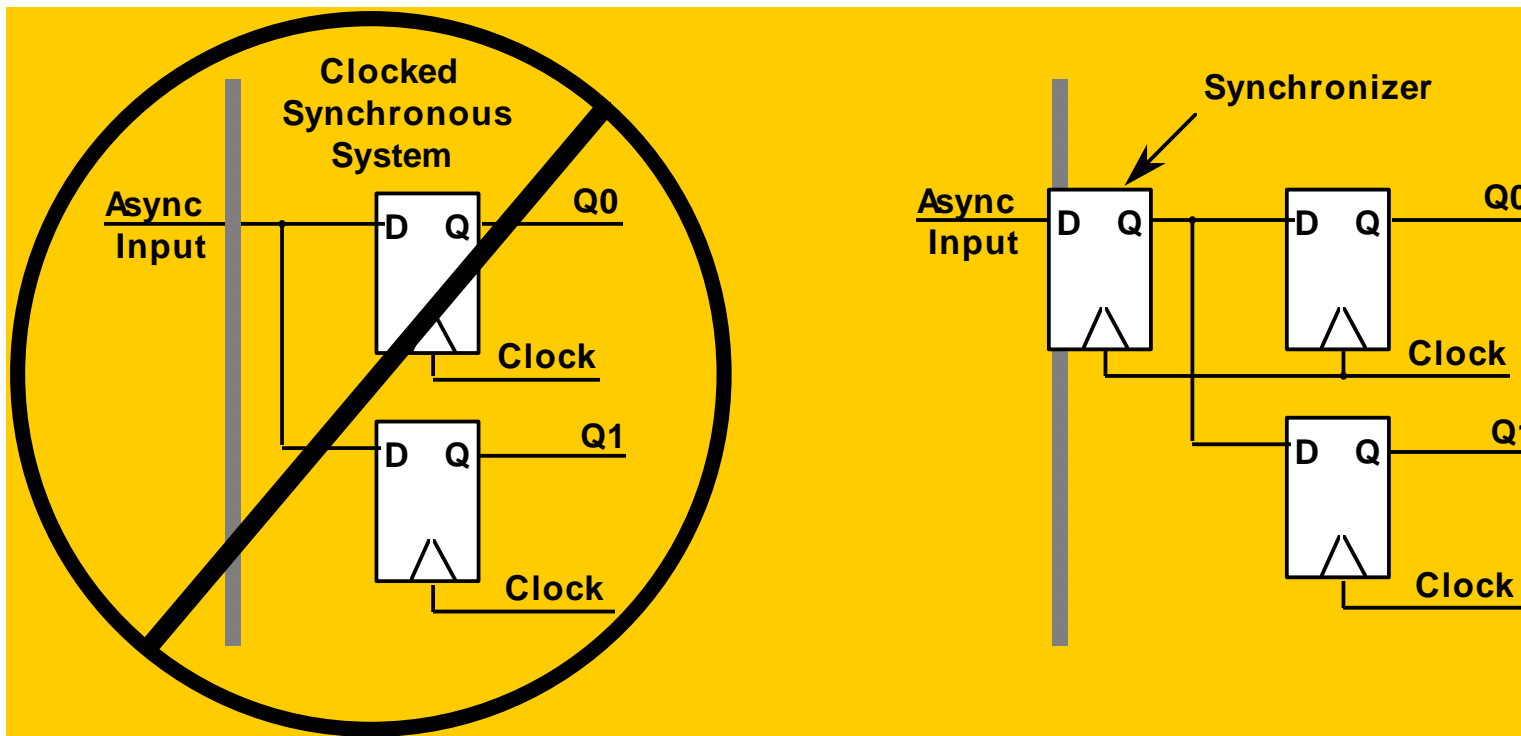


**Never allow asynchronous inputs to be fanned out to more than one FF within the synchronous system**

# Metastability and Asynchronous Inputs

45

## *What Can Go Wrong*

 

In is asynchronous  
Fans out to D0 and D1  
One FF catches the  
signal, one does not


*impossible state might  
be reached!*

**Single FF that receives the asynchronous signal is a *synchronizer***

# Metastability and Asynchronous Inputs


46

## Synchronizer Failure

 


When FF input changes close to clock edge, the FF may enter the *metastable* state: neither a logic 0 nor a logic 1

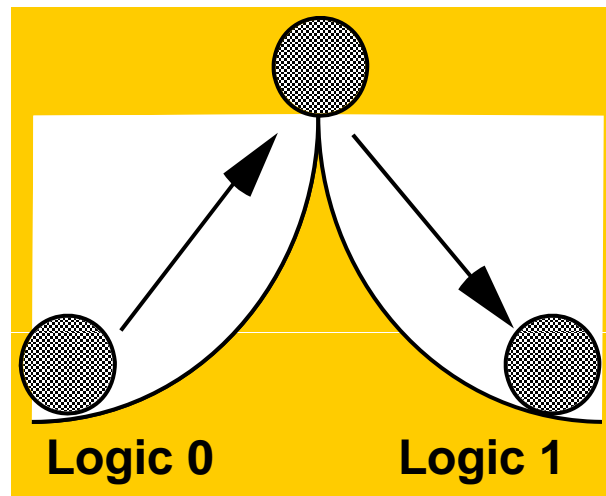It may stay in this state an indefinite amount of time, although this is not likely in real circuits



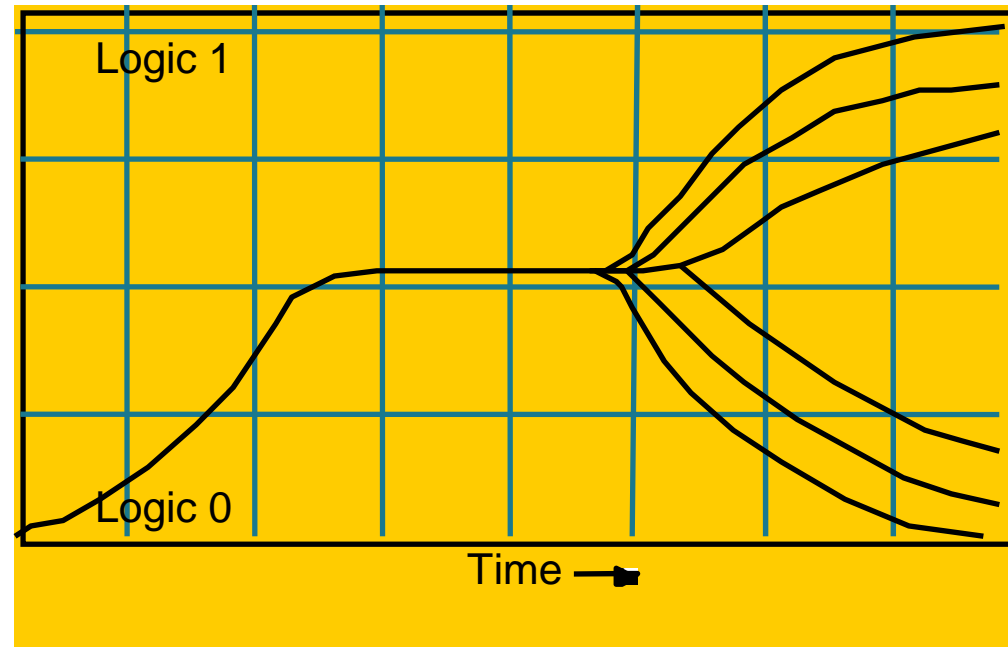Small, but non-zero probability that the FF output will get stuck in an in-between state



Oscilloscope Traces Demonstrating Synchronizer Failure and Eventual Decay to Steady State

# Metastability and Asynchronous Inputs

47

## ***Solutions to Synchronizer Failure***

- the probability of failure can never be reduced to 0, but it can be reduced
- slow down the system clock  
this gives the synchronizer more time to decay into a steady state  
synchronizer failure becomes a big problem for very high speed systems
- use fastest possible logic in the synchronizer  
this makes for a very sharp "peak" upon which to balance  
S or AS TTL D-FFs are recommended
- cascade two synchronizers

