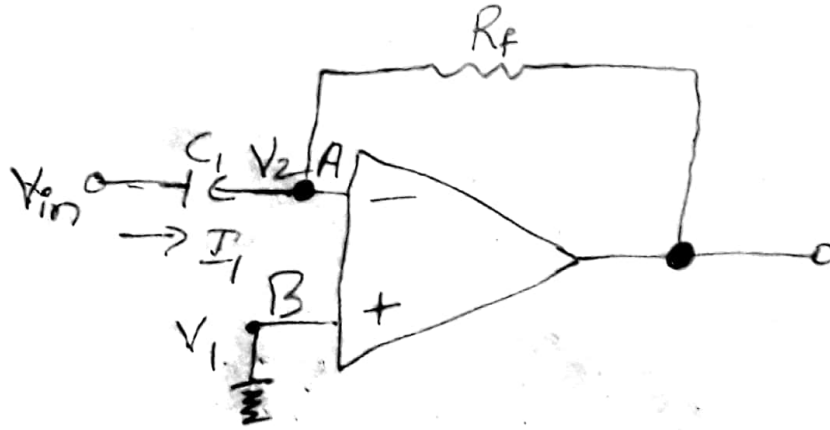


Ideal op-amp Differentiator:-



Due to virtual ground concept $V_1 = V_2 = 0$
Inside the op-amp input is zero.

From the input side Differentiator

$$I_1 = C_1 \frac{d}{dt} (V_{in} - V_2) \quad (\because V_2 = 0)$$

$$= C_1 \left[\frac{dV_{in}}{dt} \right] \quad \text{--- (1)}$$

From the output side Differentiator

$$I_1 = \frac{V_2 - V_{out}}{R_f} \quad (\because V_2 = 0) \quad (2)$$

$$I_1 = \frac{-V_{out}}{R_f}$$

Equate the eq (1) & (2)

$$C_1 \frac{dV_{in}}{dt} = \frac{-V_{out}}{R_f}$$

$$C_1 R_f \frac{dV_{in}}{dt} = -V_{out}$$

$$V_{out} = -C_1 R_f \frac{dV_{in}}{dt}$$


→ Above equation shows that output of differentiator is $C_1 R_f$ times.

→ Negative sign indicates that there is a phase shift of 180° between input & output.

a) Step Input Signal :-


Let the input wave form is of step type with a magnitude of "A" units is expressed as

$V_{in}(t) = A \text{ for } t \geq 0$

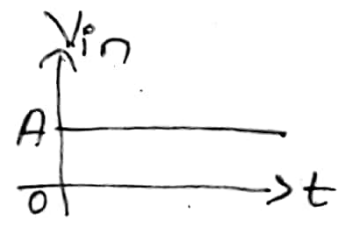

Now output of differentiator

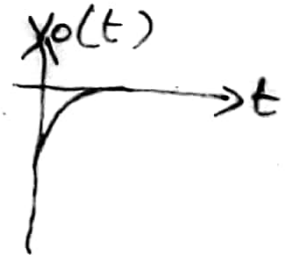$V_o(t) = \frac{-dV_{in}}{dt} = \frac{-d(A)}{dt} = 0$



This is because "A" is constant.

Note :- Actually the step input takes limit time to rise from 0 to A volts.

b) Square wave Input signal :-



The square wave is made of steps i.e

step of "A" volts from $t=0$ to $t=T/2$
 while a step of "-A" volts from
 $t=T/2$ to $t=T$ so

$$V_{in}(t) = A ; 0 < t < T/2$$

$$= -A ; T/2 < t < T$$

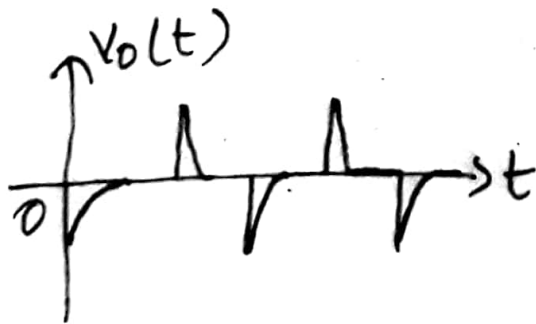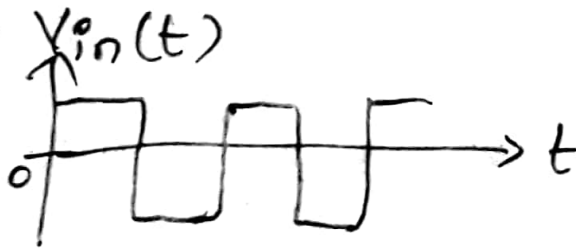→ so total output in the form of
 train of impulses or spikes.



Sine wave input:-

let the input wave form purely sinusoidal
 - da |

5

$$V_{in}(t) = V_m \sin \omega t$$

V_m = amplitude

T = Time period of wave for 'm'

So $V_o(t) = -\frac{dV_{in}(t)}{dt}$ for $R_f C_1 = 1$

$$= -\frac{d}{dt} (V_m \sin \omega t)$$

$$V_o(t) = -\frac{d}{dt} (V_m \sin \omega t)$$

$$V_o(t) = -V_m \cos \omega t \cdot \omega$$



So at $t=0$, $V_o(t) = -V_m \cdot \omega$

$t = \frac{T}{4}$, $V_o(t) = 0$

$t = \frac{T}{2}$, $V_o(t) = +V_m \cdot \omega$

The output of the differentiator is a cosine for a sine wave input

(6)

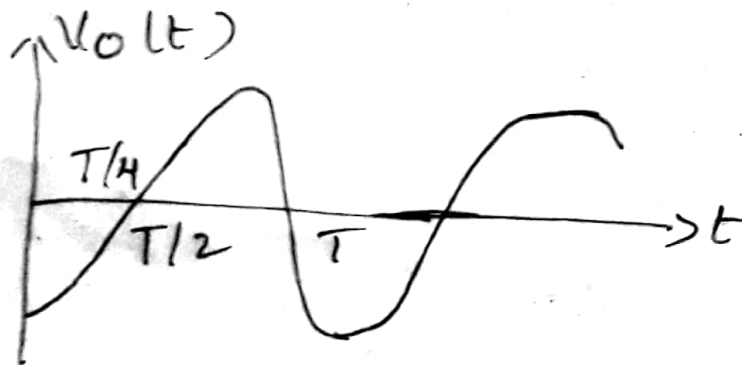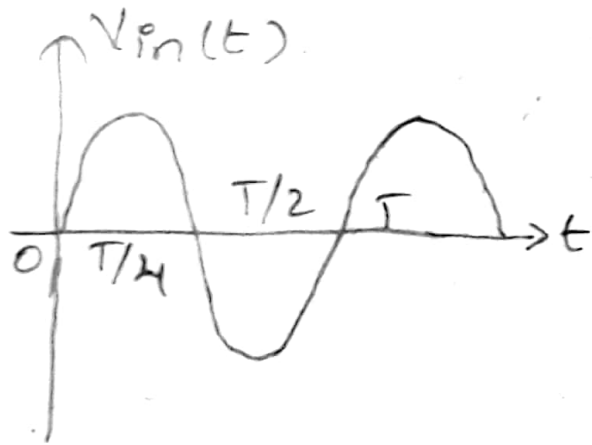

Frequency Response :-

Consider the output equation of an ideal differentiator

$$V_o(t) = -R_f C_1 \frac{dV_{in}}{dt}$$

The Laplace transform of this equation

$$V_o(s) = -s R_f C_1 V_{in}(s)$$

To get the frequency response, replace "s" by $j\omega$

(7)

$$V_o(j\omega) = -j\omega R_f C_1 V_{in}(j\omega)$$

$$\frac{V_o(j\omega)}{V_{in}(j\omega)} = -j\omega R_f C_1$$

Magnitude of gain

$$A = \left| \frac{V_o(j\omega)}{V_{in}(j\omega)} \right| = \left| -j\omega R_f C_1 \right| \quad (\because -j=1)$$

$$A = \omega R_f C_1$$

$$= 2\pi f R_f C_1$$

at low frequency ($f=0$) the gain is zero.

and frequency increases gain also increase

$$A = \frac{f}{f_c}$$

$$\therefore f_c = \frac{1}{2\pi R_f C_1}$$