

Mono-stable

AA-stable


Schmitt

Trigger

Triangular

wave generator

Transistor Wave Generator

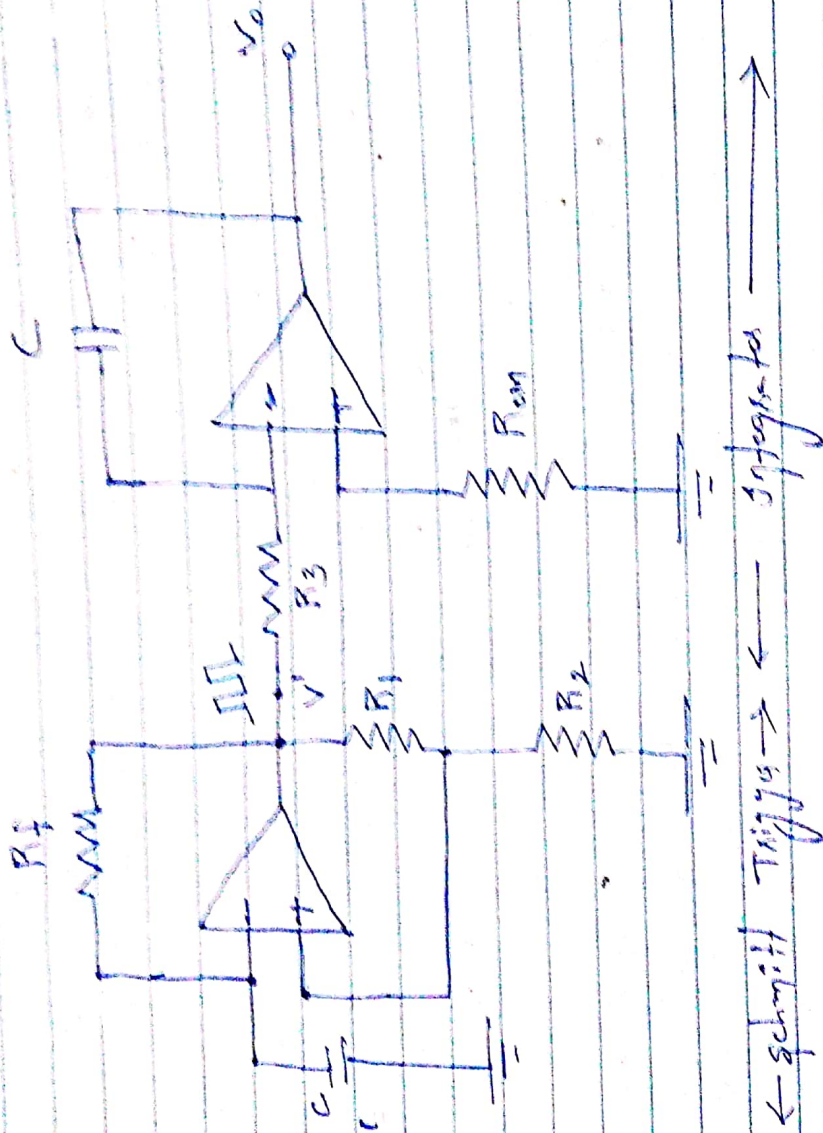

Determination of frequency and

Amplitude :-

The frequency and amplitude of the triangular wave can be determined as under

When comparator output is at $+V_{sat}$, the effective voltage at point "P" is given by

$$-V_{\text{comp}} + \frac{R_2}{R_2 + R_3} [+V_{\text{sat}} - (-V_{\text{comp}})]$$

Effective voltage "P" equal to zero

Then

$$-V_{\text{comp}} + \frac{R_3}{R_2 + R_3} (V_{\text{comp}}) + \frac{R_2}{R_2 + R_3} + V_{\text{sat}} = 0$$

$$-V_{\text{comp}} = 0$$

$$-\frac{R_3}{R_2 + R_3} V_{\text{comp}} = \frac{R_2}{R_2 + R_3} (+V_{\text{sat}})$$

$$-V_{\text{ramp}} = \frac{R_2}{R_2 + R_3} \times \frac{R_2 + R_3}{R_3} (+V_{\text{sat}})$$

$$-V_{\text{ramp}} = -\frac{R_2}{R_3} (+V_{\text{sat}})$$

$$V_{\text{ramp}} = -\frac{R_2}{R_3} (-V_{\text{sat}})$$

If $|+V_{\text{sat}}| = |-V_{\text{sat}}|$ then, we can

write

$$\boxed{V_{o(\text{pp})} = \frac{R_2}{R_3} V_{\text{sat}}}$$

$$V_{o(\text{pp})} = +V_{\text{ramp}} - (-V_{\text{ramp}})$$

$$V_{o(\text{pp})} = -\frac{R_2}{R_3} (-V_{\text{sat}}) - \left(-\frac{R_2}{R_3}\right) (+V_{\text{sat}})$$

$$V_{o(\text{pp})} = \frac{R_2}{R_3} V_{\text{sat}} + \frac{R_2}{R_3} V_{\text{sat}}$$

$$\boxed{V_{o(\text{pp})} = 2\frac{R_2}{R_3} V_{\text{sat}}} \quad \text{--- ①}$$

③
be taken by output to swing

from. -V_{ramp} to +V_{ramp} is equal
to half of time period T/2

$$V_o(\text{PP}) = \frac{-1}{R_1 C_1} \int_0^{T/2} (-V_{\text{sat}}) \cdot dt \\ = \left(\frac{V_{\text{sat}}}{R_1 C_1} \right) \cdot \frac{T}{2}$$

Substitute V_{opp} value in eq ①

$$\frac{2R_2}{R_3} V_{\text{sat}} = \frac{V_{\text{sat}} T}{R_1 C_1} \cdot \frac{1}{2}$$

$$\frac{T}{2} \frac{V_{\text{sat}}}{R_1 C_1} = \frac{2R_2}{R_3} V_{\text{sat}}$$

$$T = \frac{4R_2 R_1 C_1}{R_3}$$

The frequency of oscillation can be

$$f_0 = \frac{1}{T} \Rightarrow f_0 = \frac{R_3}{4R_1 R_2 C_1}$$