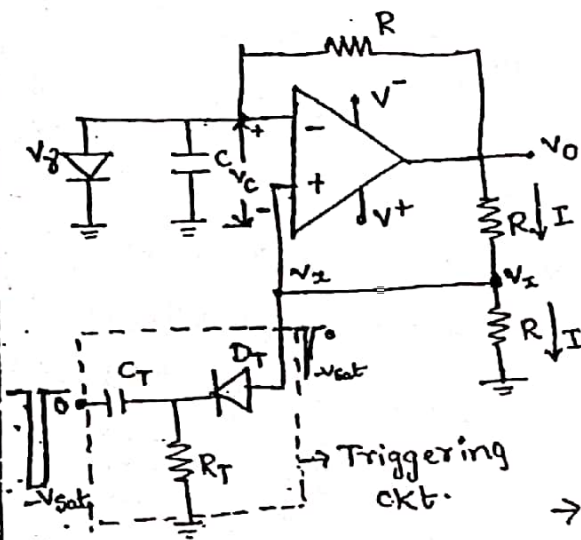


\* Monostable Multivibrator :- (Pulse Generator).

- The MMV has one stable & one Quasi state.
- once the supply given the MMV in the stable state. To change the state apply a trigger pulse [negative going amplitude pulse of short duration  $T_p \ll \tau$ ].
- After trigger pulse applied, the MMV enters into Quasi state. It remains in the quasi state for a predetermined time ( $\tau$ ), after this time the MMV automatically come back to origin state (stable state). In the Quasi state, it generates a pulse of duration ( $\tau$ ) - "pulse generator".
- It is also called as "voltage to Time Converter". ~~(It is also)~~  $\times$  c  
 "UNIVIBRATOR" ( $\delta$ ) "one shoot vibrator".



$$V_x = V_0 \left( \frac{R_2}{R_1 + R_2} \right) = \beta V_0$$

Let the  $C$  is initially uncharged  
 $V_C = 0 \rightarrow D$ -off.

once the supply given, the MMV in the stable state.

Let  $V_0 = +V_{sat} \rightarrow$  stable state of

$$V_0 = +V_{sat} \quad V_x = \beta V_{sat}$$

$\rightarrow$  As  $V_0 = V_{sat}$  is given to  $C$  & diode

combination through  $R$ . Now the  $C$  starts charging towards  $+V_{sat}$  through  $R$  with  $T = RC$ .

when  $V_C = V_x$ ,  $D$ - becomes ON  $\rightarrow$  replaced by  $V_0$ .

Now the  $C$  stops charging  $\left\{ \begin{array}{l} V_C = V_x, V_0 = V_{sat} \\ D = \text{ON}, V_x = \beta V_{sat} \end{array} \right\} \rightarrow$  stable state of MMV.

$\rightarrow$  Now apply a trigger pulse to change the state.

After trigger pulse, the potential at non-inv. terminal becomes  $(\beta V_{sat} - V_{sat}) \rightarrow -ve$ .

The  $V_c > (\beta V_{sat} - V_{sat}) \Rightarrow V_o = -V_{sat}$

Now  $V_o = -V_{sat}$   $V_x = -\beta V_{sat}$



As  $V_o = -V_{sat}$  is given to 'c' & diode combination D-off. Now the 'c' discharges towards  $-V_{sat}$  through R with  $T = RC$ .

When  $V_c < -\beta V_{sat} \Rightarrow V_o = V_{sat}$


Now  $V_o = +V_{sat}$ ,  $V_x = \beta V_{sat}$ .

As  $V_o = V_{sat}$  is given to 'c' & diode combination D-on. Now 'c' starts charging towards  $V_{sat}$  through R with  $T = RC$ . When  $V_c = V_o \Rightarrow$  D-ON - The 'c' stops charging

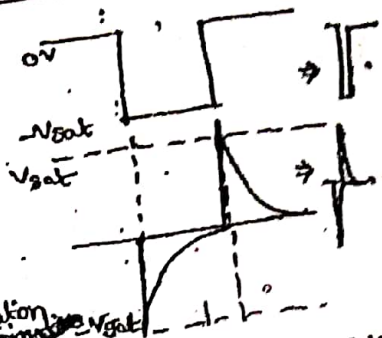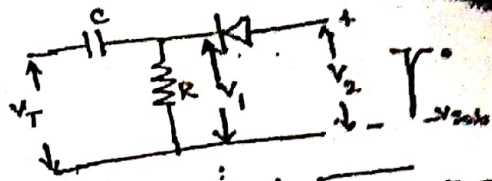$\left. \begin{matrix} V_c = V_o & V_o = V_{sat} \\ D-ON & V_x = \beta V_{sat} \end{matrix} \right\}$  stable states.



opwave form :-

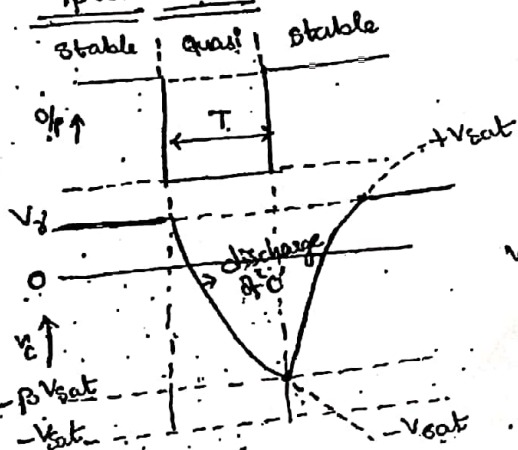

pulse width (T) :-

To calculate T, consider discharging of 'c'.  $V_c = V_f + (V_i - V_f) e^{-t/T}$

$V_i = V_j$ ,  $V_f = -V_{sat}$ ,  $T = RC$ , at  $t = T$ ,  $V_c = -\beta V_{sat}$

$$-\beta V_{sat} = -V_{sat} + (V_j + V_{sat}) e^{-T/RC}$$

$$V_{sat}(1-\beta) = (V_j + V_{sat}) e^{-T/RC}$$

$$e^{T/RC} = \frac{V_j + V_{sat}}{V_{sat}(1-\beta)}$$

$$T = RC \ln \left[ \frac{V_j + V_{sat}}{V_{sat}(1-\beta)} \right]$$

$$\beta = \frac{R_2}{R_1 + R_2} \Rightarrow 1 - \beta = \frac{R_1}{R_1 + R_2}$$

$$\frac{1}{(1-\beta)} = \frac{(R_1 + R_2)}{R_1}$$

$$= \left( 1 + \frac{R_2}{R_1} \right)$$


$$T = RC \ln \left[ \frac{V_j + V_{sat}}{V_{sat}} \left( 1 + \frac{R_2}{R_1} \right) \right]$$

If  $V_j \ll V_{sat}$  (or)  $V_j$  Neglected

$$T = RC \ln \left( 1 + \frac{R_2}{R_1} \right)$$

Prob 2

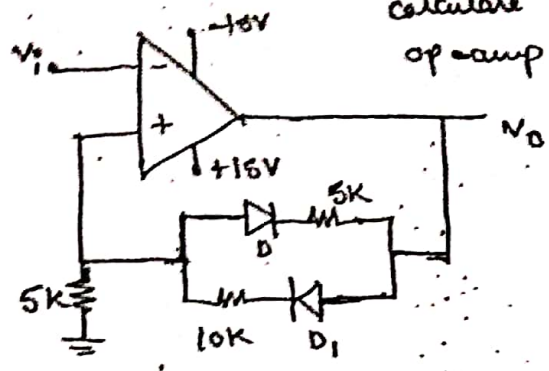calculate UTP & LTP value for the op-amp ckt shown



Sol:-

$$V_{LTP} = V_{ref} + (V_{sat} - V_{ref}) \left( \frac{R_2}{R_1 + R_2} \right)$$

$$= 0 - 15 \left( \frac{5}{15} \right)$$


$$V_{LTP} = -\frac{15}{2} V = -7.5V$$

$$V_{UTP} = +15 \left[ \frac{5}{15} \right] = +5V$$

when  $V_o = +15V$



$D_1$  - ON - S-C

$D_2$  - OFF - O-C

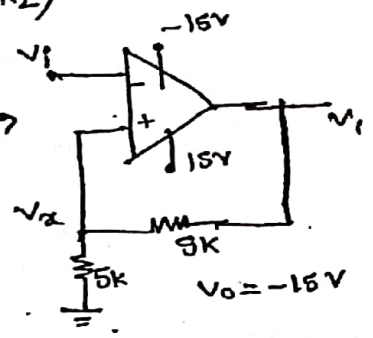

$D_1$  - OFF - O-C

$D_2$  - ON - S-C

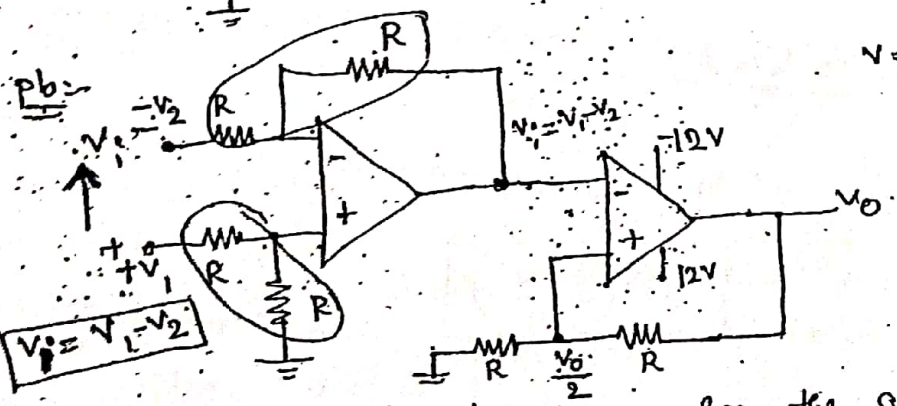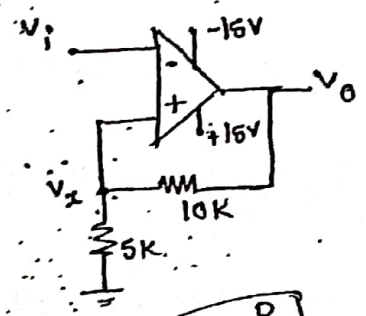



$$V_1 = V_2$$

Draw the Transfer char. curve for the op-amp ckt shown

$$V_{LTP} = V_{UTP} = +12 \left( \frac{1}{2} \frac{R_2}{R_1} \right)$$

$$= 6V$$

$$V_{LTP} = -6V$$

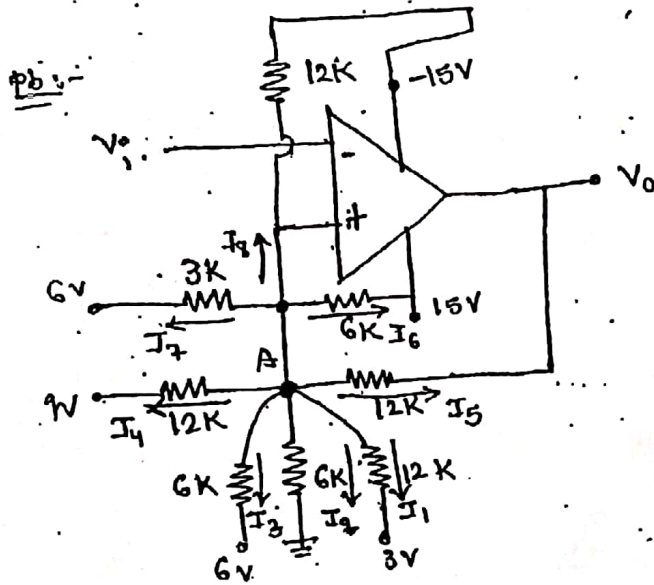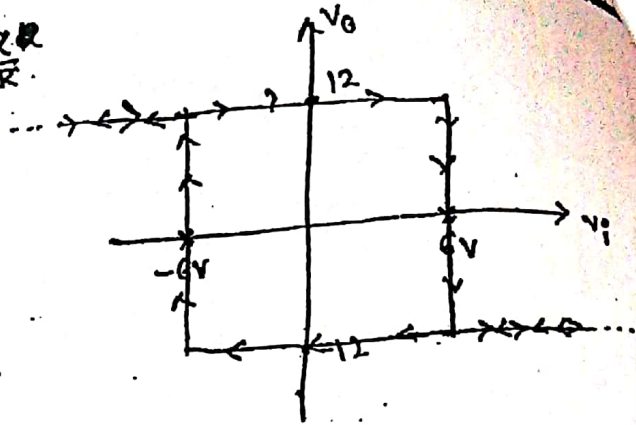

Calculate the UTP & LTP values.

Sol:- when ever the multiple voltages are there apply KCL at point A:

$$I_1 + I_2 + I_3 + I_4 + I_5 + I_6 + I_7 + I_8 = 0$$

$$\frac{V_A - 3}{12K} + \frac{V_A - 0}{6K} + \frac{V_A - 6}{6K} + \frac{V_A - 9}{12K} + \frac{V_A - V_O}{12K} + \frac{V_A - 15}{6K} + \frac{V_A - 6}{3K} + \frac{V_A + 15}{12K} = 0$$

$$-V_O + \cancel{V_A} + 2\cancel{V_A} + 2\cancel{V_A} + V_A - 9 + V_A + 2V_A - 30 + 4V_A - 24 + \cancel{V_A} = 0$$

$$14V_A - 63 - V_O = 0$$

$$V_A = \left( \frac{V_O + 63}{14} \right)$$

when  $V_O = 15V$

$$V_A = V_{UTP} = \frac{15 + 63}{14} = \frac{78}{14} = 5.571V$$

when  $V_O = -15V$

$$V_A = V_{LTP} = \frac{-15 + 63}{14} = \frac{48}{14} = 3.428V$$

\* Astable Multivibrator :-

(Square wave Generator)

\* The Astable Multivibrator has no stable states.


- Two states are QUASI

\* The op of AMV continuously changes b/w two states. As its op continuously changes b/w two states the op is a square wave.

→ AMV is also called free Running oscillator.

→ AMV is also called a Relaxation oscillator.

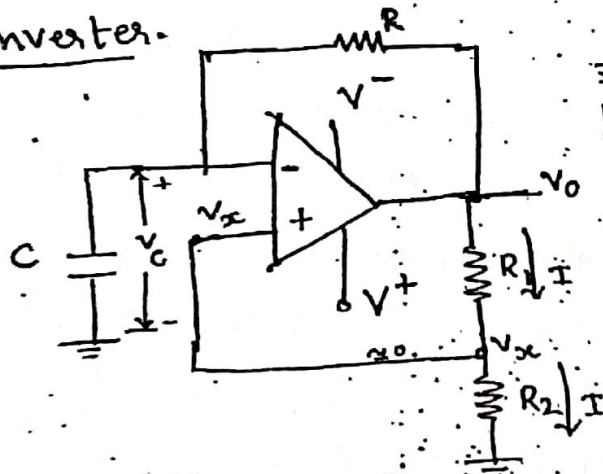→ AMV is also called voltage to frequency Converter.



~~It produces only~~  
[It generates the square wave.]

$$I = \frac{V_0}{R_1 + R_2}$$

$$V_x = I R_2 = V_0 \left[ \frac{R_2}{R_1 + R_2} \right]$$

$$V_x = \beta V_0, \beta < 1$$


Let the 'c' is initially uncharged.  $V_c = 0$

Once the supply given, the AMV is in one of its QUASI state.

Let  $V_0 = +V_{sat}$

$$V_x = \beta V_{sat}$$

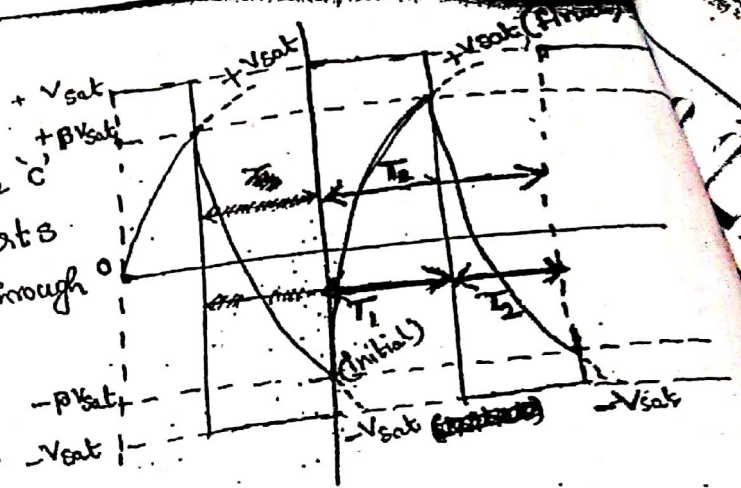As  $V_0 = +V_{sat}$  is given to the 'c' through R, Now the 'c' starts charging towards  $+V_{sat}$  through R with  $T = RC$ .



When  $V_c > \beta V_{sat} \Rightarrow V_0 = -V_{sat}$

Now  $V_0 = -V_{sat}$

$$V_x = -\beta V_{sat}$$

As  $V_0 = -V_{sat}$  is given to 'c' through R. Now the 'c' discharges towards  $-V_{sat}$  through R with  $T = RC$ .

When  $V_c < -\beta V_{sat} \Rightarrow V_0 = +V_{sat}$

Now  $V_0 = +V_{sat}$ ;  $V_c = \beta V_{sat}$

As  $V_0 = +V_{sat}$  is given to 'c' through R. The 'c' starts charging towards  $+V_{sat}$  through R with  $T = RC$ .

\* Like this the process is goes on. Due to continuous charging & discharging of 'c' b/w  $\beta V_{sat}$  &  $-\beta V_{sat}$  square wave oscillations generated at the o/p.

Calculation of freq of oscillations:-

$$f = \frac{1}{T} = \frac{1}{T_1 + T_2}$$

$$T = T_1 + T_2$$

T<sub>1</sub> :- To calculate  $T_1$  consider charging of 'c'.

$$V_c = V_f + (V_i - V_f) e^{-t/\tau}$$

$V_i$  = Initial value  
 $V_f$  = final value

$V_i = -\beta V_{sat}$ ,  $V_f = +V_{sat}$ ,  $T = RC$ , at  $t = T_1$ ,  $V_c = \beta V_{sat}$

$$\beta V_{sat} = V_{sat} + (-\beta V_{sat} - V_{sat}) e^{-T_1/RC}$$

$$-V_{sat}(1-\beta) = -V_{sat}(1+\beta) e^{-T_1/RC}$$

$$1-\beta = (1+\beta) e^{-T_1/RC}$$

$$e^{T_1/RC} = \left(\frac{1+\beta}{1-\beta}\right)$$

$$T_1 = RC \ln \left(\frac{1+\beta}{1-\beta}\right)$$

T<sub>2</sub>:- To calculate T<sub>2</sub>, consider discharging of C:

$$V_i = \beta V_{sat}, V_f = -V_{sat}, T = RC, \text{ at } t = T_2, V_C = \beta V_{sat}$$

$$-\beta V_{sat} = -V_{sat} + (\beta V_{sat} + V_{sat}) e^{-T_2/RC}$$

$$V_{sat}(1-\beta) = V_{sat}(1+\beta) e^{-T_2/RC}$$

$$(1-\beta) = (1+\beta) e^{-T_2/RC}$$

$$e^{T_2/RC} = \left(\frac{1+\beta}{1-\beta}\right)$$

$$T_2 = RC \ln \left(\frac{1+\beta}{1-\beta}\right)$$

As T<sub>1</sub> = T<sub>2</sub> ⇒ The o/p wave form is  $\left(\frac{1+\beta}{1-\beta}\right)$

where  $\beta = \frac{R_2}{R_1 + R_2}$

$$\left(\frac{1+\beta}{1-\beta}\right) = \frac{1 + \frac{R_2}{R_1 + R_2}}{1 - \frac{R_2}{R_1 + R_2}} = \frac{R_1 + 2R_2}{R_1 + R_2 - R_2} = \frac{R_1 + 2R_2}{R_1} = \left(1 + \frac{2R_2}{R_1}\right)$$

$$T = T_1 + T_2 = 2RC \ln \left(\frac{1+\beta}{1-\beta}\right)$$

$$T = 2RC \ln \left(1 + \frac{2R_2}{R_1}\right)$$


$$f = \frac{1}{T} = \frac{1}{2RC \ln \left(1 + \frac{2R_2}{R_1}\right)}$$

T<sub>2</sub>:-  $V_i = 5V, V_f = -15V, T = RC,$   
 at  $t = T_2, V_c = -7.5V$   
 $-7.5 = -15 + (5+15)e^{-T_2/RC}$   
 $7.5 = 20e^{-T_2/RC}$   
 $e^{T_2/RC} = \frac{20}{7.5}$   
 $T_2 = RC \ln(2.667)$   
 $T = T_1 + T_2$   
 $= RC [\ln(2.667) + \ln(2.25)]$   
 $= RC [\ln(2.667 \times 2.25)]$   
 $= 0.1m [\ln(2.667 \times 2.25)]$


$T = 0.179 \text{ msec}$   
 $F = \frac{1}{T} = 5.58 \text{ kHz}$

\*  $\Delta$  wave generator :-

By integrating the square wave we get  $\Delta$  wave

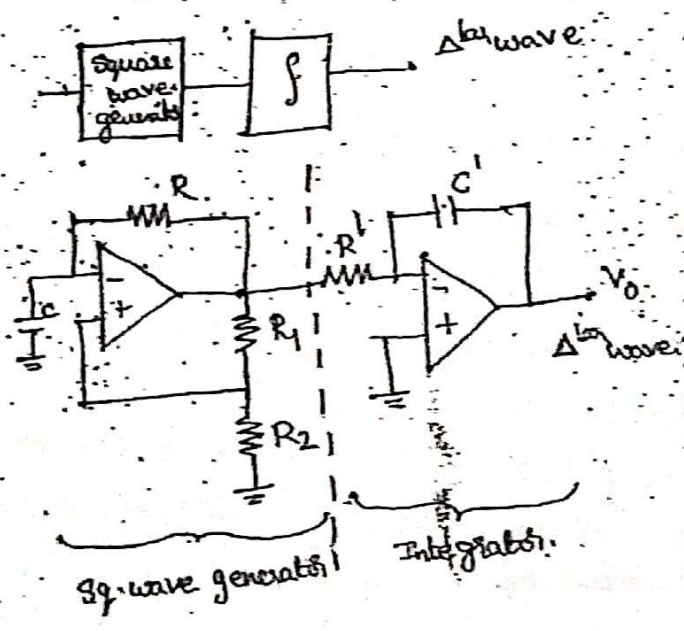

pb1:- Monostable problem

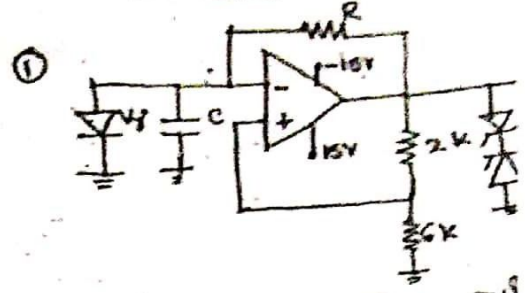

calculate for the ckt shown pul width generated by the ckt when a trigger pulse is app for (i)  $V_i = 0.7V$  (ii)  $V_i = 0V$ .

Sol:- Assume that  $T = 10 \text{ msec}$   
 $V_z = 6.3V$ .

when  $V_i = 0.7V$   
 $V_{sat} = (V_1 + V_2) = 7V$

$T = RC \ln \left[ \frac{7.7}{7} (1+3) \right]$   
 $= 10m \ln(4.4)$

$T = 14.81 \text{ msec}$

(ii) when  $V_i = 0$


$T = RC \ln \left( 1 + \frac{R_2}{R_1} \right)$   
 $= 10m \ln \left( 1 + \frac{6k}{2k} \right)$   
 $= 10m \ln(4)$   
 $= 13.86 \text{ msec}$


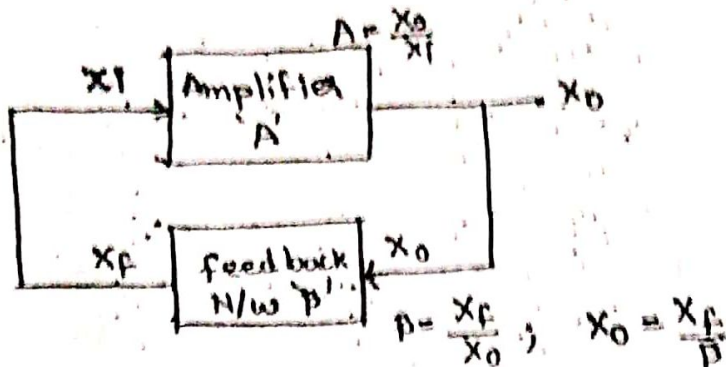
## Sinusoidal oscillators:-

A ckt which generates undamped sinusoidal oscillations is called sinusoidal or Harmonic oscillator.

\* (undamped means Amplitude constant "periodically")



In oscillator,  $X_f = X_i$

$$X_o = A X_i$$

$$\frac{X_f}{B} = A X_i \Rightarrow$$

$$X_f = A B X_i$$

$$\therefore AB = 1$$

$AB \rightarrow$  loop gain

$$AB = 1 = 1 + j0 = 1 \angle 0^\circ$$

- (i) The magnitude of loop gain = 1.  
 (ii) The total phase of the loop is  $0^\circ$  or  $360^\circ$
- } "BARKHAUSEN" CRITERIA / conditions.

To get undamped oscillations the ckt must satisfy the above conditions.

$\rightarrow$  If the amplifier introduces  $180^\circ$  of phase [Inverting amplifier CE amplifier] the remaining  $180^\circ$  must be introduced by the feedback.

$\rightarrow$  If the amplifier introduces  $0^\circ$  of phase [Non-inverting Amplifier, CE-CE cascaded Amplifier] the feedback N/w must introduce  $0^\circ$  of phase.

→ The feed back N/w consists R, L, C → in oscillators  
The transfer function of the feedback N/w.

$$\Rightarrow \frac{X_f(s)}{X_o(s)} = \beta = \beta_{real} \pm j \beta_{imaginary}$$

The gain of the amplifier 'A' → is always real value

The magnitude of the loop gain,  $\boxed{A\beta = 1}$

$$\beta = \frac{1}{A} \rightarrow \text{must be real}$$

→ To get undamped oscillation, the imaginary part of 'β' must be zero.

$$\Rightarrow \boxed{\beta_{imaginary} = 0}$$

from this we get the freq of oscillation generated by the ckt.

→ The feed back factor  $\boxed{\beta = \beta_{real}}$


The gain of the amplifier  $A = \frac{1}{\beta}$

$$\Rightarrow \boxed{A = \frac{1}{\beta_{real}}}$$


→ Depending on the components used in the feed back N/w, the oscillators are classified into:

- 1. RC oscillators
    - RC phase shift oscillator
    - Wein Bridge oscillator
  - 2. LC oscillators
    - Hartley oscillator
    - Colpitt's oscillator
- } Audio frequency oscillators.
- } Radio freq oscillators.

RC phase shift oscillator:

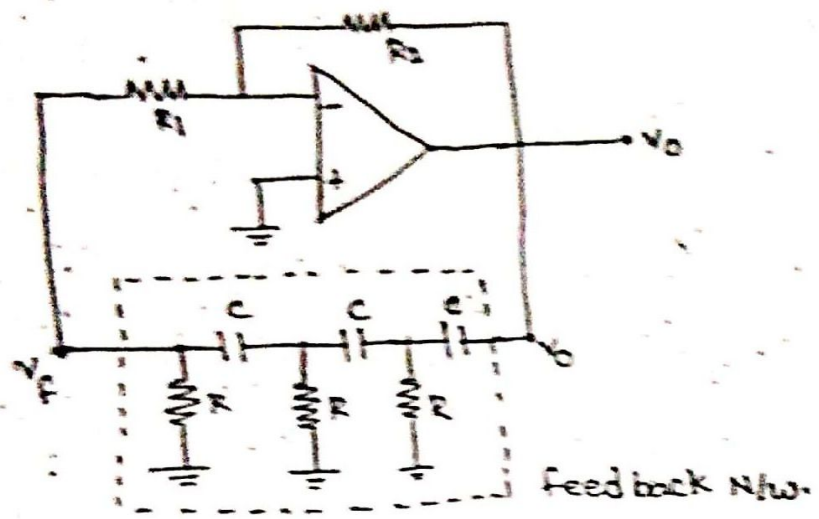

Find the transfer function:-

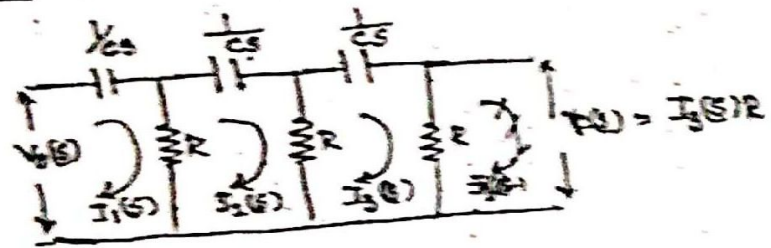

$$V_o(s) = I_1(s) \left[ R + \frac{1}{sC} \right] - I_2(s)R \rightarrow ①$$

$$0 = -I_1(s)R + I_2(s) \left[ 2R + \frac{1}{sC} \right] - I_3(s)R \rightarrow ②$$

$$0 = -I_2(s)R + I_3(s) \left[ 2R + \frac{1}{sC} \right] \rightarrow ③$$

$$\begin{bmatrix} R + \frac{1}{sC} & -R & 0 \\ -R & 2R + \frac{1}{sC} & -R \\ 0 & -R & 2R + \frac{1}{sC} \end{bmatrix} \begin{bmatrix} I_1(s) \\ I_2(s) \\ I_3(s) \end{bmatrix} = \begin{bmatrix} V_o(s) \\ 0 \\ 0 \end{bmatrix}$$

$$\Delta = R + \frac{1}{sC} \left[ (2R + \frac{1}{sC})^2 - R^2 \right] + R \left[ -R \left[ 2R + \frac{1}{sC} \right] \right]$$

$$= \left( R + \frac{1}{sC} \right) \left[ 3R^2 + \frac{1}{s^2 C^2} + \frac{4R}{sC} \right] - R^2 \left( 2R + \frac{1}{sC} \right)$$

$$= 3R^3 + \frac{R}{s^2 C^2} + \frac{4R^2}{sC} + \frac{3R^2}{sC} + \frac{1}{s^3 C^3} + \frac{4R}{s^2 C^2} - 2R^3 - \frac{R^2}{sC}$$

$$\Delta = R^3 + \frac{6R^2}{sC} + \frac{5R}{s^2C^2} + \frac{1}{s^3C^3}$$

$$\Delta_3 = \begin{bmatrix} R + \frac{1}{sC} & -R & v_0(s) \\ -R & 2R + \frac{1}{sC} & 0 \\ 0 & -R & 0 \end{bmatrix} = v_0(s) [R^2 - 0] = v_0(s) R^2$$

$$I_3(s) = \frac{\Delta_3}{\Delta} = \frac{v_0(s) R^2}{R^3 + \frac{6R^2}{sC} + \frac{5R}{s^2C^2} + \frac{1}{s^3C^3}}$$

$$V_f(s) = I_3(s) R = \frac{v_0(s) R^3}{R^3 + \frac{6R^2}{sC} + \frac{5R}{s^2C^2} + \frac{1}{s^3C^3}}$$

$$V_f(s) = \frac{v_0(s)}{1 + \frac{6R^2}{sCR^3} + \frac{5R}{s^2C^2R^3} + \frac{1}{s^3C^3R^3}}$$

$$V_f(s) = \frac{v_0(s)}{1 + \frac{6}{sCR} + \frac{5}{s^2C^2R^2} + \frac{1}{s^3C^3R^3}}$$

$$T.F. = \frac{V_f(s)}{v_0(s)} = \frac{1}{1 + \frac{6}{sCR} + \frac{5}{s^2C^2R^2} + \frac{1}{s^3C^3R^3}}$$

put  $s = j\omega$

$$T.F. = \beta = \frac{1}{1 - j \frac{6}{\omega CR} + (-1) \frac{5}{\omega^2 C^2 R^2} + j \frac{1}{\omega^3 C^3 R^3}}$$

$$= \frac{1}{\left(1 - \frac{5}{\omega^2 C^2 R^2}\right) + j \left(\frac{1}{\omega^3 C^3 R^3} - \frac{6}{\omega CR}\right)}$$

To get undamped oscillations, the imaginary part of  $\beta$  must be zero.

$$\frac{1}{\omega^3 C^3 R^3} = \frac{6}{\omega CR}$$

$$\omega^2 C^2 R^2 = \frac{1}{6} \Rightarrow \omega^2 = \frac{1}{R^2 C^2 (6)} \Rightarrow \omega = \frac{1}{RC\sqrt{6}}$$

$$2\pi f = \frac{1}{RC\sqrt{6}}$$

$$f = \frac{1}{2\pi RC\sqrt{6}}$$

The feedback factor is

$$\beta = \frac{1}{1 - \frac{5}{\omega^2 C^2 R^2}} = \frac{1}{1 - 5(6)}$$

$$\beta = \frac{-1}{29}$$

180° of phase b/w  $V_o$  &  $V_f$ .

The gain of the amplifier  $A = \frac{1}{\beta} = -29$ .


$$A = -29$$

$$A = \frac{+R_2}{R_1} = +29$$

$$R_2 = 29R_1$$


∴ Each RC N/w introduces 60° of phase in the above ckt.

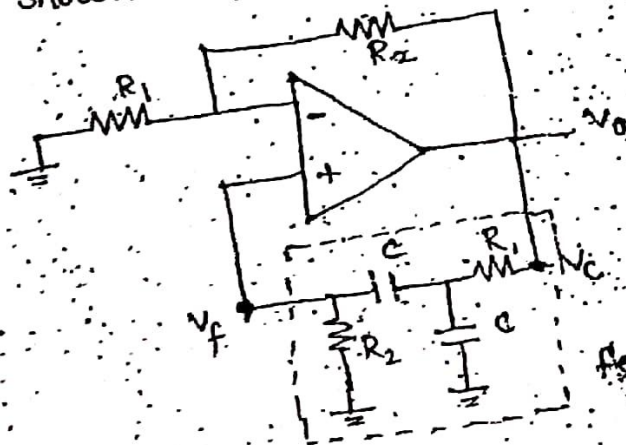1. calculate the freq of oscillations generated by the op-amp ckt shown & also calculate the relationship b/w  $R_1$  &  $R_2$ .



Feedback N/w.

Sol:-

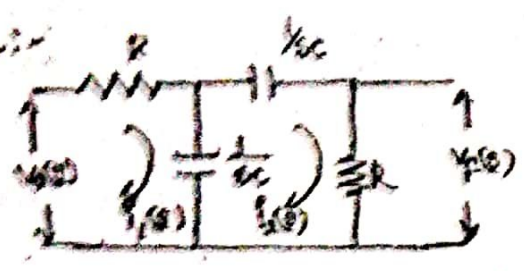

$$V_o(s) = I_1(s) \left[ R + \frac{1}{sC} \right] - I_2(s) \frac{1}{sC} \quad \rightarrow \textcircled{1}$$

$$0 = I_2(s) \left[ \frac{2}{sC} + R \right] - I_1(s) \frac{1}{sC} \quad \rightarrow \textcircled{2}$$

from eq ②

$$\frac{I_1(s)}{sC} = I_2(s) \left[ R + \frac{2}{sC} \right]$$

Substitute  $I_1(s)$  in eq ①

$$I_1(s) = I_2(s) [sCR + 2]$$

$$\begin{aligned} V_o(s) &= I_2(s) [sCR + 2] \left[ R + \frac{1}{sC} \right] - I_2(s) \frac{1}{sC} \\ &= I_2(s) \left[ sCR^2 + R + 2R + \frac{2}{sC} - \frac{1}{sC} \right] \\ &= I_2(s) \left[ sCR^2 + 3R + \frac{1}{sC} \right] \end{aligned}$$

$$V_o(s) = \frac{I_2(s)}{sC} [s^2 C^2 R^2 + 3sCR + 1]$$

But  $V_f(s) = I_2(s) R$

$$I_2(s) = \frac{V_f(s)}{R}$$

$$V_o(s) = \frac{V_f(s)}{sCR} [1 + 3sCR + s^2 C^2 R^2]$$

$$\frac{V_f(s)}{V_o(s)} = \frac{1}{\left[ \frac{3sCR}{1 + 3sCR + s^2 C^2 R^2} \right]}$$

$$T.F = \left[ \frac{1}{3 + sCR + \frac{1}{sCR}} \right]$$

Put  $s = j\omega$

$$\beta = \frac{1}{3 + j\omega CR - j \frac{1}{\omega CR}}$$

$$= \frac{1}{3 + j \left[ \omega CR - \frac{1}{\omega CR} \right]}$$

To get undamped oscillator the imaginary part of  $\beta$  must be zero.

$$\omega CR = \frac{1}{\omega CR}$$

$$\omega = \frac{1}{RC}$$

$$f = \frac{1}{2\pi RC}$$

feedback factor  $\beta = \frac{1}{3}$

Gain of the Amp  $A = \frac{1}{\beta}$


$$A = 3$$

$$A = 1 + \frac{R_2}{R_1} = 3$$

$$\frac{R_2}{R_1} = 2$$

$$\therefore R_2 = 2R_1$$

⇒

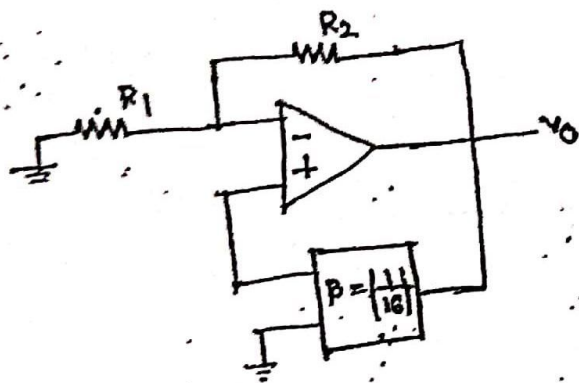

- (a)  $R_2 = 16 R_1$
- (b)  $R_1 = 16 R_2$
- ~~(c)  $R_2 = 16 R_1$~~
- (d)  $R_1 = 16 R_2$

$f = 2 \text{ kHz}$


$A\beta = 1$

$\therefore A = \frac{1}{\beta} = \frac{1}{\frac{1}{16}} = 16$

$A = 1 + \frac{R_2}{R_1} = 16$


$\Rightarrow \frac{R_2}{R_1} = 15 \Rightarrow \boxed{R_2 = 15 R_1}$

2. Wein Bridge oscillator:-

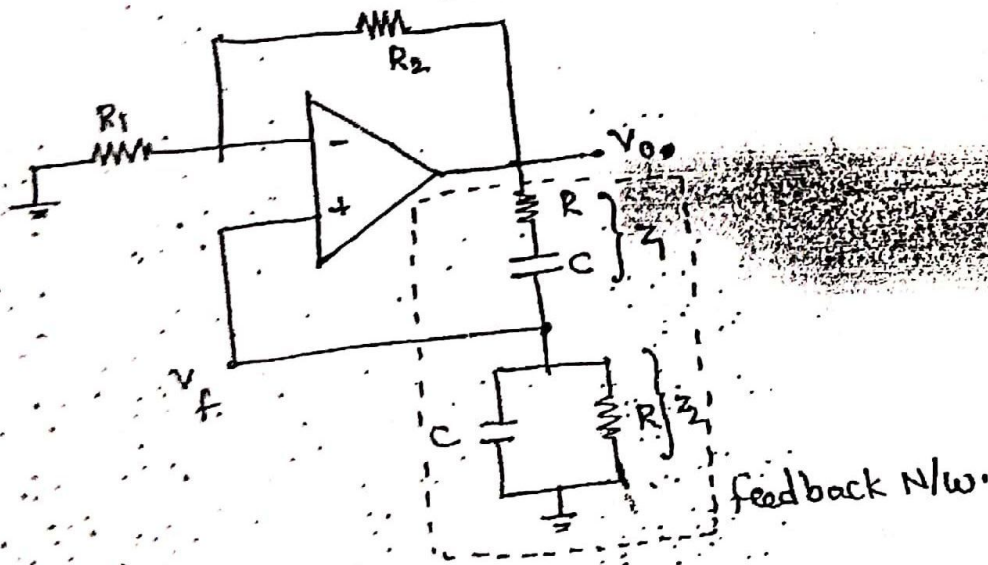

$Z_1 = R + \frac{1}{Cs} = \frac{(1 + sCR)}{sC}$

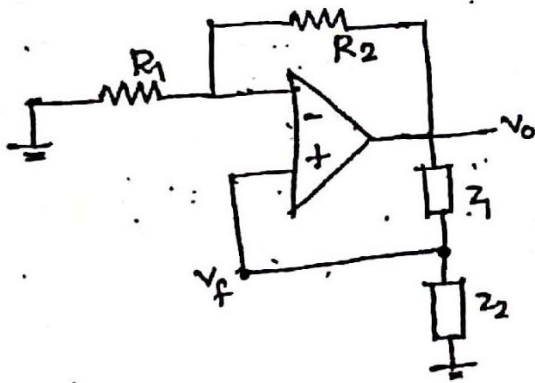$Z_2 = \frac{R \cdot \frac{1}{Cs}}{R + \frac{1}{Cs}} = \frac{RCs}{sCR + 1}$



$$V_f(s) = V_o(s) \left[ \frac{Z_2}{Z_1 + Z_2} \right]$$

$$\frac{V_f(s)}{V_o(s)} = T.F = \beta = \left( \frac{Z_2}{Z_1 + Z_2} \right)$$

$$\beta = \frac{R}{1 + sCR} + \frac{R}{1 + sCR}$$

$$\beta = \frac{\frac{R}{1 + sCR}}{\frac{(1 + sCR)^2 + sCR}{1 + sCR (sC)}} = \frac{sCR}{(1 + sCR)^2 + sCR}$$

$$= \frac{sCR}{1 + s^2 C^2 R^2 + 2sCR + sCR}$$

$$= \frac{sCR}{1 + s^2 C^2 R^2 + 3sCR}$$

$$\beta = \frac{1}{\frac{1}{sCR} + sCR + 3}$$

\* put \$s = j\omega\$

$$T.F = \beta = \frac{1}{-j \frac{1}{\omega CR} + j\omega CR + 3} = \frac{1}{3 + j \left[ \omega CR - \frac{1}{\omega CR} \right]}$$

To get undamped oscillations, the imaginary part \$\beta^2\$ must be zero.

$$\omega CR = \frac{1}{\omega CR}$$

$$\omega = \frac{1}{RC}$$

$$f = \frac{1}{2\pi RC}$$

feedback factor, \$\beta = \frac{1}{3}\$

Gain of the Amp \$A = \frac{1}{\beta}\$


$$A = 3$$

$$A = 1 + \frac{R_2}{R_1} = 3$$

$$\frac{R_2}{R_1} = 2 \Rightarrow R_2 = 2R_1$$



pts- The ckt shown

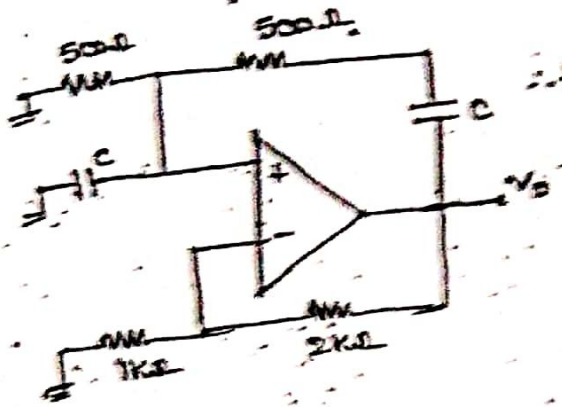


$\therefore f = 3183 \text{ Hz}$   
 $f = \frac{1}{2\pi RC} \Rightarrow C = \frac{1}{2\pi f R}$   
 $= \frac{1}{2\pi \times 3183 \times 500} = \frac{1}{10^7} \text{ F}$

LC Oscillators:-

In LC oscillators, the feedback n/w consists Inductors & Capacitors only.

General Form:-

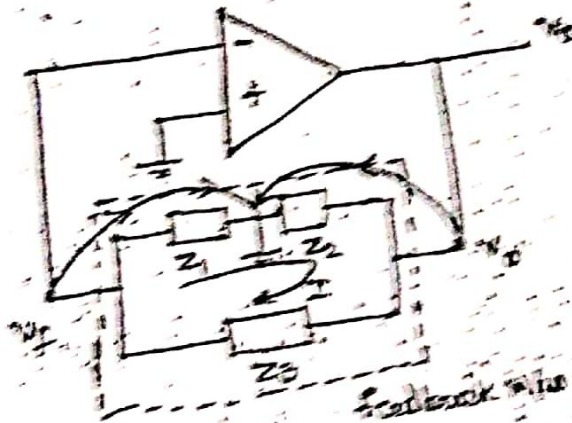

$Z_1, Z_2 \rightarrow$  same type elements (ie L or C)  
 $Z_3 \rightarrow$  opposite type element (ie C or L)

$V_i = I Z_1$

$V_o = -I Z_2$

The feed back factor,  $\beta = \frac{V_i}{V_o} = \frac{I Z_1}{-I Z_2} \Rightarrow \beta = \frac{-Z_1}{Z_2}$

The gain of the amp,  $A = \frac{1}{\beta} = \frac{-Z_2}{Z_1} \Rightarrow A = \frac{-Z_2}{Z_1}$

for freq. of oscillations, Apply KVL to feedback n/w

$$0 - I(z_1 + z_2 + z_3) = 0$$

$$I(z_1 + z_2 + z_3) = 0$$

To satisfy this condition,

$$(z_1 + z_2 + z_3) = 0$$


from this we get the freq of oscillations generated from the ckt.

1. Hartley oscillator:-

$z_1$  &  $z_2$  → Inductors

$z_3$  → capacitor
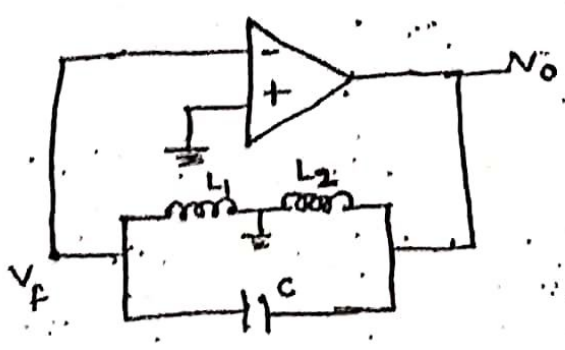
$$z_1 = j\omega L_1, z_2 = j\omega L_2, z_3 = \frac{1}{j\omega C} = \frac{-j}{\omega C}$$



→ The feed back factor,

$$\beta = \frac{-z_1}{z_2} = \frac{-j\omega L_1}{j\omega L_2}$$

$$\beta = \frac{-L_1}{L_2}$$

$$L_2 > L_1$$

$$\therefore \beta < 1$$

→ The gain of the Amp.  $A = \frac{1}{\beta} = \frac{-z_2}{z_1}$

$$A = \frac{-L_2}{L_1}$$

→ For freq of oscillations

$$z_1 + z_2 + z_3 = 0$$

$$j\omega L_1 + j\omega L_2 - \frac{j}{\omega C} = 0$$

$$j\omega [L_1 + L_2] = \frac{j}{\omega C}$$


$$\omega^2 = \frac{1}{(L_1 + L_2)C} \Rightarrow \omega = \frac{1}{\sqrt{4C(L_1 + L_2)}}$$

## 2. Colpitts oscillator :-

$Z_1$  &  $Z_2 \rightarrow$  capacitors

$Z_3 \rightarrow$  Inductor
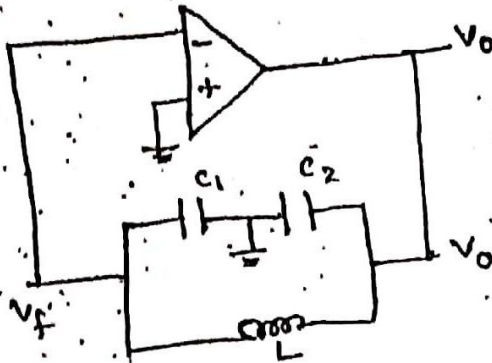
$$Z_1 = \frac{1}{j\omega C_1}, \quad Z_2 = \frac{1}{j\omega C_2} \quad \& \quad Z_3 = j\omega L$$



$\rightarrow$  The feed back factor,  $\beta = \frac{-Z_1}{Z_2}$

$$\beta = \frac{-\frac{1}{j\omega C_1}}{\frac{1}{j\omega C_2}} = -\frac{j\omega C_2}{j\omega C_1} = -\frac{C_2}{C_1}$$

$$\boxed{\beta = -\frac{C_2}{C_1}}$$

$$\boxed{C_1 > C_2}$$

$\rightarrow$  The gain of the Amp,  $A = \frac{1}{\beta}$

$$\boxed{A = -\frac{C_1}{C_2}}$$

$\rightarrow$  for freq. of oscillations,

$$Z_1 + Z_2 + Z_3 = 0$$

$$\frac{-j}{\omega C_1} - \frac{j}{\omega C_2} + j\omega L = 0$$

$$\frac{-j}{\omega} \left[ \frac{1}{C_1} + \frac{1}{C_2} \right] + j\omega L = 0$$


$$j\omega L = \frac{j}{\omega} \left[ \frac{1}{C_1} + \frac{1}{C_2} \right]$$

$$\omega^2 L = \left[ \frac{C_2 + C_1}{C_1 C_2} \right]$$

$$\omega^2 L = \frac{1}{\left[ \frac{C_1 C_2}{C_2 + C_1} \right]}$$

$$\omega = \frac{1}{\sqrt{L \left( \frac{C_1 C_2}{C_1 + C_2} \right)}}$$

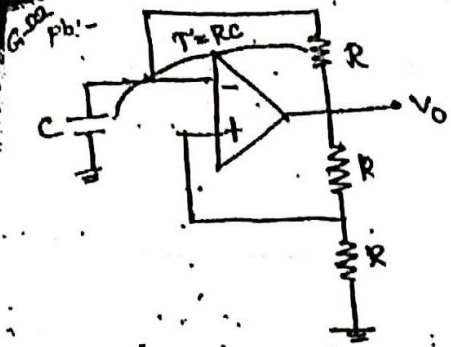
$$\boxed{f = \frac{1}{2\pi} \times \frac{1}{\sqrt{L \left( \frac{C_1 C_2}{C_1 + C_2} \right)}}$$




calculate the time period of oscillation generated by op-amp ckt?

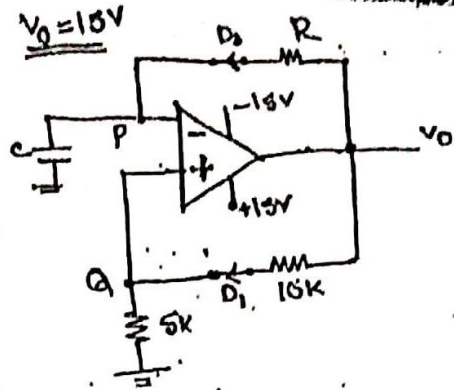- (a)  $T \ln 2$
- (b)  $2T \ln 2$
- (c)  $T \ln 3$
- (d)  $2T \ln 3$


Sol:  $T = 2RC \ln \left( 1 + \frac{2R_2}{R_1} \right)$   
 $= 2RC \ln \left( 1 + \frac{2R}{R} \right)$   
 $= 2T \ln (3)$



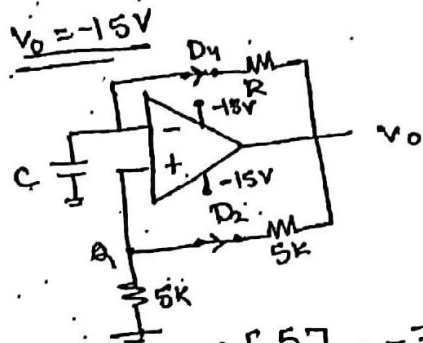
$V_Q = 15 \left[ \frac{5}{15} \right] = 5V$



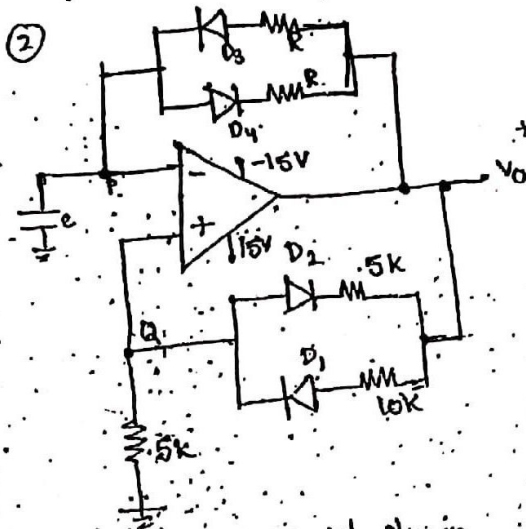$V_Q = -15 \left[ \frac{5}{10} \right] = -7.5V$



op wave form:-

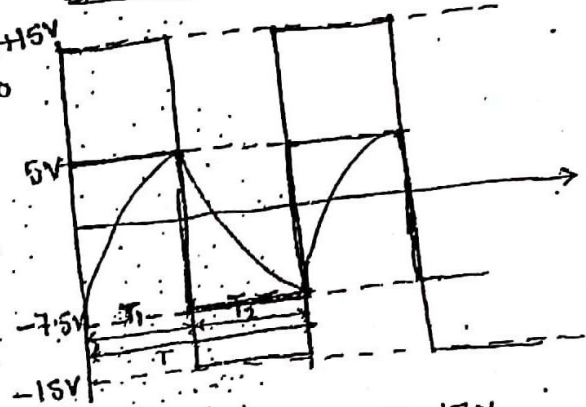

For the op-amp ckt shown draw the wave forms at p & q & o/p. calculate the freq of oscillations generated by this ckt. Assume that  $T = 0.1 \text{ msec}$

$T_1 = \tau = RC$  at  $t = T_1$ ,  $V_C = 5V$   
 $5 = 15 + (-7.5 - 15) e^{-T_1/RC}$   
 $-10 = -22.5 e^{-T_1/RC}$   
 $e^{T_1/RC} = \frac{22.5}{10} = 2.25$

$T_1 = RC \ln(2.25)$

$$A_{CL} = \frac{1 + \frac{R_2}{R_1}}{1 - \frac{j}{\omega RC}}$$

Replace  $1 + \frac{R_2}{R_1}$  with  $A_{max}$  and  $\frac{1}{RC}$  with  $\omega_c$ .


(12)

$$\Rightarrow A_{CL} = \frac{A_{max}}{1 - j \frac{f_c}{f}}$$


$$|A_{CL}| = \frac{|A_{max}|}{\sqrt{1 + \left(\frac{f_c}{f}\right)^2}} \quad \angle A_{CL} = \tan^{-1}\left(\frac{f_c}{f}\right)$$

$$* \quad f_c = \frac{1}{2\pi RC}$$

→ Second Order HPF :-

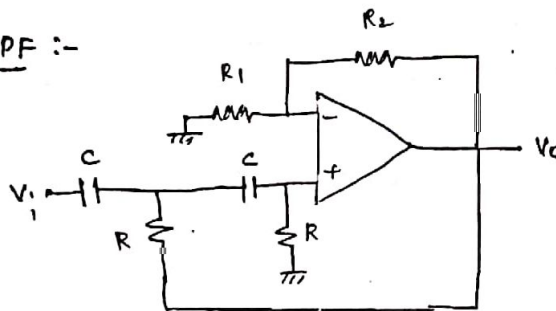

Q. Design 2<sup>nd</sup> order active HPF having cutoff frequency 5 kHz?

 **MAMATHA XEROX**  
D.No. 5-1-7 2 & 3, Beside SBH Gate,  
Opp. Tourist Palace, Bank Street,  
Koti, Hyderabad-55.


## 19. Differentiator :-

$$V_a = 0$$

$$\text{KCL at } a: I_1 + I_2 = 0$$

$$C \times \frac{d(V_i - 0)}{dt} + \frac{V_o - 0}{R_F} = 0$$
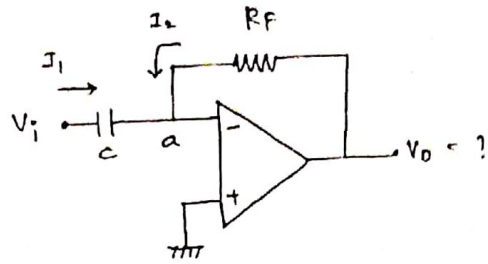
$$\Rightarrow V_o = -CR_F \frac{dV_i}{dt}$$



### Gain of Differentiator:-

$$A_{CL} = \frac{V_o}{V_i} = -\frac{Z_F}{Z}$$

$$Z_F = R_F, \quad Z = \frac{1}{sC}$$

$$A_{CL} = \frac{-R_F}{\frac{1}{sC}} = -sR_FC$$

Transfer function of Differentiator.

put  $s = j\omega$  we get

$$A_{CL} = -j\omega R_FC$$

$$A_{CL} = -j \frac{\omega}{\omega_a} \quad \text{where} \quad R_FC = \frac{1}{\omega_a}$$

$$\Rightarrow A_{CL} = -j \frac{f}{f_a}$$

$$|A_{CL}| = \frac{f}{f_a}, \quad \angle A_{CL} = -90^\circ \text{ or } 270^\circ$$

$$\text{At } f = f_a \Rightarrow |A_{CL}| = 1$$

$f_a$  is unity gain frequency of differentiator.

$$f_a = \frac{1}{2\pi R_FC}$$

If  $f \rightarrow \infty$  then  $|A_{CL}| \rightarrow \infty$

Due to infinite gain differentiator becomes unstable at very high frequencies.

If input  $V_i$  is not applied, differentiator may become high frequency noise and may provide non-zero output which is unwanted.

To overcome this drawback of instability or high frequency noise amplification, a resistor  $R$  can be connected in series with capacitor  $C$ . Such circuit is called practical differentiator.

$V_i$	$V_o$
Sine	Inverted Cosine.