

Monostable Multivibrator:-

①

The pulse width 'T' of Monostable Multivibrator is calculated as follows

The general solution for a single time constant low pass RC circuit with V_i & V_f as initial and final values

For low pass RC circuit we have

$$V_o = V_f + (V_i - V_f) e^{-t/RC} \quad \text{---} \textcircled{1}$$

For the circuit $V_f = -V_{sat}$ & $V_i = V_D$

The output ' V_c ' is (V_D = diode forward voltage)
Substitute V_f & V_i values in eq (1)

~~V_c~~

$$V_c = -V_{sat} + (V_D + V_{sat}) e^{-t/RC} \quad \text{---} \textcircled{2}$$

$$\text{at } t = T \quad V_c = -\beta V_{sat} \quad (2)$$

Substitute "t" & V_c values in eq (2)

$$-\beta V_{sat} = -V_{sat} + (V_D + V_{sat}) e^{-T/RC}$$

$$V_{sat} - \beta V_{sat} = (V_D + V_{sat}) e^{-T/RC} \quad (3)$$

$$(V_D + V_{sat}) e^{-T/RC} = V_{sat} (1 - \beta)$$

$$e^{-T/RC} = \frac{V_{sat} (1 - \beta)}{V_D + V_{sat}}$$

Take log on both sides

$$\frac{T}{RC} = \ln \frac{(V_D + V_{sat})}{V_{sat} (1 - \beta)}$$

$$T = RC \ln \frac{(V_D + V_{sat})}{V_{sat} (1 - \beta)}$$

$$T = RC \ln \frac{\cancel{V_{sat}} \left(1 + \frac{V_D}{V_{sat}}\right)}{\cancel{V_{sat}} (1 - \beta)}$$

(3)

$$T = RC \ln \frac{\left(1 + \frac{V_D}{V_{sat}}\right)}{(1-\beta)}$$

We have

$$\beta = \frac{R_2}{R_1 + R_2}$$

If $R_1 = R_2$ and $V_{sat} \gg V_{D1}$, the expression for T modifies as,

$$T = RC \log_e \left[\frac{\left(1 + \frac{V_D}{V_{sat}}\right)}{\left(1 - \frac{R_2}{2R_1}\right)} \right]$$

$$T = RC \log_e \left(\frac{1}{1 - 1/2} \right)$$

$$T = RC \log_e 2$$

$$= 0.6931 RC$$

pulse duration (or) gate width

$$T = 0.6931 RC$$

1) A μ V is a electronic chd - that generates mag. signal waves such as Δ wave, \square wave, saw-tooth waves etc.

2) A μ V is a switching chd which depends for operation on the f/h , basically two stage amp with o/p of one $1/2$ to the other.

* Diode D_1 is F.B and hence conducts if it is F.B. (C) gets charged but v_{tg} clamps to $(0.7V)$.

The potential divides R_1 & R_2 in association with Zener diodes,

it controls the v_{tg} at the +ve terminal of an op-amp and it is in stable state $\Rightarrow \beta V_o (= \beta V_{sat})$

$$\beta = R_2 / R_1 + R_2$$


* \rightarrow -ve triggering pulse of amp V_t is applied to the +ve terminal of an op-amp. Net v_{tg} is at this terminal $(\beta V_{sat} - V_t)$ which is less than $0.7V$.

* $v_{o/p}$ switches to $-V_{sat}$. D_1 becomes F.B.

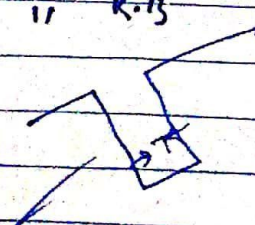(C) gets discharged through (R) exponentially to $-V_{sat}$, with a time constant $= RC$.

v_{tg} at +ve terminal $-\beta V_{sat}$. As soon as (C) $v_{tg} \rightarrow -ve$ this value becomes βV_{sat} . The $v_{o/p}$ switches back to the S.B. with $v_{o/p}$ level at $+V_{sat}$.

again D_1 is F.B \rightarrow it switches SS to q.s.s.
 D_1 " R.B " " " " " " " " " " " "



*) Monostable M.V has one stable state and one quasi-stable state.

*) This M.V is normally in the stable state, if an external triggering pulse is applied it switches from stable to the quasi-stable state.

It remains in the q.s.s for short while (os) period but automatically it reverts (i.e) switch back to its original state, without any external triggering pulse.

(Ckt)


*) The ckt uses - two diodes D_1 & D_2
 " " Zener Z_1 & Z_2
 capacitor C and several R in conjunction

*) $D_1 \rightarrow$ cut in vty ($0.7V$) (assume)
 D_1 connected across the (C)
 it clamps $V_C = 0.7V$, when the op vty is at +ve saturation level.


*) The triggering of the M.V by means of -ve pulse V_t applied to the +ve terminal of the op-amp through Diode D_2 .


*) If understood the operation of the M.V \rightarrow assumed to be stable state, so V_o is +ve saturation level (V_{sat})

Free

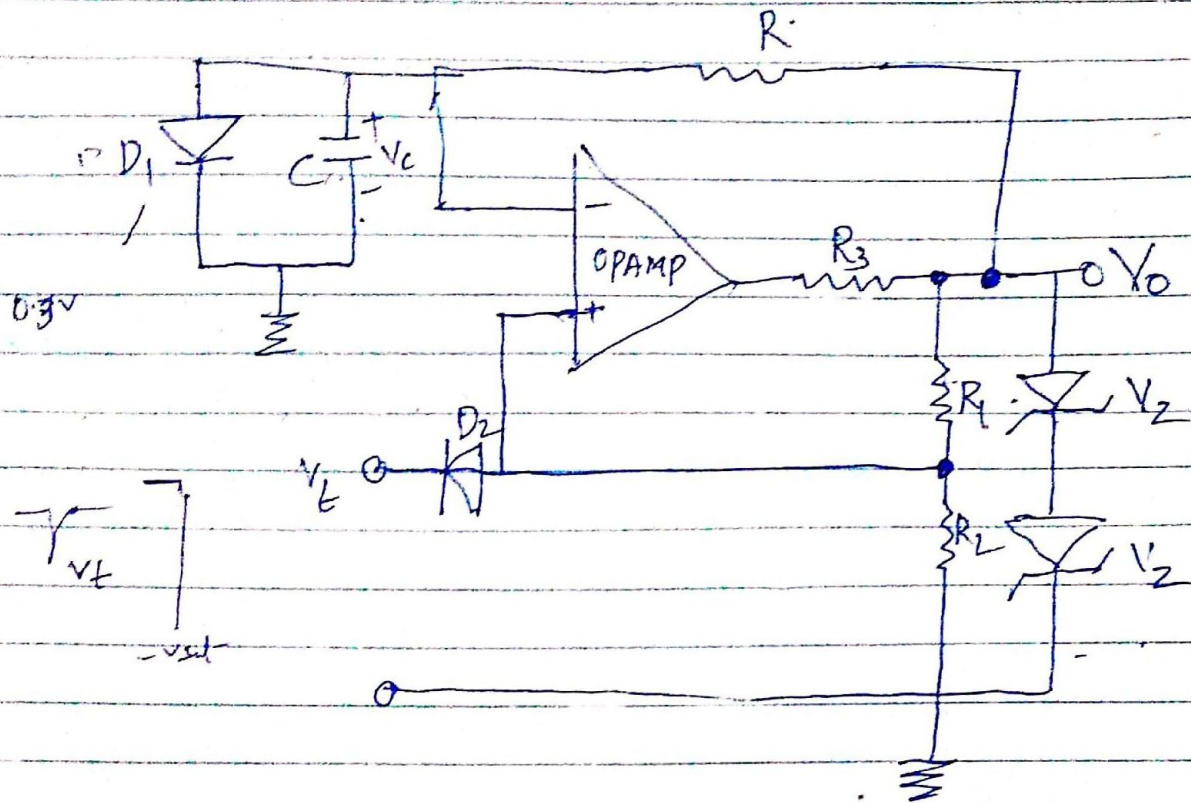

(part 1)

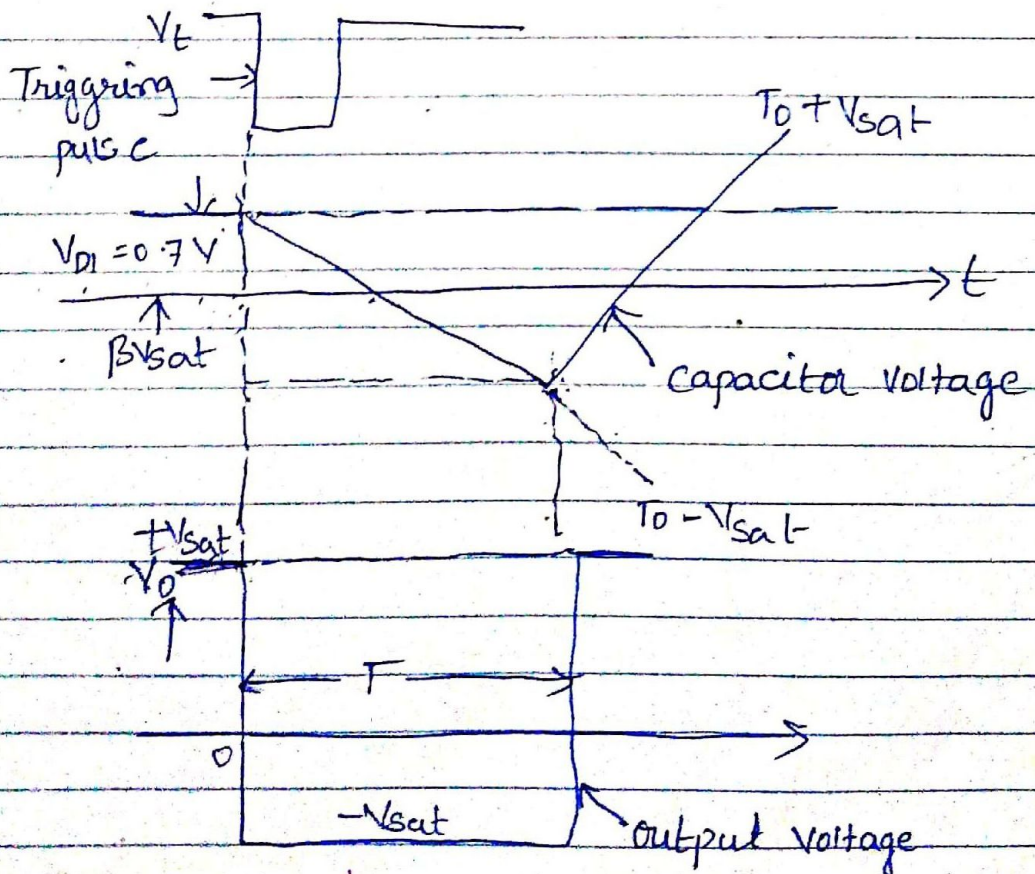

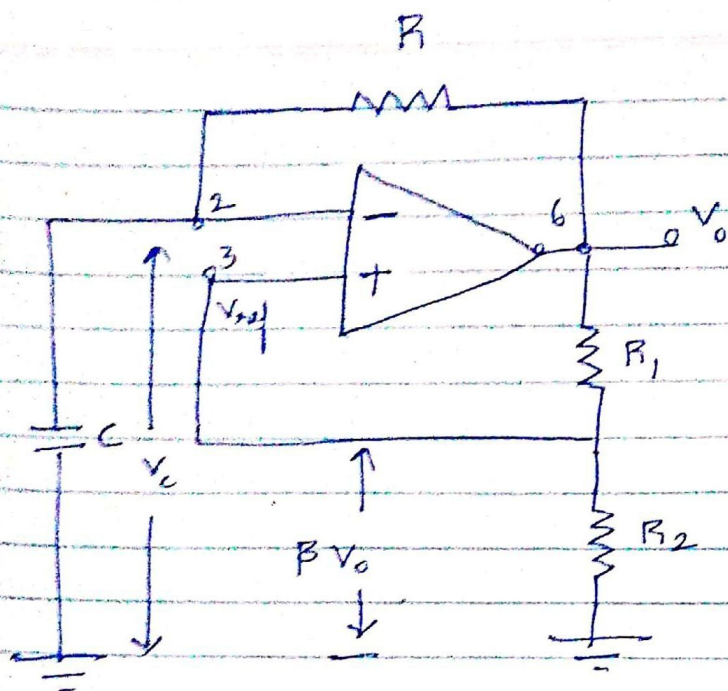

Square wave generator

Free running oscillator

(without any i/p getting the o/p)

Description:

1) Main principle is op-amp should operate in saturation region to get square wave form

2) Here R_1 & R_2 called as β fraction

$$\beta = \frac{R_2}{R_1 + R_2}$$

this β fraction is fed back +ve terminal of op-amp through resistor.

this $\beta V_0 \rightarrow$ reference V_{ref}
 either $+\beta V_{sat}$
 or $-\beta V_{sat}$

* And also same o/p (i.e) through R & C fed back to -ve terminal of an op-amp

o/p $+V_{sat}$ in time \rightarrow
 $-$ " " $-V_{sat}$

operation:

considers instant of time the o/p should be in $+V_{sat}$ when capacitor is charging.

* \rightarrow whenever i/p at the (-) i/p terminal just exceeds V_{ref}
 $\rightarrow V_{ref} (+)$ then ^{only} switching takes place

resulting square wave o/p

in \rightarrow stable both states are quasi stable state

* \rightarrow And v_o at the +ve terminal is

held at $+ \beta V_{sat}$ by R_1 & R_2 combination

~~at~~ C charges when $\rightarrow +V_{ref}$
~~above~~ $+V_{sat}$ above $+ \beta V_{sat}$

when C discharge $+V_{sat} \uparrow$ more $-V_{ref}$
 and it crosses $-V_{sat}$ in -ve terminal.

from again

(i) when C is charges \ominus $+V_{set} \uparrow$ more and more
 \uparrow vely and it crosses the $+ \beta V_{set}$.

$$+V_{set} > +\beta V_{set}.$$

(ii) when C is discharges \oplus $-V_{set} \downarrow$ more & more
 \downarrow vely and it crosses $-\beta V_{set}$.


$$-V_{set} > -\beta V_{set}.$$

from again \ominus is back to the \oplus
 saturation cycle is go on

C \rightarrow charging when it is +ve same vty. region

C \rightarrow dis " " " " -ve " " "

Rapidly changing the op state.

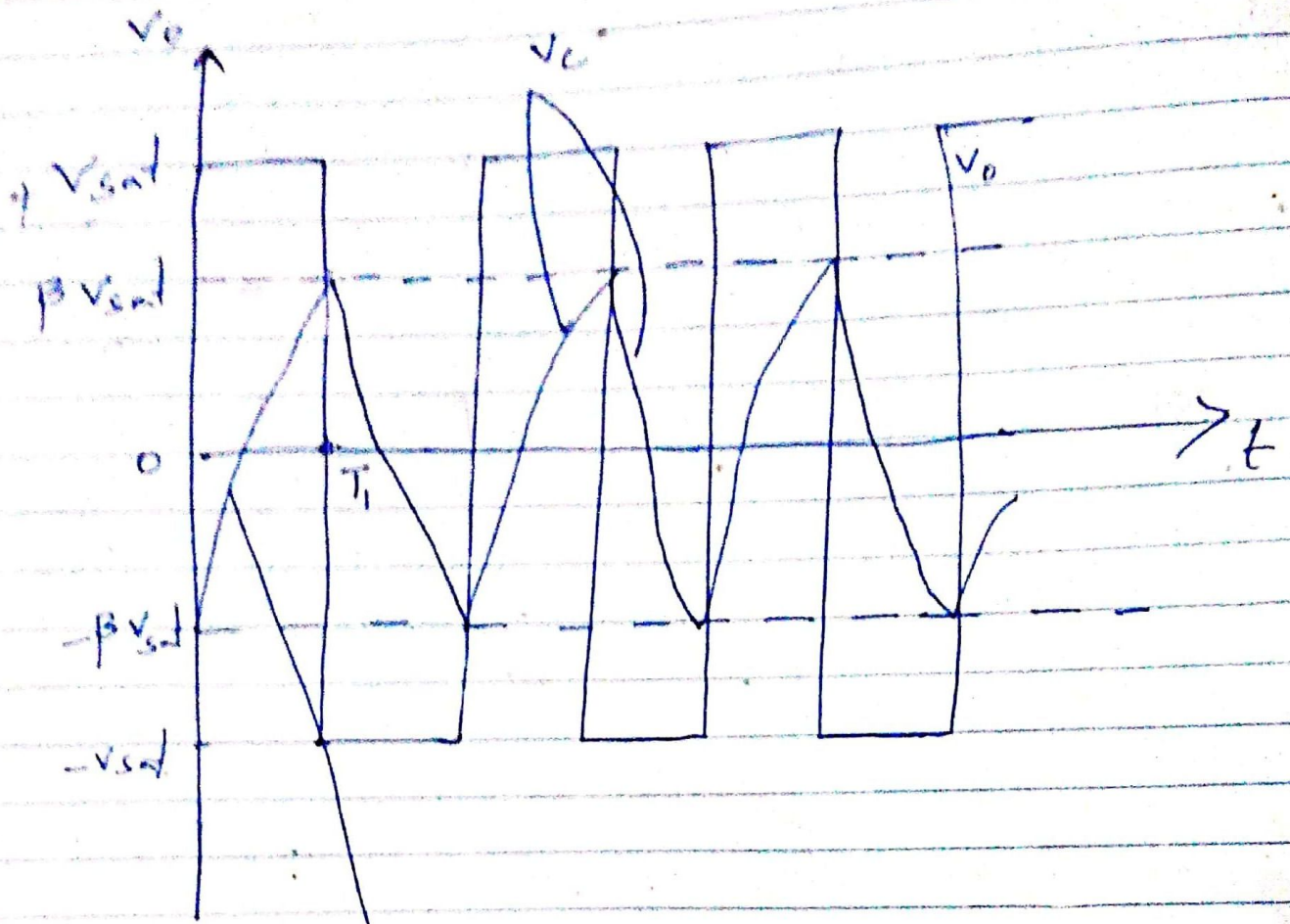

$$V_{sat} \left[1 - (1 + \beta) e^{-t/Rc} \right]$$

wave forms of astable M.V

Stable Multi Vibrator:-

The voltage across the capacitor as function of time is given by

$$V_c = V_f + (V_i - V_f) e^{-t/RC} \quad \text{--- (1)}$$

When final value $V_f = +V_{sat}$

and initial value $V_i = -\beta V_{sat}$

Substitute V_i & V_f values in eq (1) we get

$$V_c = V_{sat} + (-\beta V_{sat} - V_{sat}) e^{-t/RC}$$

Voltage across capacitor reaches βV_{sat} and switching takes place.

$$(\because V_c = \beta V_{sat}) \Rightarrow V_c = V_{sat} - V_{sat}(1+\beta) e^{-T_1/RC} \quad \text{--- (2)}$$

Substitute V_c value in eq (2) ($\because T_1 = t$)

$$\beta V_{sat} = V_{sat} - V_{sat}(1+\beta) e^{-T_1/RC}$$

$$V_{sat}(1+\beta)e^{-T/RC} = V_{sat} - \beta V_{sat}$$

(2)

$$V_{sat}(1+\beta)e^{-T/RC} = V_{sat}(1-\beta)$$

$$(1+\beta)e^{-T/RC} = (1-\beta)$$

$$e^{-T/RC} = \frac{(1-\beta)}{(1+\beta)}$$

Take log on both sides

$$\frac{T}{RC} = \ln\left(\frac{1+\beta}{1-\beta}\right)$$

$$T = RC \ln\left(\frac{1+\beta}{1-\beta}\right)$$

This is give only half of the period
Total time period

$$T = 2T_1 = 2RC \ln\left(\frac{1+\beta}{1-\beta}\right)$$

And output wave form is
symmetrical

(3)

If $R_1 = R_2$, then $\beta = 0.5$ and $T = 2RC$

173.

And for $R_1 = 1.414 R_2$, it can be

seen that $T = RC$

$$\text{or } f_0 = \frac{1}{2RC}$$

output swings from $+V_{sat}$ to $-V_{sat}$

$$V_{o \text{ peak-to-peak}} = 2V_{sat}$$

