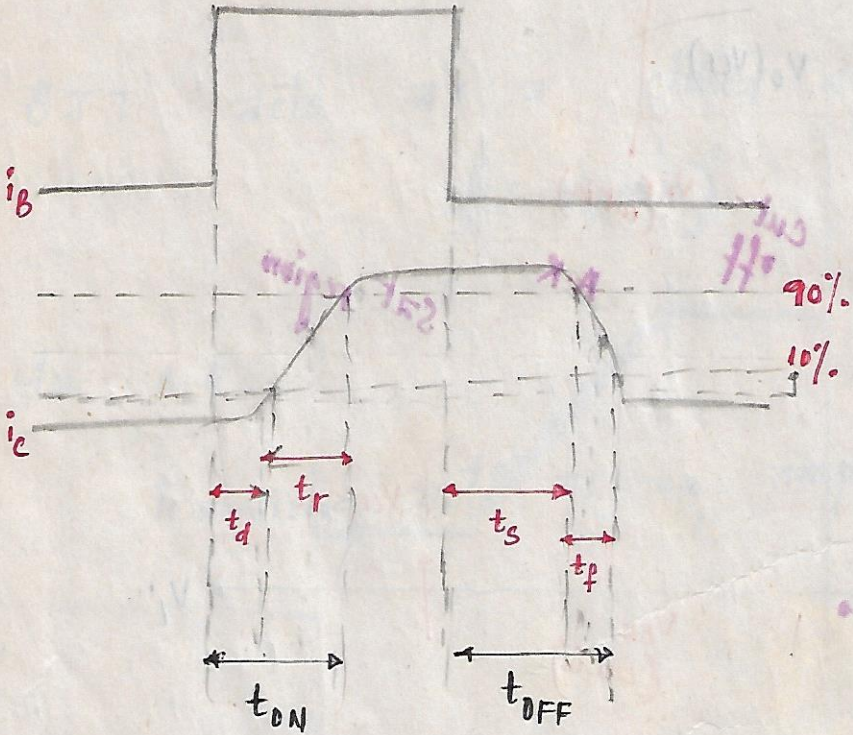


Transistor switching times:

Def:

- * Delay time: " t_d "
- * Rise time: " t_r "
- * Storage time: " t_s "
- * Fall time: " t_f "



Delay time (t_d):

The time interval between the application of (i_B) and the commencement of (i_C) is called as " t_d ".

Rise time (t_r):

The time req for the (i_C) to rise from 10% to 90% of the maximum value is called " t_r ".

Storage time (t_s):

The time interval between the instant ($i_B = 0$) and the instant when (i_C) has fallen to 90% of its max value is called " t_s ".

Fall time (t_f):

The time required for the (i.e) to fall from (90% to 10%) of the max value is called " t_f ".


$$* \underline{t_{ON} = t_d + t_r}$$

$$* \underline{t_{OFF} = t_s + t_f}$$

Storage time (t_s):

② * Linear wave shaping circuits : *

Int : * time constant of R.C ckt :

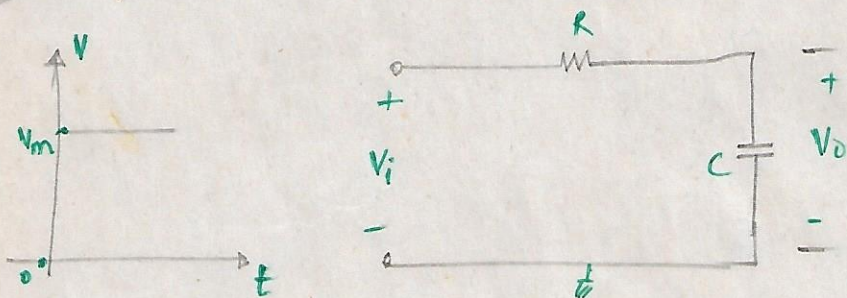

Let, ' V_i ' be the step input.

At $t=0$, i/p changes suddenly from 0 to V_m .

but, the cap opposes sudden change in voltages.

$$V_c(t) = V_{f_i} + (V_i - V_f) e^{-(t-t')/RC}$$

* at $t=0$ *

$$V_i = 0, \quad V_f = V_m, \quad t' = 0$$

$$V_c(t) = V_o = V_m + (0 - V_m) \cdot e^{-(t-0)/RC}$$

$$V_o = V_m - V_m \cdot e^{-t/RC}$$

$$V_o = V_m (1 - e^{-t/RC})$$

①

Sub $t = RC$ in eqⁿ ①

$$V_0 = V_m (1 - e^{-1})$$

$$\therefore V_0 = 0.632 V_m$$

Note :


At $t = RC$, the voltage across the cap becomes equal to 63.2% of the final steady value.

The product $R.C$ \longrightarrow time constant and is denoted by τ .


Def: Time constant ' τ ' for R.C circuit:

The ' τ ' of R.C ckt is the time req for the output voltage (i.e., the voltage across the cap) to attain 63.2% of the final steady value.

plot from eqⁿ ① ---

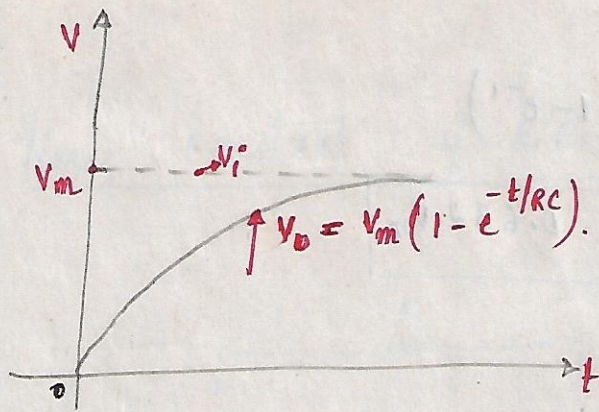

Low pass R.C circuit:

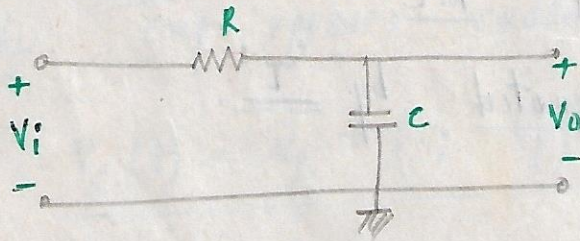

$$X_c = \frac{1}{j\omega C}$$

* For low freq --- ' X_c ' becomes high.
and hence, the total ' V_i ' will
appear across the cap (C).

$$\therefore V_0 \approx V_i$$

* For high freq --- ' X_c ' becomes low compared to ' R ' and hence, the total ' V_i ' will appear across ' R ' and no voltage appear across ' C '.

$$\boxed{V_o \approx 0}$$

* This circuit produces output same as input for low freq, but it produces '0' output for high freq and hence, it is called as L.P R.C circuit.

Cal of Gain:

By using voltage division rule,

$$V_o = \left[\frac{X_c}{X_c + R} \right] \cdot V_i$$

$$\frac{V_o}{V_i} = A = \left(\frac{X_c}{X_c + R} \right)$$

$$X_c = \frac{1}{j\omega C}$$

on sub --

$$A = \frac{1/j\omega C}{1/j\omega C + R}$$

$$A = \frac{1}{1 + j\omega RC}$$

$$A = \frac{1}{1 + j\omega/ \omega_H}$$

where, " ω_H " = $\frac{1}{RC}$.

$$A = \frac{1}{1 + \frac{f}{f_H}}$$

where, " f_H " = $\frac{1}{2\pi RC}$. (cut-off freq of LP RC ckt)

$$|A| = \frac{1}{\sqrt{1 + \left(\frac{f}{f_H}\right)^2}} \longrightarrow \text{mag of the gain}$$


$$\angle A = -\tan^{-1} \left[\frac{f}{f_H} \right] \longrightarrow \text{phase of the gain}$$

from the mag of gain ---

as $f \rightarrow 0$, $|A| = 1$

$f \rightarrow \infty$, $|A| = 0$

$f = f_H$, $|A| = \frac{1}{\sqrt{2}}$.

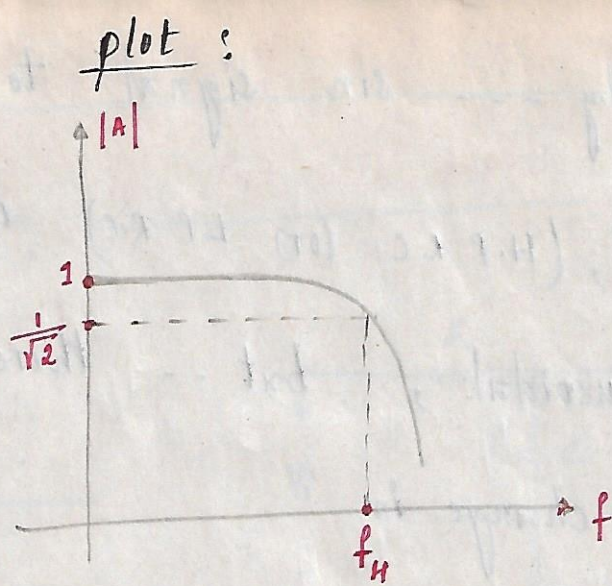

Cut-off freq " f_H " of L.P RC ckt :

If the freq at which the gain is $\frac{1}{\sqrt{2}}$ times of max gain. ... is called cut-off freq.


Response of L.P RC ckt *** Imp for external -
to the □^{re} wave input : external -
 100% sure

→ If we apply --- sin signal to L.W.S circuits, (H.P.R.C (or) L.P.R.C) output is also sinusoidal, but -- there may be a change in

* Amplitude


* phase displacement b/w (input and output)

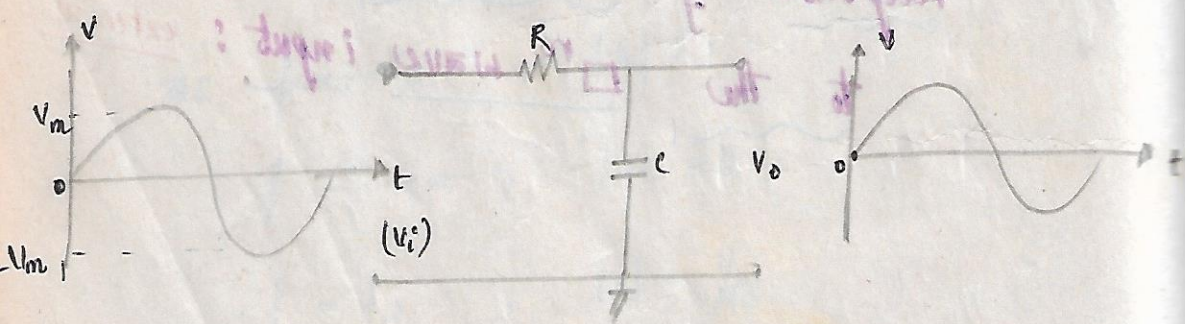→ If we apply non-sin signal -- we get the distorted output.



Response of L.P. R.C circuit

Int: to the step input:

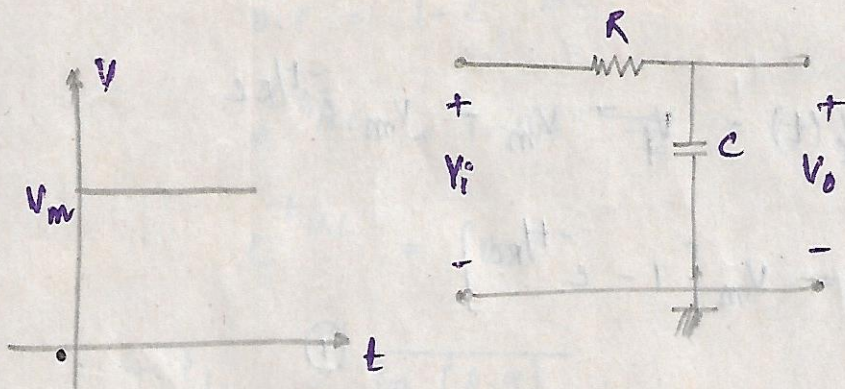

At, $(t=0)$... V_i changes suddenly from $(0 - V_m)$ but, cap opposes the sudden changes in v_t 's. $\therefore V_o$ increases gradually.

Cap vtg eqⁿ - - -

$$V_o(t) = V_c(t) = V_f + (V_i - V_f) e^{-\frac{(t-t')}{RC}} \quad (*)$$

At $t = 0$ - -

$$V_i = 0$$

$$V_f = V_m$$

$$t' = 0.$$

sub the values of V_i , V_f and t' -
we get ---

$$V_o(t) = V_c(t) = \frac{V_f}{1} - V_m e^{-t/RC}$$

$$V_o(t) = V_m [1 - e^{-t/RC}] \quad \text{--- (1)}$$

Rise time (t_r):

The time taken by the output to increase from 10% to 90% of the final value.

Let --

$$V_o = 0.1 V_m \text{ at } \dots t = t_1$$

$$V_o = 0.9 V_m \text{ at } \dots t = t_2$$

$$t_r = t_2 - t_1 \quad \text{--- (2)}$$

put -- $V_o = 0.1 V_m$ and $t = t_1$ in eqⁿ - (1)

we get...

$$0.1 V_m(t) = V_m \left[1 - e^{-t_1/RC} \right]$$

$$0.1 = 1 - e^{-t_1/RC}$$

$$e^{-t_1/RC} = 1 - 0.1$$

$$e^{-t_1/RC} = 0.9$$

$$\frac{-t_1}{RC} = \ln(0.9)$$

$$\frac{t_1}{RC} = 0.1$$

$$\therefore t_1 = 0.1 RC \quad (3)$$

put... $V_0 = 0.9 V_m$ and $t = t_2$ in eqⁿ (1)...

we get...

$$0.9 V_m = V_m \left[1 - e^{-t_2/RC} \right]$$

$$0.9 = 1 - e^{-t_2/RC}$$

$$e^{-t_2/RC} = 1 - 0.9$$

$$e^{-t_2/RC} = 0.1$$


$$\frac{-t_2}{RC} = \ln(0.1)$$

$$\frac{t_2}{R.C} = 2.30$$


$$\therefore t_2 = 2.2 R.C$$

$$\Rightarrow t_r = 2.2 R.C$$

response :

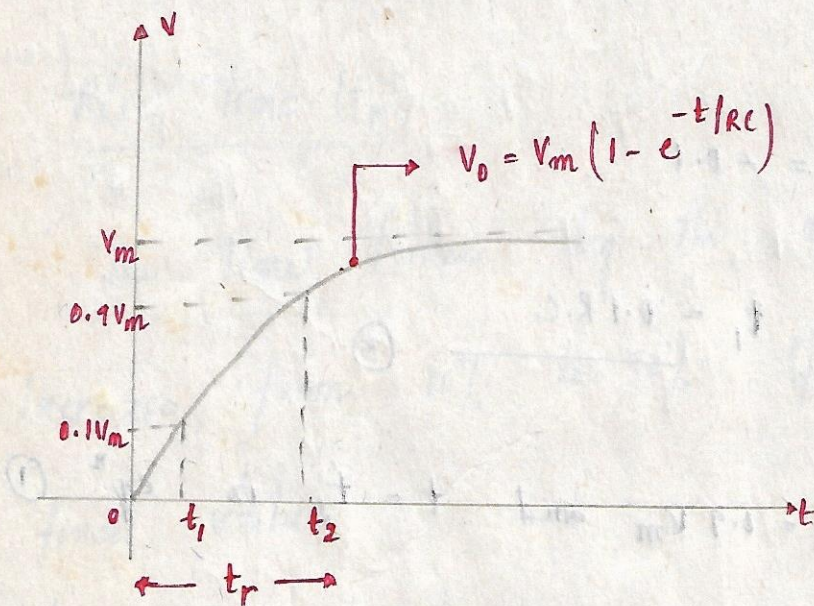

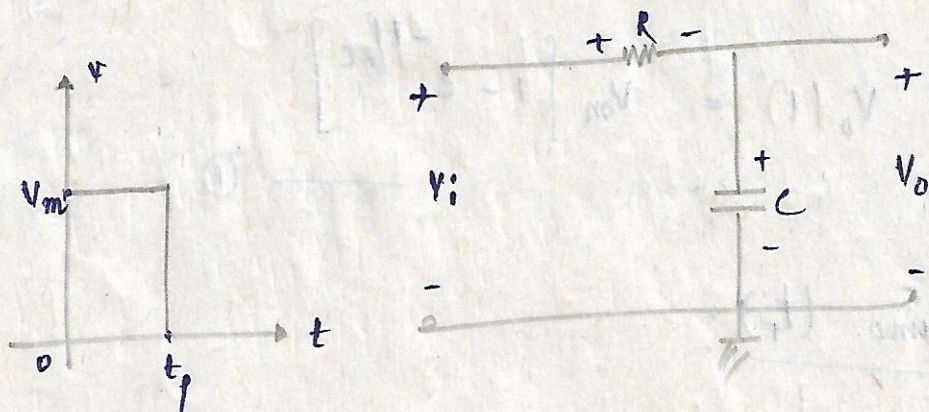Response of L.P R.C circuit to the pulse input:



At, $(t=0)$... V_i changes suddenly
from $(0 - V_m)$, but cap opposes sudden
change in v_t $\therefore V_o$ inc gradually

Cap v_t eqⁿ

$$V_o(t) = V_c(t) = V_f + (V_i - V_f) e^{-\frac{(t-t')}{RC}} \quad \text{--- } \textcircled{+}$$

At ... $t=0$...

$$V_i = 0$$

$$V_f = V_m$$

$$t' = 0$$

sub the values of V_i , V_f and t'
in eqn (1) -- we get --

$$V_o(t) = V_m - V_m \cdot e^{-t/RC}$$

$$V_o(t) = V_m \left[1 - e^{-t/RC} \right] \quad \text{--- (1)}$$

Rise time (t_r):

Let --

$$V_o = 0.1 V_m \quad \text{at } t = t_1$$

$$V_o = 0.9 V_m \quad \text{at } t = t_2$$

$$\therefore t_r = t_2 - t_1 \quad \text{--- (2)}$$

put $V_o = 0.1 V_m$ and $t = t_1$ in eqn (1) --

$$0.1 V_m = V_m \left[1 - e^{-t_1/RC} \right]$$

$$0.1 = 1 - e^{-t_1/RC}$$

Case - (2) :

At, $(t = t_p)$. . .

Here, V_i changes suddenly from $(V_i \text{ to } 0)$ but, cap opp the sudden change in v_t 's. $\therefore V_o$ dec gradually.

At, $(t = t_p)$. . .

$$V_i = V_m$$

$$V_f = 0$$

$$t' = t_p$$

sub the values in the exp.

$$V_o(t) = V_c(t) = V_f + (V_i - V_f) e^{-(t-t')/RC}$$

$$V_o(t) = V_m \left[e^{-(t-t_p)/RC} \right] \quad \text{--- (6)}$$

Fall time : (t_f)

The time taken by the output to fall from 90% to 10% of final value

Let --

$$V_0 = 0.9 V_m \quad \text{at } t = t_3$$

$$V_0 = 0.1 V_m \quad \text{at } t = t_4$$

$$\therefore t_f = t_4 - t_3 \quad (7)$$

put, $V_0 = 0.9 V_m$ and $t = t_3$ in eqⁿ (6) --

we get,

$$0.9 V_m = V_m \left[e^{-\frac{(t_3 - t_p)}{RC}} \right]$$

$$0.9 = \left[e^{-\frac{(t_3 - t_p)}{RC}} \right]$$

$$0.9 = \left[e^{-\frac{t_3}{RC}} \right]$$

$$e^{-\frac{t_3}{RC}} = 0.9$$

$$-\frac{t_3}{RC} = \ln(0.9)$$

$$\frac{-t_3}{RC} = -0.1$$

$$\therefore t_3 = 0.1 RC + t_p$$

(8)

put, $V_0 = 0.1 V_m$ and $t = t_4$ in eqⁿ

we get ---


$$t_4 = 2.3 R.C + t_p \quad (9)$$

sub (8) and (9) in eqⁿ (7) ---

we get ---

$$t_f = 2.2 R.C$$

Response :

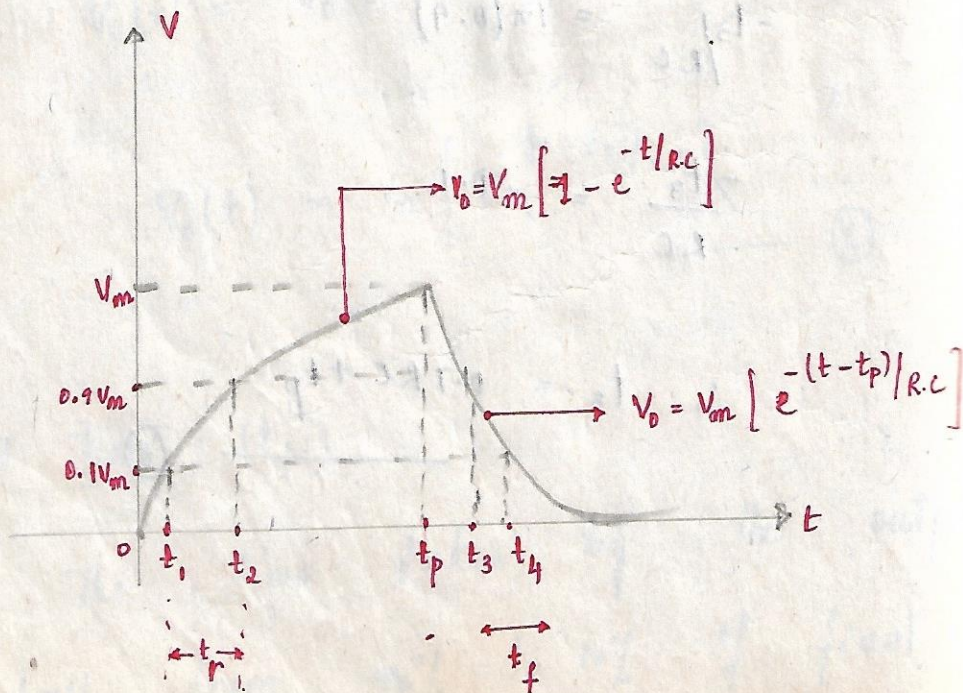


Response of L-R-C circuit

to the square wave

Imp
100%
care

Int:

input:

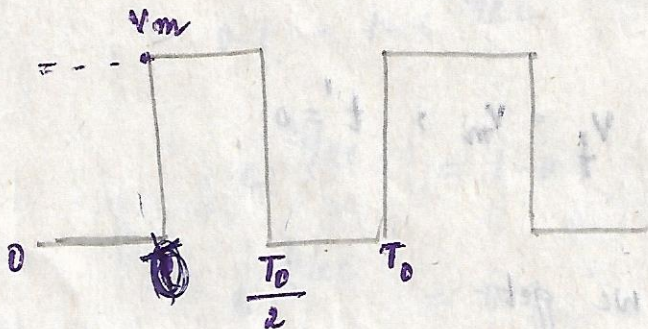

Consider, input to a \square^{re} wave
varying from $(0 - V_m)$ with 50% duty cycle.

Case - (i)

$$\text{of } (0 < t < \frac{T_0}{2})$$

At $t = 0$... (V_i) changes suddenly
from $(0 - V_m)$, but cap opp the
sudden change in the voltage. \therefore
 $(V_o) \uparrow$ gradually.

cap vty eqⁿ

$$V_o(t) = V_c(t) = V_f + (V_i - V_f) \cdot e^{-(t-t')/RC}$$

at (t=0) - - -

$$V_i = 0 ; \quad V_f = V_m, \quad t' = 0$$

on sub - - - we get - - -

$$V_o = V_m [1 - e^{-t/RC}] \quad \text{--- (1)}$$

Rise time (t_r)

The time req. for (or) by the output to inc from 10% to 90% of the max value.

Let,

$$V_o = 0.1 V_m \quad \text{at} \quad t = t_1$$

$$V_o = 0.9 V_m \quad \text{at} \quad t = t_2$$

$$t_r = t_2 - t_1 \quad \text{--- (2)}$$

put $V_0 = 0.1 V_m$ and $t = t_1$ in eqⁿ ① ...

we get ...

$$0.1 V_m(t) = V_m \left[1 - e^{-t_1/RC} \right]$$

$$0.1 = 1 - e^{-t_1/RC}$$

$$e^{-t_1/RC} = 1 - 0.1$$

$$e^{-t_1/RC} = 0.9$$

$$\frac{-t_1}{RC} = \ln(0.9)$$

$$\rightarrow \frac{t_1}{RC} = -0.1$$

$$\therefore t_1 = \underline{0.1 RC} \quad \text{③}$$

put $V_0 = 0.9 V_m$ and $t = t_2$ in eqⁿ

① ... we get ...

$$0.9 V_m = V_m \left[1 - e^{-t_2/RC} \right]$$

$$0.9 = 1 - e^{-t_2/RC}$$

$$e^{-t_2/RC} = 1 - 0.9$$

$$e^{-t_2/RC} = 0.1$$

$$\frac{-t_2}{RC} = \ln(0.1)$$

$$\tau_{RC} = 2.30$$

$$\therefore t_2 = 2.2 R \cdot C$$

$$\Rightarrow t_r = 2.2 R \cdot C$$

Case - (2) :

at $t = \frac{T_0}{2}$... (V_i) changes²

suddenly from (V_m to 0), but cap
the sudden change in vtg. i.e. (V_o)
gradually.

In the interval, $\left(\frac{T_0}{2} < t < T_0\right)$

$$V_i = V_m, \quad V_f = 0, \quad t' = \frac{T_0}{2}$$

in sub -- we get ---

$$V_o = V_m \left[e^{-\left(t - \frac{T_0}{2}\right) / RC} \right]$$

(4)

Fall time (t_f) :

The time taken by the output

to fall from 90% to 10% of the
max value

$$\text{let } \dots V_0 = 0.9 V_m \quad \text{at } t = t_3 \dots$$

$$V_0 = 0.1 V_m \quad \text{at } t = t_4 \dots$$

$$\therefore t_f = \frac{t_4 - t_3}{\quad} \quad (5)$$

put, $V_0 = 0.9 V_m$ and $t = t_3$ in eqⁿ (4)...

we get,

$$0.9 V_m = V_m \left[e^{-\left(t_3 - \frac{T_0}{2}\right)/RC} \right]$$

$$0.9 = \left[e^{-\left(t_3 - \frac{T_0}{2}\right)/RC} \right] \quad \text{[still]}$$

$$0.9 = \left[e^{-t_3/RC} \right]$$

$$e^{-t_3/RC} = 0.9$$

$$\frac{-t_3}{RC} = \ln(0.9)$$

$$\frac{-t_3}{RC} = -0.1$$

$$\therefore t_3 = 0.1 RC + \frac{T_0}{2}$$

(6)

put, $V_o = 0.1 V_m$ and $t = t_4$ in eqⁿ

we get - -

$$t_4 = 2.5 R.C + \frac{T_0}{2} \quad (7)$$

sub - eqⁿ (6) & (7) in eqⁿ (5) - -

we get

$$t_f = 2.2 R.C$$

Note:


$$t_r = t_f = 2.2 R.C$$

$$t_r = t_f \propto R.C$$


[If R_c is much smaller, $V_o \uparrow$ rapidly from $(0 - V_m)$.]

Response :


① $R_c \ll \frac{T_0}{2}$

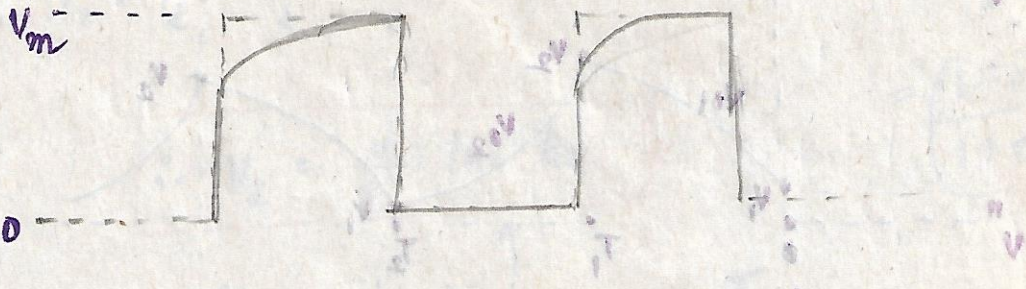

② $R_c = \frac{T_0}{2}$

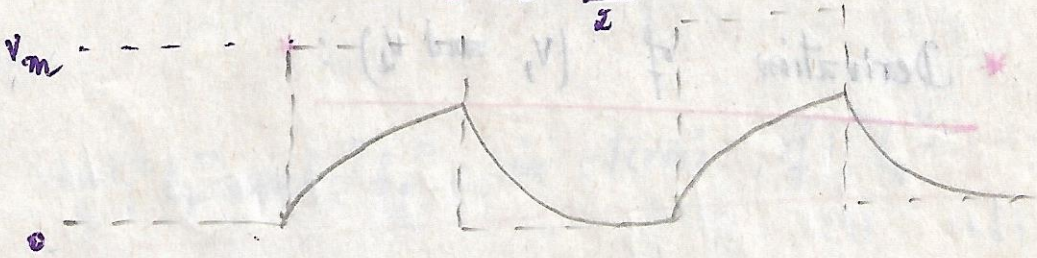

③ $R_c \gg \frac{T_0}{2}$

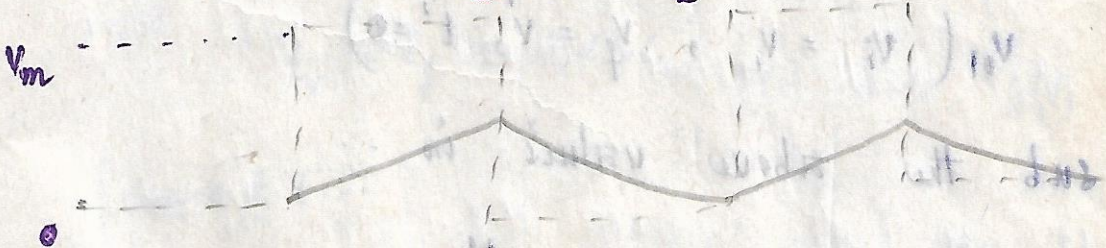


$\frac{1}{2} (V - V) + V = 10V$

$\frac{1}{2} (V - V) + V = 10V$

$\frac{1}{2} (V - V) + V = 10V$

$\frac{V}{2} = 10V - 10V$

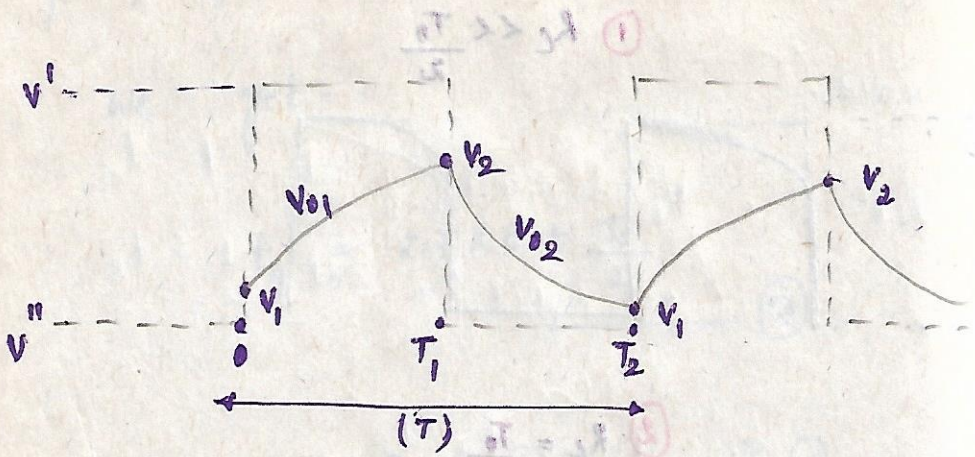

* Derivation of $(V_1$ and $V_2)$: *

$$V_{01} = ?$$

$\tau \ll \tau_1$ (2)

$$V_{01} (V_i = V_1, V_f = V', t' = 0)$$

sub the above values in --

$$V_{01} = V' + (V_1 - V') e^{-t/RC}$$

$$V_{02} (V_i = V_2, V_f = V'', t' = T_1)$$

sub the values in --

$$V_{02} = V'' + (V_2 - V'') e^{-(t - T_1)/RC}$$

we can also say that --

$$V' = -V'' = \frac{V}{2}$$

$$V_2 = -V_1; \quad V_1 = -V_2$$

$$T_1 = T_2 = \frac{T}{2}$$

$$\tanh x = \frac{e^x - e^{-x}}{e^x + e^{-x}} = \left(\frac{1 - e^{-2x}}{1 + e^{-2x}} \right)$$

$$V_2 = \frac{V}{2} \tanh \alpha$$

cal... (V_1 and V_2) $\alpha = \frac{T}{4RC}$

" t_r " and " t_f " in terms of " f_H "

w.k.t --

$$t_r = t_f = 2.2RC$$


w.a.k.t --

$$f_H = \frac{1}{2\pi RC} \implies RC = \frac{1}{2\pi f_H}$$

$$t_r = t_f = \frac{2.2}{2\pi f_H}$$

$$t_r = t_f = \frac{0.35}{f_H}$$

*** High pass R.C circuit: ***

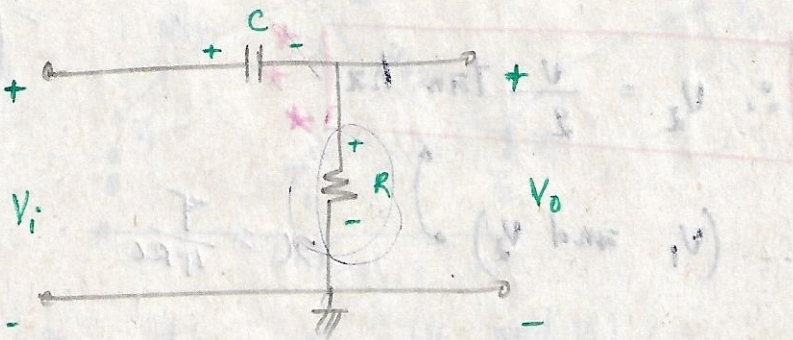

→ For low freq --- (X_c) becomes high compared to (R). \therefore the total (V_i) will appear across (C) and there

is no vtg across (R). $\therefore V_o \approx 0$

→ For high freq --- (X_c) becomes low compared to (R). \therefore the total

(V_i) will appear across (R)

$\therefore V_o \approx V_i$

\rightarrow For high freq, this circuit produces output same as input for high freq, but it produces zero output for low freq. Hence, this circuit is called as H.P R.C circuit.

Calculation of Gain: $(A) = ?$

By using vtg - division rule, ---

$$V_o = \left[\frac{R}{X_c + R} \right] \cdot V_i$$

$$V_o = \left[\frac{R}{R + \frac{1}{j\omega C}} \right] \cdot V_i$$

$$A = \frac{V_o}{V_i} = \frac{R}{R \left(1 + \frac{1}{j\omega RC} \right)}$$

$$A = \frac{1}{1 + \frac{\omega_L}{j\omega}}$$

where, $\omega_L = \frac{1}{R.C}$

$$f_L = \frac{1}{2\pi RC}$$

$$A = \frac{1}{1 + \frac{f_L}{jf}}$$

$$\therefore A = \frac{1}{1 - j\frac{f_L}{f}}$$

$$|A| = \frac{1}{\sqrt{1 + \left(\frac{f_L}{f}\right)^2}} \quad \longrightarrow \text{mag of gain}$$


$$\angle A = \tan^{-1} \left[\frac{f_L}{f} \right] \quad \longrightarrow \text{phase of gain}$$

As, $f \rightarrow 0 \Rightarrow |A| \rightarrow 0$



$f \rightarrow \infty \Rightarrow |A| \rightarrow 1$

$f \rightarrow f_L \Rightarrow |A| \rightarrow \frac{1}{\sqrt{2}}$

(Mag (vs) freq plot :)

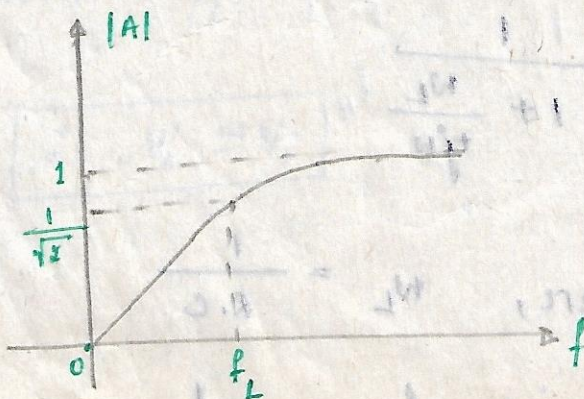

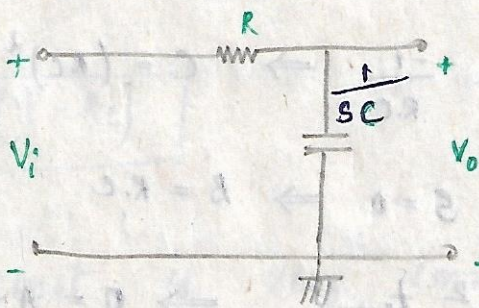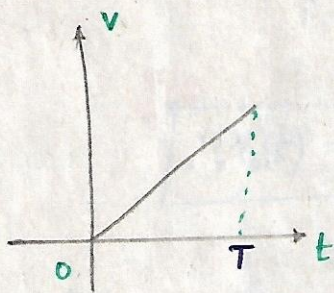Response of LP R.C circuit to the Ramp input:



Math rep of ramp input ...

$$V_i(t) = \alpha t^2 ; \quad V_i(s) = \frac{\alpha}{s^2}$$

By using voltage division rule ...

$$V_o(s) = \left(\frac{\frac{1}{s \cdot C}}{\left(R + \frac{1}{s \cdot C} \right)} \right) V_i(s)$$

$$V_o(s) = \left[\frac{1}{1 + R \cdot s \cdot C} \right] \cdot \frac{\alpha}{s^2}$$

$$= \frac{\alpha}{R \cdot C} \left[\frac{1}{s^2 \left(s + \frac{1}{R \cdot C} \right)} \right]$$

P-F ...

$$V_o(s) = \frac{\alpha}{R \cdot C} \left[\frac{A}{s} + \frac{B}{s^2} + \frac{C}{\left(s + \frac{1}{R \cdot C} \right)} \right]$$

$$A = ? ; \quad B = ? ; \quad C = ?$$

$$V_0(s) = \frac{\alpha}{R.C} \left[\frac{A}{s} + \frac{B}{s^2} + \frac{C}{\left(s + \frac{1}{R.C}\right)} \right]$$

$$1 = A.s \left(s + \frac{1}{R.C} \right) + B \cdot \left(s + \frac{1}{R.C} \right) + C.s^2$$

$$s = \frac{-1}{R.C} \Rightarrow C = (R.C)^2$$

$$s = 0 \Rightarrow B = R.C$$

$$s^2 \text{ terms} \Rightarrow 0 = A + C$$

$$\Rightarrow A = -C = -(R.C)^2$$

$$V_0(s) = \frac{\alpha}{R.C} \left[\frac{-(R.C)^2}{s} + \frac{R.C}{s^2} + \frac{(R.C)^2}{\left(s + \frac{1}{R.C}\right)} \right]$$

$$V_0(s) = \frac{-\alpha.R.C}{s} + \frac{\alpha}{s^2} + \frac{\alpha.R.C}{\left(s + \frac{1}{R.C}\right)}$$

Now:

Applying inverse lap. transform on b.s.

we get,

$$V_0(t) = -\alpha.R.C + \alpha t + \alpha.R.C e^{-t/R.C}$$

$$\left[\because e^{-x} = 1 - \frac{x}{1!} + \frac{x^2}{2!} - \frac{x^3}{3!} + \frac{x^4}{4!} - \frac{x^5}{5!} + \dots \right]$$

→ If time const $R.C$ is very small --

we can neglect the expo. term

$$\text{i.e., } e^{-t/R.C} \approx 0.$$

$$\therefore V_o(t) = \alpha (t - R.C)$$

→ When time const is very small

relative to the total ramp time " T ",

the ramp will be transmitted with

min distortion..

→ The output follows the input, but it is delayed by 1 time const from

the input.

→ If the time const is large compared with (T) . . . i.e., $\frac{R.C}{T} \gg 1 \Rightarrow \frac{R.C}{T} \gg 1$.

$$\rightarrow \text{If } V_o(t) = \alpha (t - R.C) + \alpha \cdot R.C e^{-t/R.C}$$

$$= \alpha (t - R.C) + \alpha \cdot R.C \left[1 - \frac{t}{R.C} + \frac{(t/R.C)^2}{2!} - \frac{(t/R.C)^3}{3!} + \dots \right]$$

if $(RC \gg T)$ - - we can neglect


the higher order terms. - -

$$= \alpha(t - RC) + \alpha \cdot RC \left[1 - \frac{t}{RC} + \frac{t^2}{2(RC)^2} \right]$$


$$= \cancel{\alpha t} - \cancel{\alpha RC} + \cancel{\alpha RC} - \cancel{\alpha t} + \frac{\alpha t^2}{2RC}$$

$$\therefore V_o(t) = \frac{\alpha t^2}{2RC}$$

Response:

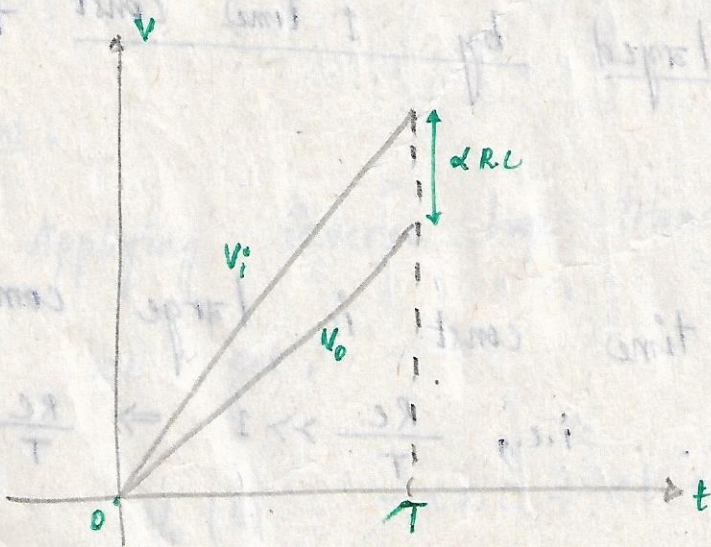

if $RC \ll T$ - -

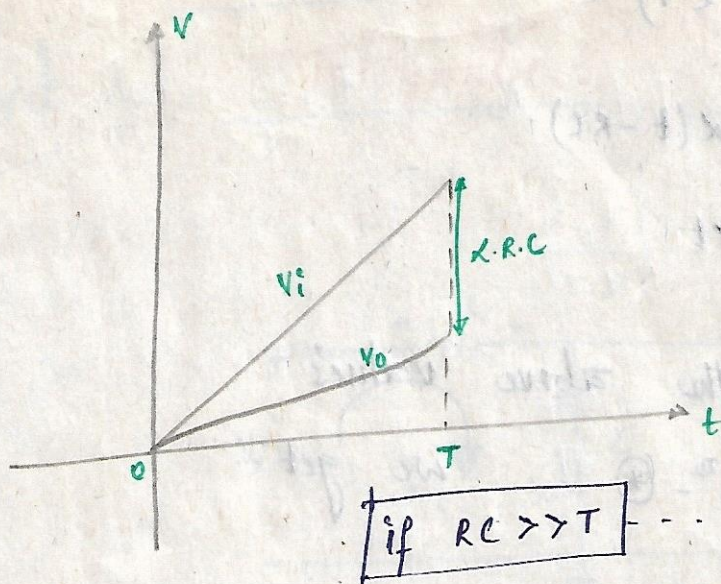

Transmission Errors (e_t)

Int:

It is defined as, the ratio of the diff between input and output to the input at the end of the ramp ($t = T$).

Mathematically

$$e_t = \frac{V_i - V_o}{V_i}$$

$$t = T.$$

⊛

if -- (RC < T) ...

$$V_o(t) = \alpha(t - RC) \dots$$

$$V_i(t) = \alpha t$$

on sub the above values

in eqⁿ (*) we get ..

$$e_t = \frac{\cancel{\alpha t} - \alpha(t - RC)}{\cancel{\alpha t}}$$

$$e_t = \frac{\cancel{\alpha t} - \cancel{\alpha t} + \alpha RC}{\cancel{\alpha t}} = \frac{\alpha RC}{\cancel{\alpha t}}$$

$$e_t = \frac{RC}{T}$$

(e_t) in terms of (f_H) ...


w.k.t ...

$$f_H = \frac{1}{2\pi RC} \Rightarrow RC = \frac{1}{2\pi f_H}$$

$$e_t = \frac{RC}{2\pi f_H T}$$

LP R.C circuit as an

Int integrator:

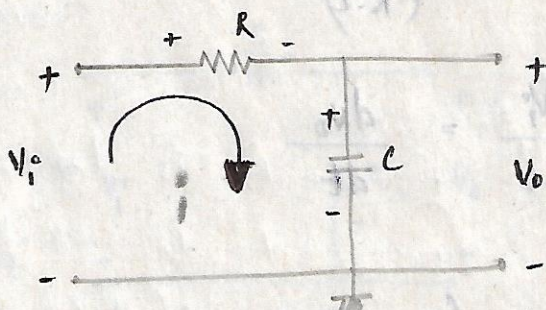

applying k.v.l ... $V_o = \frac{1}{C} \int i dt$

we get - -

$$i = C \frac{dV_o}{dt}$$

$$-V_i + iR + V_o = 0$$

$$V_i = R.C \frac{dV_o}{dt} + V_o$$

$$\frac{V_i}{R.C} = \frac{dV_o}{dt} + \frac{V_o}{R.C}$$

$$V_o = \frac{1}{C} \int i dt$$

$$i = C \frac{dV_o}{dt}$$

$\left(\frac{dV_o}{dt} \right) \longrightarrow$ transient response

$\left(\frac{V_o}{R.C} \right) \longrightarrow$ steady state response.

If T.C R.C is very high

we can neglect the steady state

response i.e., $\left(\frac{V_o}{R.C}\right)$

$$\therefore \frac{V_i}{R.C} = \frac{dV_o}{dt}$$

$$V_o = \frac{1}{R.C} \int V_i dt$$


$$V_o \propto \int V_i dt$$

\therefore L.P R.C circuit, with R.C \gg Pulse width
is called as "R.C integrator"

Int:

Response of H.P R.C ckt

to the step input:

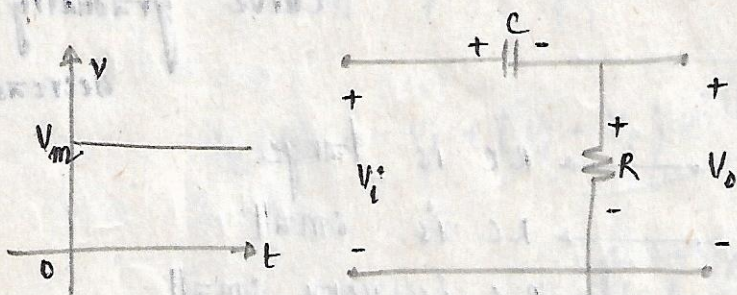

applying k.v.l to the loop...

we get ...

$$-V_i + V_c + V_o = 0$$

$$V_o = V_i - V_c \dots$$

at ... $t = 0 \dots$

$$\begin{aligned} V_i &= 0 \\ V_f &= V_m \\ t' &= 0 \end{aligned}$$

$$V_c(t) = V_f + (V_f - V_i) \cdot e^{-(t-t')/RC}$$

$$V_c(t) = V_m \left[1 - e^{-t/RC} \right] \quad \text{--- (1)}$$


at, $t = 0$; $V_i = V_m$ and $V_c = V_m \left[1 - e^{-t/RC} \right]$

$$V_o = V_m - V_m \left(1 - e^{-t/RC} \right)$$

$$V_o = \cancel{V_m} - \cancel{V_m} + V_m \cdot e^{-t/RC}$$

$$\therefore V_o(t) = V_m \cdot e^{-t/RC}$$



Response :

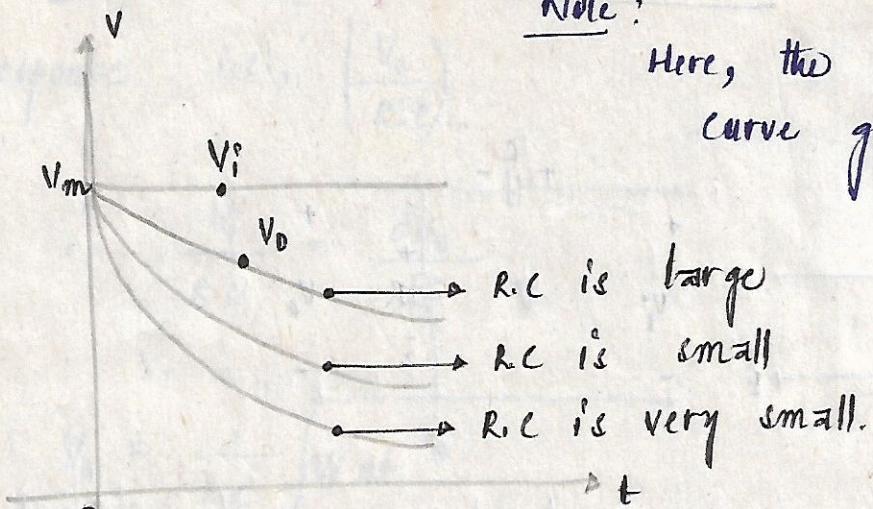

Note :

Here, the output curve gradually decreases

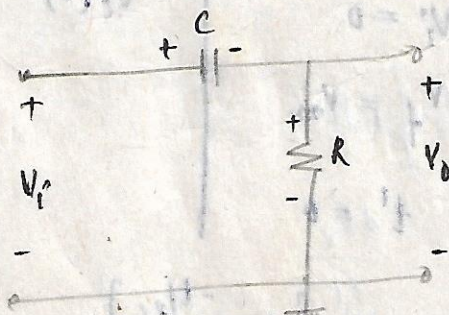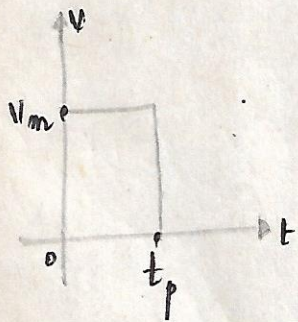Response of H.P. R.C ckt to the pulse input :



applying K.V.L to the loop --

we get --

$V_i - V_o - (1/s) dV_o/dt = 0$

$$-V_i + V_c + V_o = 0$$

$$V_o = V_i - V_c \dots$$

at, $t = 0$: ---

$$V_i = 0; \quad V_f = V_m; \quad t' = 0$$

$$V_c(t) = V_f + (V_i - V_f) e^{-(t-t')/RC}$$

$$\therefore V_c(t) = V_m [1 - e^{-t/RC}]$$

at, $t = 0$: ---

$$V_i = V_m$$


$$V_c = V_m [1 - e^{-t/RC}]$$

$$V_o = V_m - V_m [1 - e^{-t/RC}]$$

$$V_o = \cancel{V_m} - \cancel{V_m} + V_m e^{-t/RC}$$

$$\therefore V_o(t) = V_m e^{-t/RC}$$

Response :

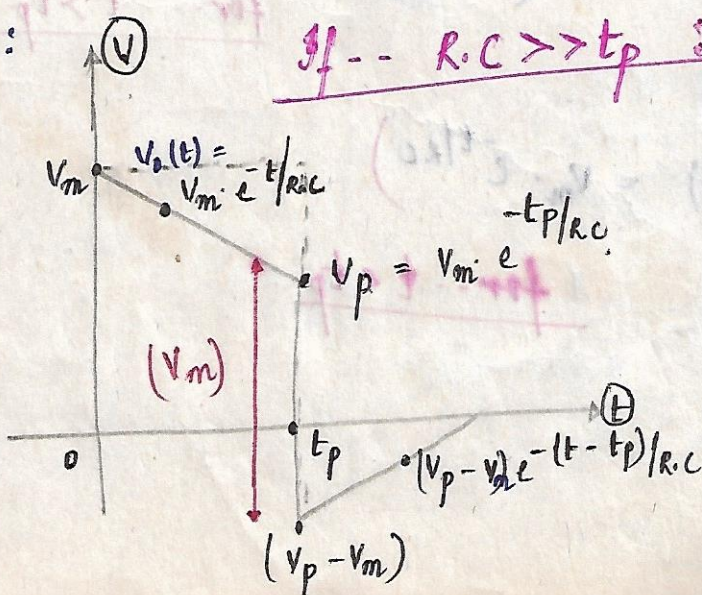

* At, $t = t_p$ ----- $V_o(t) = V_p = V_m \cdot e^{-t_p/RC}$

* At, $t = t_p$ ----- \therefore the input falls

by V_m (v) suddenly and \therefore the

voltage across the cap (V_o) can not change instantaneously, the output also falls suddenly from $(V_p - V_m)$.

* For $(t > t_p)$ ----- the output rises exponentially towards zero with a

T.C \rightarrow R.C

$$\therefore V_o = (V_p - V_m) e^{-(t-t_p)/RC}$$

$$(\therefore V_o(t) = (V_m e^{-t/RC} - V_m) e^{-(t-t_p)/RC})$$


for $t > t_p$

$$(\therefore V_o(t) = V_m \cdot e^{-t/RC})$$


for $t < t_p$

(mV)

if $R.C \approx t_p$:

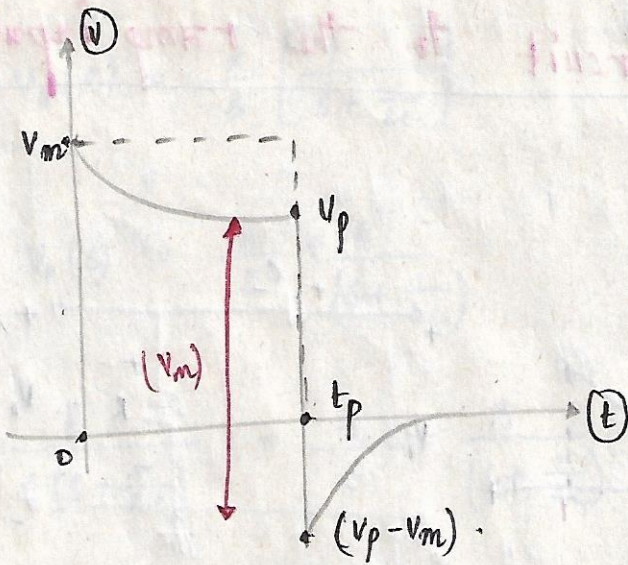


if $R.C \ll t_p$:

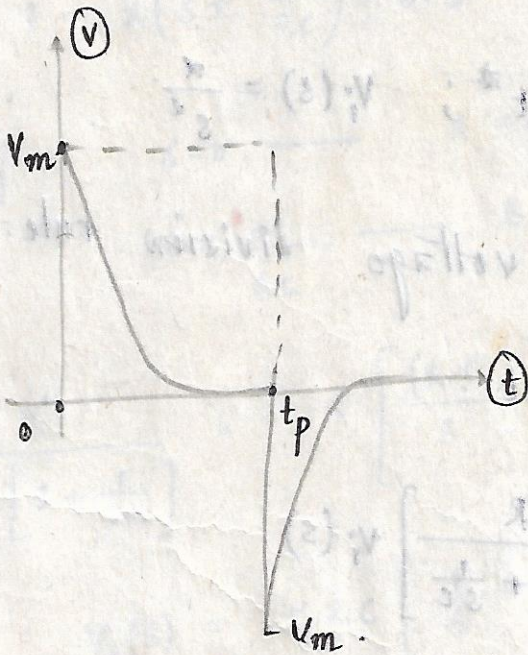

Response of H.P R.C

circuit to the ramp input:

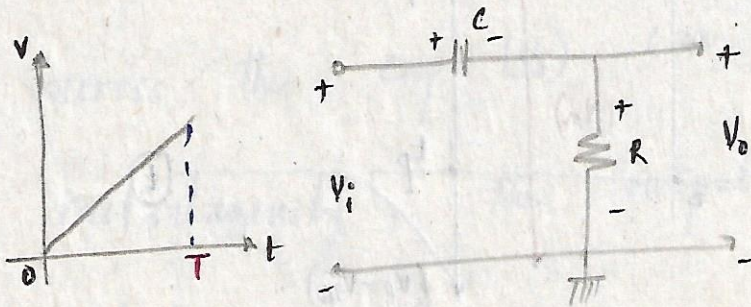

Math rep of ramp input:

$$V_i(t) = \alpha t ; \quad V_i(s) = \frac{\alpha}{s^2}$$

By using voltage division rule -
we get - - -

$$V_o(s) = \left[\frac{R}{R + \frac{1}{sC}} \right] V_i(s)$$

$$V_o(s) = \frac{\left[\frac{RSC}{1 + RSC} \right]}{sC} \cdot V_i(s)$$

$$V_o(s) = \frac{R}{R \left(1 + \frac{1}{sRC} \right)} \cdot V_i(s)$$

$$V_o(s) = \frac{1}{R.C} \left[\frac{s.R.C}{s + \frac{1}{R.C}} \right] \cdot \frac{\alpha}{s^2}$$

$$V_o(s) = \frac{\alpha}{s} \left[\frac{1}{s + \frac{1}{R.C}} \right]$$

$$V_o(s) = \frac{A}{s} + \frac{B}{\left(s + \frac{1}{R.C}\right)}$$

$$\frac{\alpha}{s \left(s + \frac{1}{R.C}\right)} = \frac{A}{s} + \frac{B}{\left(s + \frac{1}{R.C}\right)}$$

partial fractions ...

$$1 = A \left(s + \frac{1}{R.C}\right) + B \cdot s$$

If ... $s=0 \longrightarrow A = R.C$

$s = \frac{-1}{R.C} \longrightarrow B = -R.C$

$$\frac{\alpha}{s \left[s + \frac{1}{R.C}\right]} = \alpha \left[\frac{(R.C)}{s} - \frac{(R.C)}{\left(s + \frac{1}{R.C}\right)} \right]$$

$$V_o(s) = \alpha \cdot R.C \left[\frac{1}{s} - \frac{1}{\left(s + \frac{1}{R.C}\right)} \right]$$

apply ... ILT ... on b.s ... we get ...

$$V_o(t) = \alpha \cdot R.C \left[1 - e^{-t/R.C} \right] \text{ --- (1)}$$

$$V_o(t) = \alpha \cdot R.C \left[1 - \left(1 - \frac{t}{R.C} + \left(\frac{t}{R.C}\right)^2 \cdot \frac{1}{2!} \dots \right) \right]$$

If $R.C \gg T$ then, we can neglect the higher order terms.

$$V_o(t) = \alpha \cdot R.C \left[\cancel{1} - \cancel{1} + \frac{t}{R.C} - \frac{t^2}{2(R.C)^2} \right]$$

$$V_o(t) = \alpha t - \frac{\alpha t^2}{2 \cdot R.C}$$

$$V_o(t) = \alpha t \cdot \left(1 - \frac{t}{R.C} \right) \quad \text{--- (2)}$$

Response 2

