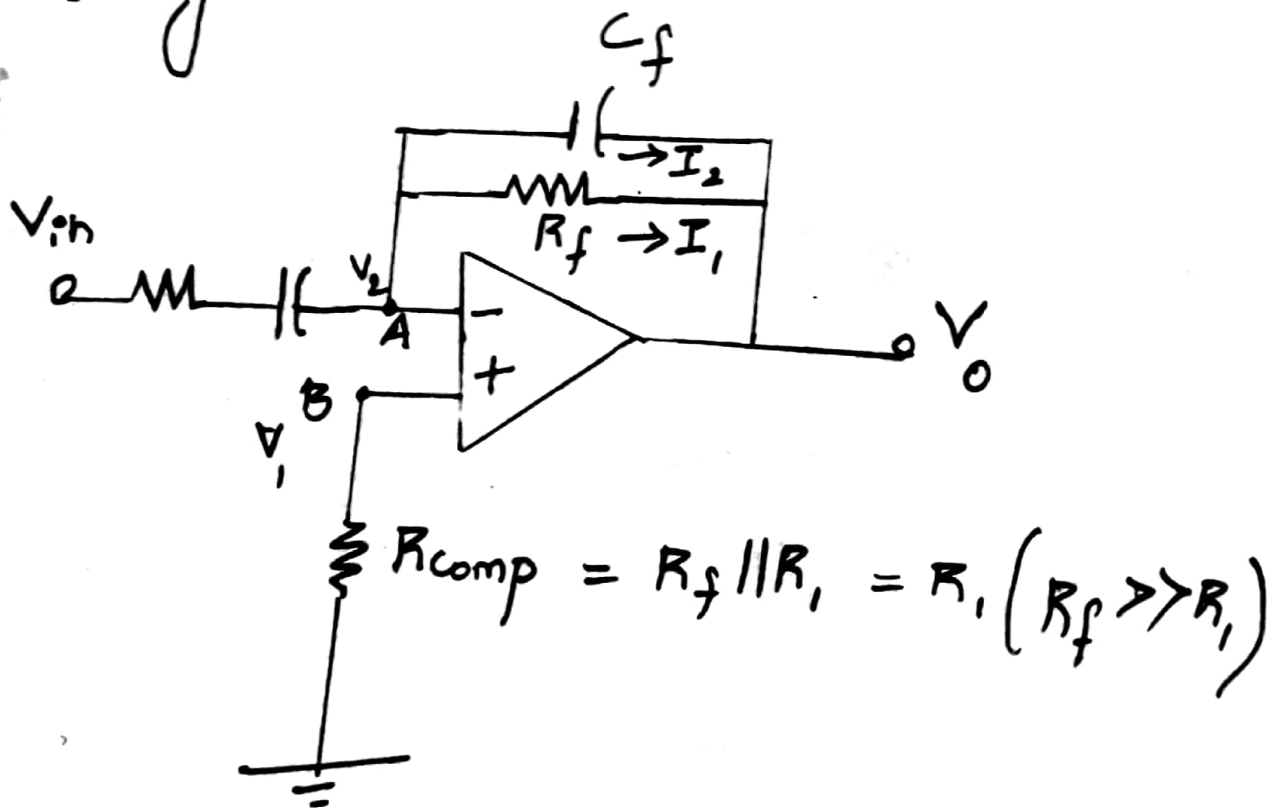


Practical Differentiator \Rightarrow

\rightarrow The noise and stability at high frequency can be corrected, But in the Practical differentiator circuit by using resistance R_1 in series with C



Analysis of Practical Differentiator

- \rightarrow Inside the op-amp current is "zero"
- \rightarrow There is no current i/p at node B
- $\rightarrow V_1 = V_2 = 0$

The current I is given by $\textcircled{2}$

$$I = \frac{V_{in} - V_2}{Z_1} = \frac{V_{in}}{Z_1} \rightarrow \textcircled{1}$$

Where $Z_1 = R_1$ in series with C_1 ,

So in Laplace domain we can write

$$Z_1 = R_1 + \frac{1}{sC_1} = \frac{1 + sR_1C_1}{sC_1}$$

Substitute the Z_1 value in eq $\textcircled{1}$

$$I = \frac{V_{in}(s)}{\frac{1 + sR_1C_1}{sC_1}} = \frac{sC_1 V_{in}(s)}{1 + sR_1C_1}$$

Now the current I_1 is given by $\textcircled{2}$

$$I_1 = \frac{V_2 - V_{out}}{R_f} = -\frac{V_{out}}{R_f}$$

In Laplace form, we have $\textcircled{3}$

$$I_1 = \frac{-V_{out}(s)}{R_f}$$

$$\text{and } I_2 = C_f \frac{d(V_2 - V_{out})}{dt}$$

$$= -C_f \frac{dV_{out}}{dt} \rightarrow \textcircled{4}$$

Taking Laplace transform, we obtain

$$I_2 = -sC_f V_{out}(s)$$

Applying KCL at node A,

$$I = I_1 + I_2 \text{ --- } \textcircled{5}$$

substitute Equ. in $\textcircled{2}$, $\textcircled{3}$ & $\textcircled{4}$
Equ in $\textcircled{5}$

$$\frac{sC_1 V_{in}(s)}{(1 + sR_1C_1)} = \frac{-V_{out}(s)}{R_f} - sC_f V_{out}(s)$$

$$\frac{sC_1 V_{in}(s)}{(1 + sR_1C_1)} = -V_{out}(s) \left[\frac{1}{R_f} + sC_f \right]$$
$$= -V_{out}(s) \left[\frac{1 + R_f sC_f}{R_f} \right]$$

$$\frac{SR_f C_1 V_{in}(s)}{(1 + R_f s C_f)(1 + SR_f)} = -V_{out}(s)$$

If $R_1 C_1 = R_f C_f$ then

$$V_{out}(s) = \frac{-SR_f C_1 V_{in}(s)}{(1 + SR_f C_f)^2}$$

→ (6)

→ $R_f C_1$ is much greater than $R_1 C_1$ & $R_f C_f$ we can write above equ.

$$V_{out}(s) = -SR_f C_1 V_{in}(s)$$

on applying inverse laplace transform we get

$$V_{out} = -R_f C_1 \left[\frac{d}{dt} V_{in}(t) \right]$$

final equ →