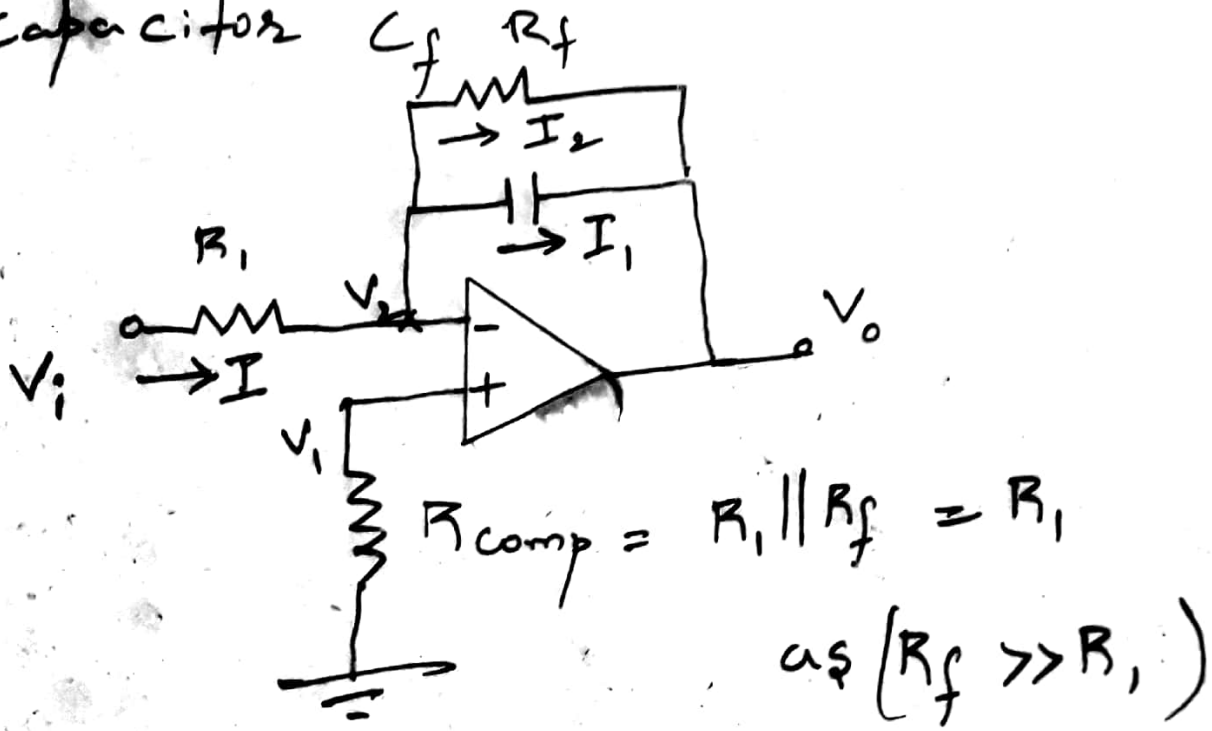


Practical Integrators: The limitations of an ideal integrator can be minimized in the practical ckt, which use a resistance R_f in parallel with capacitor C_f I_o



* The Resistance R_{comp} is also used to overcome the error due to bias current.

Analysis of practical Integrator

→ Since i/p I inside op-amp is zero, the node 'B' is ground potential

from the concept of virtual ground I (2)

$$V_1 = V_2 = 0$$

$$I = \frac{V_1 - V_2}{R_1}$$

$$= V_1 / R_1 \quad (\because V_2 = 0)$$

$$\text{By } I_1 = \frac{C_f d(V_2 - V_0)}{dt}$$

$$= -\frac{C_f dV_0}{dt}$$

$$I_2 = \frac{V_2 - V_0}{R_f}$$

$$I_2 = \frac{-V_0}{R_f}$$

Applying KCL at node A'

$$I = I_1 + I_2$$

substitute I_1, I, I_2 values in above eqn

$$\frac{V_{in}}{R_1} = -\frac{C_f dV_0}{dt}$$

$$= -\frac{V_0}{R_f}$$

Taking Laplace transform to the above eqn

$$\frac{V_i(s)}{R_1} = -\frac{C_f V_0(s)}{R_f}$$

$$\frac{V_i(s)}{R_1} = -V_o(s) \left(sC_f - 1/R_f \right)$$

23

$$\frac{V_i(s)}{R_1} = \frac{-V_o(s) (1 + sC_f R_f)}{R_f}$$

$$-\frac{V_i(s) R_f}{(1 + sC_f R_f) R_1} = V_o(s)$$

$$V_o(s) = \frac{R_f}{R_1 (1 + sC_f R_f)} V_i(s)$$

$$= \frac{1}{\frac{R_1}{R_f} (1 + sC_f R_f)} V_i(s)$$

$$= \frac{1}{\frac{R_1}{R_f} + \frac{sR_1 C_f R_f}{R_f}} V_i(s)$$

When R_f is large then R_1/R_f can be neglected

$$V_o(s) = \frac{1}{\left(\frac{R_1}{R_f} + sR_1 C_f \right)} V_i(s)$$

I 4

$$V_o(s) = \frac{1}{s R_1 C_f} V_i(s)$$

on applying inverse laplace
to above equ

$$V_o(t) = \frac{1}{R_1 C_f} \int V_i(t) dt$$