

Difference Amplifier (Subtractor):-


(1)

→ The difference amp gives an o/p which is proportional to the difference in voltages applied to inverter and Non-inverter i/p

→ The difference amp V_i is applied to the inverter i/p through a resistance R_1 . The 2nd voltage is applied to the non-inverter i/p through a resistance R_1 .

→ R_f is the usual feedback resistance R_2 is another resistance connected between the non-inverter i/p and ground.

(2)

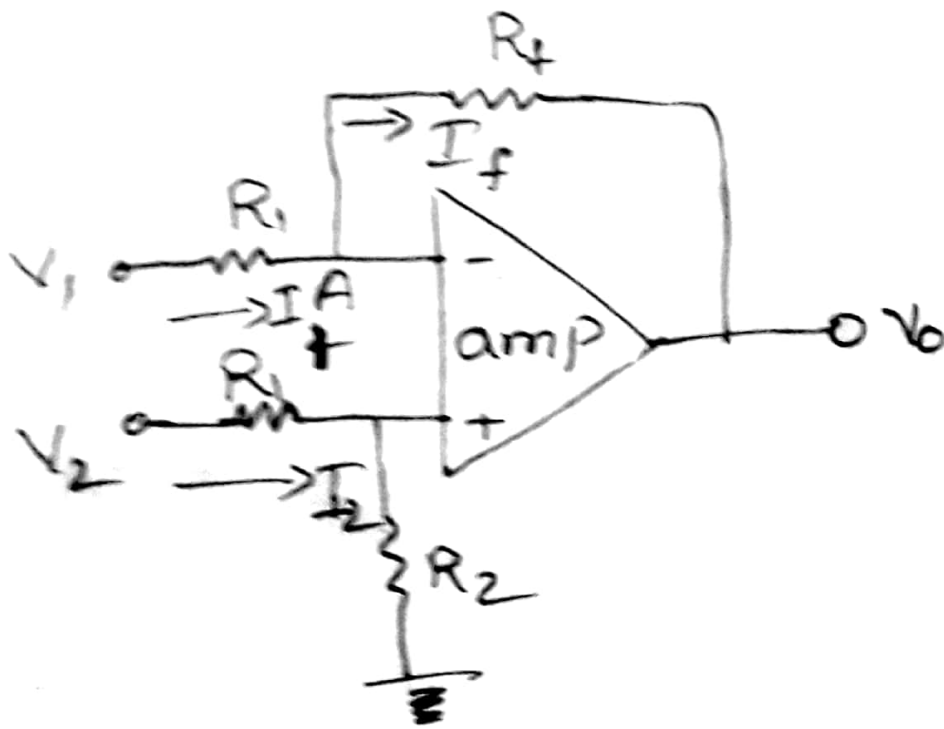

→ Let the potential of node "B" be V_B . The potential of node "A" is same as B. (By using virtual ground concept)

ie $V_A = V_B$

Applying KCL at node B, we obtain

$$\frac{V_2 - V_B}{R_1} = \frac{V_B - 0}{R_2}$$

(3)

$$\frac{V_2}{R_1} = \frac{V_B}{R_1} + \frac{V_B}{R_2}$$

$$\frac{V_2}{R_1} = V_B \left[\frac{1}{R_1} + \frac{1}{R_2} \right]$$

Voltage at node "A", $V_A = V_B$

$$\therefore V_B = \frac{V_2}{R_1 \left[\frac{1}{R_1} + \frac{1}{R_2} \right]}$$

$$V_B = \frac{V_2}{\left[1 + \frac{R_1}{R_2} \right]} \longrightarrow \textcircled{1}$$

Applying KCL at node A, we have

$$\frac{V_1 - V_A}{R_1} = \frac{V_A - V_0}{R_2}$$

$$\frac{V_1}{R_1} - \frac{V_A}{R_1} = \frac{V_A}{R_2} - \frac{V_0}{R_2}$$

(4)

$$\frac{V_1}{R_1} = \frac{V_A}{R_2} + \frac{V_A}{R_1} - \frac{V_0}{R_2}$$

$$\frac{V_1}{R_1} = V_A \left[\frac{1}{R_1} + \frac{1}{R_2} \right] - \frac{V_0}{R_2}$$

$$\frac{V_1}{R_1} = V_A \left[1 + \frac{R_1}{R_2} \right] - V_0 \frac{R_1}{R_2} \rightarrow (2)$$

Since $V_A = V_B$ thus substitute V_B value

(2) in eq (2)

$$V_1 = \frac{V_2}{1 + \frac{R_1}{R_2}} \left[1 + \frac{R_1}{R_2} \right] - V_0 \frac{R_1}{R_2}$$

$$V_1 = \underline{V_2} - V_0 \left[\frac{R_1}{R_2} \right]$$

$$V_1 - V_2 = -V_0 \left[\frac{R_1}{R_2} \right]$$

$$-(V_2 - V_1) = -V_0 \left[\frac{R_1}{R_2} \right]$$

$$V_o = \frac{R_2}{R_1} [V_2 - V_1]$$

⑤

That the o/p voltage is proportional to the difference b/w the two i/p voltages.

Thus it acts as subtractor or Differential amp.