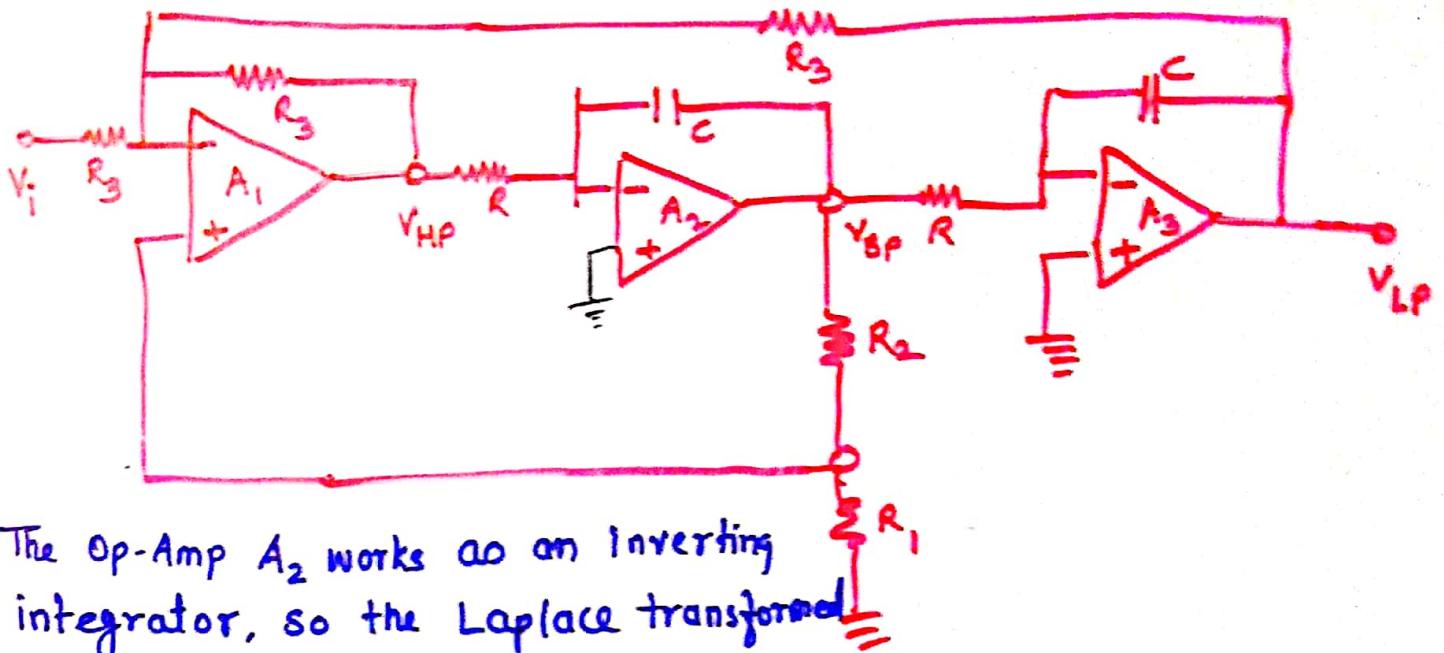


STATE VARIABLE FILTER :-



The Op-Amp A_2 works as an inverting integrator, so the Laplace transformed o/p V_{BP} is given by,

$$V_{BP} = -\frac{1}{sRC} V_{HP} \quad \text{--- (1)}$$

If $R = 1 \text{ M}\Omega$ and $C = 1 \mu\text{F}$, so that $RC = 1$, we get,

$$V_{BP} = -\frac{1}{s} V_{HP} \quad \text{--- (2)}$$

Also for inverting integrator A_3 , we may write

$$V_{LP} = \frac{1}{s} V_{BP} = \frac{1}{s^2} V_{HP} \quad \text{--- (3)}$$

The Op-Amp A_1 is a three I/P summer. The o/p V_{HP} can be written using superposition theorem. That is,

$$V_{HP} = -\left(\frac{R_3}{R_3}\right) V_i - \left(\frac{R_3}{R_3}\right) V_{LP} + \left(1 + \frac{R_3}{R_3 \parallel R_3}\right) \left(\frac{R_1}{R_1 + R_2}\right) V_{BP}$$

$$= -V_i - V_{LP} + 3\left(\frac{R_1}{R_1 + R_2}\right) V_{BP}$$

$$\text{Put } d = 3\left(\frac{R_1}{R_1 + R_2}\right)$$

$$\text{Then } V_{HP} = -V_i - V_{LP} + d V_{BP} \quad \text{--- (4)}$$

Eliminating V_{BP} and V_{LP} using eq.ⁿ (2) and (3)

$$V_{HP} = -V_i - \frac{V_{HP}}{s^2} - \frac{d}{s} V_{HP}$$

$$V_{HP} \left(1 + \frac{d}{s} + \frac{1}{s^2}\right) = -V_i$$

So, the high pass transfer function $H_{HP}(s)$ is

$$H_{HP} = \frac{V_o}{V_i} = \frac{-s^2}{s^2 + \alpha s + 1}$$

The damping factor α can be set by R_1 and R_2 for Bessel, Butterworth or Chebyshev response

Comparing to the std. high pass transfer fun.ⁿ

$$\frac{A_0 s^2}{s^2 + \alpha \omega_0 s + \omega_0^2}$$

So for high-pass filter of state variable filter,

$A_0 = -1$ and $\omega_0 = 1$ is obtained by eliminating

The low pass transfer fun.ⁿ is obtained by eliminating V_{HP} and V_{BP} from eqⁿ (4)

$$H_{LP} = \frac{V_o}{V_i} = \frac{-1}{s^2 + \alpha s + 1}$$

As in High Pass Filter, the low-pass filter has

$$A_0 = -1, \omega_0 = 1$$

$$\alpha = 3 \left(\frac{R_1}{R_1 + R_2} \right)$$

Finally the band-pass impulse response is obtained from eqⁿ

(4) by eliminating V_{HP} and V_{LP} as

$$H_{BP} = \frac{V_o}{V_i} = \frac{s}{s^2 + \alpha s + 1}$$

The std. band pass transfer fun.ⁿ is $A_0 \alpha \omega_0 s$

Comparing these eqⁿ

$$A_0 \alpha \omega_0 = 1$$

$\omega_0 = 1/R_C = 1$ (RC has been assumed to be 1)

$$A_0 = \frac{1}{\alpha} = \frac{R_1 + R_2}{3R_1}$$

From the analysis, we found that the band-pass response can be generated by integrating the high-pass response and that the low pass is generated by integrating the band-pass.