

UNIT - IV

II] LAPLACE TRANSFORM APPLICATIONS FOR NETWORKS *

let $f(t)$ be a funcⁿ of time 't'

$$F(s) = \mathcal{L}\{f(t)\} = \int_0^{\infty} e^{-st} f(t) dt \rightarrow \textcircled{1}$$

$$s = \sigma + j\omega$$

↓
Neper
freq

↓
radian
freq

(Np/sec)

(Rad/sec)

$\omega \rightarrow$ no. of oscillations

$\sigma \rightarrow$ magnitude of oscillations

Conditions for existence of L.T:-

if $f(t)$ is a funcⁿ of 't'


I) $f(t)$ must be piece-wise continuous

II) $f(t)$ must be exponential order.

$\rightarrow$ let $f(t)$ be a funcⁿ defined in 't' in the $[a, b]$

such that a, b are divided into subintervals

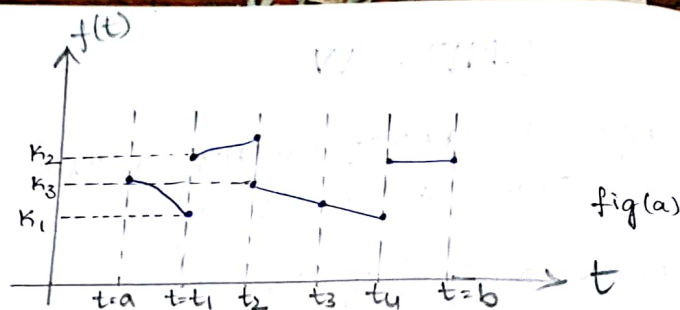$\rightarrow$ each subinterval $f(t)$ must be continuous.



$\Rightarrow f(t)$ is said to be exponential order
iff

$$\lim_{t \rightarrow \infty} e^{-st} f(t) = 0$$

Concept of t^+ & t^- :-

* $\rightarrow$ At $t = t_1^-$ (instant before step) $\Rightarrow f(t) = k_1$
 $t = t_1^+$ (instant after step) $\Rightarrow f(t) = k_2$

* $\rightarrow$ At $t = t_3 \Rightarrow f(t) = k_3$
 $t = t_3^+ = t_3^- \Rightarrow f(t) = k_3$

From eqn ①; $t = 0^+ = 0^- = 0$

$\rightarrow$ If $f(t)$ is continuous at $t=0$ then

$\rightarrow$ If $f(t)$ is discontinuous at $t=0$ then $t=0^+ \neq t=0^-$

Some Important

1) $L[k] = \frac{k}{s}$

2) $L[e^{-at}] = \frac{1}{s+a}$

3) $L[e^{at}] = \frac{1}{s-a}$

4) $L[\sin at] = \frac{a}{s^2+a^2}$

5) $L[\cos at] = \frac{s}{s^2+a^2}$

6) $L[t^n] = \frac{n!}{s^{n+1}}$

If n is an integer

ie $L[t^n] = \frac{n!}{s^{n+1}}$

7) $L[\sinh at] = \frac{a}{s^2-a^2}$

8) $L[\cosh at] = \frac{s}{s^2-a^2}$

9) If $L[f_1(t)] = F_1(s)$

$L[k_1 f_1(t)] = k_1 F_1(s)$

10) If $L[f(t)] = F(s)$

$L[e^{at} f(t)] = F(s-a)$

11) If $L[f(t)] = F(s)$

$L[f(at)] = \frac{1}{a} F\left(\frac{s}{a}\right)$

Important Formulae:-

$$L[1] = \frac{1}{s} ; s > 0$$

$$L[e^{at}] = \frac{1}{s-a} ; s > -a$$

$$L[e^{at}] = \frac{1}{s-a} ; s > a$$

$$L[\sin at] = \frac{a}{s^2 + a^2} ; s > 0$$

$$L[\cos at] = \frac{s}{s^2 + a^2} ; s > 0$$

$$L[t^n] = \frac{n!}{s^{n+1}} ; s > 0$$

If n is an integer, $n! = n \cdot (n-1) \cdot \dots \cdot 1$

$$L[t^n] = \frac{n!}{s^{n+1}} ; s > 0$$

$$L[\sinh at] = \frac{a}{s^2 - a^2} ; s > |a|$$

$$L[\cosh at] = \frac{s}{s^2 - a^2} ; s > |a|$$

If $L[f_1(t)] = F_1(s)$ & $L[f_2(t)] = F_2(s)$ then

$$L[k_1 f_1(t) + k_2 f_2(t)] = k_1 F_1(s) + k_2 F_2(s)$$

If $L[f(t)] = F(s)$ then

$$L[e^{at} f(t)] = F(s-a)$$

$$12> \text{ If } L[f(t)] = F(s)$$

$$L[f(at)] = \frac{1}{|a|} F\left(\frac{s}{a}\right)$$

$$13> L[t^n f(t)] = (-1)^n \frac{d}{ds^n} F(s)$$

$$14> f(0^+) = \lim_{s \rightarrow \infty} s F(s) \rightarrow \text{initial value th.}$$

$$15> L\left[\frac{d}{dt} f(t)\right] = sF(s) - f(0)$$

$$16> \text{ If } f(t) = f(t+T) \rightarrow \text{periodic signal}$$

$$L[f(t)] = \frac{1}{1-e^{-sT}} \int_0^T e^{-st} f(t) \cdot dt$$

$$17> \text{ If } L[f(t)] = F(s)$$

$$f(\infty) = \lim_{s \rightarrow 0} s F(s) \rightarrow \text{Final value th.}$$

$$18> \text{ If } f^n(t) = \frac{d^n}{dt^n} f(t) \text{ then;}$$

$$L[f^n(t)] = s^n F(s) - s^{n-1} f(0) - s^{n-2} f'(0) - \dots - s f^{(n-1)}(0) - f(0)$$

$$19> \text{ If } L[f(t)] = F(s) \text{ then}$$

$$L\left[\frac{f(t)}{t}\right] = \int_s^\infty F(s) \cdot ds$$

$$20> \text{ If } L[f(t)] = F(s) \text{ then}$$

$$L\left[\int_0^t f(t) \cdot dt\right] = \frac{F(s)}{s} + \frac{\bar{f}'(0)}{s}$$

where $\bar{f}' \rightarrow$ integral of $f(t)$

Find the L.T of $\cosh at \cdot \cos bt$.

$$\therefore L[\cosh at \cdot \cos bt]$$

$$= L\left[\frac{e^{at} + e^{-at}}{2} \cdot \cos bt\right]$$

$$= \frac{1}{2} L[(e^{at} + e^{-at}) \cos bt]$$

$$= \frac{1}{2} L[e^{at} \cos bt] + \frac{1}{2} L[e^{-at} \cos bt]$$

$$= \frac{1}{2} \left[\frac{(s-a)}{(s-a)^2 + b^2} \right] + \frac{1}{2} \left[\frac{(s+a)}{(s+a)^2 + b^2} \right]$$

∴

Find the L.T of $t \cdot e^{-2t} \sin 3t$

$$\therefore L[t \cdot e^{-2t} \sin 3t]$$

$$L[f(t)] = L[\sin 3t] = \left(\frac{3}{s^2 + 9} \right) \Rightarrow F(s)$$

$$L[t \cdot \sin 3t] = (-1) \frac{d}{ds} F(s)$$

$$= -1 \frac{d}{ds} \left(\frac{3}{s^2 + 9} \right)$$

$$= -3 \frac{[s^2 + 9(0) - 1(2s)]}{(s^2 + 9)^2}$$

$$= \frac{6s}{(s^2 + 9)^2}$$

$$L[e^{-2t} (t \sin 3t)] = \frac{6(s+2)}{[(s+2)^2 + 9]^2}$$

INVERSE LAPLACE TRANSFORMS [ILT]

If the L.T of a func $f(t)$ is $F(s)$ then I.L.T is applied to convert from frequency domain to time domain & is given as:-

$$L[f(t)] = F(s)$$

$$f(t) = \bar{L}'[F(s)]$$

$\bar{L}' \rightarrow$ ILT operator

Properties:-

- ① $\bar{L}'[k_1 F_1(s) + k_2 F_2(s)] = k_1 f_1(t) + k_2 f_2(t)$
- ② If $\bar{L}'[F(s)] = f(t)$ then $\bar{L}'[F(s-a)] = e^{at} f(t)$
- ③ If $\bar{L}'[F(s)] = f(t)$ then $\bar{L}'[F(as)] = \frac{1}{a} f\left(\frac{t}{a}\right)$

PARTIAL FRACTIONS

$$* \rightarrow Q(s) = a_n s^n + a_{n-1} s^{n-1} + \dots + a_1 s + a_0$$

where $a_n, a_{n-1}, \dots, a_1, a_0 \rightarrow$ real constants

If $a_n \neq 0$ then $Q(s) \rightarrow$ polynomial of degree 'n'.

$$\Rightarrow \text{If } P(s) = \frac{N(s)}{D(s)} \rightarrow \text{polynomial of degree 'n'}$$

↓
Rational
polynomial

proper rational p
improper Rational
 $\rightarrow$ Every improper
can be expressed
as a proper pol
 $\rightarrow$ Consider $P(s)$

case-i:- of roots
i.e. $D(s) = (s - \lambda)$

$$\frac{N(s)}{D(s)} = \frac{k_1}{(s - \lambda_1)} + \frac{k_2}{(s - \lambda_2)} + \dots$$

if $j = 1, 2, \dots$

$$k_j = \frac{N(s)}{D(s)}$$

case-ii:- of roots

$$\text{i.e. } D(s) = (s - \alpha)^2$$

$$\frac{N(s)}{D(s)} = \frac{a_0}{(s - \alpha)^2} + \dots$$

where

$$a_j = \frac{1}{j!} \dots$$

→ Every improper fraction can be expressed as the sum of polynomial & a proper polynomial ($n < m$) → $P(s) = Q + \frac{R}{D}$.

→ Consider $P(s) = \frac{N(s)}{D(s)}$ → 'n' degree ($n < m$)
 $D(s)$ → 'm' degree

Case-i:- If roots of $D(s)$ are real & distinct:

$$\text{i.e. } D(s) = (s - \lambda_1)(s - \lambda_2) \dots \dots (s - \lambda_m)$$

$$\frac{N(s)}{D(s)} = \frac{k_1}{(s - \lambda_1)} + \frac{k_2}{(s - \lambda_2)} + \dots \dots + \frac{k_m}{(s - \lambda_m)}$$

if $i = 1, 2, \dots \dots m$ then

$$k_i = \left. \frac{N(s) \cdot (s - \lambda_i)}{D(s)} \right|_{s = \lambda_i}$$

Case-ii:- If roots are real & repeated:

$$\text{i.e. } D(s) = (s - \alpha)^a (s - \lambda_1)(s - \lambda_2) \dots \dots (s - \lambda_n)$$

$$\frac{N(s)}{D(s)} = \frac{a_0}{(s - \alpha)^a} + \frac{a_1}{(s - \alpha)^{a-1}} + \dots \dots + \frac{a_{a-1}}{(s - \alpha)} + \frac{k_1}{(s - \lambda_1)} + \dots \dots + \frac{k_c}{(s - \lambda_c)}$$

where

$$a_j = \left. \frac{1}{j!} \frac{d^j}{ds^j} [(s - \alpha)^a P(s)] \right|_{s = \alpha} \quad j = 0, 1, 2, \dots \dots a-1$$

$$K_i = p(s) \cdot (s - \lambda_i) \Big|_{s = \lambda_i}$$

$$i = 1, 2, 3, \dots, C$$

case-iii: If roots are quadratic in nature & not-repeating.

$$\text{i.e } D(s) = (a_1 s^2 + b_1 s + c_1)(a_2 s^2 + b_2 s + c_2)$$

$$\frac{N(s)}{D(s)} = \frac{k_1 s + k_2}{a_1 s^2 + b_1 s + c_1} + \frac{k_3 s + k_4}{a_2 s^2 + b_2 s + c_2}$$

case-iv: If roots are quadratic & Repeated

$$\text{i.e } D(s) = (a_1 s^2 + b_1 s + c_1)^a (a_2 s^2 + b_2 s + c_2)$$

$$\frac{N(s)}{D(s)} = \frac{\alpha_a s + \beta_a}{(a_1 s^2 + b_1 s + c_1)^a} + \frac{\alpha_{a-1} s + \beta_{a-1}}{(a_1 s^2 + b_1 s + c_1)^{a-1}} + \dots + \dots + \frac{\alpha_1 s + \beta_1}{(a_1 s^2 + b_1 s + c_1)} + \frac{k_1 s + k_2}{(a_2 s^2 + b_2 s + c_2)}$$

case-v: If roots are complex-conjugates

$$\text{i.e } D(s) = [s - (\alpha_1 + j\beta_1)][s - (\alpha_1 - j\beta_1)][s - (\alpha_2 + j\beta_2)][s - (\alpha_2 - j\beta_2)]$$


$$\frac{N(s)}{D(s)} = \frac{k_1}{[s - (\alpha_1 + j\beta_1)]} + \frac{k_1^*}{[s - (\alpha_1 - j\beta_1)]} + \frac{k_2}{[s - (\alpha_2 + j\beta_2)]} + \frac{k_2^*}{[s - (\alpha_2 - j\beta_2)]}$$

where $k_1^* \rightarrow$ complex conjugate of k_1

Laplace Transform Application to circuit elements:-

I] Resistor:-

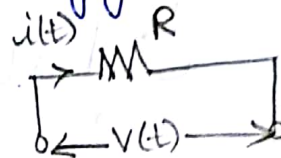Resistor dissipates the energy
 $v(t)$ voltage across 'R'
 $i(t)$ current through 'R'



time domain
equivalent circuit

According to Ohm's law

$$v(t) = Ri(t)$$

$$L[v(t)] = L[Ri(t)]$$

$$\boxed{V(s) = RI(s)}$$

where $V(s)$ is L.T of $v(t)$
 & $I(s)$ is L.T of $i(t)$

II] Capacitor:-

$$i(t) = C \frac{dv(t)}{dt}$$


Apply LT

$$I(s) = C [sV(s) - v(0^+)]$$


$$I(s) = CSV(s) - Cv(0^+)$$

$$I(s) = \frac{V(s)}{Z(s)} + [-Cv(0^+)]$$

$$\text{where } Z(s) = \frac{1}{Cs}$$

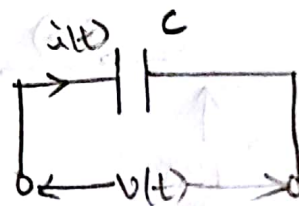

cap

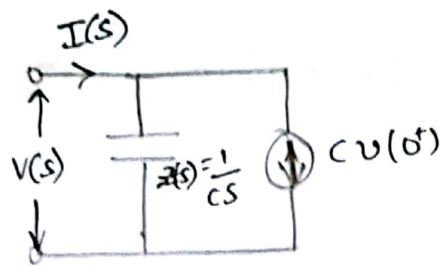

Norton's equivalent ckt in freq. domain

$$v(t) = \frac{1}{C} \int_0^t i(t) dt$$

Apply LT


$$V(s) = \frac{1}{C} \left\{ \frac{I(s)}{s} + \frac{i'(0^+)}{s} \right\}$$

$$\begin{aligned} i'(t) &= \int_0^t i(t) dt \\ &= Cv(t) \end{aligned}$$

$$V(s) = \frac{I(s)}{Cs} + \frac{Cv(0^+)}{Cs}$$


$$V(s) = \underbrace{Z(s) \cdot I(s)}_{V_1} + \underbrace{\frac{v(0^+)}{s}}_{V_2}$$

where $Z(s) = \frac{1}{Cs}$

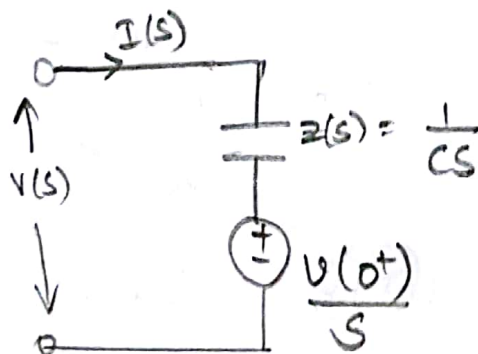

Thevenin's equivalent in freq. domain

III. Inductor:-

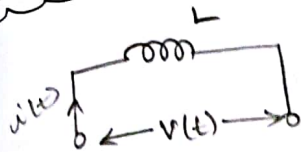

$$V(t) = L \frac{di(t)}{dt}$$


Apply L.T

$$V(s) = L \{ s I(s) - i(0^+) \}$$

$$V(s) = s L I(s) - L i(0^+)$$

$$V(s) = \underbrace{Z(s) \cdot I(s)}_{V_1} + \underbrace{[-L i(0^+)]}_{V_2}$$

where $Z(s) = LS$

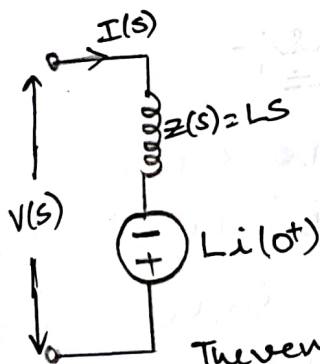

Thevenin's equivalent in freq. domain.

Now,

$$i(t) = \frac{1}{L} \left\{ \int_0^t v(t) dt \right\}$$

$$\begin{aligned} \dot{v}(t) &= \int_0^t v(t) dt \\ &= L i(t) \end{aligned}$$

$$I(s) = \frac{1}{L} \left\{ \frac{V(s)}{s} + \frac{\dot{v}(0^+)}{s} \right\}$$


$$I(s) = \frac{V(s)}{sL} + \frac{L i(0^+)}{sL}$$

$$I(s) = \frac{V(s)}{sL} + \frac{i(0^+)}{s}$$

$$I(s) = \underbrace{Y(s) \cdot V(s)}_{I_1} + \underbrace{\frac{i(0^+)}{s}}_{I_2}$$

where
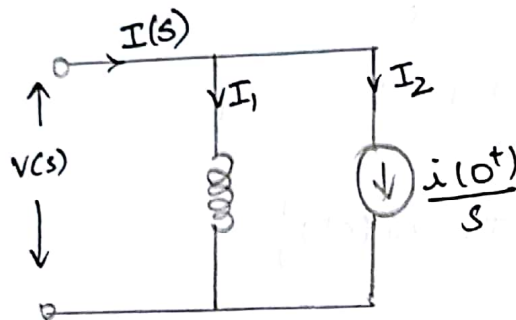
$$Y(s) = \frac{1}{sL} \Rightarrow Z(s) = sL$$



Norton's equivalent in freq. domain.

Initial Conditions:-

* Inductor does not allow sudden changes in current i.e. if ' i_0 ' is initial current through the inductor before the application of voltage source $v(t)$ at $t=0$ i.e. $i(0^-) = i_0$. Then, after applying voltage source ' $v(t)$ ' at $t=0$ is

$$i(0^+) = i(0^-) = i_0$$


* Capacitor does not allow sudden changes in voltage i.e.

$$v(0^+) = v(0^-) = v_0$$

where ' v_0 ' is initial voltage across capacitor before $v(t)$ is applied.

L.T of $u(t)$ i.e $L[u(t)] = \frac{1}{s}$
 " " $\delta(t)$ i.e $L[\delta(t)] = 1$

RL-Series Circuit Analysis:-

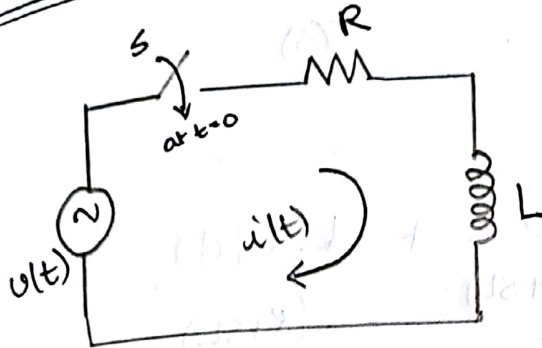

Let $i(0^-)$ is initial current through inductor

Apply KVL;

$$v(t) = Ri(t) + L \frac{di}{dt}$$

$$V(s) = RI(s) + sLI(s) - i(0^-)L$$

since for inductor: $i(0^+) = i(0^-)$


$$V(s) = I(s)[R + sL] - Li(0^-) \rightarrow (2)$$

A) considering step input:-

$$v(t) = v_0 u(t)$$

$$L[v(t)] = v_0 \{u(t)\}$$

$$V(s) = \frac{v_0}{s}$$

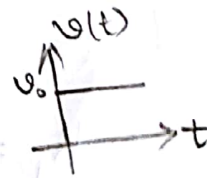

subⁿ in eqⁿ ②

$$\frac{V_0}{s} = I(s)(R+SL) - Li(0^+)$$

$$\frac{\left(\frac{V_0}{s}\right) + Li(0^+)}{R+SL} = I(s)$$

$$I(s) = \frac{V_0}{s(R+SL)} + \frac{Li(0^+)}{(R+SL)}$$

$$I(s) = \frac{(V_0/L)}{s\left(s + \frac{R}{L}\right)} + \frac{i(0^+)}{\left(s + \frac{R}{L}\right)} \longrightarrow \textcircled{3}$$

Now consider,

$$\frac{\left(\frac{V_0}{L}\right)}{s\left(s + \frac{R}{L}\right)} = \frac{k_1}{s} + \frac{k_2}{s + \frac{R}{L}}$$

$$k_1 = \frac{\left(\frac{V_0}{L}\right)}{s\left(s + \frac{R}{L}\right)} \cdot (s) \Big|_{s=0}$$

$$k_1 = \frac{\left(\frac{V_0}{\cancel{L}}\right)}{\left(\frac{\cancel{R}}{\cancel{L}}\right)} = \frac{V_0}{R}$$

$$k_2 = \frac{\left(\frac{V_0}{L}\right)}{s\left(s + \frac{R}{L}\right)} \cdot \left(s + \frac{R}{L}\right) \Big|_{s = -\frac{R}{L}} \Rightarrow k_2 = -\frac{V_0}{R}$$

From eqn ③

$$I(s) = \frac{\left(\frac{V_0}{R}\right)}{s} + \frac{\left(-\frac{V_0}{R}\right)}{s + \frac{R}{L}} + \frac{i(0^+)}{s + \frac{R}{L}}$$

Apply ILT

$$i(t) = \frac{V_0}{R} u(t) - \frac{V_0}{R} e^{-\frac{R}{L}t} u(t) + i(0^+) e^{-\frac{R}{L}t}$$

$$\text{if } i(0^+) = 0$$

$$i(t) = \frac{V_0}{R} (1 - e^{-\frac{R}{L}t}) u(t)$$

let $\tau = \frac{L}{R} \rightarrow$ called time constant of RL series R/L

$$i(t) = \frac{V_0}{R} (1 - e^{-\frac{t}{\tau}}) u(t)$$

$$\text{if } t = \tau$$


$$i(t) = \frac{V_0}{R} (1 - e^{-1}) u(t)$$

$$i(t) = 0.633 \frac{V_0}{R}$$

8) Considering Impulse Input :-

$$V(t) = V_0 \delta(t)$$

$$L[V(t)] = V_0 L[\delta(t)]$$

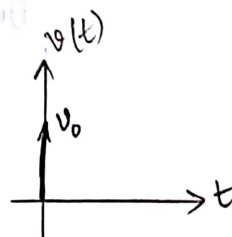

$$\boxed{V(s) = V_0}$$

subⁿ in eqn (2)

$$V_0 = I(s)(R + sL) - Li(0^+)$$

$$I(s) = \frac{[V_0 + Li(0^+)]}{R + sL}$$

$$I(s) = \frac{V_0 + Li(0^+)}{L(s + \frac{R}{L})}$$

$$I(s) = \frac{\left[\frac{V_0}{L} + i(0^+)\right]}{\left(s + \frac{R}{L}\right)}$$

Apply ILT


$$i(t) = \left[\frac{V_0}{L} + i(0^+)\right] e^{-\frac{R}{L}t} \cdot u(t)$$

$$\text{If } i(0^+) = 0$$

$$\boxed{i(t) = \frac{V_0}{L} e^{-\frac{t}{\tau}} \cdot u(t)}$$

$$\text{where } \boxed{\tau = \frac{L}{R}} \text{ (time const)}$$

RC-series circuit :-

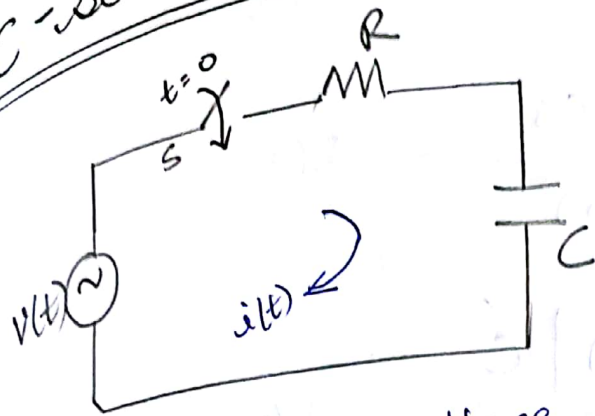

$V(0^+)$ is initial voltage across capacitor

Apply KVL

$$V(t) = Ri(t) + \frac{1}{C} \int_0^t i(t) dt$$

Apply LT

$$V(s) = RI(s) + \frac{1}{C} \left[\frac{I(s)}{s} + \frac{i'(0^+)}{s} \right]$$

$$V(s) = RI(s) + \frac{I(s)}{Cs} + \frac{C V(0^+)}{Cs}$$

$$V(s) = I(s) \left[R + \frac{1}{Cs} \right] + \frac{V(0^+)}{s}$$

$$\left[V(s) - \frac{V(0^+)}{s} \right] = I(s) \left[R + \frac{1}{Cs} \right] \rightarrow (4)$$

considering step input:-

$$V(t) = V_0 u(t) \Rightarrow V(s) = \frac{V_0}{s}$$

subⁿ in eqn (4)

$$\frac{V_0}{s} - \frac{v(0^+)}{s} = I(s) \left[\frac{1+RCs}{Cs} \right]$$

$$\frac{[V_0 - v(0^+)] Cs'}{s(1+RCs)} = I(s)$$

$$\frac{[V_0 - v(0^+)] C'}{R[s + \frac{1}{RC}]} = I(s)$$

$$\therefore I(s) = \left[\frac{V_0 - v(0^+)}{R} \right] \cdot \frac{1}{(s + \frac{1}{RC})}$$

Apply ILT

$$i(t) = \left[\frac{V_0 - v(0^+)}{R} \right] e^{-\frac{t}{RC}} \cdot u(t)$$


$$i(t) = \left[\frac{V_0 - v(0^+)}{R} \right] \cdot e^{-\frac{t}{\tau}} \cdot u(t)$$

where $\tau = RC$ (time constant)

if $v(0^+) = v(0^-) = 0$

$$\therefore i(t) = \frac{V_0}{R} \cdot e^{-t/\tau} u(t)$$

g) RC Series

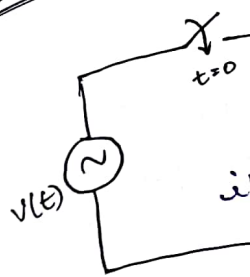

Let $v(t) =$
Apply

$V(s)$

from


$[V(s) -$

$I(s)$

$I(s)$

I

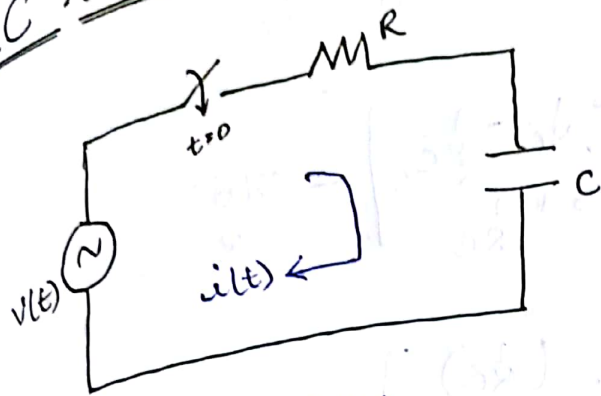8] RC series circuit with Impulse Input:-



let $v(t) = V_0 \delta(t)$

Apply L.T

$$V(s) = V_0$$

$$[\because L\{\delta(t)\} = 1]$$

from eqn (A)

$$\left[V(s) - \frac{V(0^+)}{s} \right] = I(s) \left[R + \frac{1}{Cs} \right]$$

$$I(s) = \frac{\left[V_0 - \frac{V(0^+)}{s} \right]}{R + \frac{1}{Cs}}$$

$$I(s) = \frac{V_0}{\left(R + \frac{1}{Cs}\right)} - \frac{V(0^+)}{s \left(R + \frac{1}{Cs}\right)}$$

$$I(s) = \frac{V_0 Cs}{(RCs + 1)} - \frac{V(0^+) Cs}{s(1 + RCs)}$$

$$I(s) = \frac{V_0 Cs}{R \left[s + \frac{1}{RC} \right]} - \frac{V(0^+)}{R \left[s + \frac{1}{RC} \right]}$$

$$I(s) = \frac{V_0 s}{R(s + \frac{1}{RC})} - \frac{V(0^+)}{R(s + \frac{1}{RC})}$$

$$I(s) = \frac{V_0}{R} \left[\frac{s + \frac{1}{RC} - \frac{1}{RC}}{s + \frac{1}{RC}} \right] - \frac{V(0^+)}{R} \cdot \frac{1}{(s + \frac{1}{RC})}$$

$$I(s) = \frac{V_0}{R} \left[1 - \frac{(\frac{1}{RC})}{(s + \frac{1}{RC})} \right] - \frac{V(0^+)}{R} \cdot \frac{1}{(s + \frac{1}{RC})}$$

Apply ILT

$$i(t) = \frac{V_0}{R} \left[\delta(t) - \frac{1}{RC} e^{-\frac{1}{RC}t} \right] - \frac{V(0^+)}{R} e^{-\frac{1}{RC}t}$$

$$\text{if } V(0^+) = V(0^-) = 0$$

$$\therefore i(t) = \frac{V_0}{R} \left[\delta(t) - \frac{1}{RC} e^{-\frac{1}{RC}t} \right]$$




NOTE:-

→ Assume if switch 'S' is moved from position ① to position ② at $t=0$ then the conditions exist [behaviour of inductor or capacitor] at $t=0^+$ (instant after switch 'S' is moved) are called as "Initial Conditions".



→ One switch is moved the conditions

exist at $t = \infty$ is called "final conditions"
 or "steady state conditions"




Capacitor [C]:

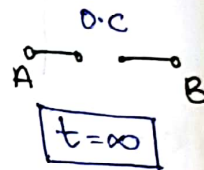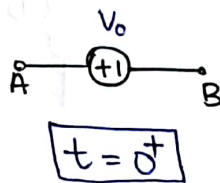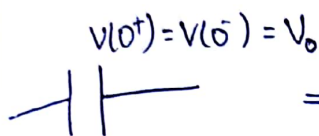



$v(0^+) = v(0^-) = 0$

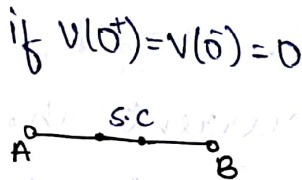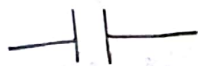



Inductor [L]:

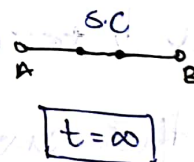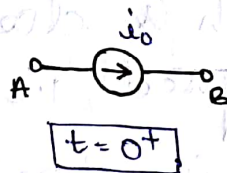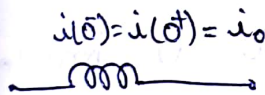


$i(0^+) = i(0^-) = 0$

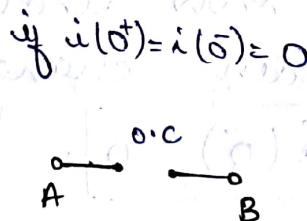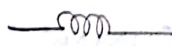

Resistor [R]:

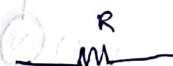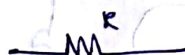

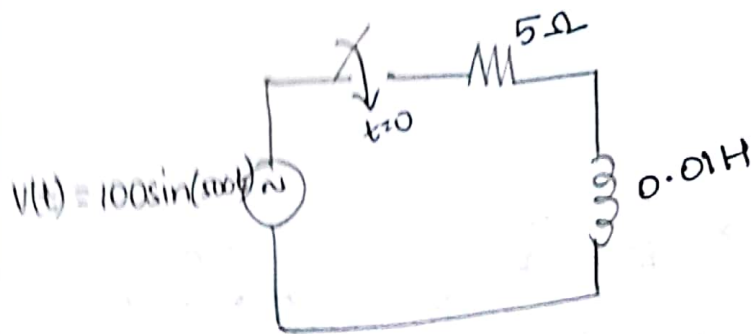problem:
Q1) Consider the RL ckt shown below




Initially inductor is deenergised & switch 'S' is closed at $t=0$. Then, calculate current through the ckt after switch is closed.

Sol:- Before switch is closed at $t=0$, inductor is de-energised i.e. $i(0^-) = 0$

→ After switch is closed at $t=0$, as already we know inductor doesn't allow sudden changes in "current"

i.e. $i(0^+) = i(0^-) = 0$

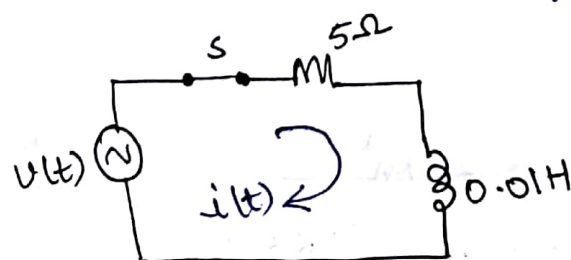→ After switch is closed (the ckt becomes) some current $i(t)$ is flowing



Apply KVL ;

$$v(t) = 5i(t) + L \frac{di(t)}{dt}$$

$$100 \sin(500t) = 5i(t) + 0.01 \frac{di(t)}{dt}$$

Apply L.T

$$100 \left[\frac{500}{s^2 + 500^2} \right] = 5I(s) + 0.01 [sI(s) - i(0^+)]$$

$$\frac{100 \times 500}{s^2 + 500^2} = 5I(s) + 0.01 sI(s) - 0$$

$$I(s) [0.01s + 5] = \frac{5 \times 10^4}{s^2 + 500^2}$$

$$I(s) = \frac{5 \times 10^4}{(s^2 + 500^2)(0.01s + 5)}$$

$$I(s) = \frac{5 \times 10^4 \times 10^2}{(s^2 + 500^2)(s + 500)}$$

0.01 common. $\frac{1}{0.01} = 10^2$

$$I(s) = \frac{5 \times 10^6}{(s + 500)(s + j500)(s - j500)}$$

$$\begin{aligned} s^2 + 500^2 &= 0 \\ s^2 &= -500^2 \\ s &= \pm j500 \end{aligned}$$

(P.F)

$$\therefore I(s) = \frac{k_1}{(s + 500)} + \frac{k_2}{(s + j500)} + \frac{k_2^*}{(s - j500)}$$

using case - ①
↳ case - ④ (α = 0)

$$\frac{N(s)}{D(s)} \bigg|_{s = -500}$$

$$K_1 = \frac{5 \times 10^6}{(s+500)(s+500)} \times (s+500) \quad \Big|_{s=-500}$$

$$K_1 = \frac{5 \times 10^6}{(500+500)}$$

$$\boxed{K_1 = 10}$$

$$\text{Now; } K_2 = \frac{5 \times 10^6}{(s+500)(s-j500)} \quad \Big|_{s=-j500}$$

$$= \frac{5 \times 10^6}{(500-j500)(-2j \times 500)}$$

$$= \frac{5 \times 10^6}{500(1-j) \times (-1000j)} \quad \left(\frac{-1}{j} = j \right)$$

$$= \frac{j 5 \times 10^6}{500(1-j) \times 1000}$$

$$= \frac{j 5 \times 10^6}{5 \times 10^5(1-j)} \times \frac{1+j}{1+j}$$

$$\boxed{K_2 = -5 + 5j}$$

$$\therefore \boxed{K_2^* = -5 - 5j}$$

1900, usual.

$$\Rightarrow I(s) = \frac{10}{s+500} + \frac{-5+5j}{(s+j500)} + \frac{-5-5j}{s-j500}$$

Apply ILT

$$i(t) = 10e^{-500t} + (-5+5j)e^{-j500t} + (-5-5j)e^{j500t}$$

$$i(t) = 10e^{-500t} - 2 \times 5 \left[\frac{e^{-j500t} + e^{j500t}}{2} \right] - 2j \times 5j \left[\frac{e^{j500t} - e^{-j500t}}{2j} \right]$$

$$i(t) = 10e^{-500t} - 10 \cos 500t + 10 \sin 500t$$


$$\cos \theta = \frac{e^{j\theta} + e^{-j\theta}}{2}$$

$$\sin \theta = \frac{e^{j\theta} - e^{-j\theta}}{2j}$$


$$e^{j\theta} = \cos \theta + j \sin \theta$$

$$e^{-j\theta} = \cos \theta - j \sin \theta$$

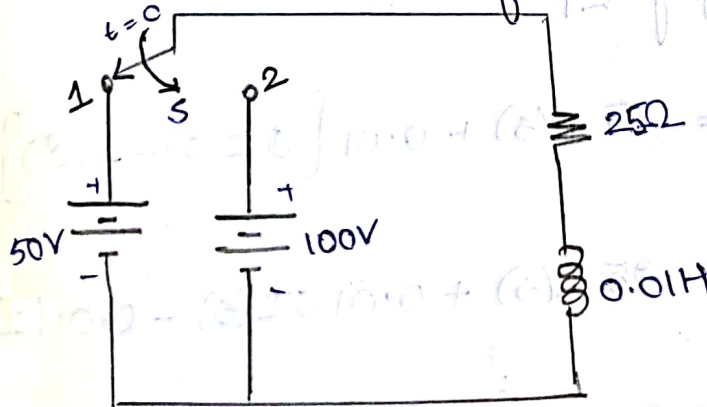2) In the series RL ckt shown below, switch 'S' is at position '1' for a long time to establish steady state condition & at $t=0$ switch is moved from position ① to pos. ②. Find the resultant current after switch is moved.




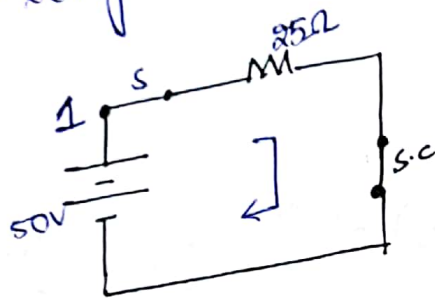sol:
 → If the switch is at position '1' for a long time then the ckt is:



$$i(0^-) = \frac{50}{25} \Rightarrow 2A$$

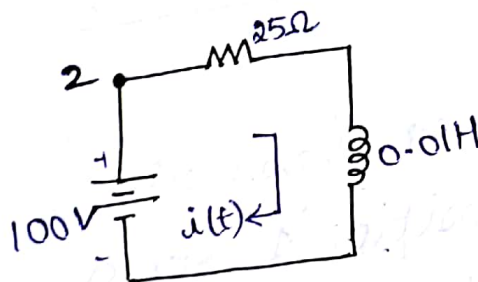→ After switch is moved to position '2' then
 $i(0^+) = i(0^-) = 2A$



Apply KVL;

$$100 = 25 i(t) + 0.01 \frac{di(t)}{dt}$$

Apply LT

$$\frac{100}{s} = 25 I(s) + 0.01 [s I(s) - i(0^+)]$$

$$\frac{100}{s} = 25 I(s) + 0.01 s I(s) - 0.01(2)$$

$$\frac{100}{s} + 0.02 = [25 + 0.01s] I(s)$$

$$I(s) = \frac{100 \times 10^2}{s(s+2500)} + \frac{2}{(s+2500)} \quad \text{--- (1)}$$

(P.F)

consider

$$\frac{10^4}{s(s+2500)} = \frac{k_1}{s} + \frac{k_2}{s+2500}$$

$$\text{Now: } k_1 = \frac{10^4}{s(s+2500)} \times s \Big|_{s=0}$$

$$= \frac{10^2 \times 10^2}{25 \times 10^2}$$

$$\boxed{k_1 = 4}$$

$$\text{Now: } k_2 = \frac{10^4}{s(s+2500)} \times (s+2500) \Big|_{s=-2500}$$

$$k_2 = \frac{10^4}{s} \Big|_{s=-2500}$$


$$= - \frac{10^2 \times 10^2}{25 \times 10^2}$$

$$\boxed{k_2 = -4}$$

$$i(t) = 4 - 2e^{-2500t}$$

Compok-
~~Step~~

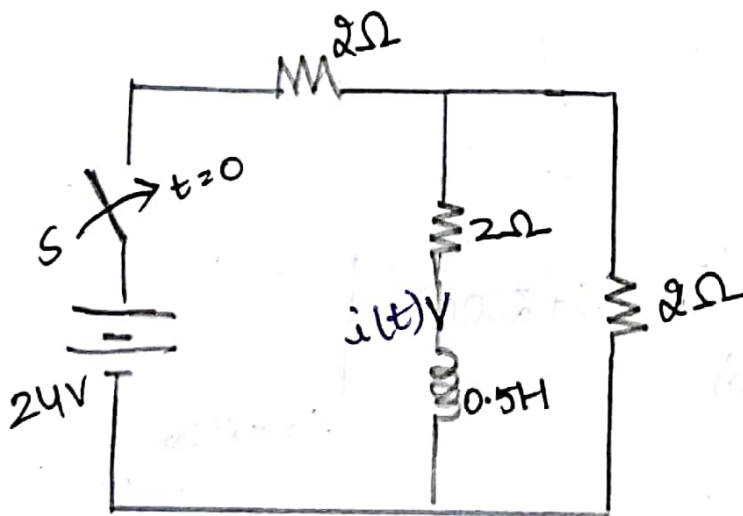
Q. Calculate steady state current $i(t)$ for the network shown below by assuming initial zero conditions.



Sol:-

→ Before switch is closed $i(0^-) = 0$

→ After switch 's' is closed

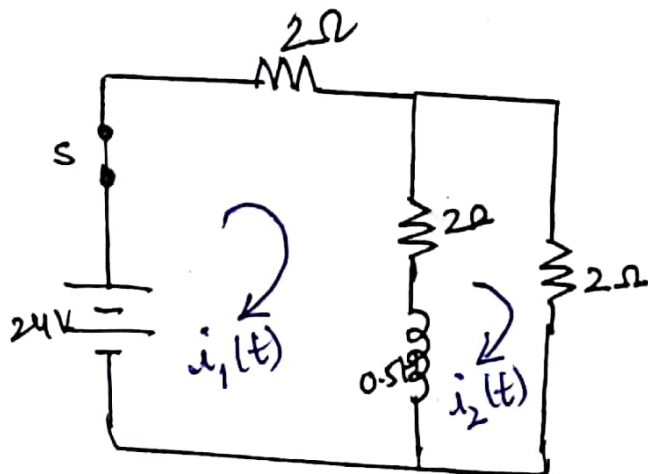

KVL, for loop ①

$$24 = 2i_1(t) + 2[i_1(t) - i_2(t)] + 0.5 \frac{d}{dt} [i_1(t) - i_2(t)]$$

$$24 = 2i_1(t) + 2i_1(t) - 2i_2(t) + 0.5 \frac{di_1(t)}{dt} - 0.5 \frac{di_2(t)}{dt}$$

Apply L.T

$$\frac{24}{s} = 4I_1(s) - 2I_2(s) + 0.5[sI_1(s) - i_1(0^+)] - 0.5[sI_2(s) - i_2(0^+)]$$

$$\frac{24}{s} = 4I_1(s) - 2I_2(s) + 0.5[sI_1(s)] + 0.5[sI_2(s)]$$

$$\frac{24}{s} = I_1(s)[4 + 0.5s] - I_2(s)[2 + 0.5s]$$

Mul by '2' on b.s to get rid of 0.5

$$\frac{48}{s} = (8 + s)I_1(s) - (4 + s)I_2(s) \longrightarrow \text{①}$$

Now, KVL for loop ②

$$2[i_2(t) - i_1(t)] + 2i_2(t) + 0.5 \frac{d}{dt} [i_2(t) - i_1(t)] = 0$$

$$-2i_1(t) + 4i_2(t) - 0.5 \frac{di_1(t)}{dt} + 0.5 \frac{di_2(t)}{dt} = 0$$

Apply L.T

$$-2I_1(s) + 4I_2(s) - 0.5sI_1(s) + 0.5sI_2(s) = 0$$

$$-(2 + 0.5s)I_1(s) + (4 + 0.5s)I_2(s) = 0$$

mult by 2'

$$-(4 + s)I_1(s) + (8 + s)I_2(s) = 0 \rightarrow (2)$$

on solving (1) & (2) Solving using "Cramer's Rule."

$$\begin{bmatrix} (s+8) & -(s+4) \\ -(s+4) & (s+8) \end{bmatrix} \begin{bmatrix} I_1(s) \\ I_2(s) \end{bmatrix} = \begin{bmatrix} \frac{48}{s} \\ 0 \end{bmatrix}$$

$$\begin{aligned} |X| &= (s+8)^2 - (s+4)^2 \\ &= \cancel{s^2} + 64 + 16s - \cancel{s^2} - 16 - 8s \\ &= 8s + 48 \end{aligned}$$

$$|X| \Rightarrow 8(s+6)$$

Replace const in 1st row.

Now $|X_1| = \begin{vmatrix} \frac{48}{s} & -(s+4) \\ 0 & (s+8) \end{vmatrix}$

$$|X_1| = \frac{48}{s} (s+8) + 0$$

$$= 48 + \frac{48 \times 8}{s}$$

$$|X_1| \Rightarrow 48 + \frac{384}{s}$$

$$\text{Now } |X_2| = \begin{vmatrix} s+8 & \frac{48}{s} \\ -(s+4) & 0 \end{vmatrix}$$

$$|X_2| = 0 + (s+4) \frac{48}{s}$$

$$|X_2| = 48 + \frac{192}{s}$$

$$\text{Now } I_1(s) = \frac{|X_1|}{|X|} \Rightarrow$$

$$\frac{\cancel{48} + \frac{384}{s}}{\cancel{8}(s+6)} \Rightarrow \frac{48s+384}{s(s+6)}$$

$$\Rightarrow \frac{\frac{48}{s}(s+8)}{8(s+6)} \Rightarrow \frac{6(s+8)}{s(s+6)}$$

$$\& I_2(s) = \frac{|X_2|}{|X|} \Rightarrow$$

$$\frac{\frac{48}{s}(s+4)}{8(s+6)} = \frac{6(s+4)}{s(s+6)}$$

$$I(s) = I_1(s) - I_2(s)$$

$$= \frac{6(s+8)}{s(s+6)} - \frac{6(s+4)}{s(s+6)}$$

$$= \frac{6s+48-6s-24}{s(s+6)}$$

$$I(s) = \frac{24}{s(s+6)}$$

To get steady state condition. apply ILT to get $i(t)$ then subⁿ $t = \infty$

(5)

Applying Final Value Th.

∴ steady state current :


$$i(\infty) = \lim_{s \rightarrow 0} s I(s)$$

$$= \lim_{s \rightarrow 0} s \left[\frac{24}{s(s+6)} \right]$$


$$i(\infty) = \frac{24}{6}$$

$$i(\infty) = 4A$$

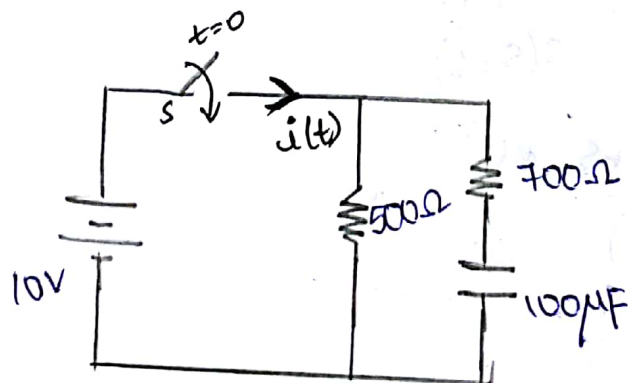Q.7 By considering zero initial conditions for the ckt shown below, supply voltage is applied at $t=0$. Then, how much time it will take to reach 25mA.



I] LT Analysis of series RLC circuit

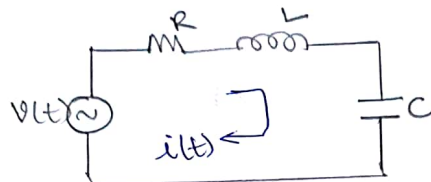

consider zero initial conditions
i.e. $v(0^+) = 0 \rightarrow$ Initial voltage across capacitor

$i(0^+) = 0 \rightarrow$ Initial current through inductor

Apply KVL

$$v(t) = Ri(t) + L \frac{di(t)}{dt} + \frac{1}{C} \int_0^t i(t) dt$$

$$V(s) = RI(s) + L[sI(s) - i(0^+)] + \frac{1}{C} \left[\frac{I(s)}{s} + \frac{v(0^+)}{s} \right]$$

$$\Rightarrow V(s) = \left[R + sL + \frac{1}{Cs} \right] I(s)$$

$$I(s) = \frac{V(s)}{R + sL + \frac{1}{Cs}}$$

$$I(s) = \frac{V(s)Cs}{1 + s^2LC + sRC}$$

$$I(s) = \frac{V(s)}{L[s^2 + \dots]}$$

$$I(s) = \frac{V(s)}{L[s^2 + \dots]}$$

also w.r.t. $\omega_0 = \frac{1}{\sqrt{LC}}$

A) Series RLC

let $v(t) = V_m \sin \omega t$

subⁿ in

$$I(s) =$$

$$I(s)$$

Roots:

$$I(s) = \frac{V(s)}{L \left[s^2 + \frac{R}{L}s + \frac{1}{LC} \right]}$$

also w.k.T for series resonance ckt

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

A) Series RLC for "step-input" :-

$$\text{let } v(t) = V_0 u(t) \Rightarrow V(s) = \frac{V_0}{s}$$

subⁿ in eqn ⑤

$$I(s) = \frac{\left(\frac{V_0}{s} \right)}{L \left[s^2 + \frac{R}{L}s + \frac{1}{LC} \right]}$$

$$I(s) = \frac{\left(\frac{V_0}{L} \right)}{\left[s^2 + \frac{R}{L}s + \frac{1}{LC} \right]} \rightarrow \textcircled{6}$$

Roots :-

$$s = \frac{-\frac{R}{L} \pm \sqrt{\left(\frac{R}{L} \right)^2 - 4 \left(\frac{1}{LC} \right)}}{2}$$

$$s = \frac{-R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

let

$$s_1 = \frac{-R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}} \quad \& \quad s_2 = \frac{-R}{2L} - \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

Now consider a parameter ' ζ ' such that

$$\zeta \omega_0 = \frac{R}{2L} \Rightarrow \zeta = \frac{R}{2L} \cdot \frac{1}{\omega_0}$$

$$\zeta = \frac{R}{2L} \cdot \sqrt{LC}$$

$$\boxed{\zeta = \frac{R}{2} \sqrt{\frac{C}{L}}} \quad \text{damping Ratio}$$

$$s_1 = -\zeta \omega_0 + \sqrt{(\zeta \omega_0)^2 - \omega_0^2} \quad ; \quad s_2 = -\zeta \omega_0 - \sqrt{(\zeta \omega_0)^2 - \omega_0^2}$$

$$\boxed{s_1 = -\zeta \omega_0 + \omega_0 \sqrt{\zeta^2 - 1} \quad ; \quad s_2 = -\zeta \omega_0 - \omega_0 \sqrt{\zeta^2 - 1}}$$

From eqn (6)

$$\begin{aligned} I(s) &= \frac{\left(\frac{V_0}{L}\right)}{(s-s_1)(s-s_2)} = \frac{k_1}{(s-s_1)} + \frac{k_2}{(s-s_2)} \\ &= k_1(s-s_2) + k_2(s-s_1) \end{aligned}$$

$$r_1 = \frac{V_0}{2\omega_0 L \sqrt{\beta^2 - 1}}$$

$$r_2 = \frac{-V_0}{2\omega_0 L \sqrt{\beta^2 - 1}}$$

sub r_1 & r_2 in $I(s)$

$$I(s) = \frac{V_0}{2\omega_0 L \sqrt{\beta^2 - 1}} \left[\frac{1}{s-s_1} - \frac{1}{s-s_2} \right]$$

apply ILT

$$i(t) = \frac{V_0}{2\omega_0 L \sqrt{\beta^2 - 1}} [e^{s_1 t} - e^{s_2 t}]$$

$$i(t) = \frac{V_0}{2\omega_0 L \sqrt{\beta^2 - 1}} \left[e^{-(\omega_0 + \omega_0 \sqrt{\beta^2 - 1})t} - e^{-(\omega_0 - \omega_0 \sqrt{\beta^2 - 1})t} \right]$$

$$i(t) = \frac{V_0 e^{-\omega_0 t}}{2\omega_0 L \sqrt{\beta^2 - 1}} \left[e^{(\omega_0 \sqrt{\beta^2 - 1})t} - e^{-(\omega_0 \sqrt{\beta^2 - 1})t} \right]$$

→ (7)

$$S = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

let

$$S_1 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}} \quad \& \quad S_2 = -\frac{R}{2L} - \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

Now consider a parameter ' ζ ' such that

$$\zeta \omega_0 = \frac{R}{2L} \Rightarrow \zeta = \frac{R}{2L} \cdot \frac{1}{\omega_0}$$

$$\zeta = \frac{R}{2L} \cdot \sqrt{LC}$$

$$\boxed{\zeta = \frac{R}{2} \sqrt{\frac{C}{L}}} \quad \text{damping Ratio}$$

$$S_1 = -\zeta \omega_0 + \sqrt{(\zeta \omega_0)^2 - \omega_0^2} \quad ; \quad S_2 = -\zeta \omega_0 - \sqrt{(\zeta \omega_0)^2 - \omega_0^2}$$

$$\frac{V_0}{L} = k_1 (s_1 - s_2)$$

$$k_1 = \frac{V_0}{2\omega_0 L \sqrt{\zeta^2 - 1}}$$

$$k_2 = \frac{-V_0}{2\omega_0 L \sqrt{\zeta^2 - 1}}$$

subⁿ k_1 & k_2 in $I(s)$

$$\therefore I(s) = \frac{V_0}{2\omega_0 L \sqrt{\zeta^2 - 1}} \left[\frac{1}{s - s_1} - \frac{1}{s - s_2} \right]$$

apply ILT

$$i(t) = \frac{V_0}{2\omega_0 L \sqrt{\zeta^2 - 1}} \left[e^{s_1 t} - e^{s_2 t} \right]$$

$$i(t) = \frac{V_0}{2\omega_0 L \sqrt{\zeta^2 - 1}} \left[e^{-(3\omega_0 + \omega_0 \sqrt{\zeta^2 - 1})t} - e^{-(3\omega_0 - \omega_0 \sqrt{\zeta^2 - 1})t} \right]$$

$$i(t) = \frac{V_0 e^{-3\omega_0 t}}{2\omega_0 L \sqrt{\zeta^2 - 1}} \left[e^{(\omega_0 \sqrt{\zeta^2 - 1})t} - e^{-(\omega_0 \sqrt{\zeta^2 - 1})t} \right]$$

case-i):

$$\text{if } \zeta > 1 \quad \text{or} \quad \frac{R}{2L} > \frac{1}{\sqrt{LC}}$$

[over damped conditions]

eqn ① becomes

$$i(t) = \frac{V_0 e^{-\zeta \omega_0 t}}{\omega_0 L \sqrt{\zeta^2 - 1}} \sinh(\omega_0 \sqrt{\zeta^2 - 1} t)$$

case-ii):

$$\zeta < 1 \quad \text{or} \quad \frac{R}{2L} < \frac{1}{\sqrt{LC}} \quad [\text{under damped}]$$

$$\sqrt{\zeta^2 - 1} = j \sqrt{1 - \zeta^2}$$

from eqn ①

$$i(t) = \frac{V_0 e^{-\zeta \omega_0 t}}{j \omega_0 L \sqrt{1 - \zeta^2}} \left\{ \frac{e^{j(\omega_0 \sqrt{1 - \zeta^2}) t} - e^{-j(\omega_0 \sqrt{1 - \zeta^2}) t}}{2j} \right\}$$

$$i(t) = \frac{V_0 e^{-\zeta \omega_0 t}}{\omega_0 L \sqrt{1 - \zeta^2}} \sin(\omega_0 \sqrt{1 - \zeta^2} t)$$

case-iii):

$$\zeta = 1 \quad \text{or} \quad \frac{R}{2L} = \frac{1}{\sqrt{LC}} \quad [\text{critically damped}]$$

from eqn ⑥

$$\frac{R}{2L} = \frac{1}{\sqrt{LC}} \Rightarrow \frac{R}{2L} = \frac{1}{\sqrt{LC}} \Rightarrow (2\omega_0)$$

$$I(s) = \frac{\left(\frac{V_0}{L}\right)}{s^2 + \frac{R}{L}s + \omega_0^2}$$

$$= \frac{\left(\frac{V_0}{L}\right)}{s^2 + 2\omega_0 s + \omega_0^2}$$

$$I(s) = \frac{\left(\frac{V_0}{L}\right)}{(s + \omega_0)^2}$$

Apply ILT

$$i(t) = \frac{V_0}{L} t \cdot e^{-\omega_0 t}$$

b) Series RLC for "Impulse-Input" :-

$$\text{let } v(t) = V_0 \delta(t) \Rightarrow V(s) = V_0$$

from eqn ⑤

$$I(s) = \frac{V_0 s}{L \left[s^2 + \frac{R}{L}s + \frac{1}{LC} \right]} \longrightarrow \textcircled{8}$$

$$I(s) = \frac{\left(\frac{V_0}{L}\right) s}{(s - s_1)(s - s_2)}$$

where

$$s_1 = -\frac{R}{2L} + \omega_0 \sqrt{\frac{R^2}{4L^2} - 1} \quad ; \quad s_2 = -\frac{R}{2L} - \omega_0 \sqrt{\frac{R^2}{4L^2} - 1}$$

$$\gamma = \frac{R}{2} \sqrt{\frac{C}{L}}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$I(s) = \frac{k_1}{(s-s_1)} + \frac{k_2}{(s-s_2)}$$

$$k_1 = \left. \frac{\left(\frac{V_0}{L}\right)s}{s-s_2} \right|_{s=s_1} \quad k_2 = \left. \frac{\left(\frac{V_0}{L}\right)s}{s-s_1} \right|_{s=s_2}$$

$$k_1 = \frac{\left(\frac{V_0}{L}\right)s_1}{2\omega_0 L \sqrt{\gamma^2 - 1}}$$

$$k_2 = \frac{-\left(\frac{V_0}{L}\right)s_2}{2\omega_0 L \sqrt{\gamma^2 - 1}}$$

subⁿ k_1 & k_2 in $I(s)$

$$\therefore I(s) = \frac{V_0}{2\omega_0 L \sqrt{\gamma^2 - 1}} \left[\frac{s_1}{s-s_1} - \frac{s_2}{s-s_2} \right]$$

$$\dot{I}(s) = \frac{V_0}{2\omega_0 L \sqrt{\gamma^2 - 1}} \left[s_1 e^{s_1 t} - s_2 e^{s_2 t} \right]$$

$$\dot{I}(t) = \frac{V_0}{2\omega_0 L \sqrt{\gamma^2 - 1}} \left\{ \cancel{\left(\frac{1}{\gamma} \right)} \cancel{\omega_0} e^{s_1 t} + \cancel{\omega_0} \sqrt{\gamma^2 - 1} e^{s_2 t} \right\}$$

$$i(t) = \frac{V_0}{2\omega_0 L \sqrt{\gamma^2 - 1}} \left\{ \left(-\gamma \omega_0 + \omega_0 \sqrt{\gamma^2 - 1} \right) e^{-\gamma \omega_0 t} \cdot e^{\omega_0 \sqrt{\gamma^2 - 1} t} + \left(\gamma \omega_0 + \omega_0 \sqrt{\gamma^2 - 1} \right) e^{-\gamma \omega_0 t} \cdot e^{-(\omega_0 \sqrt{\gamma^2 - 1}) t} \right\}$$

$$i(t) = \frac{V_0 e^{-\zeta \omega_0 t}}{2 \omega_0 L \sqrt{\zeta^2 - 1}} \left\{ -\zeta \omega_0 \left[e^{(\omega_0 \sqrt{\zeta^2 - 1})t} - e^{-(\omega_0 \sqrt{\zeta^2 - 1})t} \right] + \omega_0 \sqrt{\zeta^2 - 1} \left[e^{(\omega_0 \sqrt{\zeta^2 - 1})t} + e^{-(\omega_0 \sqrt{\zeta^2 - 1})t} \right] \right\}$$

→ ⑨

case-i: $\zeta > 1$ [over damped conditions]

from eqn ⑨

$$i(t) = \frac{V_0 e^{-\zeta \omega_0 t}}{\omega_0 L \sqrt{\zeta^2 - 1}} \left\{ -\zeta \omega_0 \sinh[(\omega_0 \sqrt{\zeta^2 - 1})t] + \omega_0 \sqrt{\zeta^2 - 1} \cosh[(\omega_0 \sqrt{\zeta^2 - 1})t] \right\}$$

case-ii: $\zeta < 1$ [underdamped conditions]

$$\sqrt{\zeta^2 - 1} = j \sqrt{1 - \zeta^2}$$

from eqn ⑨

$$i(t) = \frac{V_0 e^{-\zeta \omega_0 t}}{2 j \omega_0 L \sqrt{1 - \zeta^2}} \left\{ -\zeta \omega_0 \left[e^{j(\omega_0 \sqrt{1 - \zeta^2})t} - e^{-j(\omega_0 \sqrt{1 - \zeta^2})t} \right] + j \omega_0 \sqrt{1 - \zeta^2} \left[e^{j(\omega_0 \sqrt{1 - \zeta^2})t} + e^{-j(\omega_0 \sqrt{1 - \zeta^2})t} \right] \right\}$$

$$i(t) = \frac{V_0 e^{-\zeta \omega_0 t}}{\omega_0 L \sqrt{1 - \zeta^2}} \left\{ -\zeta \omega_0 \sin(\omega_0 \sqrt{1 - \zeta^2} t) + \omega_0 \sqrt{1 - \zeta^2} \cos(\omega_0 \sqrt{1 - \zeta^2} t) \right\}$$

Case-iii:-

$$\zeta = 1 \quad \text{or} \quad \frac{R}{2L} = \frac{1}{\sqrt{LC}} \quad [\text{critically damped}]$$

from eqn (8)

$$I(s) = \frac{\left(\frac{V_0}{L}\right)s}{\left[s^2 + \frac{R}{L}s + \frac{1}{LC}\right]}$$

$$I(s) = \frac{\left(\frac{V_0}{L}\right)s}{s^2 + 2\omega_0 s + \omega_0^2}$$

$$I(s) = \frac{\left(\frac{V_0}{L}\right)s}{(s+\omega_0)^2} = \frac{k_1}{(s+\omega_0)^2} + \frac{k_2}{(s+\omega_0)}$$

$$k_1 = \left(\frac{V_0}{L}\right)s \bigg|_{s=-\omega_0} \quad \bigg| \quad k_2 = \frac{d}{ds} \left[\left(\frac{V_0}{L}\right)s \right] \bigg|_{s=-\omega_0}$$

$$k_1 = \frac{-\omega_0 V_0}{L}$$

$$k_2 = \frac{V_0}{L}$$

$$\therefore I(s) = \frac{V_0}{L} \left[\frac{-\omega_0}{(s+\omega_0)^2} + \frac{1}{(s+\omega_0)} \right]$$

$$i(t) = \frac{V_0}{L} \left[e^{-\omega_0 t} - \omega_0 t \cdot e^{-\omega_0 t} \right]$$

$$\boxed{i(t) = \frac{V_0}{L} e^{-\omega_0 t} [1 - \omega_0 t]}$$

* NETWORK FUNCTIONS *


Network is a interconnection of different electrical elements.

Generally a N/W is represented by a box.

port:-

A pair of terminals across which a device is connected.

Based on ports, N/Ws are classified into

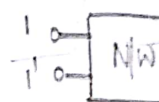→ one-port N/W → 

→ Two-port N/W → 

→ Multi-port N/W → 

Network Function:-


It is defined as a funcⁿ that relates voltages currents at diff parts of N/W.

Generally, a N/W funcⁿ is denoted by:-

$$F(s) = \frac{N(s)}{D(s)} \rightarrow \begin{matrix} N \rightarrow \text{polynomial} \\ D \rightarrow \text{polynomial} \end{matrix}$$

Network functions of one-port N/w:-

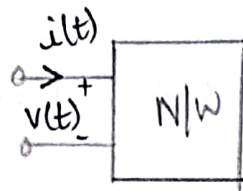Consider a one-port N/w with zero initial conditions & "no-independent" internal sources (except controlled sources) as shown in fig. below:-




$$\frac{L[v(t)]}{L[i(t)]}$$

Transform Impedance Fun^c:- $Z(s) = \frac{V(s)}{I(s)}$

Transform Admittance Fun^c:- $Y(s) = \frac{I(s)}{V(s)} \Rightarrow \frac{1}{Z(s)}$

Network functions of two-port N/w's:-

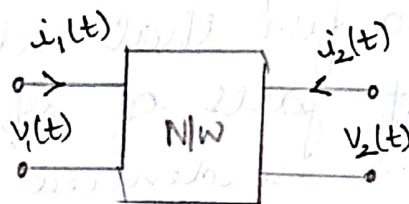consider a two-port N/w as shown in fig with zero initial conditions & "no-independent" internal sources (except controlled sources)



i) Transfer Functions:- (defined for two diff ports)

Transfer Function for a two-port N/w is defined as the ratio of L.T of o/p to i/p @ i/p to o/p.

Voltage Transfer Functions :-

$$G_{12} = \frac{V_1(s)}{V_2(s)} \quad ; \quad G_{21} = \frac{V_2(s)}{V_1(s)}$$

Current Transfer Functions :-

$$\alpha_{12} = \frac{I_1(s)}{I_2(s)} \quad ; \quad \alpha_{21} = \frac{I_2(s)}{I_1(s)}$$

Transfer Impedance Functions :-

$$Z_{12} = \frac{V_1(s)}{I_2(s)} \quad ; \quad Z_{21} = \frac{V_2(s)}{I_1(s)}$$

Transfer Admittance Functions :-

$$Y_{12} = \frac{I_1(s)}{V_2(s)} \quad ; \quad Y_{21} = \frac{I_2(s)}{V_1(s)}$$

(ii) Driving point Functions :- (defined for same ports)

Driving pt. Impedance Functions :-

$$Z_{11}(s) = \frac{V_1(s)}{I_1(s)} \quad ; \quad Z_{22}(s) = \frac{V_2(s)}{I_2(s)}$$

Driving pt. Admittance Functions :-

$$Y_{11}(s) = \frac{I_1(s)}{V_1(s)} \quad ; \quad Y_{22}(s) = \frac{I_2(s)}{V_2(s)}$$

Def: Ratio of L.T of voltage to current / current to volt at same port.

problem 1

Q1. Calculate the driving pt Impedance of the following one-port N/w.

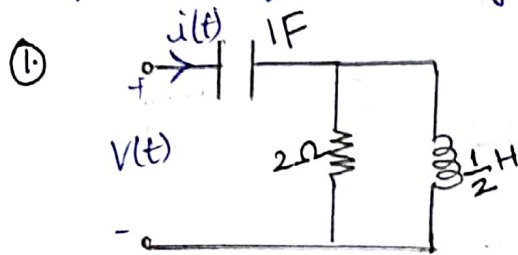


fig (a)


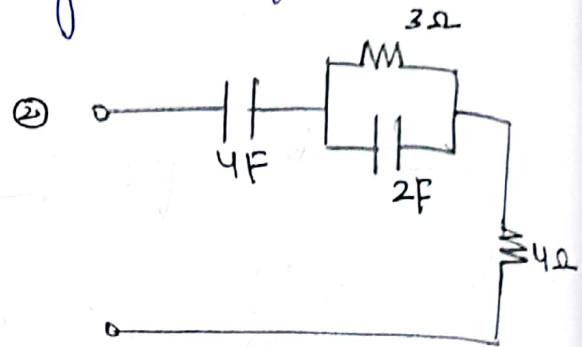


fig (b)

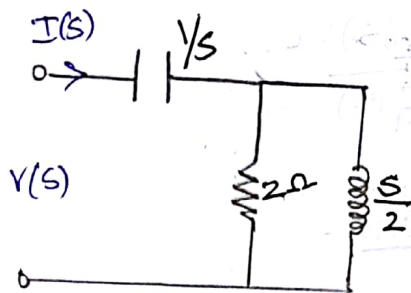converting into 'freq' domain (i.e Apply L.T)



$$Z(s) = \frac{V(s)}{I(s)} \Rightarrow \frac{1}{s} + (2) \parallel \left(\frac{s}{2}\right)$$


$$Z(s) \Rightarrow \frac{1}{s} + \frac{2(\frac{s}{2})}{2 + \frac{s}{2}}$$

$$Z(s) = \frac{1}{s} + \frac{2s}{s+4}$$

$$Z(s) = \frac{s+4+2s^2}{s(s+4)}$$

$$Z(s) = \frac{2s^2+s+4}{s^2+4s}$$

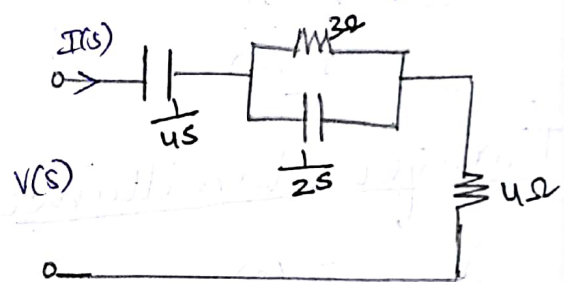converting into 'freq' domain (i.e Apply LT)



$$Z(s) = \frac{V(s)}{I(s)} = \frac{1}{4s} + (3) \parallel \left(\frac{1}{2s}\right) + 4$$



$$Z(s) = \frac{1}{4s} + 4 + \frac{\frac{3}{2s}}{3 + \frac{1}{2s}}$$

$$Z(s) = \frac{1}{4s} + 4 + \frac{3}{6s+1}$$

$$Z(s) = \frac{6s+1+4(6s+1)(4s)+12s}{(6s+1)(4s)}$$


$$Z(s) =$$

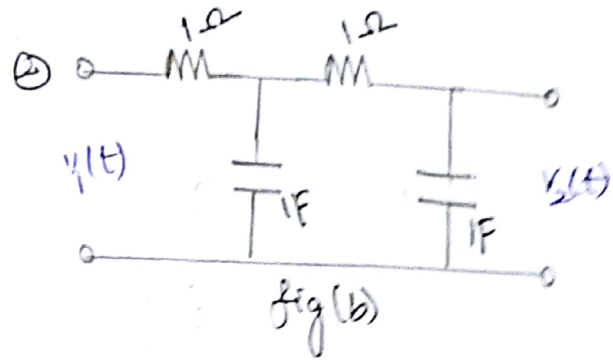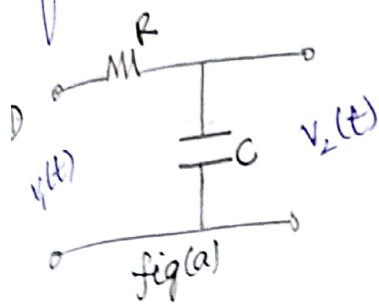22) Determine voltage Transfer Ratio $G_{21}(s)$ for the following w/w.



∴ Voltage Transfer Ratio $G_{21}(s) = \frac{V_2(s)}{V_1(s)}$

Apply LT to fig(a)

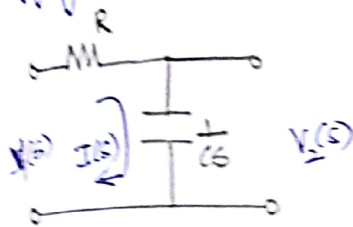

$$V_1(s) = RI(s) + \frac{1}{s}I(s)$$


$$V_1(s) = \left(R + \frac{1}{s}\right) I(s) \quad \rightarrow \textcircled{1}$$

$$V_2(s) = \frac{1}{s} I(s) \quad \rightarrow \textcircled{2}$$

$$\therefore \text{Rat.}, G_{21}(s) = \frac{V_2(s)}{V_1(s)} = \frac{\frac{1}{s} I(s)}{\left(R + \frac{1}{s}\right) I(s)}$$

$$G_{21}(s) = \frac{1}{1 + RCs}$$

Apply L.T to fig(b)

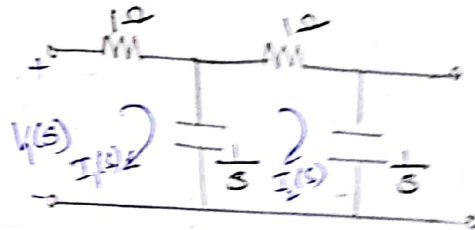

KVL to $\textcircled{1}$

$$-V_1(s) + I_1(s)(1) + [I_1(s) - I_2(s)] \frac{1}{s} = 0$$

$$V_1(s) = I_1(s) \left[1 + \frac{1}{s}\right] - I_2(s) \frac{1}{s}$$

$\rightarrow \textcircled{1}$

KVL to $\textcircled{2}$

$$\frac{1}{s} [I_1(s) - I_2(s)] + I_2(s) + \frac{1}{s} I_2(s) = 0$$

$$\frac{1}{s} I_1(s) - \frac{1}{s} I_2(s) + I_2(s) + \frac{1}{s} I_2(s) = 0$$

$$I_1(s) \left[1 + \frac{1}{s} + \frac{1}{s}\right] - I_2(s) = 0$$

$$I_2(s) \left[\frac{s+2}{s} \right] - \frac{I_1(s)}{s} = 0 \rightarrow \textcircled{2}$$

$$V_2(s) = I_2(s) \times \frac{1}{s} \rightarrow \textcircled{3}$$

Now, from eqn ②

$$I_2(s) = \frac{I_1(s)}{s} \times \frac{s}{(s+2)}$$

$$I_2(s) = I_1(s) \times \left(\frac{1}{s+2} \right)$$

from eqn ①

$$V_1(s) = I_1(s) \left(\frac{s+1}{s} \right) - \frac{1}{s} \left(\frac{I_1(s)}{s+2} \right)$$

$$V_1(s) = \frac{I_1(s)}{s} \left[(s+1) - \frac{1}{s+2} \right]$$

$$= \frac{I_1(s)}{s} \left[\frac{(s+1)(s+2) - 1}{s+2} \right]$$



$$V_1(s) = \frac{I_1(s)}{s} \left[\frac{s^2 + 3s + 1}{(s+2)} \right] \rightarrow \textcircled{4}$$

Now ③ ÷ ④ we get


$$\frac{V_2(s)}{V_1(s)} \Rightarrow G_{21}(s) = \frac{I_1(s)}{\frac{I_1(s)(s^2 + 3s + 1)}{s(s+2)}}$$

$$G_{21}(s) = \frac{1}{s^2 + 3s + 1}$$

Q7 Calculate for the following

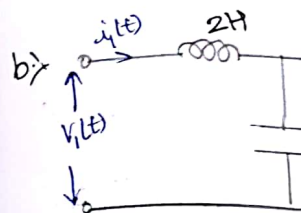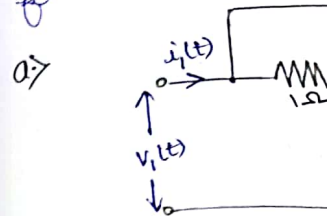

Q8 ① Apply L.T

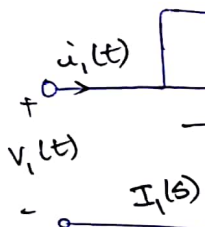

KVL to

$$V_1(s) =$$



$$V_1(s) =$$

loop ② :-


$$V_2(s)$$

$$V_2(s)$$

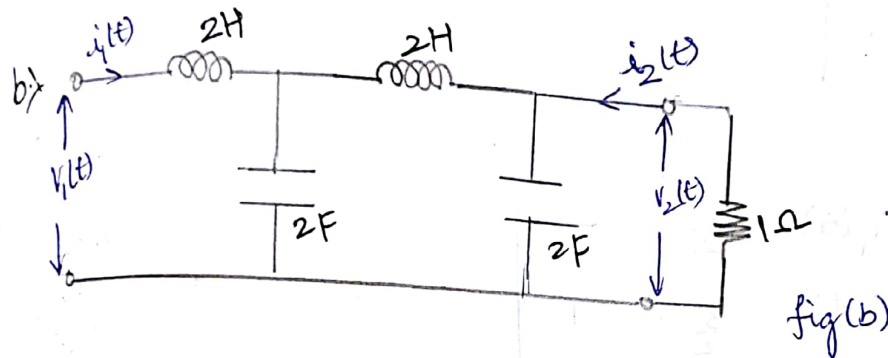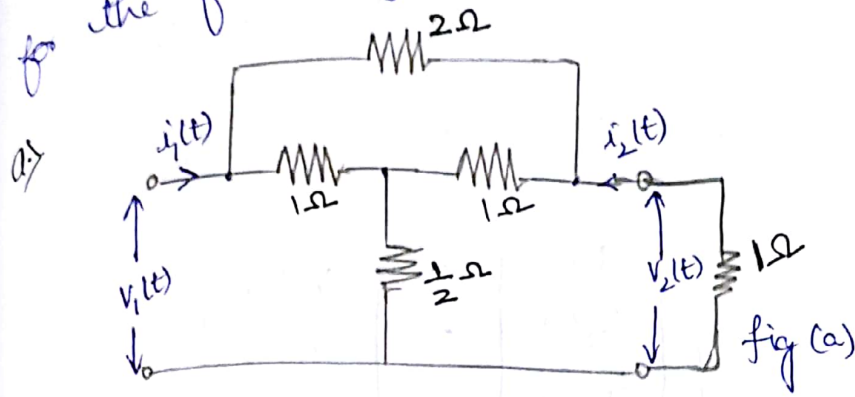Q3) Calculate current Transfer Ratio $\alpha_{21} = \frac{I_2(s)}{I_1(s)}$ for the following N/w:



Q4) Apply L.T to fig(a)

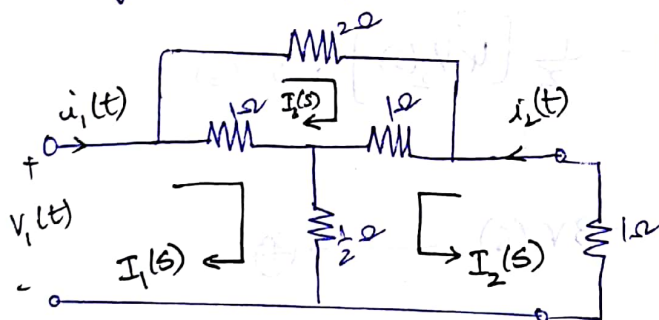

$$\frac{v_2(s)}{I_2(s)} = -1$$

$$v_2(s) = -I_2(s)$$

KVL to loop ① :-

$$V_1(s) = [I_1(s) - I_3(s)] + \frac{1}{2} [I_1(s) + I_2(s)]$$

$$V_1(s) = \frac{3}{2} I_1(s) + \frac{1}{2} I_2(s) - I_3(s) \longrightarrow ①$$

loop ② :-

$$V_2(s) = 1 [I_2(s) + I_3(s)] + \frac{1}{2} [I_2(s) + I_1(s)]$$

$$V_2(s) = \frac{1}{2} I_1(s) + \frac{3}{2} I_2(s) + I_3(s) \longrightarrow ②$$

loop ③:-

$$I_3(s) - I_1(s) + 2I_3(s) + (I_3(s) + I_2(s)) = 0$$

$$-I_1(s) + I_2(s) + 4I_3(s) = 0 \longrightarrow \textcircled{3}$$

$$\begin{bmatrix} \frac{3}{2} & \frac{1}{2} & -1 \\ \frac{1}{2} & \frac{3}{2} & 1 \\ -1 & 1 & 4 \end{bmatrix} \begin{bmatrix} I_1(s) \\ I_2(s) \\ I_3(s) \end{bmatrix} = \begin{bmatrix} V_1(s) \\ V_2(s) \\ 0 \end{bmatrix}$$

$$\boxed{|X| = 4}$$

$$X_1(s) = \begin{vmatrix} V_1(s) & \frac{1}{2} & -1 \\ V_2(s) & \frac{3}{2} & 1 \\ 0 & 1 & 4 \end{vmatrix}$$

$$|X_1(s)| = V_1(s)[5] - \frac{1}{2}[4^2 V_2(s)] - V_2(s)$$

$$|X_1(s)| = 5V_1(s) - 3V_2(s) \longrightarrow \textcircled{4}$$

$$X_2(s) = \begin{vmatrix} \frac{3}{2} & V_1(s) & -1 \\ \frac{1}{2} & V_2(s) & 1 \\ -1 & 0 & 4 \end{vmatrix}$$

$$|X_2(s)| = \left(\frac{3}{2}\right)[4^2 V_2(s)] - V_1(s)[2+1] - 1[V_2(s)]$$

$$|X_2(s)| = -3V_1(s) + 5V_2(s) \longrightarrow \textcircled{5}$$

$$X_3(s) = \begin{vmatrix} \frac{3}{2} & \frac{1}{2} & V_1(s) \\ \frac{1}{2} & \frac{3}{2} & V_2(s) \\ -1 & 1 & 0 \end{vmatrix}$$

$$\begin{aligned} |X_3(s)| &= \frac{3}{2} [V_2(s)] - \frac{1}{2} [V_2(s)] + V_1(s) \left[\frac{1}{2} + \frac{3}{2} \right] \\ &= -\frac{3V_2(s)}{2} - \frac{V_2(s)}{2} + 2V_1(s) \\ &= V_2(s) + 2V_1(s) \end{aligned}$$

$$I_3(s) = \frac{2V_1(s) + 2V_2(s)}{4} \longrightarrow \textcircled{6}$$

$$I_1(s) = \frac{X_1(s)}{|X|} \Rightarrow \frac{5V_1(s) - 3V_2(s)}{4} \longrightarrow \textcircled{1}$$

$$I_2(s) = \frac{X_2(s)}{|X|} \Rightarrow \frac{-3V_1(s) + 5V_2(s)}{4} \longrightarrow \textcircled{2}$$

$$\therefore \alpha_{21} = \frac{I_2(s)}{I_1(s)} \Rightarrow \frac{-3V_1(s) + 5V_2(s)}{5V_1(s) - 3V_2(s)}$$

from ②

$$4I_2(s) = -3V_1(s) + (-5I_2(s))$$

$$9I_2(s) = -3V_1(s)$$

$$I_2(s) = -\frac{1}{3}V_1(s)$$

$$\Rightarrow V_1(s) = -3I_2(s)$$

from ①

$$4I_1(s) = 5[-3I_2(s)] - 3[-I_2(s)]$$

$$4I_1(s) = -15I_2(s) + 3I_2(s)$$

$$4I_1(s) = -12I_2(s)$$

$$\boxed{\frac{I_2(s)}{I_1(s)} = -\frac{1}{3}} \Rightarrow A_{21}$$

Poles & Zeros of Network Fun^c:-

Any n/w function can be denoted as

$$F(s) = \frac{N(s)}{D(s)}$$

where $N(s)$ - Nr polynomial
 $D(s)$ - Dr polynomial

So $F(s)$ can be written as:-

$$F(s) = \frac{N(s)}{D(s)} = \frac{a_n s^n + a_{n-1} s^{n-1} + \dots + a_1 s + a_0}{b_m s^m + b_{m-1} s^{m-1} + \dots + b_1 s + b_0}$$
$$= k \frac{(s-z_1)(s-z_2) \dots (s-z_n)}{(s-p_1)(s-p_2) \dots (s-p_m)}$$

where $\boxed{k = \frac{a_n}{b_m}}$ called Scale Factor / Gain Factor

$\rightarrow Z_i, i = 1, 2, 3, \dots, n \rightarrow \text{roots of } N(s) \rightarrow \text{zeros}$
 $\rightarrow P_j, j = 1, 2, 3, \dots, m \rightarrow \text{roots of } D(s) \rightarrow \text{poles}$

$\rightarrow Z_i$ & P_j are roots of $N(s)$ & $D(s)$ polynomials respectively & these may be real or complex conjugate

$\rightarrow$ At $s = Z_i, i = 1, 2, \dots, n$ $F(s) = 0$

i.e. N/w fun^c becomes zero $\therefore s = Z_i$ are called "zeros" or zero frequencies

$\rightarrow$ At $s = P_j, j = 1, 2, 3, \dots, m$ $F(s) = \infty$

i.e. N/w fun^c becomes undefined $\therefore s = P_j$ are called "poles" or pole frequencies.

Any system can be described by differential eqns.

1) Find the poles & zeros of the system described by following D.E.

$$1) \frac{d^2 y}{dt^2} + 5 \frac{dy}{dt} + 6y = 2 \frac{dx}{dt} + x$$

$\therefore$ apply L.T

$$L\left\{\frac{dy}{dt}\right\} = sY(s) - y(0)$$

$$s^2 Y(s) + 5sY(s) + 6Y(s) = 2sX(s) + X(s)$$

$$Y(s) [s^2 + 5s + 6] = (2s + 1)X(s)$$

$$\frac{Y(s)}{X(s)} = \frac{2s + 1}{s^2 + 5s + 6}$$

$$F(s) = \frac{Y(s)}{X(s)} = \frac{2(s + \frac{1}{2})}{s^2 + 3s + 2}$$


$$F(s) = \frac{(s + \frac{1}{2})}{(s+3)(s+2)}$$

$\therefore s = -3$ & -2 are "poles" of $F(s)$

& $s = -\frac{1}{2}$ are "zero" of $F(s)$

& $K = 2$ is the gain factor.

pole-zero plot:-

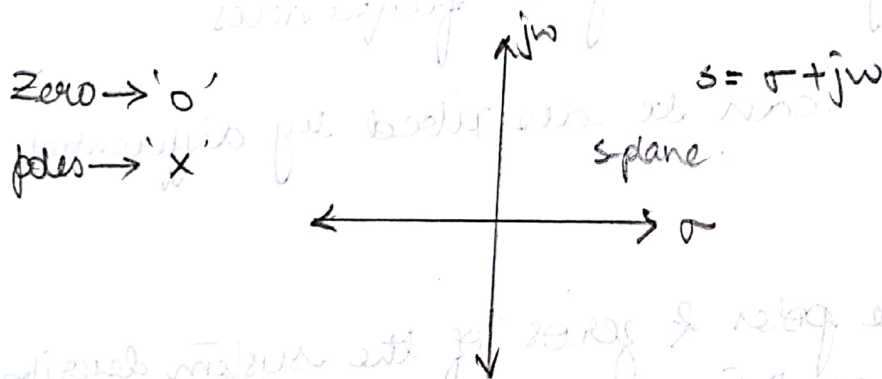

Significance of pole-Zeros for Nw Fun^{cs}:-

$$\text{let } F(s) = \frac{N(s)}{D(s)}$$

i) For driving pt Impedance fun^c:-

$$F(s) = \frac{N(s)}{D(s)} \Rightarrow Z(s) = \frac{V(s)}{I(s)}$$

poles means roots of $I(s)$
 zeros " roots of $V(s)$

→ at poles $I(s) = 0 \Rightarrow \boxed{Z(s) = \infty}$
 i.e. N/w funcⁿ $Z(s)$ becomes O.C at poles

→ at zeros $V(s) = 0 \Rightarrow \boxed{Z(s) = 0}$
 i.e. N/w funcⁿ $Z(s)$ becomes S.C at zeros.

ii) For deriving pt. Admittance funcⁿ:-

$$F(s) = Y(s) = \frac{I(s)}{V(s)}$$

poles means roots of $V(s)$
 zeros " roots of $I(s)$


→ at poles $V(s) = 0 \Rightarrow \boxed{Y(s) = \infty}$
 i.e. N/w funcⁿ $Y(s)$ becomes S.C at poles

→ at zeros $I(s) = 0 \Rightarrow \boxed{Y(s) = 0}$
 i.e. N/w funcⁿ $Y(s)$ becomes O.C at zeros.

iii) Transfer Functions:-

consider voltage ratio transfer funcⁿ

$$G_{21}(s) = \frac{V_2(s)}{V_1(s)}$$

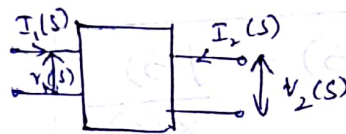

$$V_2(s) = G_{21}(s) \cdot V_1(s)$$

$$V_2(s) = \underbrace{\sum_{i=1}^n \frac{K_i}{(s-p_i)}}_{\text{part-①}} + \underbrace{\sum_{j=1}^m \frac{K_j}{(s-p_j)}}_{\text{part-②}}$$

① From part-①; $s = p_i, i = 1, 2, \dots, n$ are poles of new funcⁿ $G_{21}(s)$ & these are called "free oscillation" or "Natural oscillations". This oscillation exist without applying i/p also.

② From part-②; $s = p_j, j = 1, 2, 3, \dots, n$ are poles of new funcⁿ $V_2(s)$ & these are called "Forced oscillations".

③ K_i & K_j defines the magnitude of free & forced oscillations.

System Function: $[H(s)]$

It is defined as ratio of L.T of o/p to L.T of i/p & is denoted by " $H(s)$ ".



$$H(s) = \frac{Y(s)}{X(s)}$$

also

$$Y(s) = H(s) \cdot X(s)$$

$$Y(s) = \sum_{i=1}^n \frac{K_i}{(s-p_i)} + \sum_{j=1}^m \frac{K'_j}{(s-p'_j)} \rightarrow \textcircled{1}$$

$$y(t) = \sum_{i=1}^n K_i e^{p_i t} + \sum_{j=1}^m K'_j e^{p'_j t} \rightarrow \textcircled{2}$$

if $X(s) = 1$ i.e. $x(t) = \delta(t) \rightarrow$ unit impulse
 $L[x(t)] = 1$

from eqn ①

$$Y(s) = H(s) = \sum_{i=1}^n \frac{K_i}{(s-p_i)}$$

$$h(t) = y(t) = \sum_{i=1}^n K_i e^{p_i t}$$

→ Natural Response of a system can be explained as a system response to its impulse input.

→ Natural Response is also called "Impulse response" or "Force-free response" or "Transient response".

System Stability & poles locations:-

For a linear system to be stable, the following conditions must be satisfied:

$$\sum_{i=1}^n \lim_{t \rightarrow \infty} k_i e^{P_i t} = 0$$

i.e. P_i must be $-ve$. Therefore all poles are left half of the s -plane.

Restriction on location of poles & zeros in the s -plane for Driving pt. Fun^c:

(a) Conditions for a driving pt. Fun^c:

i) The coefficients of $N(s)$ & $D(s)$ must be real & $+ve$

ii) Complex & imaginary parts of poles must be conjugate

iii) The real parts of poles & zeros must be either zero or $-ve$. ($-ve$ half of s -plane)

iv) If the real part is zero then the pole or zero must be simple. i.e. not-repeated.

v) polynomials $N(s)$ & $D(s)$ must not have missing terms from highest order to lowest order unless all even terms (or odd terms) becomes zero. $s^3 + s^2 + 1$ X (missing s) or $(s^2 + 1) \sqrt{}$ $(s^3 + 1) \sqrt{}$

vi) The ^{highest} degree of $N(s)$ & $D(s)$ may differ by 'zero' or '1'

the lowest degree of $N(s)$ & $D(s)$ may differ by zero or '1'

check whether the following fun^s are valid driving fun^s or not.

i) $F(s) = \frac{s^4 + 2s^3 - 2s + 1}{s^3 + s^2 - 2s + 12} \rightarrow \text{"Invalid"}$
(involves -ve) 1st cond

ii) $F(s) = \frac{s^2 + s + 2}{s^4 + 5s^3 + 6s} \rightarrow \text{"Invalid"}$
(by 6th cond)

iii) $F(s) = \frac{s^2 + 5s + 4}{s^2 + 6s + 10} \rightarrow \text{"Valid"}$

Necessary conditions for Transfer Fun^s:-

(a)

Restriction on location of poles & zeroes in s-plane for Transfer Fun^s:-

i)

i, to iv, same points

- v) The polynomial $D(s)$ may not have missing terms b/w highest order to lowest order unless all even terms or odd terms are missing
- vi) The polynomial $N(s)$ may have missing terms b/w highest order to lowest order.
- vii) The degree of $N(s)$ may be as small as "zero" & independent of $D(s)$
- viii) For Voltage Transfer Ratios (G') & Current Transfer Ratios (X'), the maximum degree of $N(s)$ is the degree of $D(s)$.
- ix) For Transfer Impedance Fun^{cs} & Admittance func^s the maximum degree of $N(s)$ is degree of $D(s) + 1$ ($n \leq m+1$)