

UNIT - II

* FILTERS *

Filter:- A filter is a NPW which allows ^{desired} wanted frequencies & blocks the ^{undesired} frequencies.

- The Range of frequencies that can be allowed is called "Transmission Band" or "pass band".
- The Range of frequencies that can be blocked are called "stop Band" or "Attenuation band".
- Filters consists atleast one 'pass band' & atleast one 'stop band'.

Classification of Filters:-

① Depending on Structures or Shapes:
i) π -section ii) T-section iii) L-section

② Depending on Components used:
i) Active Filters ii) passive Filters.

③ Depending on frequencies allowed:

i) LPF ii) HPF iii) BPF iv) BRF / BEF
low pass Filter High pass F Band Pass F Band Rejected Filter, Band Stop


Based on the Relation b/w series Arm Impedance (Z_1) & shunt Arm Impedance (Z_2):

- (i) Constant - K Filters / prototype filters
- (ii) M-derived Filters


* → The frequencies which can isolate the stop band & pass bands are called "cut-off frequencies".

Characteristics:-


1) High pass Filter (HPF):

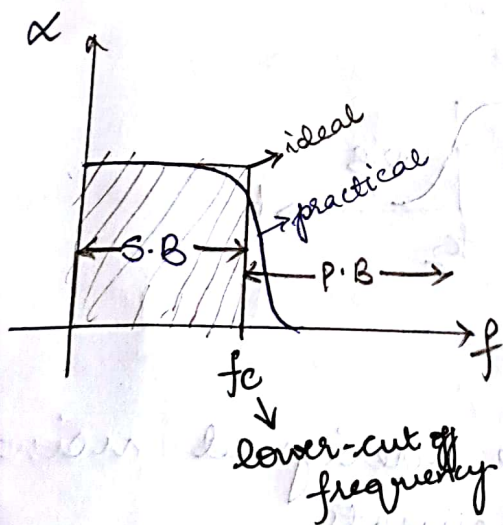


2) Low pass Filter (LPF):

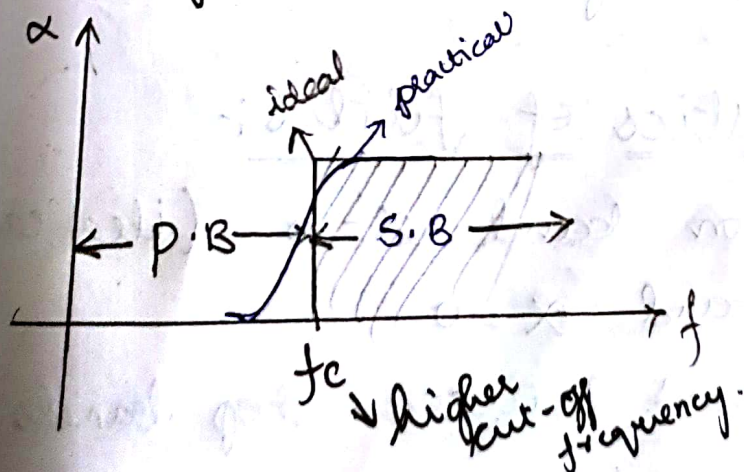

3.) Band pass Filter (BPF):

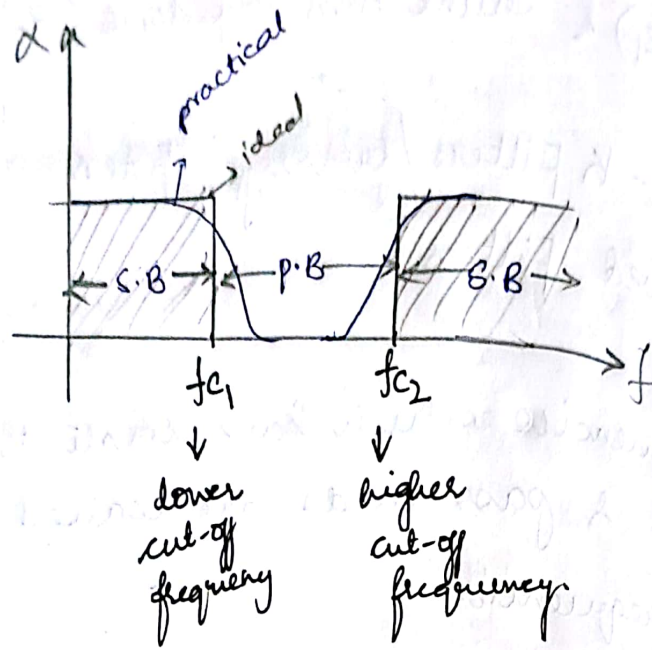

4.) Band Reject Filter (BRF):

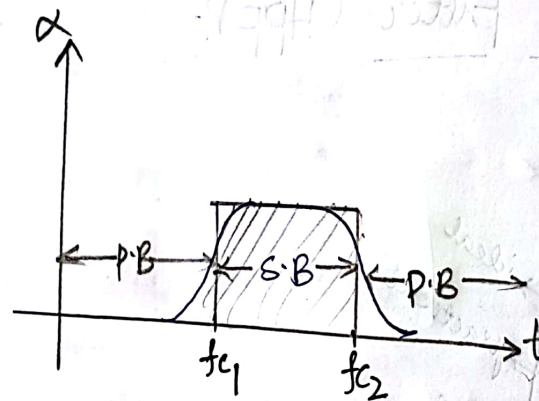

Note:-

passive Filters are designed using purely reactive elements

ex:- Inductors, capacitors.

Characteristics of Filters:-

- i) In attenuation band $\alpha = \infty$ (ideal case)
- In pass band $\alpha = 0$
- Sharp transitions between stop bands

2 pass bands

Condition for cut-off frequencies of a filter:-

if $Z_1 \rightarrow$ series arm impedance
 $Z_2 \rightarrow$ shunt " "

w.k.T

$$\cosh(p) = 1 + \frac{Z_1}{2Z_2}$$

w.k.T $p = \alpha + j\beta$

↓ ↓

Attenuation const phase shift

$$\cosh(\alpha + j\beta) = 1 + \frac{Z_1}{2Z_2}$$

$$\cosh \alpha \cdot \cosh(j\beta) + \sinh \alpha \cdot \sinh(j\beta) = 1 + \frac{Z_1}{2Z_2}$$

$$\cosh \alpha \cdot \cos \beta + j \sinh \alpha \cdot \sin \beta = 1 + \frac{Z_1}{2Z_2}$$

Since $1 + \frac{Z_1}{2Z_2}$ is a real value

$$\boxed{\cosh \alpha \cosh \beta = 1 + \frac{Z_1}{2Z_2}} \rightarrow \textcircled{1A}$$

$$\boxed{\sinh \alpha \cdot \sin \beta = 0} \rightarrow (18)$$

From eqn (18)

$$\begin{array}{l} \sinh(\alpha) = 0 \quad \text{or} \quad \sin \beta = 0 \\ \downarrow \quad \quad \quad \downarrow \\ \text{i.e. } \alpha = 0 \quad \text{or} \quad \beta = 0 \quad \text{or} \quad \pm \pi \end{array}$$

CASE-1: $\alpha = 0$ [pass bands]

from eqn (A)

$$\cosh(0) = 1$$

$$\cos \beta = 1 + \frac{z_1}{2z_2}$$

$$\boxed{\beta = \cos^{-1} \left[1 + \frac{z_1}{2z_2} \right]} \rightarrow (2)$$

W.K.T range of $\cos \beta$ is $[-1, 1]$

$$-1 < \cos \beta < 1$$

$$-1 < 1 + \frac{z_1}{2z_2} < 1$$

$$-2 < \frac{z_1}{2z_2} < 0$$

$$\boxed{-1 < \frac{z_1}{4z_2} < 0}$$

case-ii :- $\beta = 0$ or $\pm\pi$ [stop bands]

$$\text{if } \beta = 0 \Rightarrow \cos\beta = 1$$

$$\text{if } \beta = \pm\pi \Rightarrow \cos\beta = -1$$

if $\cos\beta = 1$ i.e. $\beta = 0$:-

From eqn (1A)

$$\cosh\alpha [1] = 1 + \frac{Z_1}{2Z_2}$$

$$\alpha = \cosh^{-1} \left[1 + \frac{Z_1}{2Z_2} \right]$$

w.k.t range of $\cosh\alpha$ is $[1, \infty)$

$$1 < \cosh\alpha < \infty$$

$$1 < 1 + \frac{Z_1}{2Z_2} < \infty$$

$$0 < \frac{Z_1}{2Z_2} < \infty$$

$$0 < \frac{Z_1}{4Z_2} < \infty$$

if $\cos\beta = -1$ [i.e. $\beta = \pm\pi$]:-

$$\cosh(\alpha)(-1) = 1 + \frac{Z_1}{2Z_2}$$

$$\cosh\alpha = - \left[1 + \frac{Z_1}{2Z_2} \right]$$

$$\alpha = \cosh^{-1} \left[1 + \frac{Z_1}{2Z_2} \right]$$

3)


$$1 < \cosh \alpha < \infty$$

$$1 < -\left[1 + \frac{Z_1}{2Z_2}\right] < \infty$$

$$-1 > 1 + \frac{Z_1}{2Z_2} > -\infty$$

$$-2 > \frac{Z_1}{2Z_2} > -\infty$$

$$-1 > \frac{Z_1}{4Z_2} > -\infty$$

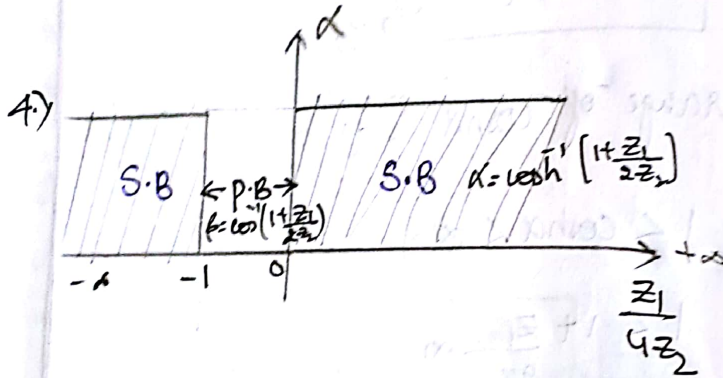

condition for deriving cut-off frequency

$$\frac{Z_1}{4Z_2} = -1$$

Constant K-Filters

If Z_1 - series arm Impedances &
 Z_2 - shunt " " "

then

In constant K-filters, Z_1 & Z_2 have relation



$$Z_1 Z_2 = R_k^2$$

where R_k is a constant called "Design impedance" / "Nominal Impedance"

→ constant k-filters are also called "prototype filters" becoz these are the fundamental blocks used for m-derived filters.

Constant-k LPF:-

Standard constant-k LPF:-

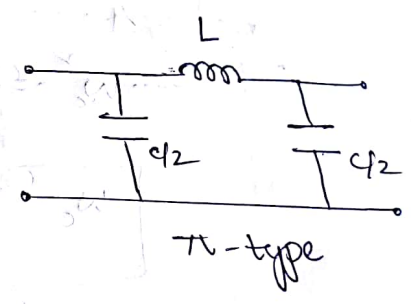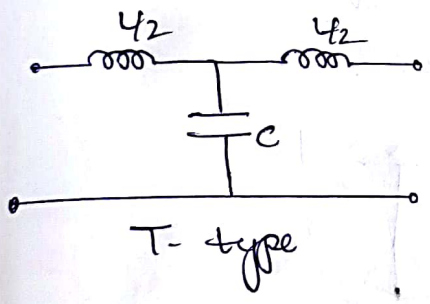

$$\frac{Z_1}{2} = \frac{j\omega L}{2}$$

$$Z_1 = j\omega L$$

$$Z_2 = \frac{1}{j\omega C}$$

w.k.T const k-filter

$$Z_1 Z_2 = R_k^2$$

$$\frac{j\omega L}{j\omega C} = R_k^2$$

$$R_{th}^2 = \frac{L}{C}$$

$$R_{th} = \sqrt{\frac{L}{C}} \quad \text{--- (4)}$$

Higher cut-off frequency (f_c);

$$\frac{Z_1}{Z_2} = -1 \quad \text{for } f = f_c$$

$$\frac{j\omega_c L}{\frac{1}{j\omega_c C}} = -1$$

$$j^2 \omega_c^2 LC = -1$$

$$\omega_c^2 = \frac{1}{LC}$$

$$\omega_c = \frac{1}{\sqrt{LC}}$$

$$f_c = \frac{\omega}{2\pi} = \frac{1}{2\pi} \left[\frac{1}{\sqrt{LC}} \right]$$

$$\therefore f_c = \frac{1}{\pi\sqrt{LC}} \quad \text{--- (5)}$$

Characteristic Impedance :- (Z_{OT}) of T-N/W:-

we know that

$$Z_{OT} = \sqrt{\frac{Z_1^2}{4} + Z_1 Z_2}$$

$$= \sqrt{\frac{(j\omega L)^2}{4} + \left[\frac{j\omega L}{j\omega C} \right]}$$

$$Z_{OT} = \sqrt{\frac{L}{C} - \frac{\omega^2 L^2}{4}}$$

$$Z_{OT} = \sqrt{\frac{L}{C} \left[1 - \frac{\omega^2 L^2}{4} \right]} \quad \left[\frac{4}{L^2} = \omega_c^2 \right]$$

$$= \sqrt{\frac{L}{C} \left[1 - \frac{\omega^2}{\omega_c^2} \right]}$$

$$= \sqrt{\frac{L}{C}} \sqrt{1 - \frac{\omega^2}{\omega_c^2}}$$

$$f_c = \frac{\omega_c}{2\pi}$$

$$\omega_c = 2\pi f_c$$

$$= R_k \sqrt{1 - \left(\frac{f}{f_c} \right)^2}$$

$$\boxed{Z_{OT} = R_k \sqrt{1 - \left(\frac{f}{f_c} \right)^2}} \rightarrow \text{⑥a}$$

Characteristic Impedance of π -N/W:-

we know that

$$Z_{OT} \cdot Z_{O\pi} = Z_1 Z_2$$


$$Z_{O\pi} = \frac{Z_1 Z_2}{Z_{OT}}$$

$$Z_{out} = \frac{R_k}{\sqrt{1 - \left(\frac{f}{f_c}\right)^2}}$$

$$Z_{out} = \frac{R_k}{\sqrt{1 - \left(\frac{f}{f_c}\right)^2}} \rightarrow (6b)$$

If $f=0 \Rightarrow Z_{in} = R_k$ & also $Z_{out} = R_k$

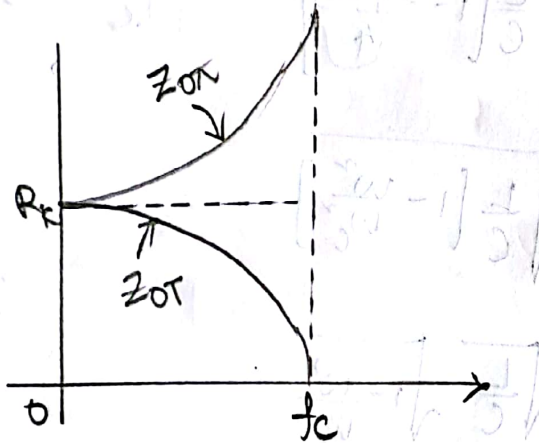If $f=f_c \Rightarrow Z_{in} = 0$ & $Z_{out} = \infty$



Design of Low pass Filter when R_k & f_c are known:-

we know that $\left(\frac{f}{f_c}\right)^2 = 1 - \frac{1}{10^{\frac{\alpha}{20}}}$

$$f_c = \frac{1}{\pi \sqrt{LC}} ; R_k = \sqrt{\frac{L}{C}}$$

$\rightarrow \textcircled{a}$

$\rightarrow \textcircled{b}$

$$\textcircled{a} \times \textcircled{b} \Rightarrow f_c \cdot R_k = \frac{1}{\pi \sqrt{LC}} \times \sqrt{\frac{L}{C}}$$

$$\frac{10^{\frac{\alpha}{20}}}{\pi} = \frac{1}{\pi} \sqrt{\frac{K}{LC \times C}}$$

$$f_c R_k = \frac{1}{\pi} \sqrt{\frac{L}{C}}$$

$$f_c R_k = \frac{1}{\pi C}$$

$$C = \frac{1}{\pi f_c R_k}$$

consider $\frac{R_k}{f_c} = \sqrt{\frac{L}{C}} [\pi \sqrt{LC}]$

$$= \sqrt{\frac{L L C}{C}} \cdot \pi$$

$$\frac{R_k}{f_c} = \pi L$$

$$L = \frac{R_k}{\pi f_c}$$

Attenuation const (α) & phase shift const (β)
of const-k LPF is:-

We know that

$$\cosh(p) = 1 + \frac{Z_1}{2Z_0}$$

$$\cosh(\alpha + j\beta) = 1 + \frac{Z_1}{2Z_0} = 1 + \frac{j\omega L}{2(j\omega C)}$$

$$\cosh \alpha \cosh j\beta + \sinh \alpha \sinh j\beta = 1 - \frac{\omega^2 LC}{2}$$

$$\cosh \alpha \cos \beta + \sinh \alpha (j \sin \beta) = 1 - \frac{\omega^2 LC}{2}$$

$$\cosh \alpha \cos \beta + j \sinh \alpha \sin \beta = 1 - \frac{\omega^2 L C}{2}$$

$$\cosh \alpha \cos \beta + j \sinh \alpha \sin \beta = 1 - \frac{\omega^2 \frac{L^2}{4}}{\omega_c^2}$$

$$\cosh \alpha \cos \beta + j \sinh \alpha \sin \beta = 1 - \frac{2\omega^2}{\omega_c^2}$$

Equating Real & Imaginary parts

$$\cosh \alpha \cos \beta = 1 - \frac{2\omega^2}{\omega_c^2} \rightarrow (6c)$$

$$\sinh \alpha \sin \beta = 0 \rightarrow (6d)$$

$$\boxed{\text{if } \alpha = 0 \text{ or } \beta = 0 \text{ or } \pm \pi}$$

Case (i) if $\alpha = 0$

from eqn (6c) $\cosh(0) = 1$

$$(i) \cos \beta = 1 - \frac{2\omega^2}{\omega_c^2}$$

$$\cos \beta = 1 - \frac{2\omega^2}{\omega_c^2}$$

$$\cos \frac{\beta}{2} - \sin^2 \frac{\beta}{2} = 1 - \frac{2\omega^2}{\omega_c^2}$$

$$1 + 2 \sin^2 \frac{\beta}{2} = 1 + \frac{2\omega^2}{\omega_c^2}$$

$$\frac{2 \sin^2 \frac{\beta}{2}}{2} = \frac{2\omega^2}{\omega_c^2}$$

$$\sin^2 \frac{\beta}{2} = \frac{\omega^2}{\omega_c^2}$$

$$\sin^2 \frac{\beta}{2} = \frac{\omega^2}{\omega_c^2}$$


$$(\sin \frac{\beta}{2})^2 = \frac{\omega^2}{\omega_c^2}$$

$$\frac{\beta}{2} = \sin^{-1} \left(\frac{\omega}{\omega_c} \right)$$

$$\beta = 2 \sin^{-1} \left(\frac{\omega}{\omega_c} \right)$$

at $f = 0 \Rightarrow$

$f = f_c \Rightarrow$

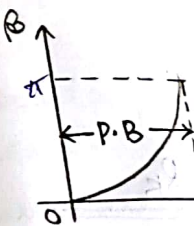

Note: if $f < f_c$
if $f > f_c$

Case (ii)

$$\cos \pi = -1$$

$$\cos \beta = -1$$

$$\beta = \pi$$

$$\sin^2 \beta/2 = \frac{\omega^2}{\omega_c^2}$$


$$(\sin \beta/2)^2 = \left(\frac{\omega}{\omega_c}\right)^2$$

$$\beta/2 = \sin^{-1} \left(\frac{\omega}{\omega_c}\right)$$

$$\boxed{\begin{aligned} \beta &= \sin^{-1} \left(\frac{\omega}{\omega_c}\right) \\ \beta &= \sin^{-1} \left(\frac{f}{f_c}\right) \end{aligned}} \quad \text{--- (C)}$$

at $f=0 \Rightarrow \beta=0$

$f=f_c \Rightarrow \beta=\pi$

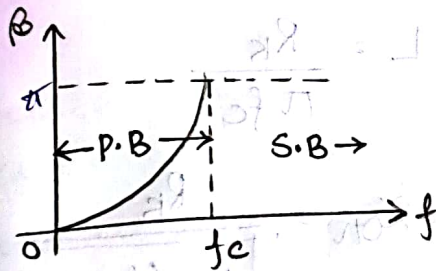

Note:-

$f < f_c \rightarrow \beta = 2 \sin^{-1} \left(\frac{f}{f_c}\right)$

$f > f_c \rightarrow \beta = \pi$ (maintained to be constant) assumption

Case - ii - $\beta = \pi$ [Neglecting 0 & $-\pi$ \therefore since after $f \geq f_c$ the phase shift β is maintained to be const i.e. ' π ' only]

$\cos \pi = -1$

Subⁿ (C)

(-1) $\cosh \alpha = 1 - \frac{2\omega^2}{\omega_c^2}$

$$\cosh \alpha = \frac{2\omega^2}{\omega_c^2} - 1$$

$$\alpha = \cosh^{-1} \left[\frac{2\omega^2}{\omega_c^2} - 1 \right]$$

$$\alpha = \cosh^{-1} \left[\frac{2f^2}{f_c^2} - 1 \right]$$

Summary of Constant-k LPF:

$$\rightarrow Z_1 Z_2 = R_k^2$$

$$R_k = \sqrt{\frac{L}{C}} \quad ; \quad f_c = \frac{1}{\pi \sqrt{LC}}$$

$$C = \frac{1}{\pi R_k f_c} \quad ; \quad L = \frac{R_k}{\pi f_c}$$

$$Z_{OT} = R_k \sqrt{1 - \left(\frac{f}{f_c}\right)^2} \quad ; \quad Z_{ON} = \frac{R_k}{\sqrt{1 - \left(\frac{f}{f_c}\right)^2}}$$

problems:

Q1) Design a constant-k LPF (π & T) to operate a load of 600Ω & have a cut-off frequency 3kHz .

sol: Given: $f_c = 3\text{kHz}$; $R_k = 600\Omega$

W.k.T: $C = \frac{1}{\pi R_k f_c} = \frac{1}{\pi \times 600 \times 3 \times 10^3}$

$$C = 0.176 \mu\text{F}$$

$$L = \frac{R_k}{\pi f_c} = \frac{600}{\pi \times 3 \times 10^3}$$

$$L = 21.83 \text{mH}$$

T-type:

π -type:

Q2) Design a cut-off impedance



$$\text{sol: } f_c =$$

$$f_c = 0$$

$$C = 0.176 \mu F$$

$$L = \frac{R_c}{\pi f_c} = \frac{600}{\pi \times 8 \times 10^3} = 63.66 \text{ mH}$$
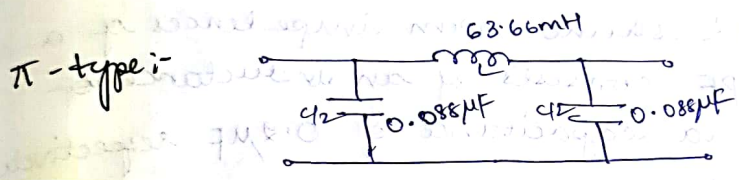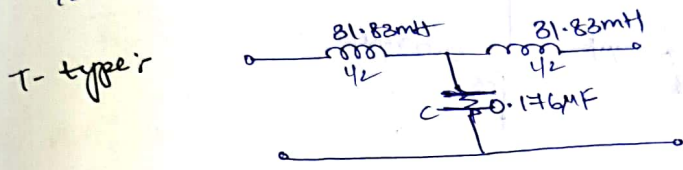
$$Y_2 = 31.83 \text{ mH} ; C_2 = 0.088 \mu F$$



Q2: Design the elements of prototype LPF have a cut-off frequency of 8kHz & Design impedance of 600Ω.

sol: $f_c = 8 \text{ kHz} ; R_c = 600 \Omega$

$$C = \frac{1}{\pi R_c f_c} ; L = \frac{R_c}{\pi f_c}$$


$$C = \frac{1}{\pi \times 600 \times 8 \times 10^3} ; L = \frac{600}{\pi \times 8 \times 10^3}$$

$$C = 0.066 \mu F$$

$$L = 0.0238$$

$$L = 23.8 \text{ mH}$$
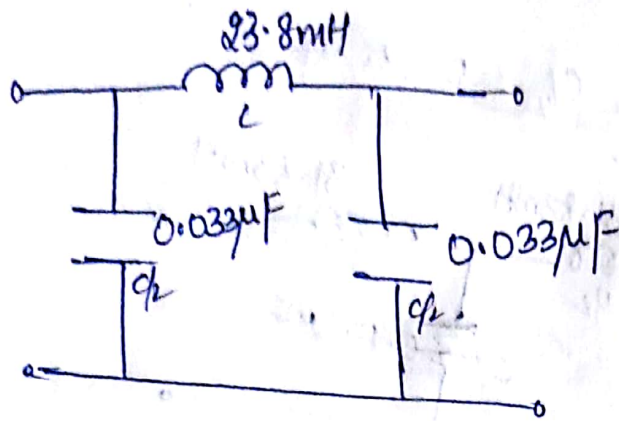
$$C_2 = 0.033 \mu F ; Y_2 = 11.9 \text{ mH}$$



Q3) Series & shunt arm impedances of a T-type LPF consists of an inductance of 60mH & a capacitance of $0.2\mu\text{F}$ respectively. Calculate:

- i) Cut-off Frequency
 - ii) Design Impedance
 - iii) Attenuation const & phase shift const
- sol: $f_c = ?$, $R_k = ?$, $\alpha = ?$, $\beta = ?$

i) $f_c = ?$

Given: $L = 60\text{mH}$, $C = 0.2\mu\text{F}$

$$f_c = \frac{1}{\pi\sqrt{LC}} \Rightarrow \frac{1}{\pi \times \sqrt{60 \times 10^{-3} \times 0.2 \times 10^{-6}}}$$

$$f_c = 2905.75 \text{ Hz}$$

$$f_c = 2.91 \text{ kHz}$$

ii) $R_k = ?$

$$R_k = \sqrt{\frac{L}{C}}$$

$$= \sqrt{\frac{60 \times 10^{-3}}{0.2 \times 10^{-6}}}$$

$$R_k = 547.72 \Omega$$

iii) $\alpha = ?$; $\beta = ?$

$$\alpha = \cosh^{-1} \left[\frac{2f^2}{f_c^2} - 1 \right] \quad ; \quad \beta = \sin^{-1} \left[\frac{f}{f_c} \right]$$

$$f = 5 \text{ kHz} > f_c$$



$$\alpha = \cosh^{-1} \left[2 \left[\frac{5 \text{ kHz}}{2.91 \text{ kHz}} \right]^2 - 1 \right]$$

$$\alpha = 2.27 \text{ Np}$$

Now phase shift const (β):-

$$f = 5 \text{ kHz}, \therefore f > f_c \quad \text{then } \beta = \pi$$

Constant-K HPF :-

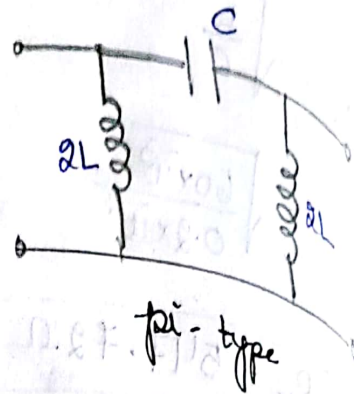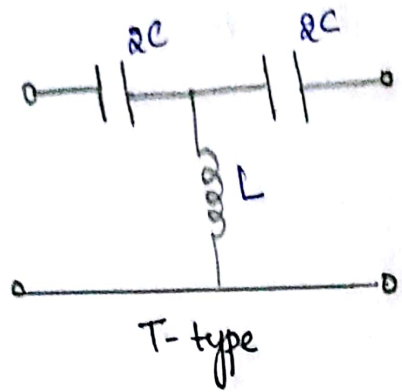

$$Z_1 = \frac{1}{j\omega C} \quad ; \quad Z_2 = j\omega L$$

Design impedance (R_k) :-

w.k.T for constant K-filter

$$Z_1 Z_2 = R_k^2$$

$$R_k^2 = \frac{1}{(j\omega C)} (j\omega L) \left(\frac{22}{2 \times 22} \right) = \frac{1}{\omega C}$$

$$R_k = \sqrt{\frac{L}{C}}$$

Cut-off frequency :-

w.k.T $\frac{Z_1}{4Z_2} = -1$ at $f = f_c$

$$\frac{1}{j\omega_c C} = -4(j\omega_c L)$$

$$1 = -4j^2 \omega_c^2 LC$$

$$\omega_c^2 = \frac{1}{4LC}$$

$$(2\pi f_c)^2 = \frac{1}{4LC}$$

$$f_c^2 = \frac{1}{4LC \times 4\pi^2}$$

$$f_c = \frac{1}{4\pi\sqrt{LC}}$$

Characteristic Impedance:-

W.K.T for T-19/w

$$Z_{OT} = \sqrt{\frac{Z_1^2}{4} + Z_1 Z_2}$$

$$= \sqrt{\frac{1}{j\omega^2 LC} + \frac{L}{C}}$$

$$= \sqrt{\frac{L}{C} - \frac{1}{4\omega^2 LC}}$$

$$= \sqrt{\frac{L}{C} \left[1 - \frac{1}{4\omega^2 LC} \right]}$$

$$= \sqrt{\frac{L}{C}} \sqrt{1 - \frac{\omega_c^2}{\omega^2}}$$

$$Z_{OT} = R_k \sqrt{1 - \left(\frac{f_c}{f}\right)^2}$$


w.k.T

$$Z_{OT} \cdot Z_{OT} = Z_1 Z_2$$

$$Z_{OT} = \frac{Z_1 Z_2}{Z_{OT}}$$

$$= \frac{R_k}{\sqrt{1 - \left(\frac{f_c}{f}\right)^2}}$$
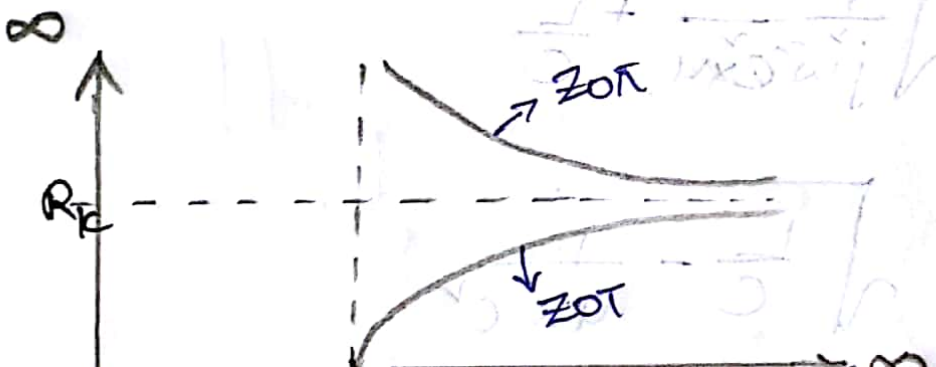
$$Z_{OT} = \frac{R_k}{\sqrt{1 - \left(\frac{f_c}{f}\right)^2}}$$



10/8/18

Design of constant-K HPF if f_c & R_k are given:-

W.K.T for constant-K HPF,

$$f_c = \frac{1}{4\pi\sqrt{LC}} \text{ and}$$

$$R_k = \sqrt{\frac{L}{C}}$$

$$f_c \times R_k = \frac{1}{4\pi\sqrt{LC}} \times \sqrt{\frac{L}{C}}$$

$$= \frac{1}{4\pi} \sqrt{\frac{K}{C^2}}$$

$$\boxed{C = \frac{1}{4\pi f_c R_k}}$$

$$\frac{R_k}{f_c} = \sqrt{\frac{L}{C}} \cdot 4\pi\sqrt{LC}$$

$$\frac{R_k}{f_c} = 4\pi L$$

$$\boxed{L = \frac{R_k}{4\pi f_c}}$$

Attenuation & phase-shift constants

$$\text{W.K.T } \cosh p = 1 + \frac{Z_L}{2Z_0}$$

$$\cosh(\alpha + j\beta) = 1 + \frac{\frac{1}{j\omega C}}{2(j\omega L)}$$

$$\Rightarrow \cosh \alpha \cos \beta + j \sinh \alpha \sin \beta = 1 + \frac{1}{2j\omega^2 LC}$$

$$\cosh \alpha \cos \beta + j \sinh \alpha \sin \beta = 1 - \frac{1}{2\omega^2 LC}$$

$$\cosh \alpha \cos \beta + j \sinh \alpha \sin \beta = 1 - \frac{2\omega_c^2}{\omega^2}$$

comparing both sides

$$\cosh \alpha \cos \beta = 1 - 2\left(\frac{f_c}{f}\right)^2 = 0$$

$$\sinh \alpha \sin \beta = 0$$

$\therefore \sinh \alpha \sin \beta$ becomes zero if either

$$\boxed{\alpha = 0}$$

(or)

$$\boxed{\beta = 0 \text{ or } \pm\pi}$$

case (i): $\boxed{\alpha = 0}$

$$\cosh \alpha = \cosh(0) = 1$$

$$\cos \beta = 1 - 2\left(\frac{f_c}{f}\right)^2$$

$$\beta = \cos^{-1} \left[1 - 2 \left(\frac{f_c}{f} \right)^2 \right]$$

(or)

$$\cos \beta/2 - \sin \beta/2 = 1 - 2 \left(\frac{f_c}{f} \right)^2$$

$$1 - 2 \sin^2 \beta/2 = 1 - 2 \left(\frac{f_c}{f} \right)^2$$


$$\sin \beta/2 = \left(\frac{f_c}{f} \right)$$

$$\beta = 2 \sin^{-1} \left[\frac{f_c}{f} \right]$$

at $f = f_c \Rightarrow \beta = \pi$
 $f = \infty \Rightarrow \beta = 0$

NOTE:-

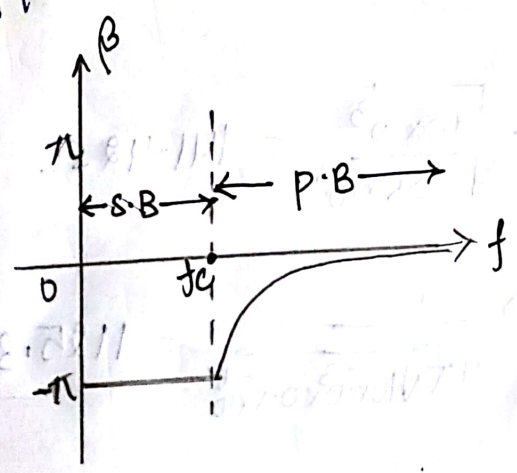But practically it has been observed that phase shift $\beta = -\pi$ for $f = f_c$. This is due to the properties of HPF or exactly opposite to LPF.



case ii: consider $\beta = -\pi$

$$\cos(\beta) \Rightarrow \cos(-\pi) = -1$$


$$\cosh \alpha (-1) = 1 - 2 \left(\frac{f_c}{f} \right)^2$$

$$-\cosh \alpha = 1 - 2 \left(\frac{f_c}{f} \right)^2$$

$$\alpha = \cosh^{-1} \left[2 \left(\frac{f_c}{f} \right)^2 - 1 \right]$$

problem:

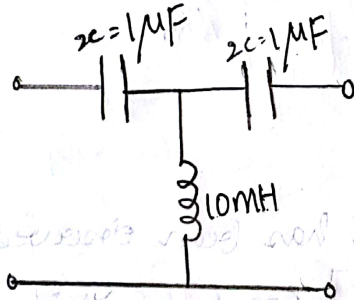Q1: For a const k HPF. given below. Calculate f_c & R_c . consider operating freq = 10 kHz



sol: $C = 0.5 \mu F$
 $L = 10 mH$

$$R_c = \sqrt{\frac{L}{C}} \Rightarrow \sqrt{\frac{10 \times 10^{-3}}{0.5 \times 10^{-6}}} = 141.42 \Omega$$



$$f_c = \frac{1}{4\pi \sqrt{LC}} \Rightarrow \frac{1}{4\pi \sqrt{10 \times 10^{-3} \times 0.5 \times 10^{-6}}} = 1125.39 Hz$$

Q2) Design a constant-K HPF with cut-off frequency 5 kHz & Design Impedance 600Ω & also calculate

1) Attenuation & phase-shift constants at $f = 2 \text{ kHz}$

2) At $f = 10 \text{ kHz}$

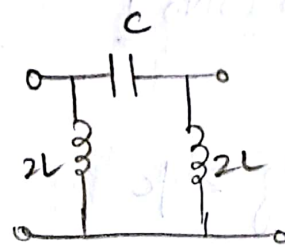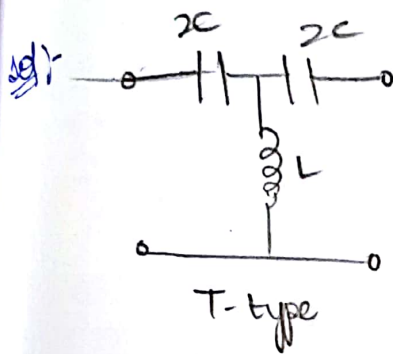3) Z_{OT} at $f = 7 \text{ kHz} = 419.91$




$$C = \frac{1}{4\pi f_c R_k} = \frac{1}{4\pi \times 5 \times 10^3 \times 600} = 0.02653 \mu\text{F}$$

$$26.53 \text{ nF}$$

$$2C \Rightarrow 53.06 \text{ nF}$$

$$L = \frac{R_k^2}{4\pi f_c} \Rightarrow \frac{600^2}{4\pi \times 5 \times 10^3} = 9.54 \text{ mH}$$

$$2L \Rightarrow 19.08 \text{ mH}$$

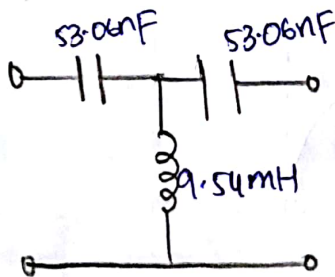

$$i) f = 2 \text{ kHz} < f_c$$

$$\therefore \alpha = 2 \text{ dB}$$

$$\alpha = 20 \log_{10} \left[2 \left(\frac{f}{f_c} \right)^2 - 1 \right]$$

$$\alpha = 20 \log_{10} \left[2 \left(\frac{2}{2} \right)^2 - 1 \right]$$

$$\alpha = 2.13 \text{ dB}$$

$$ii) f = 10 \text{ kHz} > f_c$$

$$\therefore \beta = 20 \log_{10} \left(\frac{f}{f_c} \right)$$

$$\text{approx. } \beta = 60$$

$$\beta = \frac{20}{3}$$

$$\alpha = 20 \log_{10} \left[2 \left(\frac{f}{f_c} \right)^2 - 1 \right]$$

$$\downarrow \quad \boxed{f > f_c}$$

⊙ For frequencies $> f_c$, we cannot calculate attenuation, const α .

$$iii) Z_{OT} = R_c \sqrt{1 - \left(\frac{f}{f_c} \right)^2}$$

Q3. Design a constant k-LPF with design Impedance 500Ω & cut-off frequency $f_c = 3\text{kHz}$. Calculate Attenuation & phase-shift constants at 1kHz & 5kHz respectively.

$R_k = 500\Omega$
 $f_c = 3\text{kHz}$

$C = \frac{1}{\pi f_c R_k} = \frac{1}{\pi \times 3 \times 10^3 \times 500} = 0.212\mu\text{F}$
 $C/2 = 0.106\mu\text{F}$

$L = \frac{R_k}{\pi f_c} = \frac{500}{\pi \times 3 \times 10^3} = 0.053\text{H} \Rightarrow 53.05\text{mH}$
 $L/2 = 26.52\text{mH}$

given $f = 1\text{kHz}$

\therefore Here $f_c > f$



then $\beta = 2 \sin^{-1} \left(\frac{f}{f_c} \right)$

$= 2 \sin^{-1} \left(\frac{1}{3} \right)$

$\beta = 38.94$

$\boxed{\beta = 39}$ or $\boxed{\beta = 0.67\text{rad}}$

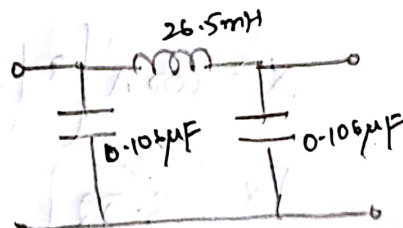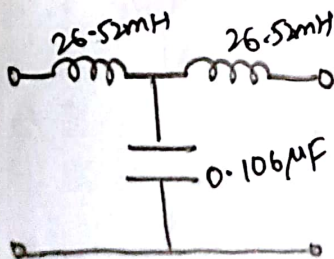$\therefore \alpha$ is not defined, coz ($f < f_c$)



∴ $f = 5 \text{ kHz}$
 Here $f > f_c$

$$\boxed{\beta = \pi}$$

$$\therefore \alpha = \cos^{-1} \left[2 \left(\frac{f}{f_c} \right)^2 - 1 \right]$$

$$= \cos^{-1} \left[2 \left(\frac{5}{3} \right)^2 - 1 \right]$$

$$\boxed{\alpha = 2.197 \text{ Np}}$$

HPF:

$$C = \frac{1}{4\pi f_c R_c} = \frac{1}{4\pi \times 2 \times 10^3 \times 500} \Rightarrow 53.05 \text{ nF}$$

$$L = \frac{R_c}{4\pi f_c} \Rightarrow 0.013 \text{ H}$$

OR

$$13.26 \text{ mH}$$

* At $f = 1 \text{ kHz}$

∴ $f_c > f$

$$\boxed{\beta = -\pi}$$

$$\alpha = \cos^{-1} \left[2 \left(\frac{f_c}{f} \right)^2 - 1 \right]$$

$$\boxed{\alpha = 3.52}$$

∴ At $f = 5 \text{ kHz}$

∴ $f_c < f$

$$\beta = \cos^{-1} \left[\dots \right]$$

$$\boxed{\beta = -36}$$

α not

$\rightarrow \omega = 5 \text{ kHz}$

$\therefore \omega_c < \omega$

$\beta = \sin^{-1} \left[\frac{\omega_c}{\omega} \right]$

$\beta = -36.86$



α' not defined.

13/8/18

Constant-K Band pass Filter (BPF):-

A Band pass Filter is a N/w which allows signals b/w a range of frequency f_{c1} to f_{c2}
 f_{c1} is lower cut-off frequency & (lcf)
 f_{c2} is higher " " " (hcf)

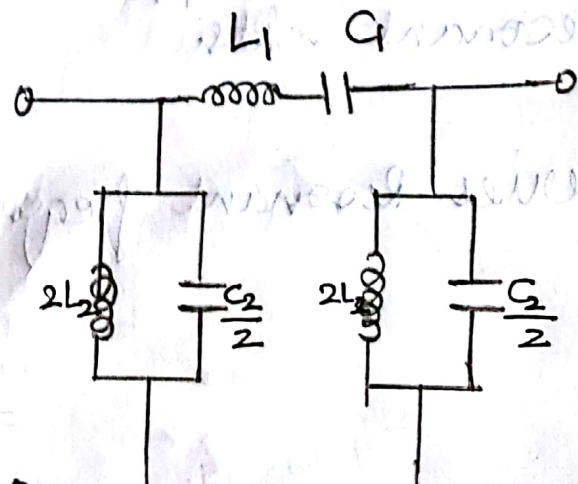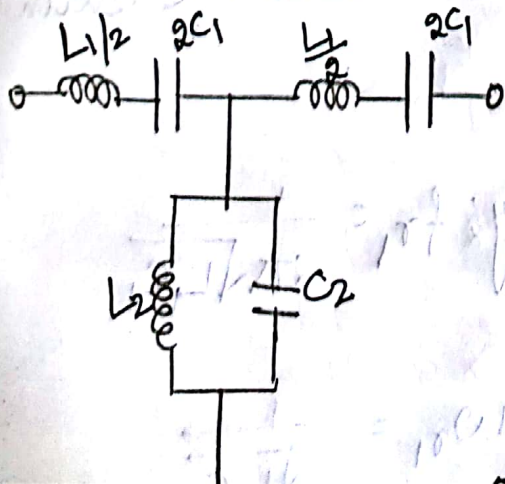Practically, a BPF can be obtained by properly joining a LPF & HPF in such a way that lcf of HPF is less than the hcf of LPF.



For T-N/W;

$$Z_1 = j\omega L_1 - \frac{j}{\omega C_1}$$

$$Z_1 = j\left[\omega L_1 - \frac{1}{\omega C_1}\right]$$

$$Z_2 = \frac{(j\omega L_2)\left(\frac{1}{j\omega C_2}\right)}{j\omega L_2 + \frac{1}{j\omega C_2}}$$

$$Z_2 = \frac{j\omega L_2}{j\omega L_2 C_2 + 1}$$

$$Z_2 = \frac{j\omega L_2}{1 - \omega^2 L_2 C_2}$$

→ Constant-K BPF consists series & shunt resonant ckt's

⊕ Series Resonant frequency; $f_{r1} = \frac{1}{2\pi\sqrt{L_1 C_1}}$

$$\Rightarrow \omega_{r1} = \frac{1}{\sqrt{L_1 C_1}}$$

Resonant Frequency; $f_{r2} = \frac{1}{2\pi\sqrt{L_2 C_2}}$

$$\Rightarrow \omega_{r2} = \frac{1}{\sqrt{L_2 C_2}}$$

In constant-k BPF design, L_1, C_1 & L_2, C_2 are selected in such a way that

$$\omega_{r1} = \omega_{r2} = \omega_0 \text{ [common Resonant Freq]}$$

$$\omega_0 = \frac{1}{\sqrt{L_1 C_1}} = \frac{1}{\sqrt{L_2 C_2}}$$

$$\omega_0^2 = \frac{1}{L_1 C_1} = \frac{1}{L_2 C_2}$$

$$\boxed{L_1 C_1 = L_2 C_2 = \frac{1}{\omega_0^2}}$$

Design Impedance:- $[R_k]$

W.K.T for const-k BPF

$$Z_1 Z_2 = R_k^2$$

$$j\left(\omega L_1 - \frac{1}{\omega C_1}\right) \left[\frac{j\omega L_2}{1 - \omega^2 L_2 C_2} \right] = R_k^2$$

$$j^2 \left[\frac{\omega L_1 C_1 - 1}{\omega C_1} \right] \left[\frac{\omega L_2}{1 - \omega^2 L_2 C_2} \right] = R_k^2$$

$$R_k^2 = \frac{L_2}{C_1} \left[\frac{1 - \omega^2 L_1 C_1}{1 - \omega^2 L_2 C_2} \right]$$

$$\text{At } \omega = \omega_0 \quad \boxed{L_1 C_1 = L_2 C_2}$$

$$R_k = \sqrt{\frac{L_2}{C_1}}$$

$$\therefore L_1 C_1 = L_2 C_2$$

$$R_k = \sqrt{\frac{L_1}{C_2}}$$

Cut-off frequency :-

W.K.T
from condition of cut-off freq.

$$\frac{Z_1}{Z_2} = -1$$

$$\Rightarrow Z_1 = -4 Z_2$$

$$\begin{aligned} j[\omega L_1 - \frac{1}{\omega C_1}] &= -4 \left[\frac{j\omega L_2}{1 - \omega^2 L_2 C_2} \right] \\ \frac{\omega^2 L_1 C_1 - 1}{\omega C_1} &= \frac{-4\omega L_2}{1 - \omega^2 L_2 C_2} \end{aligned}$$

b.s multiply with Z_1

$$Z_1 Z_1 = -4 Z_1 Z_2$$

$$Z_1^2 = -4 Z_1 Z_2$$

$$Z_1^2 = -4 R_k^2$$

$$Z_1 = \pm 2j R_k$$

i.e. $Z_1 = -j2R_k$
 $Z_2 = j2R_k$

$$[Z_1]_{f=fc}$$

$$j[\omega C_1 L_1 - \frac{1}{\omega C_1}]$$

$$\frac{\omega^2 L_1 C_1 - 1}{\omega C_1}$$

$$\omega C_1$$

$$\text{i.e. } Z_1 = -j2R_k \text{ at } f = f_{c1}$$

$$Z_1 = j2R_k \text{ at } f = f_{c2}$$

$$[Z_1]_{f=f_{c1}} = -[Z_1]_{f=f_{c2}}$$

$$j \left[\omega_{c1} L_1 - \frac{1}{\omega_{c1} C_1} \right] = -j \left[\omega_{c2} L_1 - \frac{1}{\omega_{c2} C_1} \right]$$

$$\frac{\omega_{c1}^r L_1 C_1 - 1}{\omega_{c1}} = - \left[\frac{\omega_{c2}^r L_1 C_1 - 1}{\omega_{c2}} \right]$$

$$\frac{\omega_{c1}^r L_1 C_1 - 1}{\omega_{c1}} = \frac{1 - \omega_{c2}^r L_1 C_1}{\omega_{c2}}$$

$$\frac{\omega_{c1}}{\omega_{c2}} = \frac{\omega_{c1}^r L_1 C_1 - 1}{1 - \omega_{c2}^r L_1 C_1}$$

$$\frac{\omega_{c1}}{\omega_{c2}} = \frac{\frac{\omega_{c1}^r}{\omega_0^r} - 1}{1 - \frac{\omega_{c2}^r}{\omega_0^r}}$$

$$\frac{\omega_{c1}}{\omega_{c2}} = \frac{\omega_{c1}^r - \omega_0^r}{\omega_0^r - \omega_{c2}^r}$$

$$\omega_{c1} [\omega_0^r - \omega_{c2}^r] = (\omega_{c1}^r - \omega_0^r) \omega_{c2}$$

$$\omega_{c1} \omega_0^r - \omega_{c2}^r \omega_{c1} = \omega_{c1}^r \omega_{c2} - \omega_0^r \omega_{c2}$$

$$\omega_0^2 (\omega_{c1} + \omega_{c2}) = \omega_{c1} \omega_{c2} (\omega_{c1} + \omega_{c2})$$

$$\omega_0^2 = \omega_{c1} \omega_{c2}$$

$$\omega_0 = \sqrt{\omega_{c1} \omega_{c2}}$$

$$f_0 = \sqrt{f_{c1} f_{c2}}$$

Design of Constant-k BPF:-

w.k.T for const-k BPF

$$Z_1 = -j2R_k \text{ at } f = f_c$$

$$j \left[\omega_{c1} L_1 - \frac{1}{\omega_{c1} C_1} \right] = -j2R_k$$

$$\frac{\omega_{c1}^2 L_1 C_1 - 1}{\omega_{c1} C_1} = -2R_k$$

$$1 - \omega_{c1}^2 L_1 C_1 = 2R_k \omega_{c1} C_1$$

$$\frac{1 - \omega_{c1}^2}{\omega_0^2} = 2R_k \omega_{c1} C_1 \quad \left[\because \omega_0^2 = \frac{1}{L_1 C_1} \right]$$

$$C_1 = \frac{\left[1 - \frac{\omega_{c1}^2}{\omega_0^2} \right]}{2R_k \omega_{c1}}$$

$$C_1 = \frac{\omega_0^2 - \omega_{c1}^2}{2R_k \omega_{c1} \omega_0^2}$$

$$C_1 = \frac{4\pi^2 [f_0^2 - f_{c1}^2]}{2R_k 2\pi f_{c1} 4\pi^2 f_0^2}$$

$$C_1 = \frac{f_{c2} f_{c2} - f_{c1}^2}{4\pi R_k f_{c1} f_{c1} f_{c2}} \quad [f_0 = \sqrt{f_{c1} f_{c2}}]$$

$$C_1 = \frac{f_{c2} (f_{c2} - f_{c1})}{4\pi R_k f_{c1} f_{c1} f_{c2}}$$

$$C_1 = \frac{f_{c2} - f_{c1}}{4\pi R_k f_{c1} f_{c2}}$$

w.k.T

$$\omega_0^2 = \frac{1}{L_1 C_1}$$

$$L_1 = \frac{1}{\omega_0^2 C_1}$$

$$= \frac{4\pi R_k f_{c1} f_{c2}}{4\pi^2 f_0^2 (f_{c2} - f_{c1})}$$

$$L_1 = \frac{R_k}{\pi (f_{c2} - f_{c1})}$$

$$\text{W.P.T. } R_k = \sqrt{\frac{L_2}{C_1}} \quad \text{or} \quad \sqrt{\frac{L_1}{C_2}}$$

$$\text{Let } R_k^2 = \frac{L_2}{C_1}$$

$$L_2 = R_k^2 C_1$$

$$= \frac{R_k^2 (f_{c2} - f_{c1})}{4\pi f_{c1} f_{c2}}$$

$$L_2 = \frac{R_k^2 (f_{c2} - f_{c1})}{4\pi f_{c1} f_{c2}}$$

$$\text{Also } R_k^2 = \frac{L_1}{C_2}$$

$$C_2 = \frac{L_1}{R_k^2}$$

$$C_2 = \frac{R_k^2}{\pi (f_{c2} - f_{c1}) R_k^2}$$

$$C_2 = \frac{1}{\pi R_k (f_{c2} - f_{c1})}$$

$$L_1 = \frac{R_k}{\pi (f_{c2} - f_{c1})}$$

$$L_2 = \frac{R_k (f_{c2} - f_{c1})}{4\pi f_{c1} f_{c2}}$$

Summary

$$1) L_1 C_1 = L_2 C_2$$

$$2) R_k = \sqrt{\frac{L_2}{C_1}}$$

$$3) Z_1 = -j\omega R_k$$

$$Z_2 = j\omega R_k$$

$$4) f_0 = \frac{1}{2\pi R_k C_1}$$

$$5) L_1 = \frac{R_k}{\pi (f_{c2} - f_{c1})}$$

$$6) L_2 = \frac{R_k (f_{c2} - f_{c1})}{4\pi f_{c1} f_{c2}}$$

$$L_1 = \frac{R_k}{\pi(f_2 - f_1)} \quad ; \quad C_1 = \frac{f_2 - f_1}{4\pi R_k f_1 f_2}$$

$$L_2 = \frac{R_k(f_2 - f_1)}{4\pi f_1 f_2} \quad ; \quad C_2 = \frac{1}{\pi R_k(f_2 - f_1)}$$

Summary of const-k BPF:

$$1) L_1 C_1 = L_2 C_2 = \frac{1}{\omega_0^2}$$

$$2) R_k = \sqrt{\frac{L_2}{C_1}} \quad \text{or} \quad \sqrt{\frac{L_1}{C_2}}$$

$$3) Z_1 = -j2R_k \quad \text{at} \quad f = f_1 \quad [\text{L.C.F}]$$

$$Z_2 = j2R_k \quad \text{at} \quad f = f_2 \quad [\text{H.C.F}]$$

$$4) f_0 = \sqrt{f_1 f_2} \quad \text{or} \quad \omega_0 = \sqrt{\omega_1 \omega_2}$$

$$5) L_1 = \frac{R_k}{\pi(f_2 - f_1)} \quad ; \quad C_1 = \frac{f_2 - f_1}{4\pi R_k f_1 f_2}$$

$$6) L_2 = \frac{R_k(f_2 - f_1)}{4\pi f_1 f_2} \quad ; \quad C_2 = \frac{1}{\pi R_k(f_2 - f_1)}$$

Problems:-

Q1:- Design a prototype (unit-k) BPF with cut-off frequencies. 2KHz & 5KHz respectively & design impedance of 600Ω . Also calculate Resonant frequency.

Sol:- Given:-

$$R_k = 600\Omega$$

$$f_{c1} = 2\text{KHz} = 2000\text{Hz}$$

$$f_{c2} = 5\text{KHz} = 5000\text{Hz}$$

$$f_{c2} - f_{c1} = 3000\text{Hz}$$

Resonant freq $f_0 = \sqrt{f_{c1} f_{c2}}$

$$= \sqrt{(2000)(5000)}$$

$$f_0 = \underline{3.16\text{KHz}}$$

$$L_1 = \frac{R_k}{\pi(f_{c2} - f_{c1})} \Rightarrow \frac{600}{\pi(3000)} = 63.66\text{mH}$$

$$C_1 = \frac{f_{c2} - f_{c1}}{4\pi R_k f_{c1} f_{c2}} \Rightarrow \frac{3000}{4\pi \times 600 \times 2000 \times 5000} \Rightarrow 39.79\text{nF}$$



$$L_2 = \frac{R_B (f_2 - f_1)}{4\pi f_1 f_2} \Rightarrow \frac{600 (3000)}{4\pi \times 2000 \times 5000}$$

$$= 14.32 \text{ mH}$$

$$C_2 = \frac{1}{\pi R_L (f_2 - f_1)}$$

$$= \frac{1}{\pi \times 600 \times 3000}$$

$$= 176.83 \text{ nF}$$

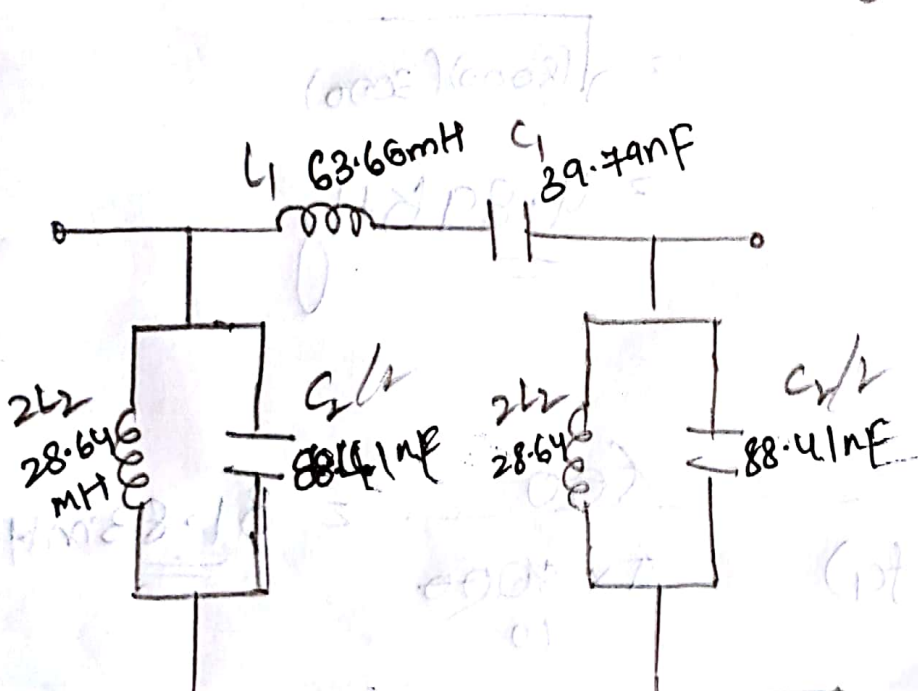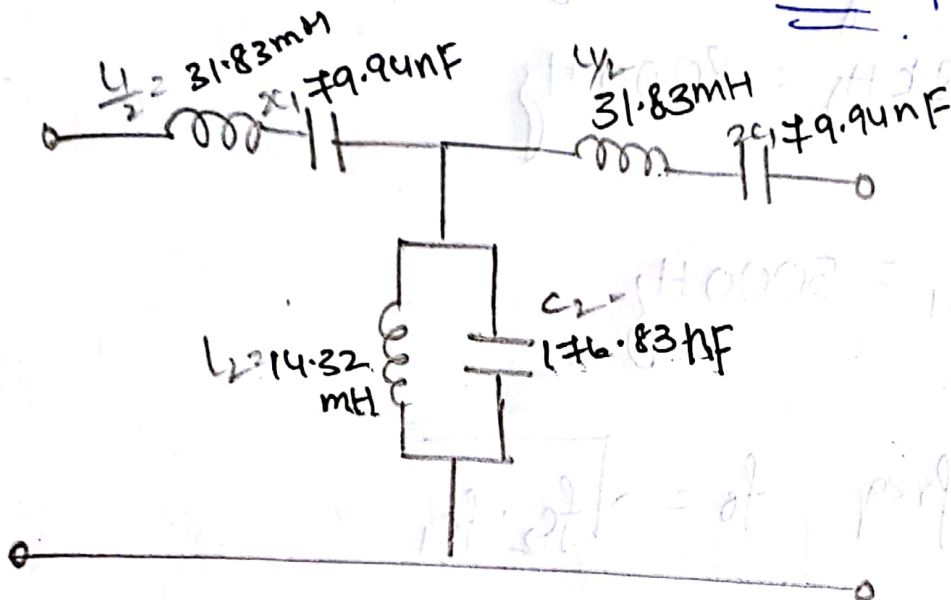

Q2: Design a const-K BPF with cut-off frequencies 3 kHz & 8 kHz respectively & design Impedance 500Ω . Also calculate Resonant Freq.

Sol: Given:

$$R_k = 500\Omega$$

$$f_{c1} = 3\text{kHz} = 3000\text{Hz}$$

$$f_{c2} = 8\text{kHz} = 8000\text{Hz}$$

$$f_{c2} - f_{c1} = 5000\text{Hz}$$

Resonant freq $f_0 = \sqrt{f_{c2} \cdot f_{c1}}$

$$= \sqrt{(8000)(3000)}$$

$$= \underline{\underline{4.89\text{kHz}}}$$



$$L_1 = \frac{R_k}{\pi(f_{c2} - f_{c1})} = \frac{500}{\pi \times 5000} = \underline{\underline{31.83\text{mH}}}$$

$$C_1 = \frac{f_{c2} - f_{c1}}{4\pi R_k f_{c1} f_{c2}} \Rightarrow \frac{5000}{4\pi \times 500 \times 3000 \times 8000} = \underline{\underline{33.15\text{nF}}}$$

$$L_2 = \frac{R_k(f_{c2} - f_{c1})}{4\pi f_{c1} f_{c2}} \Rightarrow \frac{500 \times 5000}{4\pi \times 3000 \times 8000} = \underline{\underline{8.28\text{mH}}}$$

with cut-off
 respectively
 Also calculate
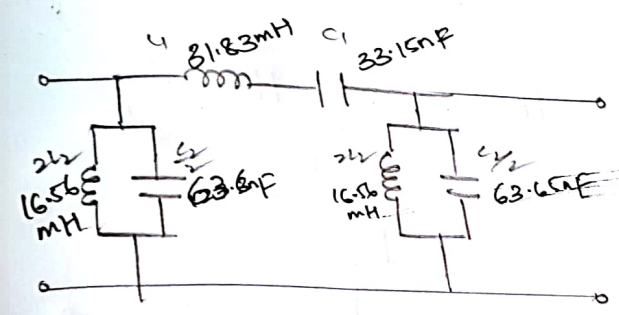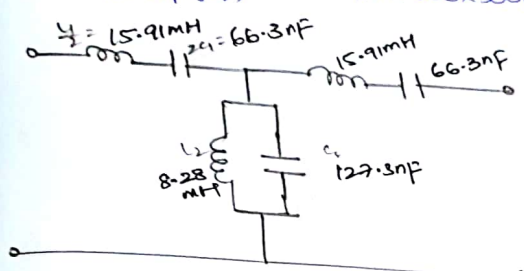
$$C_2 = \frac{1}{\pi R_c (f_c - f_s)} \Rightarrow \frac{1}{\pi \times 500 \times 5000} \Rightarrow 127.3 \text{ nF}$$



NOTE:

For constant-K BPF;


$$Z_{OT} = R_c \sqrt{1 - \left[\frac{x^2 - 1}{2nx} \right]^2}$$

$$\alpha = \cosh^{-1} \left[\frac{(1-x^2)^2}{2n^2 x^2} - 1 \right]$$


$$\beta = \cos^{-1} \left[1 - \frac{(1-x^2)^2}{2n^2 x^2} \right]$$

where
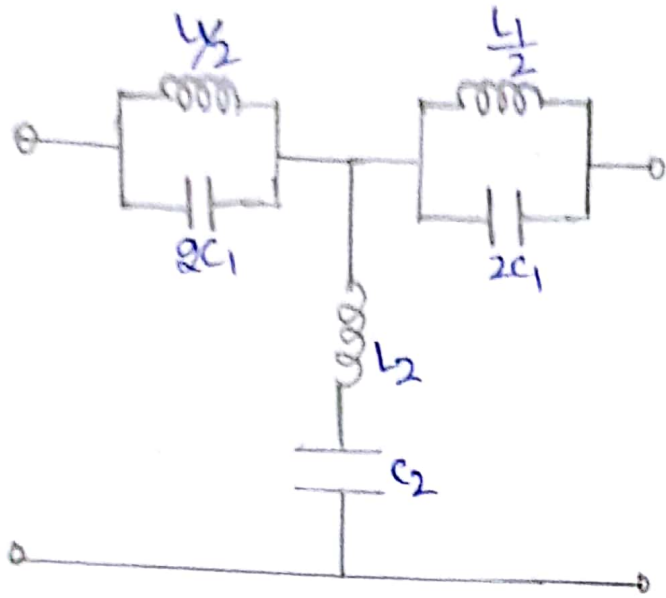
$$x = \left(\frac{f}{f_0} \right) ; \quad n = \frac{f_{c2} - f_{c1}}{2f_0}$$



T-type

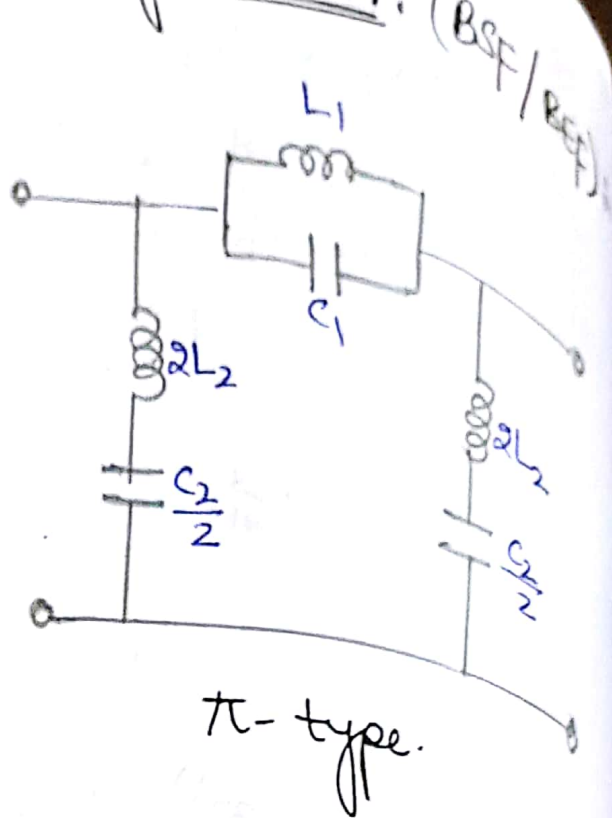

π -type.

$$Z_1 = \frac{(j\omega L_1) \left(\frac{1}{j\omega C_1}\right)}{j\omega L_1 + \frac{1}{j\omega C_1}}$$

$$Z_1 = \frac{j\omega L_1}{\frac{j\omega C_1}{j\omega L_1 C_1 + 1}}$$

$$Z_1 = \frac{j\omega L_1}{1 - \omega^2 L_1 C_1}$$

→ Series arm impedance

$$Z_2 = j\omega L_2 + \frac{1}{j\omega C_2}$$

series arm
shunt arm

$$f_{R_1} = \frac{1}{2\pi\sqrt{L_1 C_1}}$$

$$f_{R_2} = \frac{1}{2\pi\sqrt{L_2 C_2}}$$

series & shunt arm elements $L_1 C_1$ & $L_2 C_2$
are selected in such a way that:

$$\boxed{f_{R_1} = f_{R_2} = f_0}$$

$$\frac{1}{2\pi\sqrt{L_1 C_1}} = \frac{1}{2\pi\sqrt{L_2 C_2}} = f_0$$

$$\omega_0^2 = \frac{1}{L_1 C_1} = \frac{1}{L_2 C_2}$$

$$\boxed{L_1 C_1 = L_2 C_2 = \frac{1}{\omega_0^2}}$$

Design Impedance (R_k):-

W.K.T

$$Z_1 Z_2 = R_k^2$$

$$\left[\frac{j\omega L_1}{1 - \omega^2 L_1 C_1} \right] \left[\frac{1 - \omega^2 L_2 C_2}{j\omega C_2} \right] = R_k^2$$

$$\frac{L_1}{C_2} \left[\frac{1 - \omega^2 L_2 C_2}{1 - \omega^2 L_1 C_1} \right] = R_k^2$$

∴ since $\boxed{L_1 C_1 = L_2 C_2}$

$$\therefore R_k^2 = \frac{L_1}{C_2} = \frac{L_2}{C_1}$$

$$R_k = \sqrt{\frac{L_1}{C_2}} = \sqrt{\frac{L_2}{C_1}}$$

Cut-off Frequency:-

condition for cut-off Freq. is:

$$\frac{Z_1}{4Z_2} = -1$$

$$Z_1 = -4Z_2$$

b.d mul. with Z_1

$$Z_1^2 = -4Z_1 Z_2$$

$$Z_1 Z_2 = R_k^2$$

$$Z_1 = \pm j2R_k$$

As already we know, properties of BSF/BPF is exactly opposite to BPF. So, we consider

$$Z_1 = j2R_k \text{ at } f = f_{c1} \text{ (LCF)}$$

$$Z_1 = -j2R_k \text{ at } f = f_{c2} \text{ (HCF)}$$

$$[Z_1]_{f=f_{c1}} = [-Z_1]_{f=f_{c2}}$$

$$\frac{j\omega_{c1} L_1}{1 - \omega_{c1}^2 L_1 C_1} = -\frac{j\omega_{c2} L_1}{1 - \omega_{c2}^2 L_1 C_1}$$

$$j \frac{\omega_{c1}}{1 - \omega_{c1}^2 L_1 C_1} = \frac{-\omega_{c2}}{1 - \omega_{c2}^2 L_1 C_1}$$

$$\frac{\omega_{c1}}{\omega_{c2}} = \frac{\omega_{c1}^2 L_1 C_1 - 1}{1 - \omega_{c2}^2 L_1 C_1}$$

$$\frac{\omega_{c1}}{\omega_{c2}} = \frac{\frac{\omega_{c1}^2}{\omega_0^2} - 1}{1 - \frac{\omega_{c2}^2}{\omega_0^2}}$$

$$\frac{\omega_{c1}}{\omega_{c2}} = \frac{\omega_{c1}^2 - \omega_0^2}{\omega_0^2 - \omega_{c2}^2}$$

$$\omega_{c1} [\omega_0^2 - \omega_{c2}^2] = \omega_{c2} [\omega_{c1}^2 - \omega_0^2]$$

$$\omega_0^2 \omega_{c1} - \omega_{c1} \omega_{c2}^2 = \omega_{c1}^2 \omega_{c2} - \omega_0^2 \omega_{c2}$$

$$\omega_0^2 (\omega_{c1} + \omega_{c2}) = \omega_{c1} \omega_{c2} (\omega_{c1} + \omega_{c2})$$

$$\omega_0^2 = \omega_{c1} \omega_{c2}$$

$$\omega_0 = \sqrt{\omega_{c1} \omega_{c2}}$$

or

$$f_0 = \sqrt{f_{c1} f_{c2}}$$

Design of BSF:-

consider

$$Z_1 = j\omega R_K \quad \text{at } f = f_c$$

$$\frac{j\omega_c L_1}{1 - \omega_c^2 L_1 C_1} = j\omega R_K$$

$$\omega_c L_1 = R_K \left[\frac{1 - \omega_c^2}{\omega_c^2} \right]$$

$$2\pi f_c L_1 = R_K \left[\frac{f_0^2 - f_c^2}{f_0^2} \right]$$

$$\pi f_c L_1 = R_K \left[\frac{f_c f_c^2 - f_c^2}{f_c f_c} \right]$$

$$L_1 = \frac{R_K (f_c^2 - f_c^2)}{\pi f_c f_c}$$

$$L_1 = \frac{R_K (f_c^2 - f_c^2)}{\pi f_c f_c}$$

w.k.T

$$R_K^2 = \frac{L_1}{C_2} \Rightarrow C_2 = \frac{L_1}{R_K^2}$$

$$C_2 = \frac{R_K (f_c^2 - f_c^2)}{\pi f_c f_c R_K^2}$$

$$C_2 = \frac{(f_2 - f_1)}{\pi f_1 f_2 R_k}$$

Also $L_2 C_2 = \frac{1}{\omega_0^2}$

$$L_2 = \frac{1}{C_2 4\pi^2 f_0^2}$$

$$L_2 = \frac{\cancel{\pi f_1 f_2 R_k}}{(f_2 - f_1) 4\pi^2 \cancel{f_0^2} \cancel{\pi f_1 f_2}}$$

$$L_2 = \frac{R_k}{4\pi^2 (f_2 - f_1)}$$

consider;

$$R_k^2 = \frac{L_2}{C_1} \Rightarrow C_1 = \frac{L_2}{R_k^2}$$

$$C_1 = \frac{\cancel{R_k}}{4\pi^2 (f_2 - f_1) \cancel{R_k^2}}$$

$$C_1 = \frac{1}{4\pi^2 R_k (f_2 - f_1)}$$

problems:-

Q1) Design a BSF which stops the frequencies in the range 1000Hz to 4000Hz & the design impedance is given as 500Ω.

Sol:-

$$Z_{in} = 500 \Omega$$

$$Z_{out} = 500 \Omega$$

$$Z_{in} = Z_{out}$$

$$Z_{in} = Z_{out} = 500 \Omega$$

$$Z_{in} = 500 \Omega \leftarrow \frac{500 \Omega}{10}$$

$$Z_{out} = 500 \Omega$$


$$Z_{in} = 500 \Omega$$

M-derived Filters:-


Def: m-derived filters are modified constant k filter with a parameter 'm' such a way that, characteristics impedance of prototype filter is same as that of m-derived.

- Filters can be designed either in T-type or π -type. So, 1st we derive the expressions for m-derived T-type & π -type filter.

M-derived "T-type"

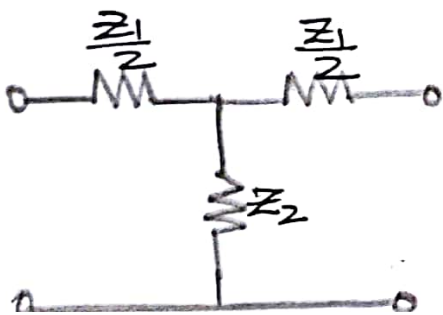

Z_{OT} Z_{OT}

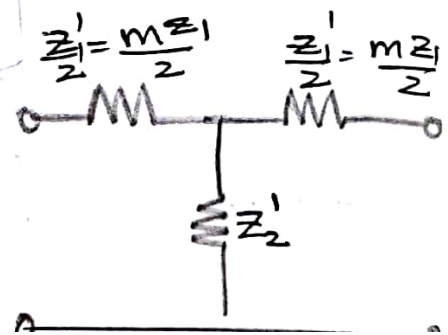

modified constant 'm' such a impedance as that

other in T-type the expressions

$$Z_1' = \frac{mZ_1}{2}$$

T-type (multi with 'm')


$$\frac{Z_1^2}{4} + Z_1 Z_2 - \frac{m^2 Z_1^2}{4} = m Z_1 Z_2'$$

$$\frac{Z_1^2}{4} (1 - m^2) + Z_1 Z_2 = m Z_1 Z_2'$$


$$\frac{Z_1}{4} (1 - m^2) + Z_2 = m Z_2'$$

$$Z_2' = \left[\frac{1 - m^2}{4m} \right] Z_1 + \frac{Z_2}{m}$$


sub Z_2' in m-derived T-type netw

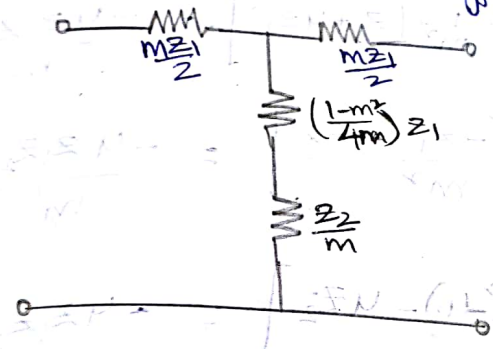

m-derived "π-type":

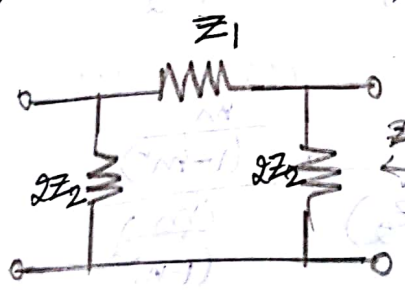

prototype π-type

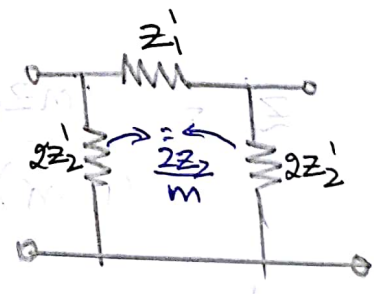

m-derived π-type (shunt arm imp div with 'm')

$$2Z_2' = \frac{2Z_2}{m}$$

$$Z_2' = \frac{Z_2}{m}$$

$$Z_{OR} = Z'_{OR}$$

$$\frac{4Z_1 Z_2^2}{Z_1 + 4Z_2} = \frac{4Z'_1 Z_2^2}{Z'_1 + 4Z_2}$$

$$4Z_1 Z_2^2 \left[Z'_1 + 4 \frac{Z_2}{m} \right] = \frac{4Z'_1 Z_2^2}{m^2} \left[Z_1 + 4Z_2 \right]$$

$$Z_1 Z'_1 + \frac{4Z_1 Z_2}{m} - \frac{Z'_1}{m^2} \left[Z_1 + 4Z_2 \right] = 0$$

$$Z'_1 \left[Z_1 - \frac{1}{m^2} (Z_1 + 4Z_2) \right] = -\frac{4Z_1 Z_2}{m}$$

$$Z'_1 \left[\frac{Z_1 m^2 - Z_1 - 4Z_2}{m^2} \right] = -\frac{4Z_1 Z_2}{m}$$


$$Z'_1 \left[Z_1 (m^2 - 1) - 4Z_2 \right] = -4Z_1 Z_2 m$$

$$Z'_1 \left[4Z_2 + (1 - m^2) Z_1 \right] = 4Z_1 Z_2 m$$

$$Z'_1 = \frac{(mZ_1)(4Z_2)}{(1 - m^2)Z_1 + 4Z_2} \times \frac{m}{\left(\frac{m}{1 - m^2}\right)}$$

$$Z'_1 = \frac{(mZ_1) \left(\frac{4m}{1 - m^2}\right) Z_2}{mZ_1 + \left(\frac{4m}{1 - m^2}\right) Z_2}$$

$$Z'_1 = (mZ_1)$$

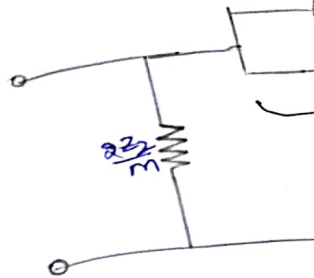

Summary:-

NOTE


1. For m-derivative by 'm' i.e. get $Z'_2 =$

2. In m-derivative by 'm' get $Z'_1 =$

get $Z'_1 =$

M-Derivative
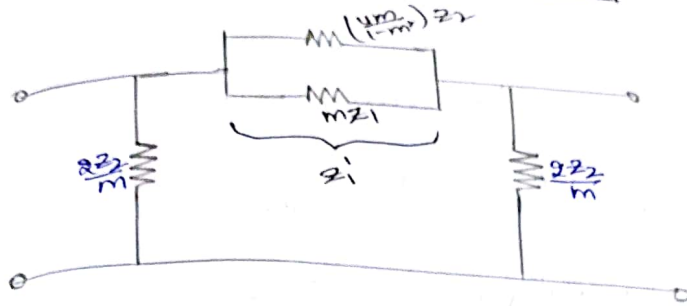
$$Z_1' = (mZ_1) \parallel \left(\frac{4m}{1-m^2} \right) Z_2$$



Summary:-

NOTE

1. For m-derived T-section, series arm is multiplied by 'm' i.e. $Z_1' = mZ_1$ so that we can get


$$Z_2' = \left(\frac{1-m^2}{4m} \right) Z_1 + \frac{Z_2}{m}$$

2. In m-derived π -section, shunt arm is divided by 'm' i.e. $Z_2' = \frac{Z_2}{m}$ so that we can


get

$$Z_1' = (mZ_1) \parallel \left(\frac{4m}{1-m^2} \right) Z_2$$

m-Derived LPF Analysis:

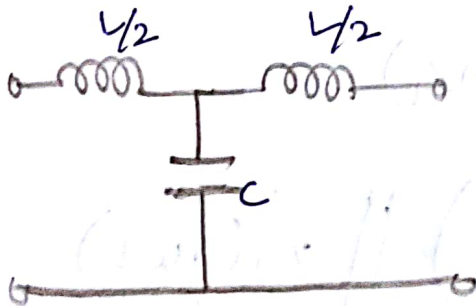

prototype LPF
T-type

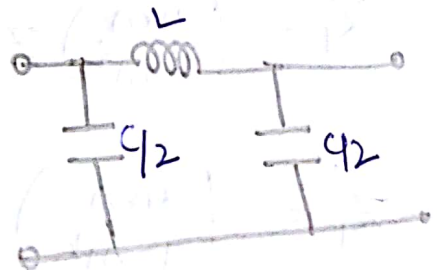

π -type

$$Z_1 = j\omega L$$


$$Z_2 = \frac{1}{j\omega C}$$

$$Z_1' = m(j\omega L) = j\omega(mL)$$

$$Z_2' = \left(\frac{1-m^2}{4m}\right)(j\omega L) + \frac{1}{j\omega cm}$$

$$Z_2' = j\omega\left(\frac{1-m^2}{4m}\right)L + \frac{1}{j\omega(cm)}$$

m-derived LPF (T-type)

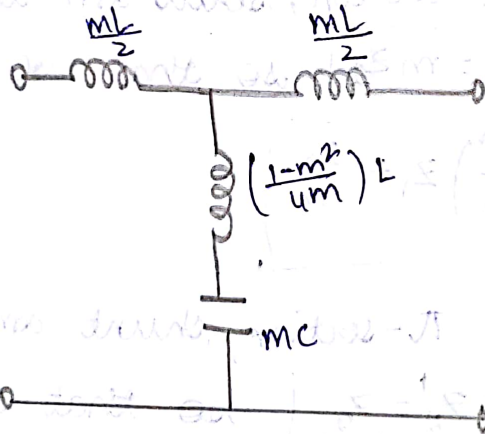

For π -type:


$$Z_2' = \frac{Z_2}{m} = \frac{1}{j\omega C \cdot m} = \frac{1}{j\omega(cm)}$$

$$Z_1' = \left(\frac{4m}{1-m^2}\right)Z_2 \parallel (mZ_1)$$

$$Z_1' = \left(\frac{4m}{1-m^2}\right)\left(\frac{1}{j\omega C}\right) \parallel m(j\omega L)$$

$$Z_1' = j\omega(mL) \parallel \left[\frac{1}{j\omega\left(\frac{1-m^2}{4m}\right)c} \right]$$

m-derived L-PF (π -type):

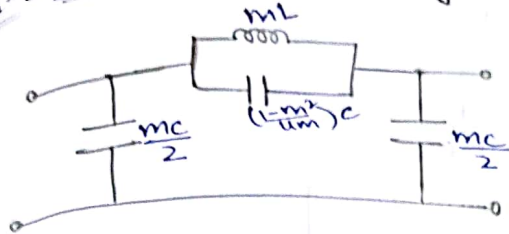

II Cut-off Frequency:

consider T-type:-

$$\frac{Z_1'}{4Z_2'} = -1 \quad \text{at } \omega = \omega_c$$

$$Z_1' = -4Z_2'$$

$$j\omega_c(mL) = -4 \left[j\omega_c \left(\frac{1-m^2}{4m} \right) L + \frac{1}{j\omega_c(mc)} \right]$$

$$j\omega_c mL = -4j\omega_c \left(\frac{1-m^2}{4m} \right) L - \frac{4}{j\omega_c mc}$$

$$j\omega_c L \left[m + \frac{1-m^2}{m} \right] = \frac{4}{\omega_c mc}$$

$$\omega_c L \left[\frac{m^2 + 1 - m^2}{m} \right] = \frac{4}{\omega_c mc}$$

$$\omega_c L = \frac{4}{\omega_c C}$$


$$\boxed{\omega_c^2 = \frac{4}{LC}}$$

$$4\pi^2 f_c^2 = \frac{4}{LC}$$

$$\boxed{f_c = \frac{1}{\pi\sqrt{LC}}}$$

II.] Frequency of Infinite Attenuation (f_0):

m-derived T-type LPF:

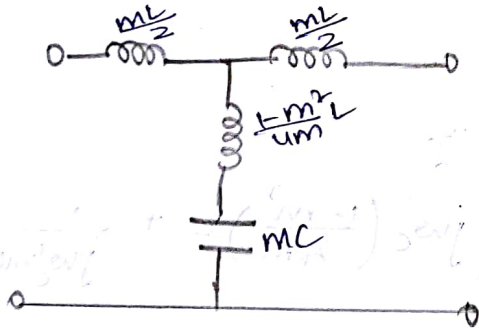

$$\omega = \omega_0 = \omega_\infty \rightarrow (\text{when } \alpha \rightarrow \infty)$$

↳ series resonant freq

$$j\omega_0 \left(\frac{1-m^2}{4m} \right) L + \frac{1}{j\omega_0 (mC)} = 0$$

$$\frac{j\omega_0^2 (1-m^2) LC + 4}{4m\omega_0 C} = 0$$

Characteristics

1) cut-off prototype

2) Character

3) Attenua

4) we can

$$f = f_0$$

freque

$$4 - \omega_0^2 (1 - m^2) LC = 0$$

$$\omega_0^2 (1 - m^2) LC = 4$$

$$(1 - m^2) = \frac{4}{\omega_0^2 LC}$$


$$1 - m^2 = \frac{\omega_c^2}{\omega_0^2} \rightarrow \boxed{\therefore \omega_c^2 = \frac{4}{LC}}$$

$$m^2 = 1 - \left(\frac{f_c}{f_0}\right)^2$$

$$\boxed{m = \sqrt{1 - \left(\frac{f_c}{f_0}\right)^2}}$$



Characteristics of m-derived Filter:

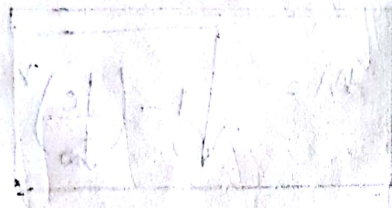- 1) cut-off frequency remains same as prototype filter
- 2) Characteristic Impedance also remain same.
- 3) Attenuation is infinity at $f = f_0$ (freq of ∞ attenuat)
- 4) we cannot expect same attenuation after $f = f_0$. Attenuation decreases as frequency increasing from f_0 to ∞ .



20/8/18
m-derived HPF Analysis:-

Standard prototype HPF:

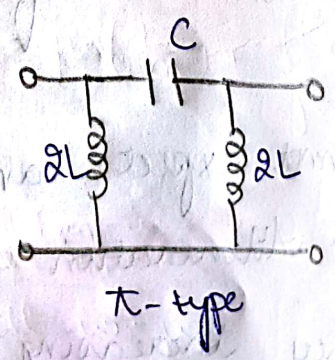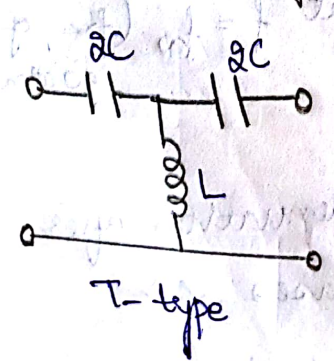

$$Z_1 = \frac{1}{j\omega C} \quad ; \quad Z_2 = j\omega L$$


m-derived T-type:
w.k.T for T-type

$$Z_1' = mZ_L = m\left(\frac{1}{j\omega C}\right) = \frac{1}{j\omega\left(\frac{C}{m}\right)}$$

$$Z_2' = \left(\frac{1-m^2}{4m}\right)Z_L + \frac{Z_2}{m}$$

$$= \left(\frac{1-m^2}{4m}\right)\left[\frac{1}{j\omega C}\right] + \frac{j\omega L}{m}$$
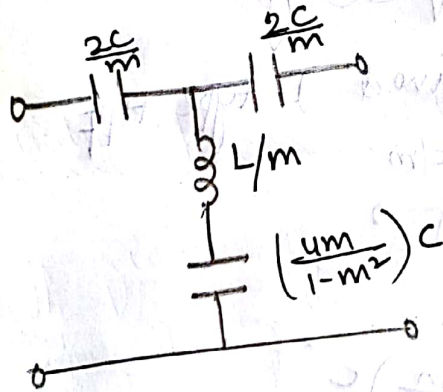
$$Z_2' = \frac{1}{j\omega\left[\frac{4m}{1-m^2}\right]C} + j\omega\left[\frac{L}{m}\right]$$



→ m-derived T-type

m-derived π-type:

w.k.T for π-type


$$Z_1' = (mZ_1) \parallel \left(\frac{4m}{1-m^2}\right)Z_2$$

$$Z_1' = m\left(\frac{1}{j\omega C}\right) \parallel \left(\frac{4m}{1-m^2}\right)j\omega L$$

$$Z_1' = \frac{1}{j\omega\left(\frac{C}{m}\right)} \parallel j\omega\left(\frac{4m}{1-m^2}\right)L$$

$$Z_2' = \frac{Z_2}{m} = \frac{j\omega L}{m}$$

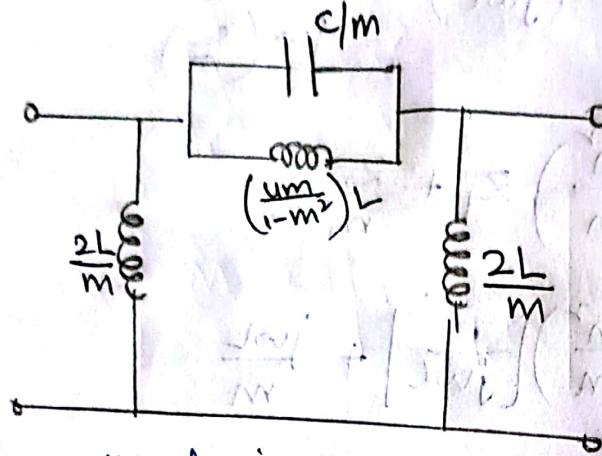
$$Z_2' = j\omega \left(\frac{L}{m}\right)$$



m-derived π -type:

Cut-off Frequency:-

consider m-derived T-type HPF

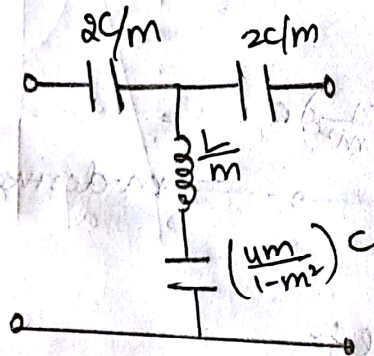

$$Z_1' = \frac{m}{j\omega C} \quad ; \quad Z_2' = j\omega \left(\frac{L}{m}\right) + \frac{(1-m^2)}{j\omega 4mC}$$

Condition for cut-off freq is $\left| \frac{Z_1'}{4Z_2'} \right| = 1$

$$\frac{Z_1'}{4Z_2'} = -1 \quad \text{at } \omega = \omega_c$$

$$\frac{m}{j\omega_c C} = -4 \left[j\omega_c \left(\frac{L}{m}\right) + \frac{1-m^2}{j\omega_c 4mC} \right]$$

$$\frac{m}{j\omega_c L} = -Y \left[\frac{4j^2 \omega_c^2 LC + 1 - m^2}{j\omega_c m C} \right]$$

$$-m^2 = -4\omega_c^2 LC + 1 - m^2$$

$$1 = 4\omega_c^2 LC$$

$$\omega_c^2 = \frac{1}{4LC}$$

$$4\pi^2 f_c^2 = \frac{1}{4LC}$$

$$f_c^2 = \frac{1}{16\pi^2 LC}$$

$$f_c = \frac{1}{4\pi\sqrt{LC}}$$

Frequency of Infinite Attenuation (f_0):

$$\text{At } \omega = \omega_0 \Rightarrow Z_2' = 0$$

↳ resonant freq of shunt arm

$$\text{let } \omega = \omega_0 = \omega_\infty$$

$$Z_2' = 0$$

$$j\omega \left(\frac{L}{m} \right) + \left(\frac{1 - m^2}{j\omega m C} \right) = 0$$

$$\frac{j\omega_\infty^2 4LC + 1 - m^2}{j\omega_\infty m C} = 0$$

$$1 - m^2 = 4LC\omega$$



$$1 - m^2 = \frac{\omega_0^2}{\omega_c^2} \quad \left[\therefore \omega_c^2 = \frac{1}{4LC} \right]$$

$$1 - \frac{f_0^2}{f_c^2} = m^2$$

$$m = \sqrt{1 - \frac{f_0^2}{f_c^2}}$$

Always frequency of attenuation (f_0) is in Stop Band

Attenuation & phase shift constants

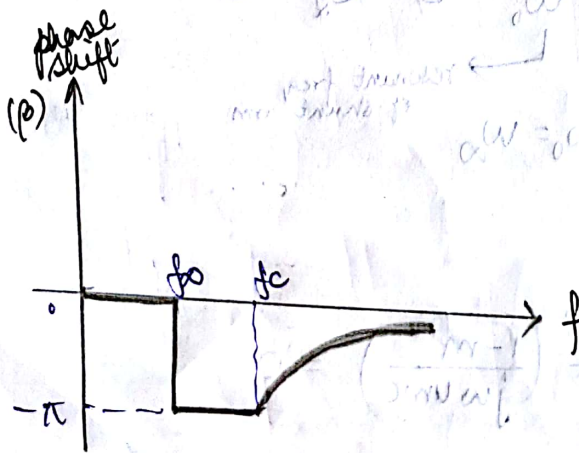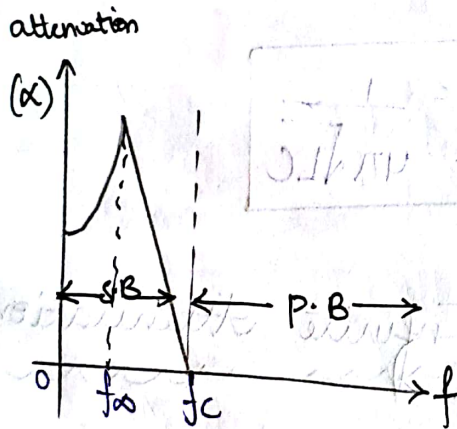

$$\beta = 0 \quad 0 \leq f < f_0$$

$$\beta = -\pi \quad f_0 \leq f < f_c$$



$$\beta = -2\sin^{-1}\left[\frac{f}{f_c}\right] \quad f \geq f_c$$

Summary:-

m-derived LPF:-

$$m = \sqrt{1 - \left(\frac{f_c}{f_0}\right)^2} ; L = \frac{R_k}{\pi f_c}$$



$$C = \frac{1}{\pi R_k f_c}$$

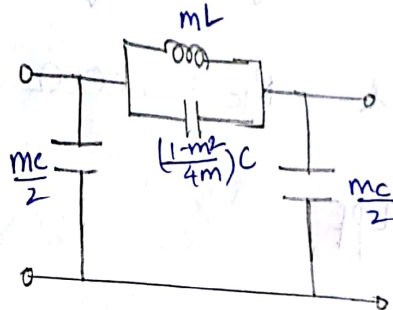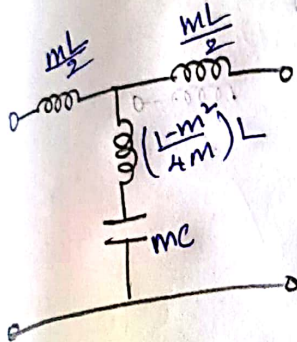

m-derived HPF:-

$$m = \sqrt{1 - \left(\frac{f_0}{f_c}\right)^2} ; L = \frac{R_k}{4\pi f_c}$$

$$C = \frac{1}{4\pi R_k f_c}$$

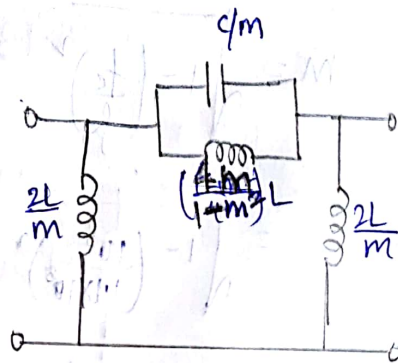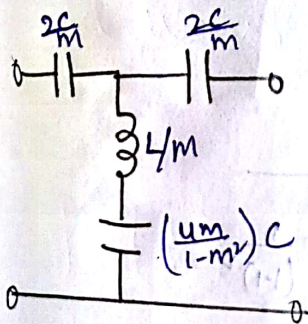

problems:-
exp.

Q1) Design an m-derived LPF filter
with cut-off Frequency 1 kHz &
frequency of attenuation $f_{\infty} = 1.1 \text{ kHz}$ &
design impedance $R_k = 600 \Omega$

Sol: Given $f_c = 1 \text{ kHz}$, $f_{\infty} = 1.1 \text{ kHz}$,

$$\& R_k = 600 \Omega$$

For LPF:-

$$L = \frac{R_k}{\pi f_c} = \frac{600}{\pi \times 1 \times 10^3} \Rightarrow \underline{190.98 \text{ mH}}$$

$$C = \frac{1}{\pi R_k f_c} \Rightarrow \frac{1}{\pi \times 600 \times 10^3} \Rightarrow \underline{530.51 \text{ nF}}$$

$$m = \sqrt{1 - \left(\frac{f_c}{f_{\infty}}\right)^2}$$

$$= \sqrt{1 - \left(\frac{10^3}{1.1 \times 10^3}\right)^2}$$

$$\Rightarrow \sqrt{1 - \frac{1}{(1.1)^2}}$$


$$m = \underline{0.416}$$

T-type:

$$\frac{mL}{2} = \frac{0.416 \times 190.98}{2} = 39.72 \text{ mH}$$

$$\left(\frac{1-m^2}{4m}\right) L = \left(\frac{1-0.416^2}{4 \times 0.416}\right) \times 190.98 \Rightarrow 94.9 \text{ mH}$$
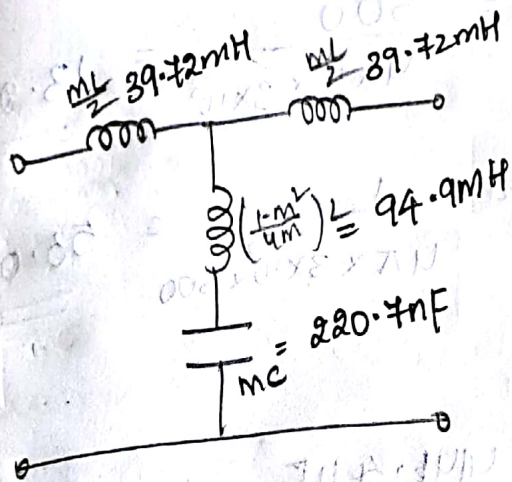
$$mC \Rightarrow 0.416 \times 530.51 = 220.7 \text{ nF}$$




π-type:

$$mL \Rightarrow 0.416 \times 190.98 \Rightarrow 79.44 \text{ mH}$$

$$\left(\frac{1-m^2}{4m}\right) C \Rightarrow \frac{1-(0.416)^2}{4 \times 0.416} \times 530.51 = 263.64 \text{ nF}$$
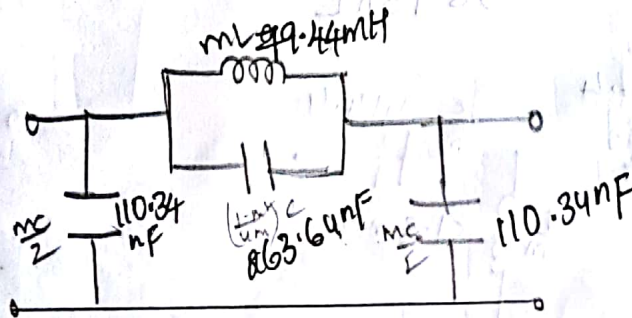
$$\frac{mC}{2} \Rightarrow \frac{0.416 \times 530.51}{2} = 110.34 \text{ nF}$$



Q2) Design an m-derived HPF with cut-off frequency 3 kHz & frequency of infinite attenuation $f_{\infty} = 2.9 \text{ kHz}$ & $R_k = 500$

sol:
$$m = \sqrt{1 - \left(\frac{f_{\infty}}{f_c}\right)^2} = \sqrt{1 - \left(\frac{2.9}{3}\right)^2} = \underline{\underline{0.256}}$$

$$L = \frac{R_k}{4\pi f_c} = \frac{500}{4 \times \pi \times 3 \times 10^3} = \underline{\underline{13.26 \text{ mH}}}$$

$$C = \frac{1}{4\pi f_c R_k} = \frac{1}{4\pi \times 3 \times 10^3 \times 500} = \underline{\underline{53.05 \text{ nF}}}$$


T-type:

$$\frac{2C}{m} \Rightarrow \frac{2 \times 53.05}{0.256} = \underline{\underline{414.4 \text{ nF}}}$$

$$\frac{L}{m} \Rightarrow \frac{13.26}{0.256} = \underline{\underline{51.8 \text{ mH}}}$$

$$\left(\frac{4m}{1-m^2}\right)C \Rightarrow \frac{4 \times 0.256}{1 - (0.256)^2} \times 53.05 \times 10^{-9}$$

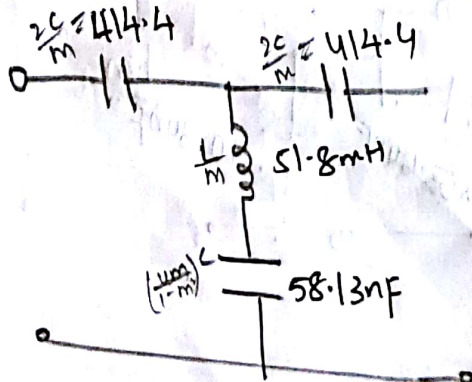
$$\Rightarrow \underline{\underline{58.13 \text{ nF}}}$$



$$\left(\frac{4\mu}{1-m^2}\right)^2 = \frac{4 \times 0.256}{1 - (0.256)^2} \times 13.26 \text{ mH} \Rightarrow 14.53 \text{ mH}$$

$$\frac{C}{m} \Rightarrow 207.22 \text{ nF}$$
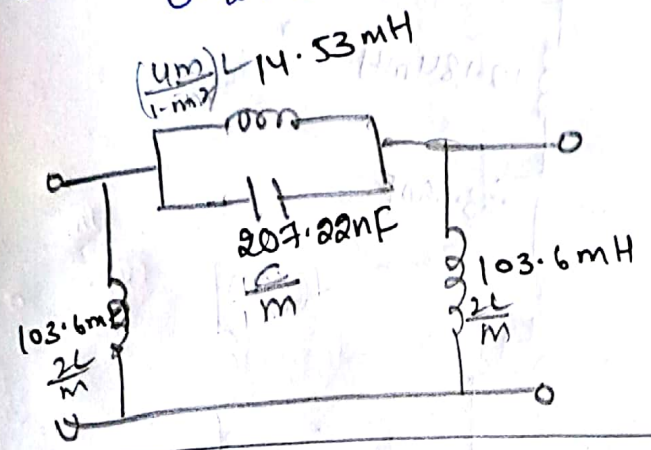
$$\frac{2L}{m} \Rightarrow \frac{2 \times 13.26}{0.256} = 103.6 \text{ mH}$$



Q3) Design an m-derived LPF with cut-off freq. $f_c = 5 \text{ kHz}$ & design imp $R_L = 600 \Omega$ & $f_o = 1.25 f_c$

$$m = \sqrt{1 - \left(\frac{f_c}{f_o}\right)^2} \Rightarrow \sqrt{1 - \left(\frac{5 \times 10^3}{1.25 \times 5 \times 10^3}\right)^2} = \underline{\underline{0.6}}$$

$$L = \frac{R_L}{\pi f_c} \Rightarrow \underline{\underline{38.19 \text{ mH}}}$$

$$C = \frac{1}{\pi R_L f_c} = \underline{\underline{106.1 \text{ nF}}}$$


T-type:

$$\frac{mL}{2} \Rightarrow \frac{0.6 \times 38.19}{2} \Rightarrow 11.457 \text{ mH}$$

$$mC \Rightarrow 0.6 \times 106.1 \text{ nF} = 63.66 \text{ nF}$$

$$\left(\frac{1-m^2}{4m}\right) L \Rightarrow \left(\frac{1-(0.6)^2}{4 \times 0.6}\right) \times 38.19$$

$$= 10.184 \text{ mH}$$

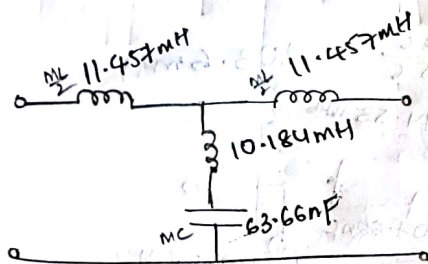


T-type:


$$ML \Rightarrow 0.6 \times 38.19 = 22.91 \text{ mH}$$

$$\left(\frac{1-m^2}{4m}\right) C \Rightarrow \frac{1-(0.6)^2}{4 \times 0.6} \times 106.1 = 28.293 \text{ nF}$$

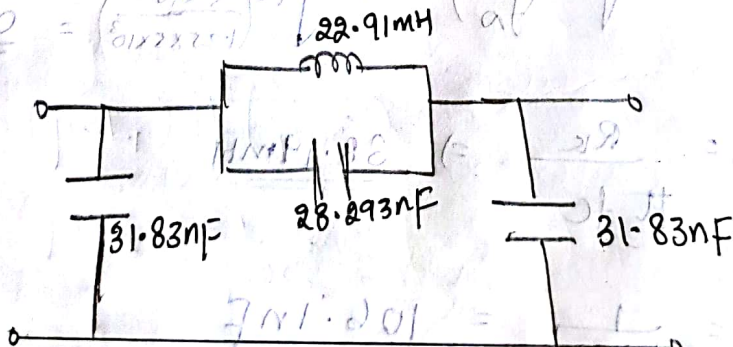
$$\frac{MC}{2} \Rightarrow \frac{0.6 \times 106.1}{2} = 31.83 \text{ nF}$$




m-derived Band-

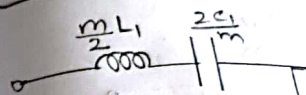


T-type

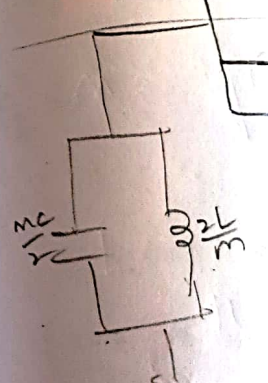

m-derived Band-pass filter

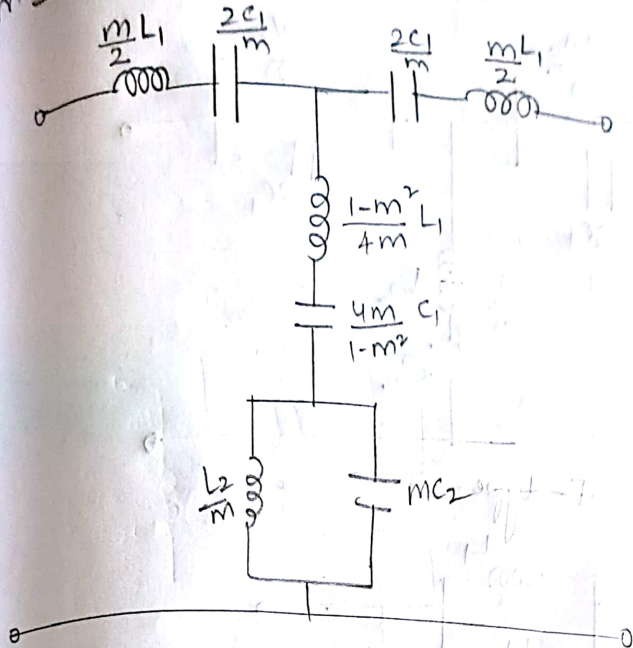



T-type

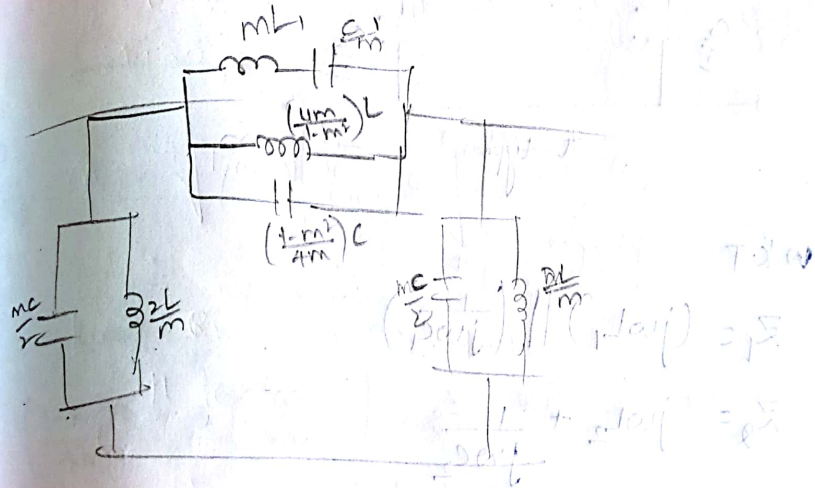

π-type

$$\left[\frac{(j\omega m L_1) (j\omega \frac{2C_1}{m})}{j\omega \frac{2C_1}{m} + j\omega m L_1} \right] m = \sqrt{1-m^2} = 1$$

M-derived "Band Stop" Filter :-

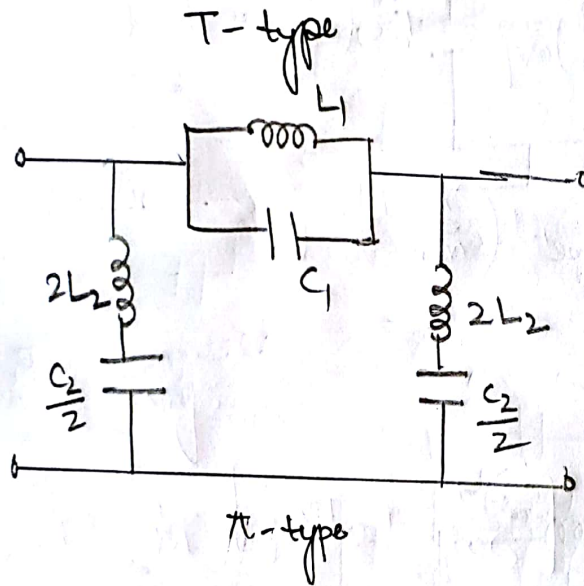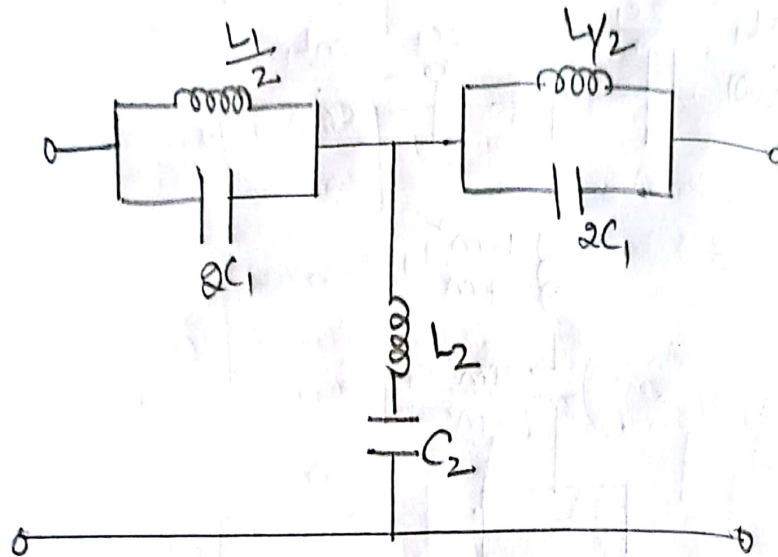

w.k.T

$$Z_1 = (j\omega L_1) \parallel \left(\frac{1}{j\omega C_1} \right)$$

$$Z_2 = j\omega L_2 + \frac{1}{j\omega C_2}$$

For T-type:

$$Z_1' = mZ_1 = m \left[\frac{(j\omega L_1) \left(\frac{1}{j\omega C_1} \right)}{j\omega L_1 + \frac{1}{j\omega C_1}} \right]$$

$$Z_1 = \frac{(j\omega L_1) \left(\frac{1}{j\omega C_1} \right)}{\frac{1}{m} \left[j\omega L_1 + \frac{1}{j\omega C_1} \right]}$$

$$Z_1' = \frac{(j\omega mL_1) \left(\frac{1}{j\omega C_1} \right)}{\left(j\omega L_1 + \frac{1}{j\omega C_1} \right)} \times \frac{3}{3}$$

$$Z_1' = \frac{j\omega (mL_1) \times \frac{1}{j\omega \left(\frac{C_1}{m} \right)}}{j\omega (mL_1) + \frac{1}{j\omega \left(\frac{C_1}{m} \right)}}$$

$$Z_1 = j\omega (mL_1) \parallel \frac{1}{j\omega \left(\frac{C_1}{m} \right)}$$

$$Z_2' = \left(\frac{1-m^2}{4m} \right) Z_1 + \frac{Z_2}{m}$$

↓
considering

$$\left(\frac{1-m^2}{4m} \right) Z_1 \Rightarrow \left(\frac{1-m^2}{4m} \right) \left[\frac{(j\omega L_1) \left(\frac{1}{j\omega C_1} \right)}{\left[j\omega L_1 + \frac{1}{j\omega C_1} \right]} \right]$$

$$= \frac{j\omega \left(\frac{1-m^2}{4m} \right) L_1 \times \frac{1}{j\omega C_1}}{\left[j\omega L_1 + \frac{1}{j\omega C_1} \right]}$$

$$\frac{\left(\frac{1-m^2}{4m} \right)}{\left(\frac{1-m^2}{4m} \right)} \left[j\omega L_1 + \frac{1}{j\omega C_1} \right]$$

$$= \frac{j\omega \left[\frac{1-m^2}{4m} \right] L_1 \left(\frac{1-m^2}{j\omega 4m C_1} \right)}{j\omega \left[\frac{1-m^2}{4m} \right] L_1 + \frac{1-m^2}{j\omega 4m C_1}}$$

$$= \frac{j\omega \left[\frac{1-m^2}{4m} \right] L_1 \times \frac{1}{j\omega \left(\frac{4m}{1-m^2} \right) C_1}}{j\omega \left(\frac{1-m^2}{4m} \right) L_1 + \frac{1}{j\omega \left(\frac{4m}{1-m^2} \right) C_1}}$$

$$\therefore \left(\frac{1-m^2}{4m} \right) Z_1 \Rightarrow j\omega \left(\frac{1-m^2}{4m} \right) L_1 \parallel \frac{1}{j\omega \left(\frac{4m}{1-m^2} \right) C_1}$$


Now considering;

$$\begin{aligned} \frac{Z_2}{m} &= \frac{1}{m} \left[j\omega L_2 + \frac{1}{j\omega C_2} \right] \\ &= j\omega \left(\frac{L_2}{m} \right) + \frac{1}{j\omega (m C_2)} \end{aligned}$$

Now we have $Z_2' = \left(\frac{1-m^2}{4m} \right) Z_1 + \frac{Z_2}{m}$

$$\therefore Z_2' = \left[j\omega \left(\frac{1-m^2}{4m} \right) L_1 \parallel \frac{1}{j\omega \left(\frac{4m}{1-m^2} \right) C_1} \right] + \left[j\omega \left(\frac{L_2}{m} \right) + \frac{1}{j\omega (m C_2)} \right]$$

SHIREEN

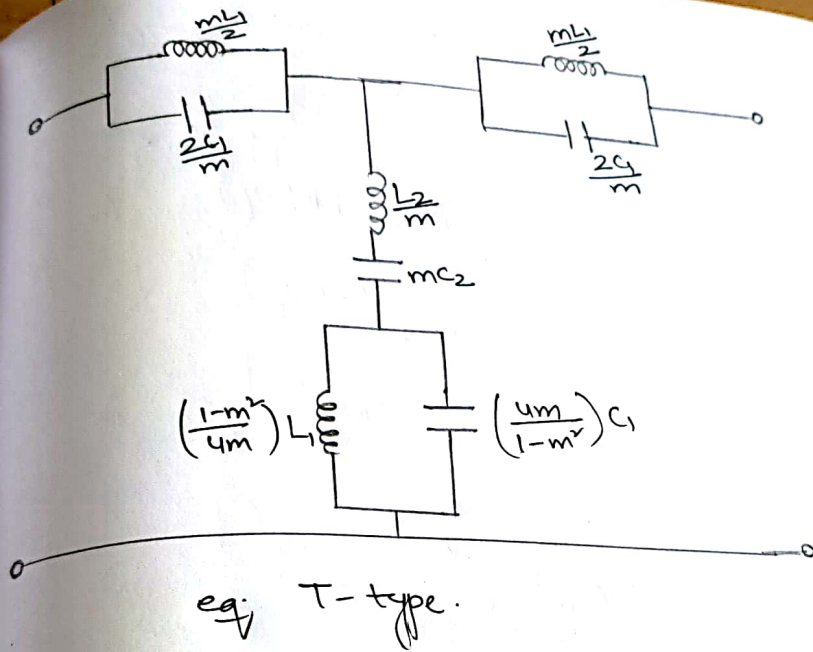

NOTE:-

For m-derived Band pass filter :

$$m = \sqrt{1 - \left(\frac{f_c2 - f_c1}{f_{\infty 2} - f_{\infty 1}} \right)^2}$$

f_{c1} → lower cut-off Freq

f_{c2} → higher " " "

$f_{\infty 1}$] → freq. of infinite attenuation.
 $f_{\infty 2}$]

$$\frac{j\omega L_2}{1 - \omega^2 L_2 C_2} + j \frac{1 - m^2}{4m} \left[\frac{\omega^2 L_1 C_1 - 1}{\omega C_1} \right] = 0$$

$$\frac{(1 - m^2)L_1}{4m} + \frac{4mC_1}{(1 - m^2)} \quad \text{series comb}$$

$$\frac{L_2}{m} \parallel mC_2 \quad \text{|| comb}$$

$$Z_1 = j\omega L_1 - \frac{j}{\omega C_1} \Rightarrow j\omega L_1 + \frac{1}{j\omega C_1}$$

$$Z_2 = j\omega C_2 \parallel \frac{1}{j\omega C_2}$$

w.p.t. series band pass filter
 $Z_1' = m Z_1$

$$= m \left[j\omega L_1 + \frac{1}{j\omega C_1} \right]$$

$$= j\omega m L_1 + \frac{1}{j\omega \frac{C_1}{m}}$$

$$Z_2' = \left(\frac{1-m^2}{4m} \right) Z_1 + \frac{Z_2}{m}$$

$$\left(\frac{1-m^2}{4m} \right) Z_1 = \left(j\omega L_1 + \frac{1}{j\omega C_1} \right) \left(\frac{1-m^2}{4m} \right)$$

$$= j\omega L_1 \left(\frac{1-m^2}{4m} \right) L_1 + \frac{1}{j\omega \left(\frac{4m}{1-m^2} \right) C_1}$$

$$\frac{Z_2}{m} = \frac{j\omega L_2 \times \frac{1}{j\omega C_2}}{j\omega L_2 + \frac{1}{j\omega C_2}} \times \frac{1}{3}$$

$$= j\omega L_2 \times \frac{1}{j\omega C_2}$$







$$j\omega m L_2 + \frac{1}{j\omega C_2}$$

$$= j\omega L_2 m \times \frac{1}{j\omega C_2}$$

$$j\omega m L_2 + \frac{1}{j\omega C_2}$$

$$\frac{Z_2}{m} = j\omega m L_2 \parallel \frac{1}{j\omega C_2}$$

↳ prototype half-sections:-

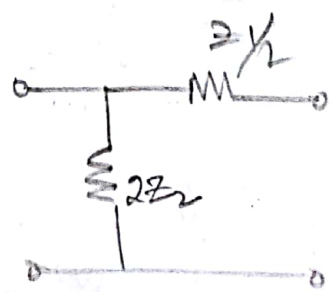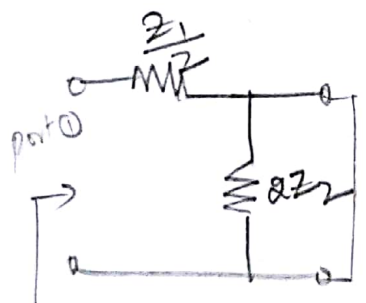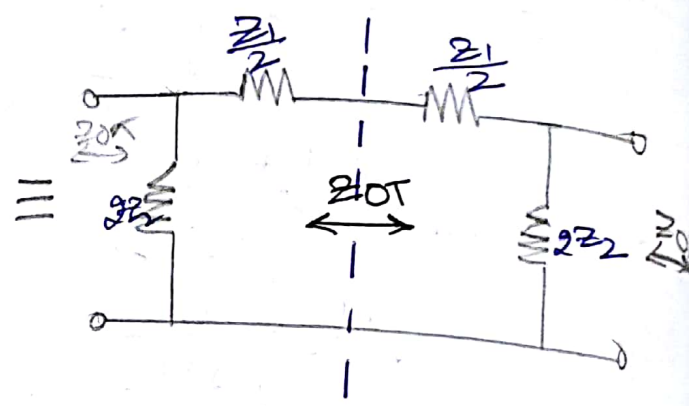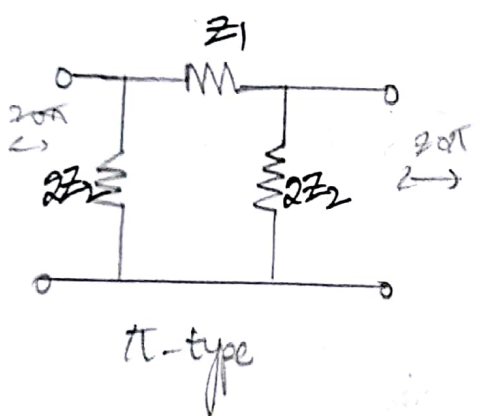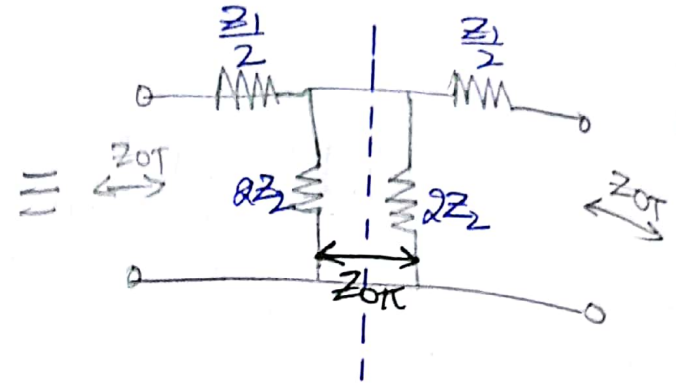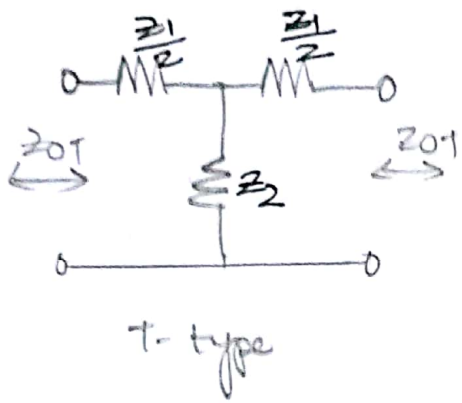

$$Z_{SC1} = \frac{Z_1}{2}$$

$$Z_{SC2} = \left(\frac{Z_1}{2}\right) \parallel (2Z_2)$$

$$Z_{OC1} = \frac{Z_1}{2} + 2Z_2$$

$$Z_{OC2} = 2Z_2$$

w.k.T

$$Z_{i1} = \sqrt{Z_{SC1} \cdot Z_{OC1}}$$

$$Z_{i2} = \sqrt{Z_{SC2} \cdot Z_{OC2}}$$

$$Z_{i1} = \sqrt{\left(\frac{Z_1}{2}\right)\left(\frac{Z_1}{2} + 2Z_2\right)}$$


$$Z_{i2} = \sqrt{\left(\frac{Z_2}{2}\right)\left(\frac{Z_2}{2} + 2Z_1\right)}$$

$$Z_{i1} = \sqrt{\frac{Z_1^2}{4} + 2Z_1Z_2}$$



$$Z_{i2} = \sqrt{\frac{4Z_1Z_2}{Z_1 + 4Z_2}}$$

$$Z_{i1} = Z_{OT}$$

$$Z_{i2} = Z_{OK}$$

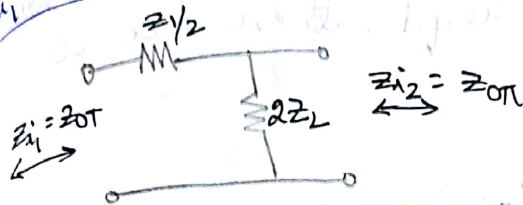

m-derived half-sections:-

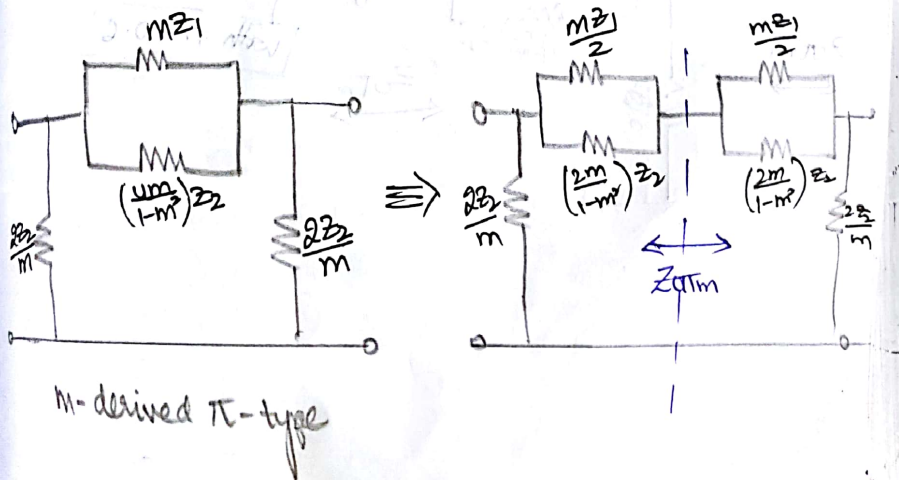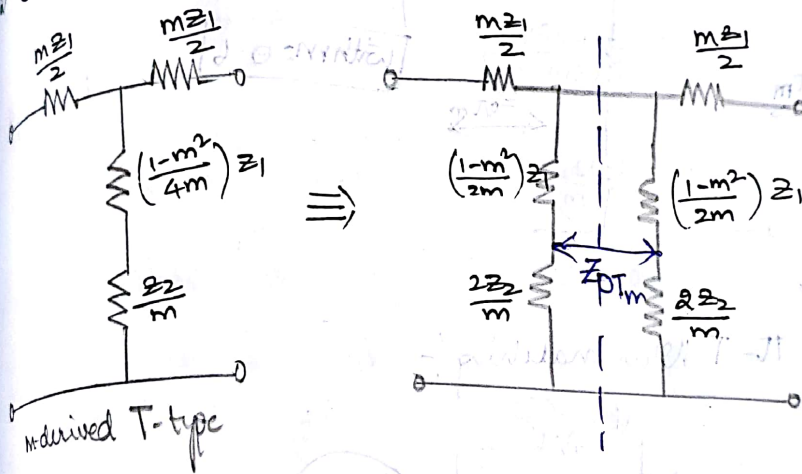


NOTE :-


- If T to π & π to T $10W$ matching is req'd, then a prototype half section (L-section) is used.
- For m-derived T to π & π to T, $10W$ matching is req'd, then we select

$m = 0.6$


For T-type:- (T- π)

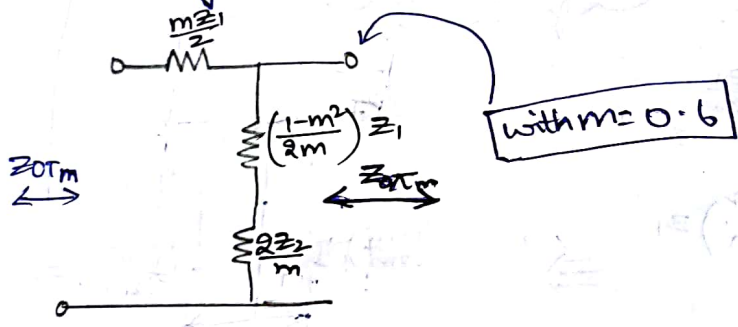

- For π -T $10W$ matching:-

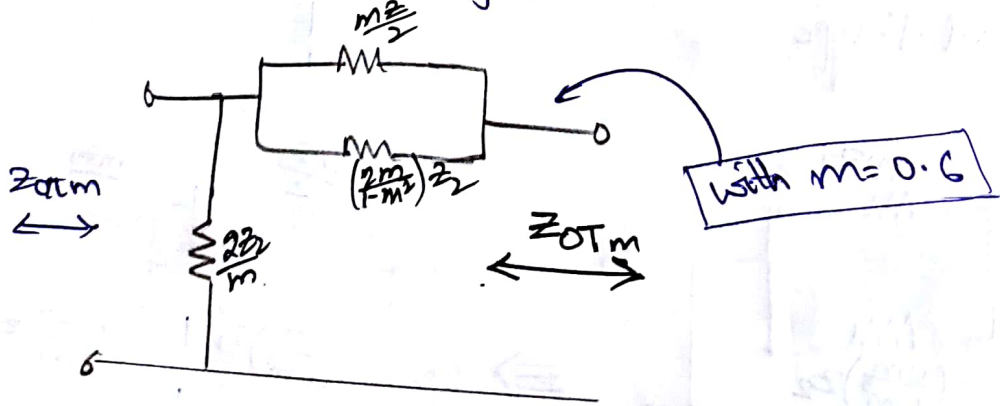

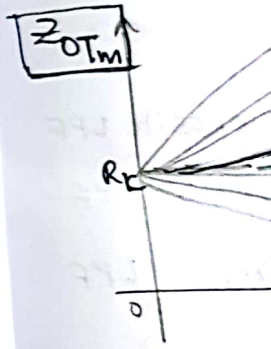Variation with 'm' :-
 m-derived impedance Z_{0Tm}
 For m-derived of 'm' vari are given



low
 From st
 except
 - resisti
 away
 curve
 so, fo
 filter



matching in half section

to T, R_{in} or select

Variation of characteristic impedance with 'm' :-



m-derived T & π -section R_{in} , characteristic impedance changes w.r.t frequency & parameter 'm'.

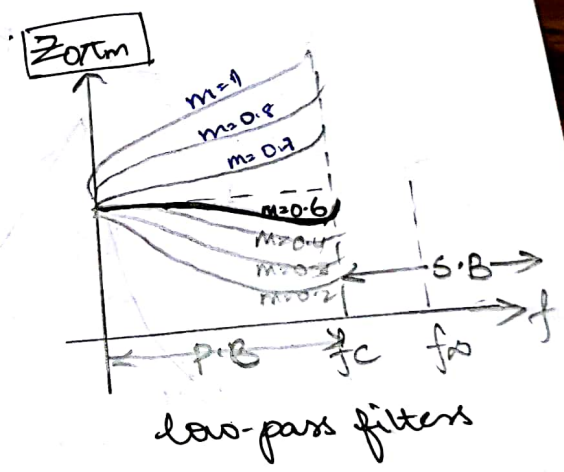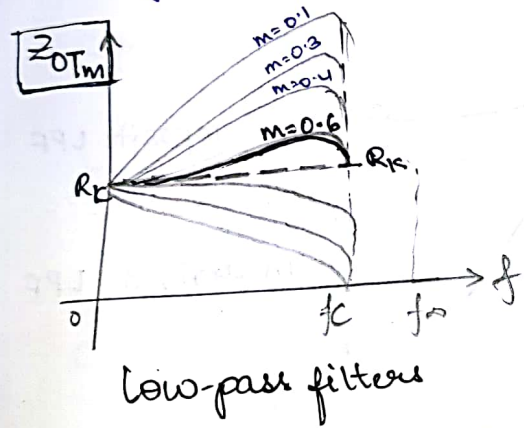For m-derived low-pass filter for diff values of 'm' variation of characteristic impedances are given below:




From the graphs, it has been observed that except $m=0.6$ for other values of 'm', characteristic impedance curve is deviated more away from the R_k line i.e. At $m=0.6$; the curve is approximated to R_k line.

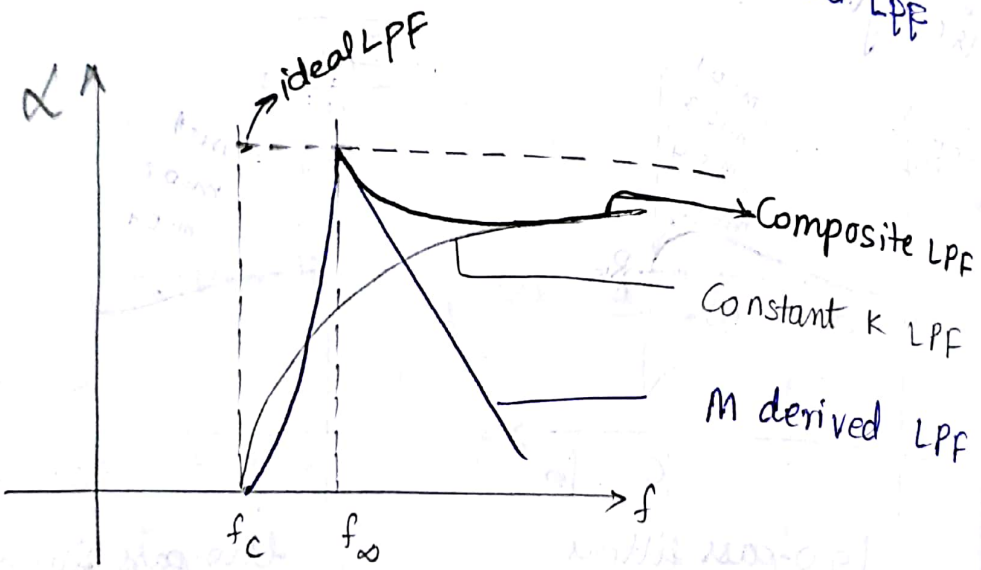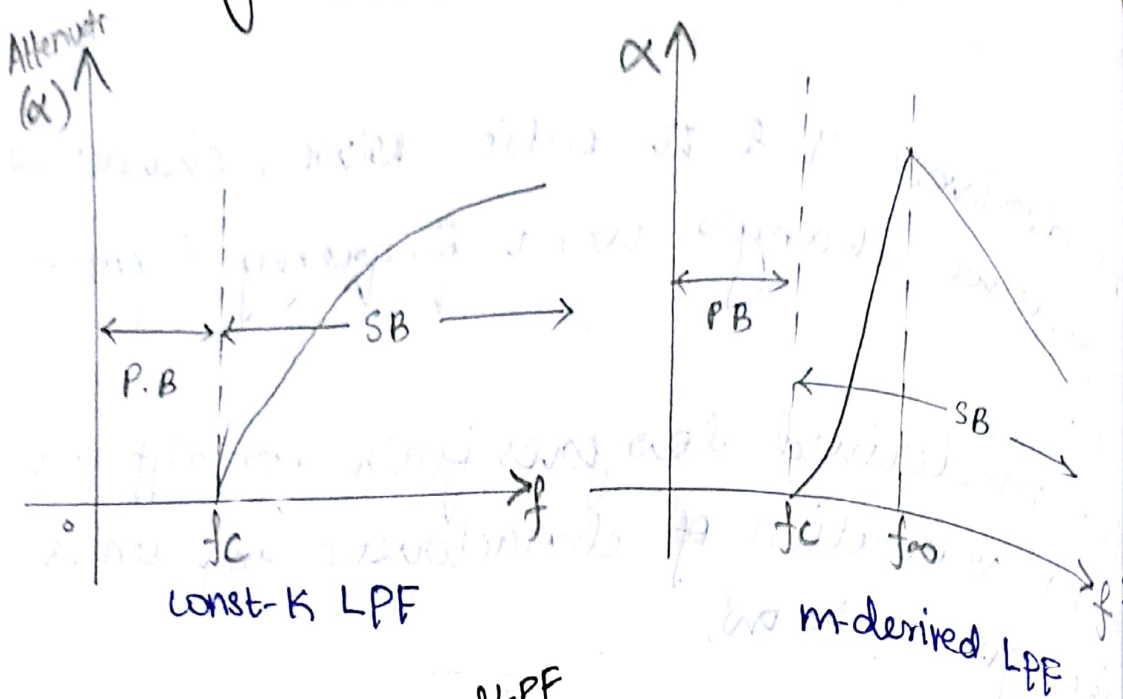So, for impedance matching in m-derived filters, we consider $m=0.6$



Block Diagram of composite Filter:-

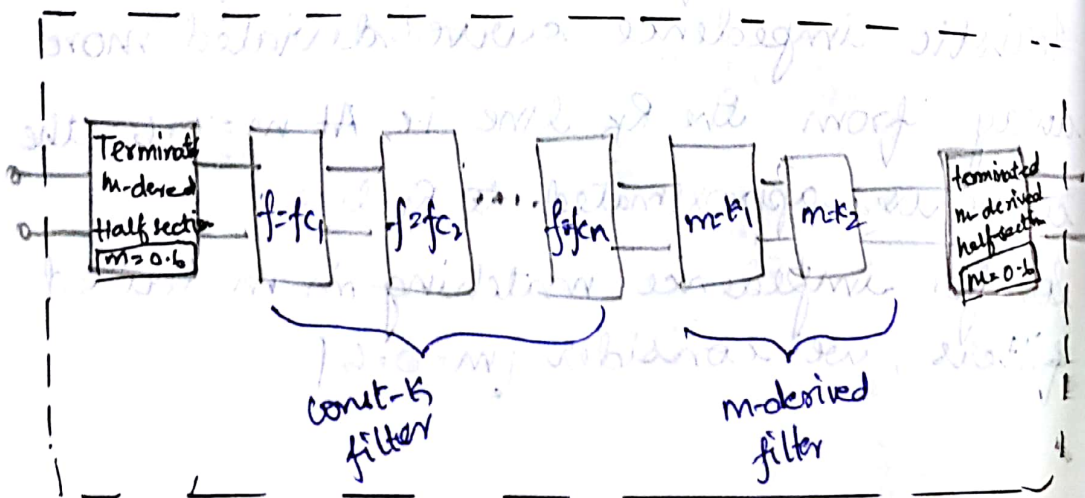

problems:

Design a composite LPF T-type with cut-off frequency 2 KHz & frequency of attenuation $f_0 = 2.05 \text{ KHz}$ & Design impedance $R_k = 500 \Omega$.

def: $f_c = 2 \text{ KHz}$

$f_0 = 2.05 \text{ KHz}$


$R_k = 500 \Omega$

i. const-K LPF:

$$L = \frac{R_k}{\pi f_c} = \frac{500}{\pi \times 2 \times 10^3} = 79.57 \text{ mH}$$

$$\frac{L}{2} \Rightarrow 39.78 \text{ mH}$$
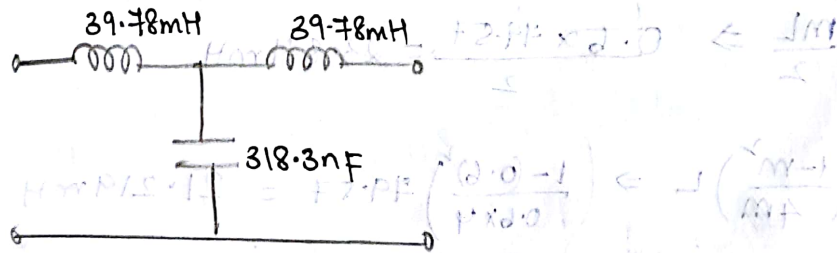
$$C = \frac{1}{\pi R_k f_c} = \frac{1}{500 \times 2 \times 10^3 \times \pi} = 318.3 \text{ nF}$$




ii. m-derived LPF:

$$m = \sqrt{1 - \left(\frac{f_c}{f_0}\right)^2} \Rightarrow \sqrt{1 - \left(\frac{2}{2.05}\right)^2} \Rightarrow 0.22$$

$$\frac{ML}{2} = \frac{0.22 \times 79.57}{2} = 8.75 \text{ mH}$$

$$\left(\frac{1-m^2}{4m}\right)L \Rightarrow \left(\frac{1-0.22^2}{4 \times 0.22}\right) \times 79.57 = 86.04 \text{ mH}$$
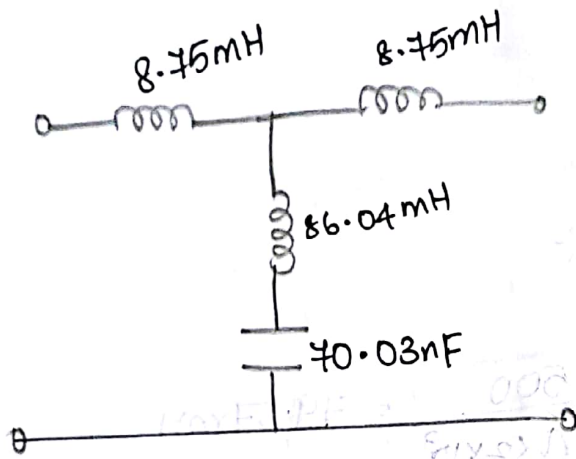
$$mC \Rightarrow 0.22 \times 318.3 \Rightarrow 70.03 \text{ nF}$$




iii) Terminating Half-Sections

let $m = 0.6$

$$\frac{mL}{2} \Rightarrow \frac{0.6 \times 79.57}{2} = 23.87 \text{ mH}$$

$$\left(\frac{1-m^2}{4m}\right)L \Rightarrow \left(\frac{1-(0.6)^2}{0.6 \times 4}\right) \times 79.57 = 21.219 \text{ mH}$$
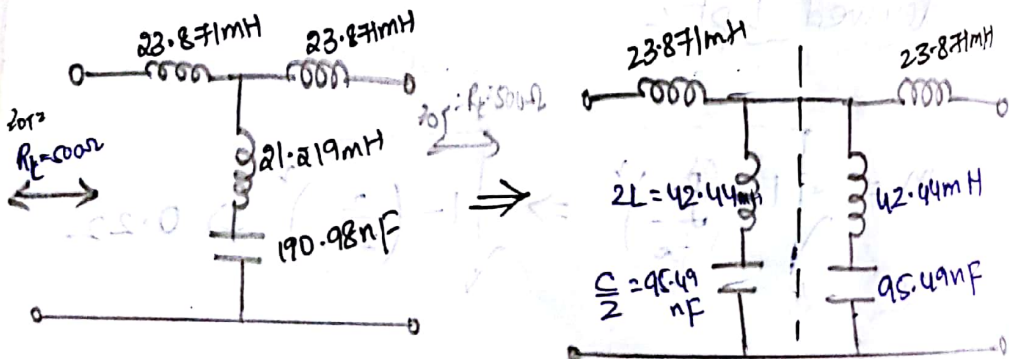
$$mC \Rightarrow 0.6 \times 318.3 = 190.98 \text{ nF}$$





28/11/18

Q) Design a composite HPF T-type to operate at $f_c = 1.2 \text{ kHz}$ & $f_o = 1.1 \text{ kHz}$ & design imp.


$R_k = 600 \Omega$

$f_c = 1.2 \text{ kHz}$
 $f_o = 1.1 \text{ kHz}$
 $R_k = 600 \Omega$

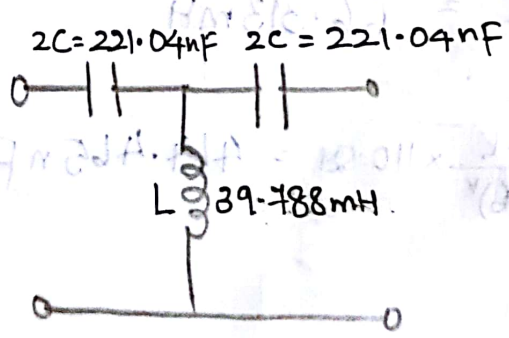i) const-K HPF :-

$$L = \frac{R_k}{4\pi f_c} = \frac{600}{4 \times \pi \times 1.2 \times 10^3} = 39.788 \text{ mH}$$

$$C = \frac{1}{4\pi f_c R_k} = \frac{1}{4 \times \pi \times 1.2 \times 10^3 \times 600} = 110.524 \text{ nF}$$




ii, m-derived HPF :-

$$m = \sqrt{1 - \left(\frac{f_c}{f_c}\right)^2} \Rightarrow \sqrt{1 - \left(\frac{1.1}{1.2}\right)^2} = 0.399$$

$$\frac{2C}{m} = \frac{110.524 \times 2}{0.399} = 554 \text{ nF}$$

$$\frac{L}{m} = \frac{39.788}{0.399} = 99.719 \text{ mH}$$
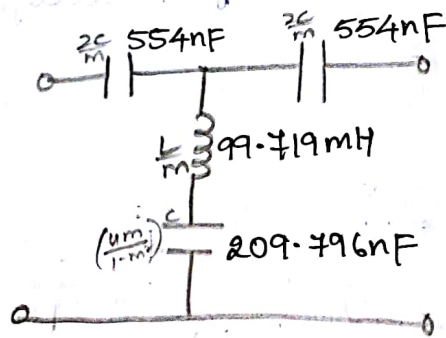
$$\left(\frac{4m}{1-m^2}\right)C \Rightarrow \frac{4 \times 0.399}{1 - (0.399)^2} \times 110.524 \Rightarrow 209.796 \text{ nF}$$






iii, Terminating half-sections;



let $m = 0.6$

$$\frac{2C}{m} \Rightarrow \frac{2 \times 110.524}{0.6} = 368.413 \text{ nF}$$



$$\frac{L}{m} \Rightarrow \frac{39.788}{0.6} = 66.313 \text{ mH}$$
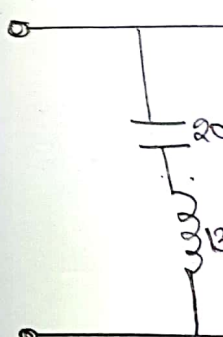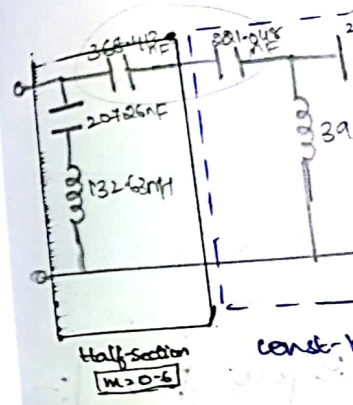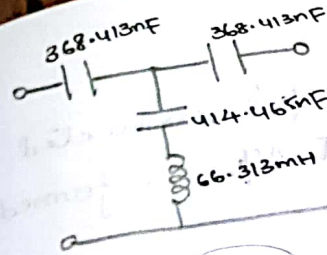
$$\left(\frac{4m}{1-m^2}\right)C \Rightarrow \frac{4 \times 0.6}{1 - (0.6)^2} \times 110.524 = 414.465 \text{ nF}$$



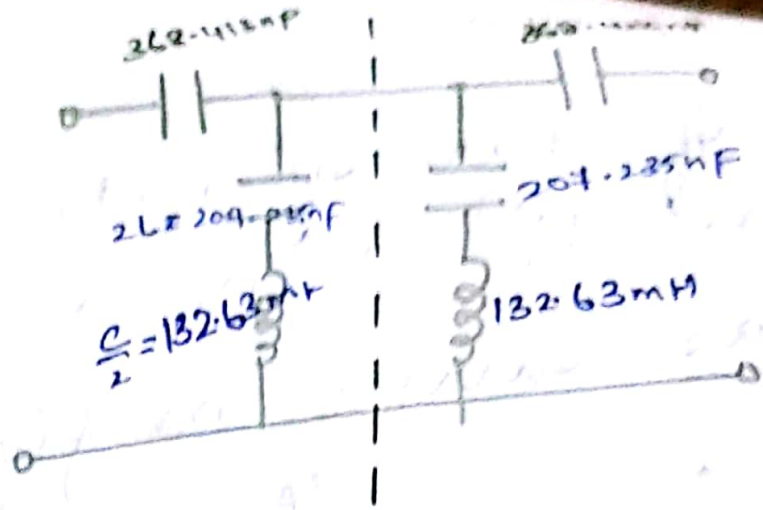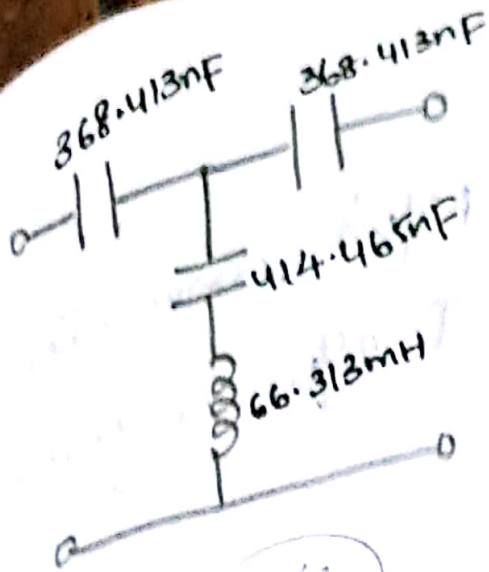


$$\frac{C_1 C_2}{C_1 + C_2}$$

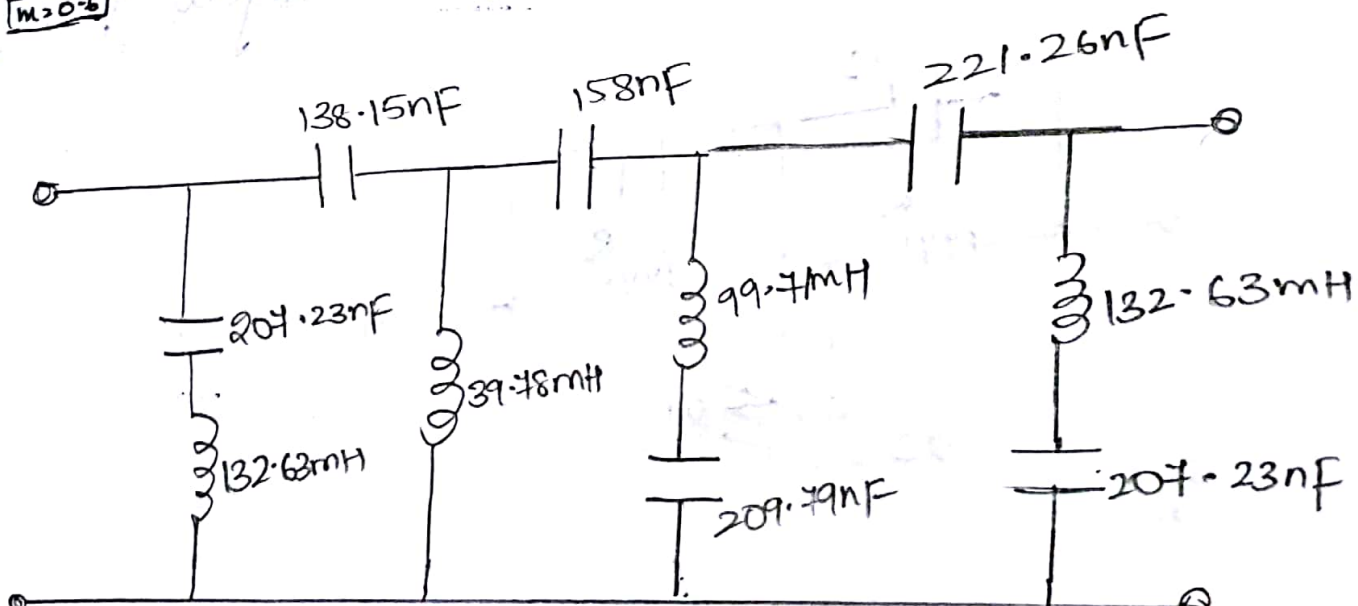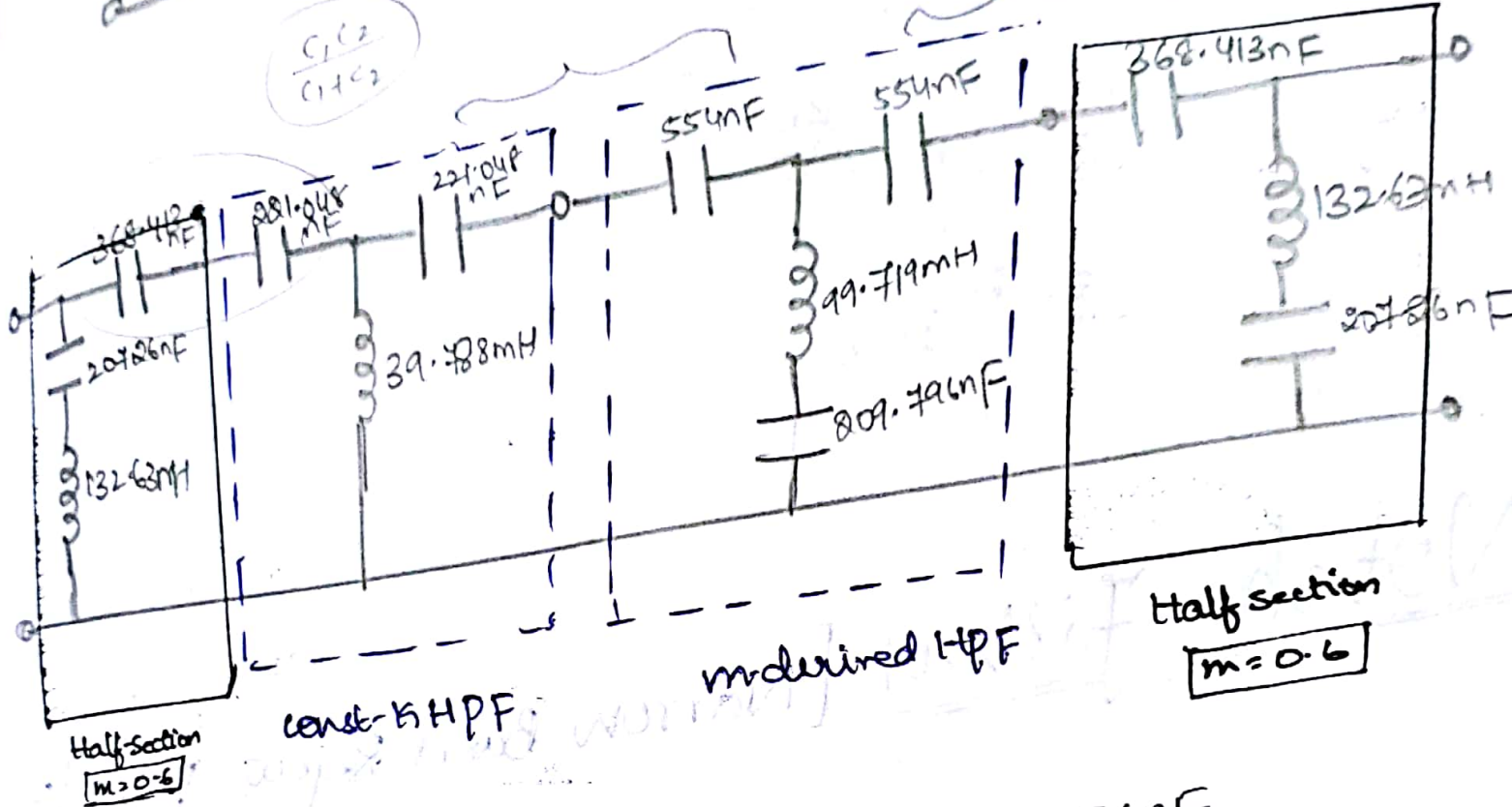


Twin-T Network:

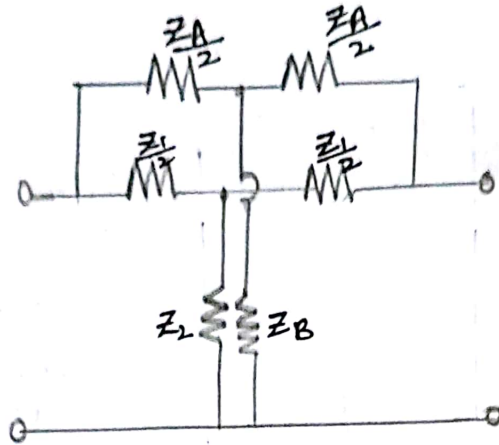If two symmetrical T-N/w are connected in Π , then a twin-T N/w is formed as shown in fig:



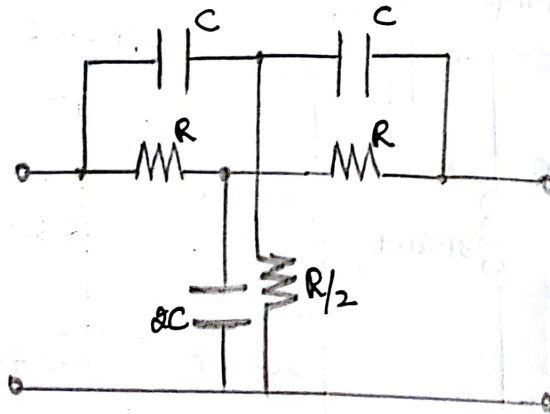Notch Filter: [Narrow Band Reject Filter]



$$\text{Reject frequency } (f_0) = \frac{1}{2\pi RC}$$

